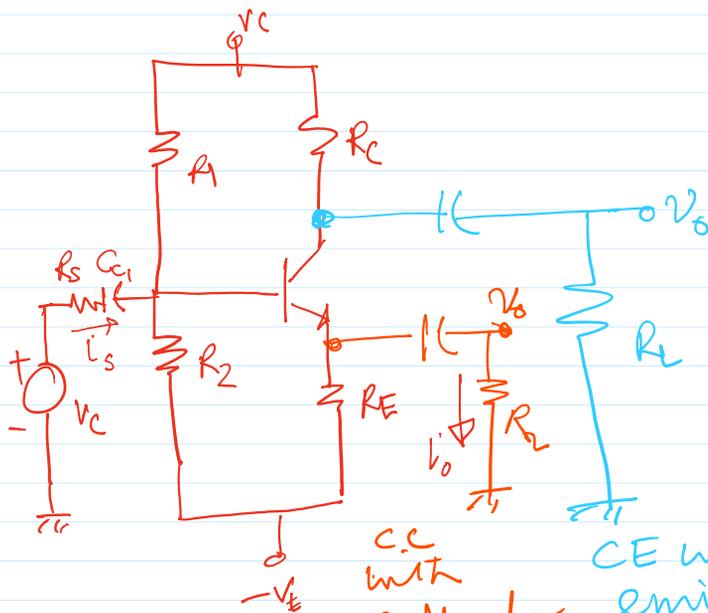



Common Collector Amplifier

Monday, October 9, 2017 8:17 AM




$$A_i = \frac{i_o}{i_s} \Big|_{\text{midband}}$$

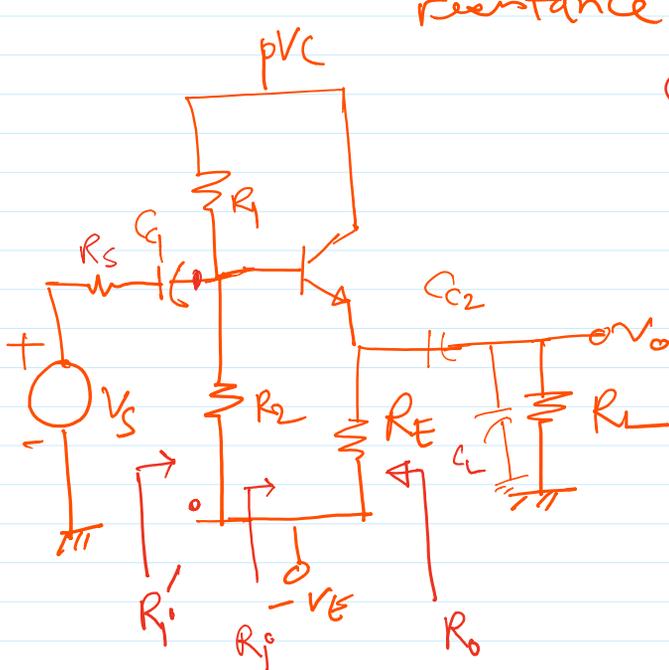
C.C. with collector resistance
CE with emitter resistance



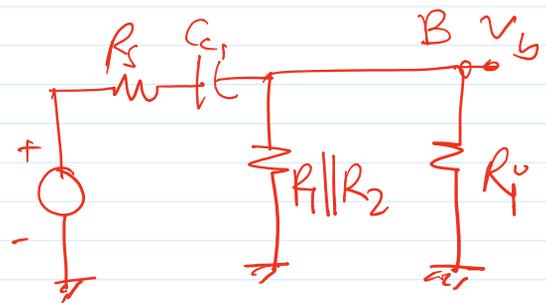
$$C_{c1} \Rightarrow A_v = A_{vA} \times \frac{R_i'}{R_i' + R_s + 1/s_{C_{c1}}}$$




Input side

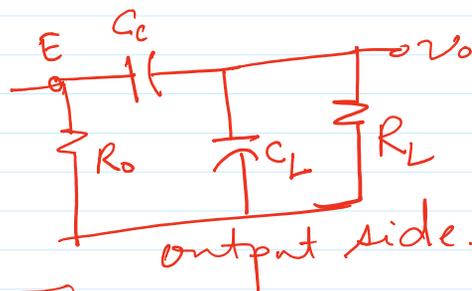


output side.

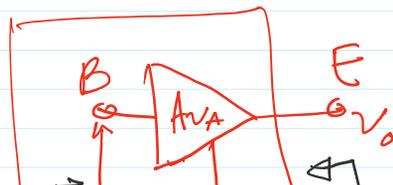


$$A_{vA} = \frac{v_o}{v_b}$$

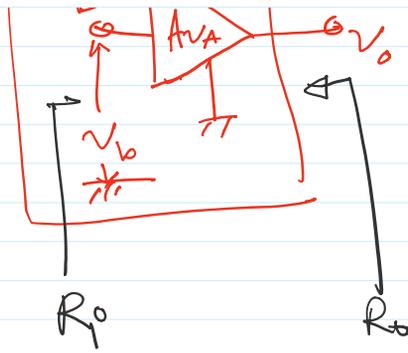

$$A_{VA} = \frac{v_o}{v_b}$$


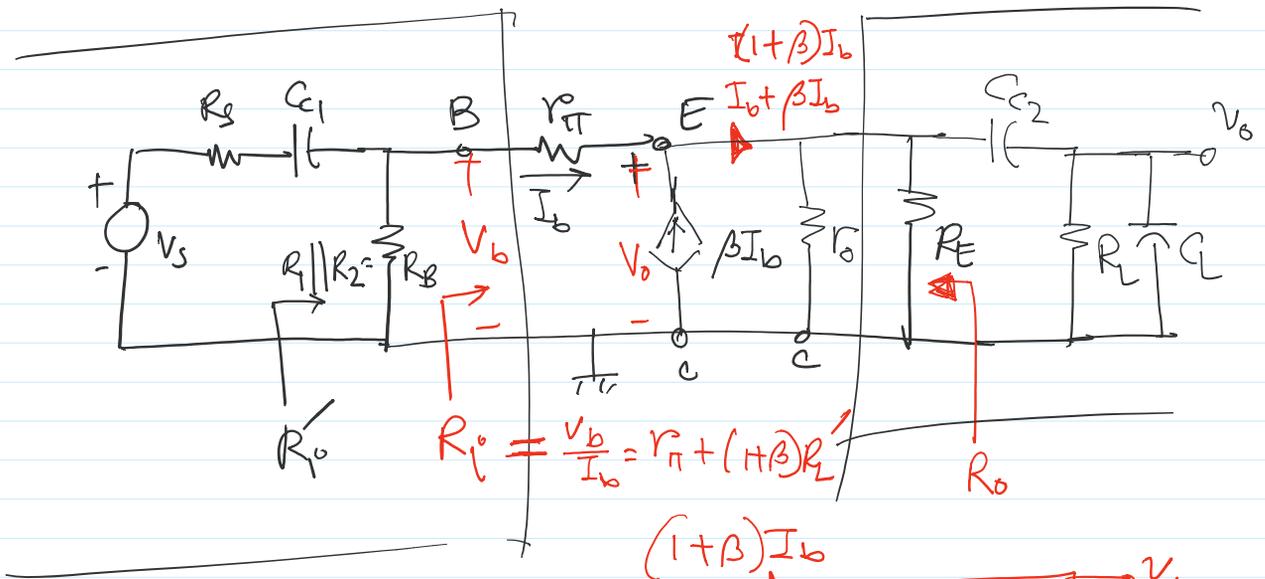

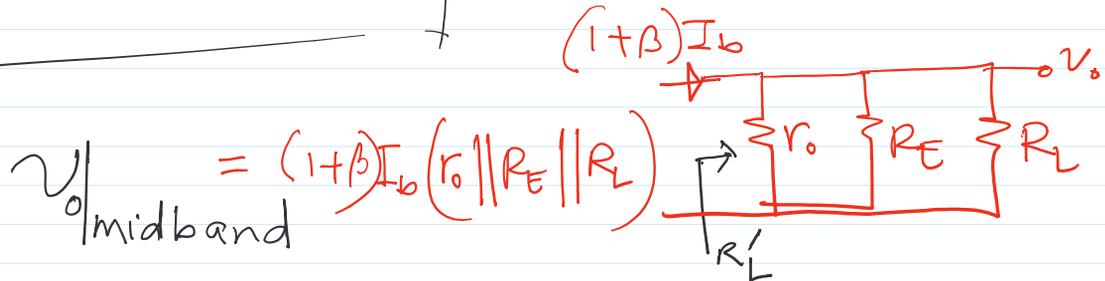
$$R_i = \frac{v_b}{I_b} = r_{\pi} + (1+\beta)R'_L$$



$$v_o |_{\text{midband}} = (1+\beta)I_b (r_o \parallel R_E \parallel R_L)$$

$$v_o |_{\text{low freq}} = (1+\beta)I_b \times Z_L$$

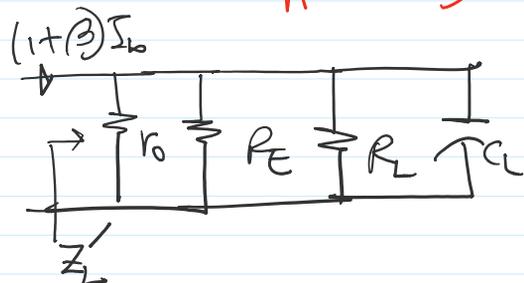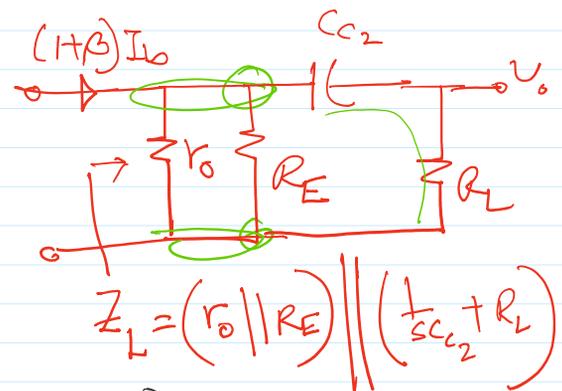


$$v_o |_{\text{high freq}} = (1+\beta)I_b Z'_L$$

$$Z_L = r_o \parallel R_E \parallel R_L \parallel \left(\frac{1}{sC_L} \right)$$

$$A_{vA} = \frac{v_o}{v_b}$$

$$v_b \Big|_{\text{midfreq}} = r_{\pi} I_b + (1+\beta) I_b R_L'$$

$$v_b = r_{\pi} I_b + v_o$$

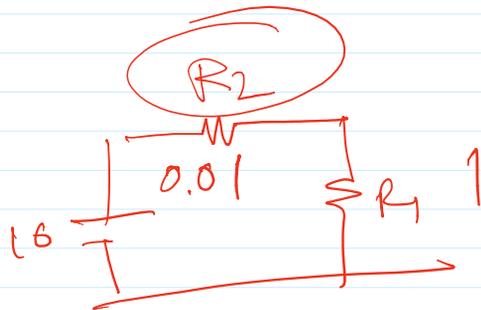

$$v_o = \frac{R_1}{R_1 + R_2} v_b$$


$$R_2 \rightarrow \infty$$

$$\frac{1}{\omega C} = \infty$$


$$A_{vA} = \frac{v_o}{v_b} = \frac{(1+\beta) I_b R_L'}{r_{\pi} I_b + (1+\beta) I_b R_L'}$$

$$= \frac{(1+\beta) R_L'}{r_{\pi} + (1+\beta) R_L'}$$

$$i_o = \frac{v_o}{R_L}$$

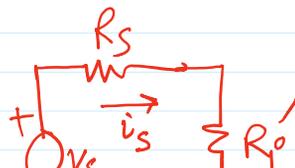

$$i_o = \frac{v_o}{R_L}$$

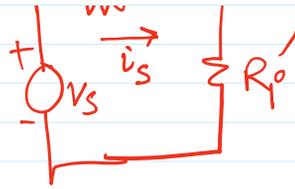

$$i_s = \frac{v_s}{R_s + R_o'}$$

$$\begin{aligned} \frac{i_o}{i_s} &= \frac{\frac{v_o}{R_L}}{\frac{v_s}{R_s + R_o'}} = \left(\frac{v_o}{v_s} \right) \frac{R_s + R_o'}{R_L} \\ &= A_v \frac{R_s + R_o'}{R_L} \\ &= A_{VA} \times \frac{R_o'}{R_s + R_o'} \times \frac{R_s + R_o'}{R_L} \\ &= A_{VA} \frac{R_o'}{R_L} \end{aligned}$$




$$= \frac{(1 + \beta) R_L'}{r_{\pi} + (1 + \beta) R_L'} \times \frac{R_o'}{R_L}$$

$$f_{L_{C_1}} = \frac{1}{2\pi C_1 (R_s + R_o')} \approx \left(\frac{R_o'}{R_L} \right)$$

$$f_{L_{C_2}} = \frac{1}{2\pi C_2 (R_o + R_L)}$$
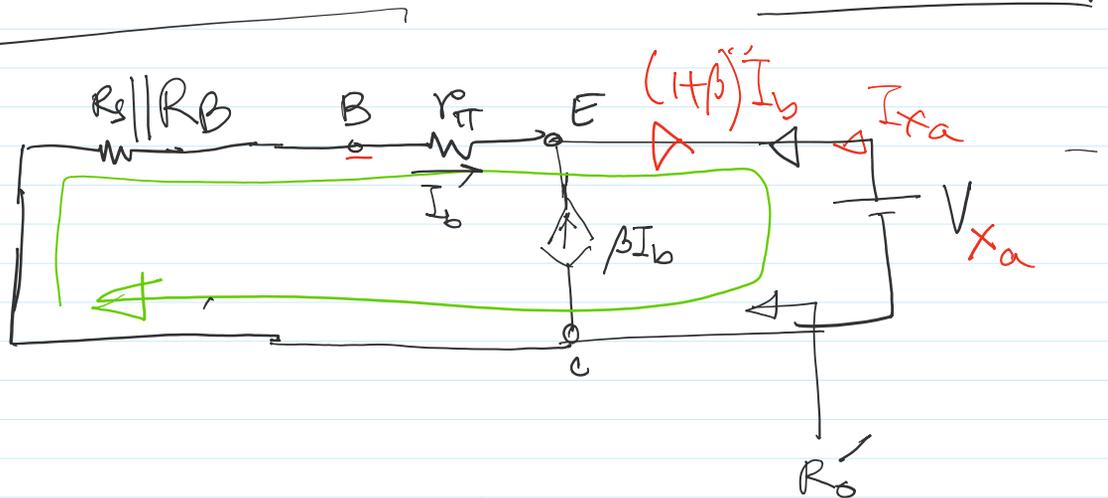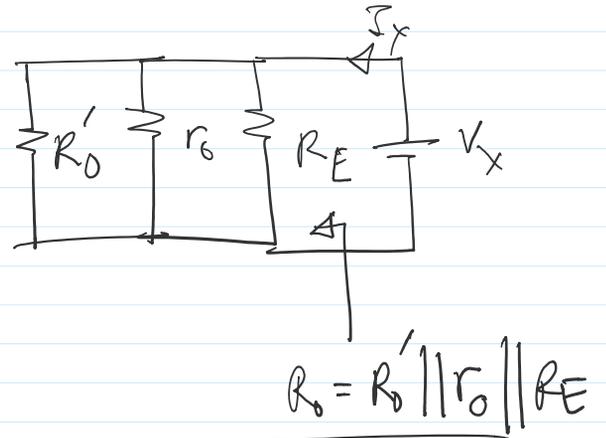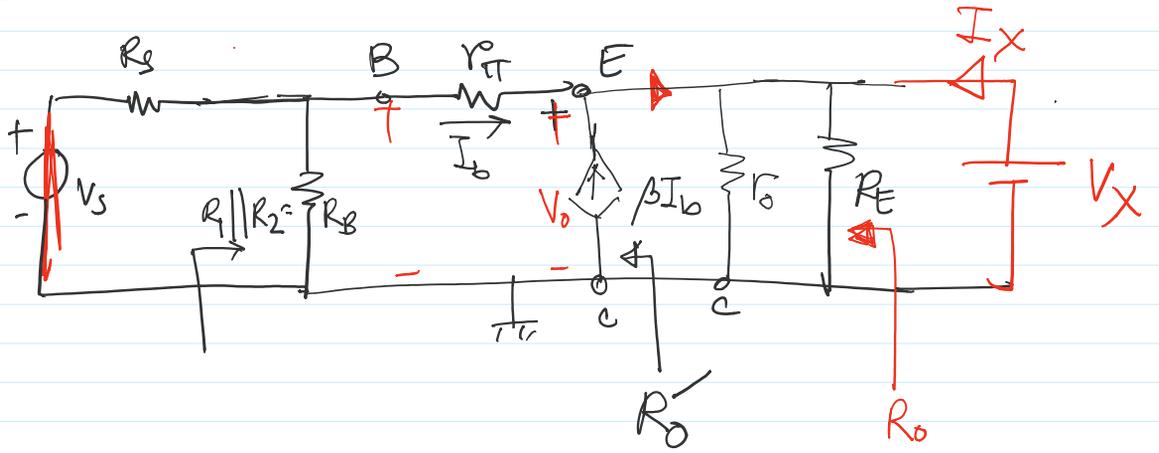
$$f_{H_{CL}} = \frac{1}{2\pi C_L R_o \parallel R_L}$$





$$I_{xa} = -(1+\beta) I_b$$

$$R'_o = \frac{V_{xa}}{I_{xa}}$$

$$R_s \parallel R_B I_b + r_{\pi} I_b + V_{xa} = 0$$

$$I_b = \frac{-V_{xa}}{(R_s \parallel R_B + r_{\pi})}$$

$$\therefore I_{x_a} = -(1+\beta) \left(- \frac{V_{x_a}}{R_S \parallel R_B + r_{\pi}} \right)$$

$$R_0' = \frac{V_{x_a}}{I_{x_a}} = \frac{R_S \parallel R_B + r_{\pi}}{(1+\beta)}$$

$$R_0 = R_0' \parallel R_E \parallel r_o$$