

Write down the corner or 3 dB frequency of common collector amplifier

1. f_H due to C_{C1}
2. f_{L2} " " C_2
3. f_H " " C_L

1.

$$\frac{v_O}{v_S} = \frac{R'_i}{R'_i + R_S} = \frac{r_{pi} + (1 + \beta) R_L'}{R'_i + R_S}$$

$$R'_i = R_1 || R_2 || R_i$$

$$f_H = \frac{1}{2\pi C_{C1} (R_S + R'_i)}$$

2.

$$f_{L2} = \frac{1}{2\pi C_2 (R_o + R_L)}$$

$$R_o = ?$$

3.

$$f_H = \frac{1}{2\pi C_L (R_o + R_L)}$$

$$R_o' = \left(\frac{R_S || R_B + r_{pi}}{(1 + \beta)} \right)$$

$$R_o = R_o' || R_E || R_o$$

① $R_S = 1K$, $R_1 = 160K$, $R_2 = 120K$, $R_E = 1K$
 $R_L = 5K$, $g_m = 40mA/V$, $r_{pi} = 3k\Omega$, $R_o = 100K$

CC Amplifier

$$\beta = g_m r_{pi} = 40_m \times 3k = \underline{\underline{120}}$$

Find

i) Midband voltage gain, dB

ii) " current gain dB

iii) $C_1 \& C_2$ for 20 Hz lower corner freq

iv) C_L for 20 kHz high corner freq


$$R_i' = r_i + (1+\beta)R_L'$$

$$= 3k + (121) \times 0.8264$$

$$= 102.99 \text{ k}\Omega$$

$$R_L' = R_L \parallel R_2 \parallel R_i' = \underline{\underline{41.16 \text{ k}\Omega}}$$

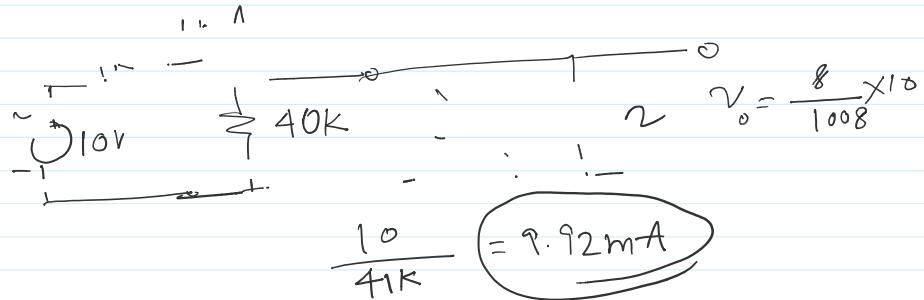
$$\begin{aligned} R_L' &= R_E \parallel r_o \parallel R_L = 1k \parallel 100k \parallel 5k \\ &= \underline{\underline{0.8264k}} \end{aligned}$$



$$\begin{aligned} R_o' &= \frac{R_S \parallel R_L \parallel R_2 + r_\pi}{(1+\beta)} = \frac{11160 \parallel 120 + 3}{121} \\ &= \underline{\underline{32.94 \Omega}} \end{aligned}$$

$$R_o = R_E \parallel r_o \parallel R_o' = 1k \parallel 100k \parallel \underline{\underline{32.94 \Omega}}$$
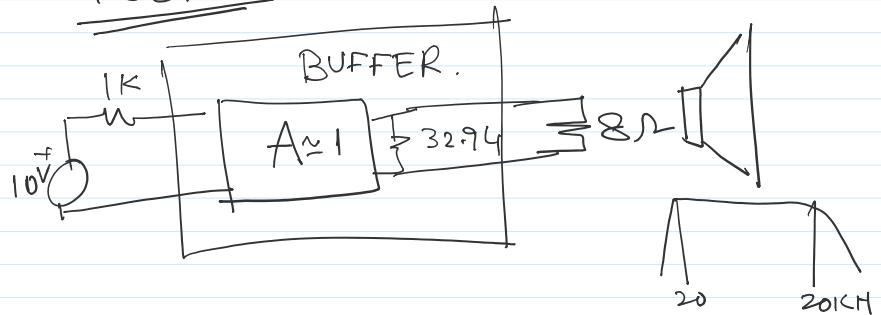
$$= \underline{\underline{31.88 \Omega}}$$



$$C_{C_1} = 0.188 \mu\text{F}$$

$$C_{C_2} = 1.58 \mu\text{F}$$

$$Q = 0.251 \mu F$$

$$A_{VA} = \frac{(1+\beta)R_L}{R_T + (1+\beta)R_L} = \frac{(1+\beta)R_L'}{R_0} = \frac{121 \times 1k || 100k || 5k}{102.91k} = 0.97$$

$$A_V = A_{VA} \times \frac{R_0}{R_{STRG}} = 0.97 \times \frac{41.16k}{1k + 41.16k} = 0.95$$

$$20 \log_{10}(0.95) = -0.47 \underline{\underline{dB}}$$



$$A_L = \frac{i_o}{i_s} = \frac{\frac{v_o}{R_L}}{\frac{v_s}{R_s + R_f}} = A_v \times \frac{\frac{v_o}{v_s} \cdot \frac{(R_s + R_f)}{R_L}}{R_s + R_f}$$

$$= 0.95 \times \frac{1K + 41.16K}{5K}$$



$$= 8.01$$

$$Ai|_{dB} = 18.1 \underline{dB}$$

Common Drain Amplifier circuit

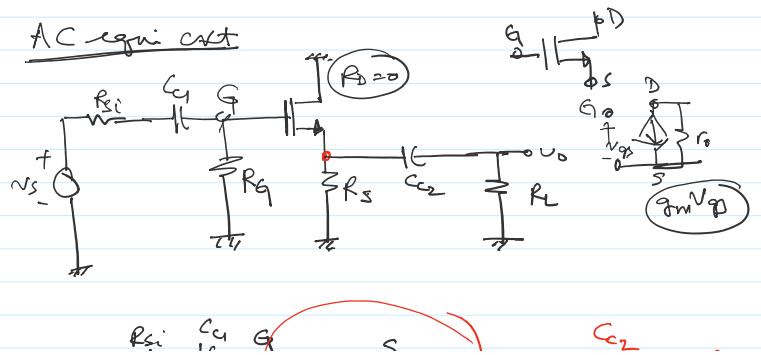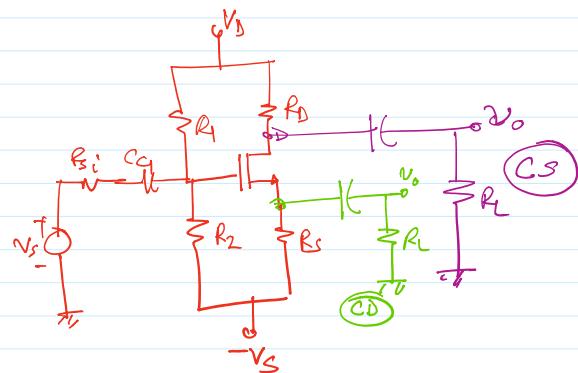

4

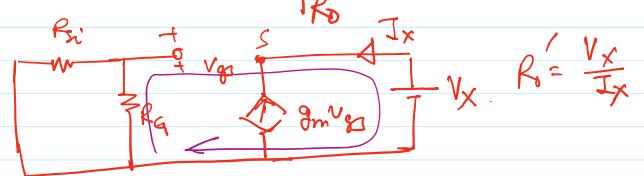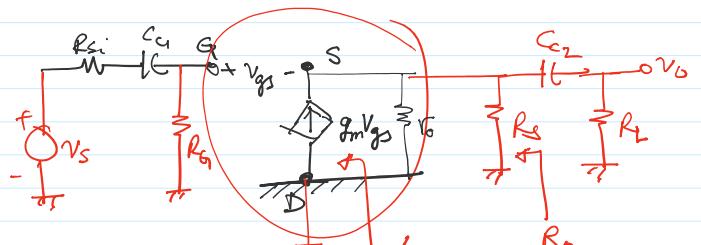

$$I_X = -g_m v_{gs}$$

$$R_G \times 0 + v_{gs} + v_X = 0$$

$$v_{gs} = -v_X$$

$$\therefore I_X = g_m v_X$$

$$R'_D = \frac{V_X}{I_X} = \frac{1}{g_m}$$

$$v_o = g_m v_{gs} \times r_0 \parallel R_s \parallel R_L$$

$$v_g = v_{gs} + g_m v_{gs} r_0 \parallel R_s \parallel R_L$$

$$A_{v_A} = \frac{v_o}{v_g} = \frac{g_m R'_L}{(1 + g_m R'_L)}$$