

Consider transconductance feedback amplifier. (i) Find A_{gf} , R_{if} and R_{of} if open loop voltage gain is $A_v = 10^5$, $R_i = 10K$, $R_o = 5K$. Feedback $\beta_2 = 0.9$. (ii) If the bandwidth of the FB amplifier is $10KHz$, find the open loop bandwidth. (iii) If FB amplifier gain variation is 1% , find the open loop gain variation.

$$A_{gf} = \frac{A_g}{1 + \beta_2 A_g}$$

$$R_{if} = R_i (1 + \beta_2 A_g)$$


$$R_{of} = R_o (1 + \beta_2 A_g)$$

$$A_g = \frac{I_o}{V_i} \quad A_o = \frac{V_o}{V_i} = \frac{I_o R_o}{V_i} = A_g R_o$$


$$= \frac{A_v}{R_o} = \frac{10^5}{5K}$$

$$\# f_{4f} = f_H (1 + \beta_2 A_g)$$
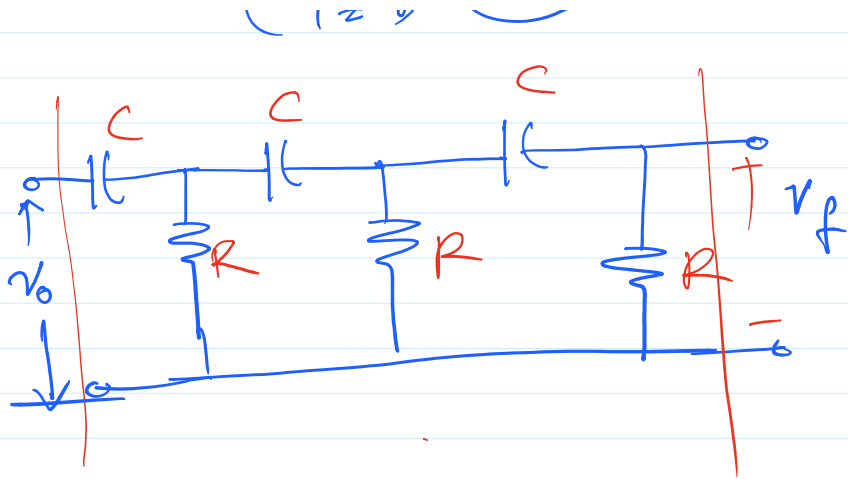
$$\# \frac{dA_f}{A_f} = \frac{1}{(1 + \beta_2 A_g)} \left(\frac{dA}{A} \right)$$



$$H(s) = \frac{V_f(s)}{V_0(s)}$$

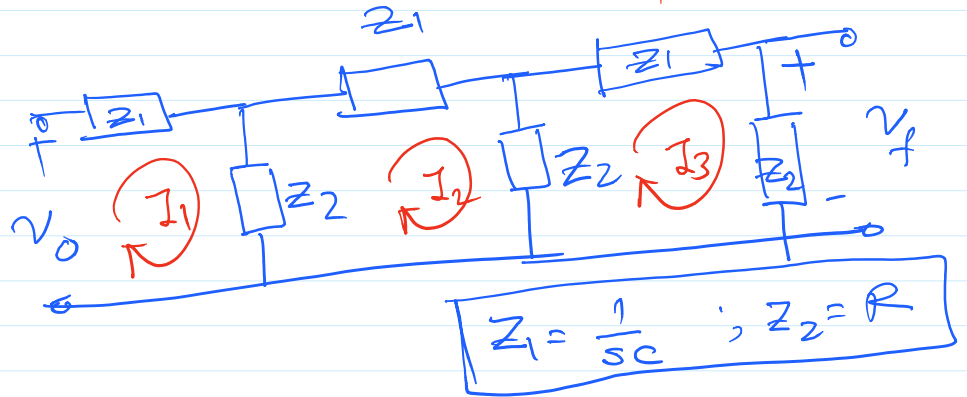

$$V_f = I_3 Z_2$$

$$-v_0 + Z_1 I_1 + Z_2 (I_1 - I_2) = 0$$

$$Z_2 (I_2 - I_1) + Z_1 I_2 + Z_2 (I_2 - I_3) = 0$$

$$Z_2 (I_3 - I_2) + Z_1 I_3 + Z_2 I_3 = 0$$

$$\begin{bmatrix} (Z_1 + Z_2) & -Z_2 & 0 \\ -Z_2 & (Z_1 + 2Z_2) & -Z_2 \\ 0 & -Z_2 & (Z_1 + 2Z_2) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} v_0 \\ 0 \\ 0 \end{bmatrix}$$

$$I_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta_3 = \begin{vmatrix} z_1+z_2 & -z_2 & V_0 \\ -z_2 & (z_1+2z_2) & 0 \\ 0 & -z_2 & 0 \end{vmatrix} = V_0 (-z_2) (-z_2) \\ = V_0 z_2^2$$

$$\Delta = \begin{vmatrix} z_1+z_2 & -z_2 & 0 \\ -z_2 & (z_1+2z_2) & -z_2 \\ 0 & -z_2 & (z_1+2z_2) \end{vmatrix}$$

$$= (z_1+z_2)(z_1+2z_2)^2 - z_2^2(z_1+z_2) - z_2^2(z_1+2z_2)$$

$$= (z_1+z_2) \left[(z_1+2z_2)^2 - z_2^2 \right] - z_2^2(z_1+2z_2)$$

$$= (z_1+z_2) \left[z_1^2 + 4z_1z_2 + 3z_2^2 - z_2^2 \right] - z_2^2(z_1+2z_2)$$

$$= z_1^3 + 4z_1^2z_2 + 3z_1z_2^2 + z_1z_2^2 + 4z_1z_2^2 + 3z_2^3 - z_1z_2^2 - 2z_2^3$$

$$+ (z_1 z_2) + (z_1 z_2) + 0 z_2^3 - z_2 z_1 - 2 z_2^3$$

$$= z_1^3 + 5 z_1^2 z_2 + 6 z_1 z_2^2 + z_2^3$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{V_0 z_2^2}{z_1^3}$$

$$\therefore \frac{V_f}{V_0} = I_3(z_2) = \frac{z_2^3}{z_1^3 + 5 z_1^2 z_2 + 6 z_1 z_2^2 + z_2^3}$$

$$\frac{V_f(s)}{V_0(s)} = \frac{R^3}{\left(\frac{1}{sC}\right)^3 + 5 \left(\frac{1}{sC}\right)^2 R + 6 \frac{1}{sC} R^2 + R^3}$$

$$= \frac{s^3 R^3 C^3}{1 + 5 s C R + 6 C^2 s^2 R^2 + C^3 R^3 s^3}$$