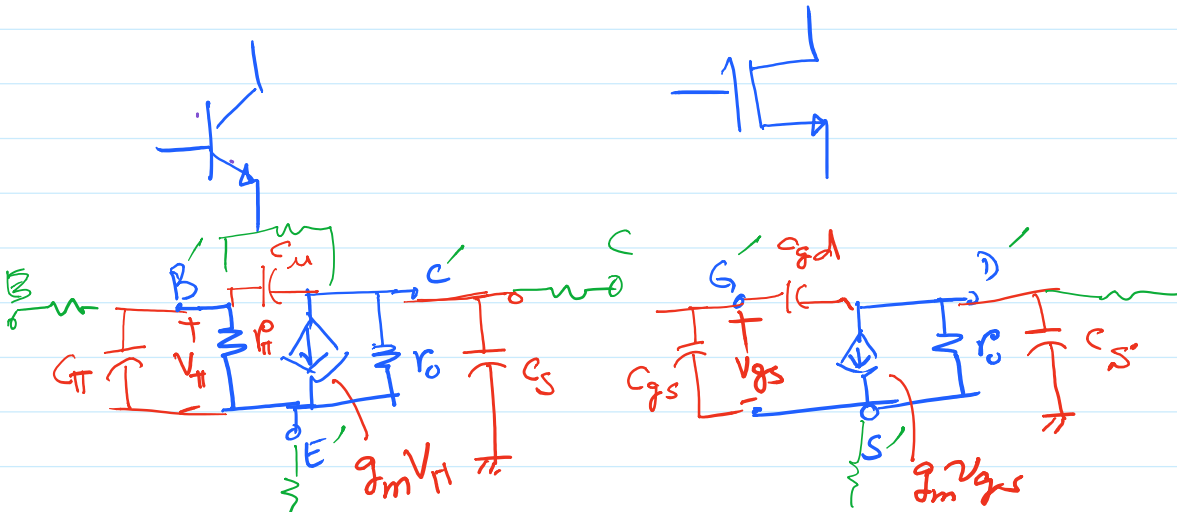




High Frequency Model

Thursday, March 2, 2017 2:34 PM






Simplified High frequency equivalent ckt diagram

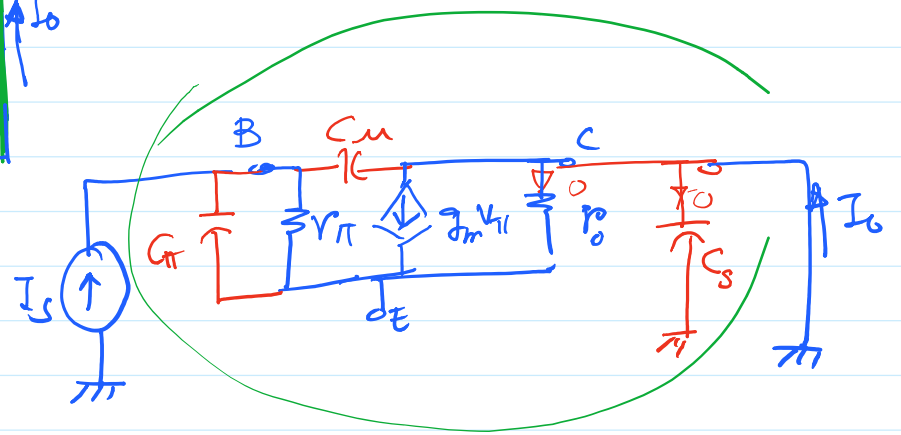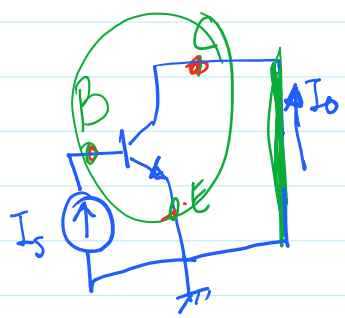Draw the simplified high frequency equivalent circuit diagram and find the short circuit current gain.



$$A_{I|sc} = \frac{I_o}{I_s}$$

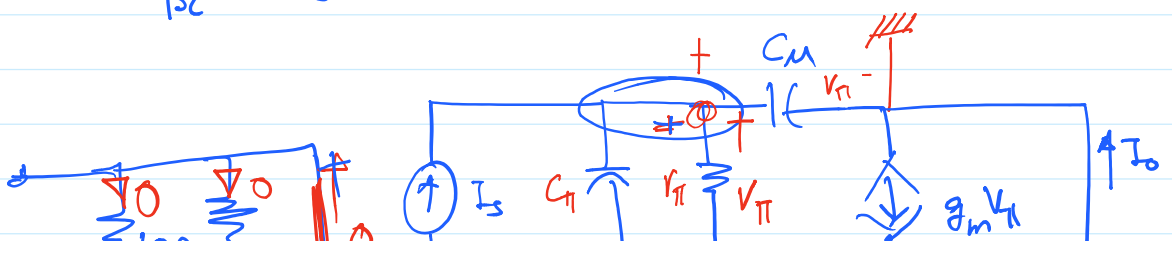

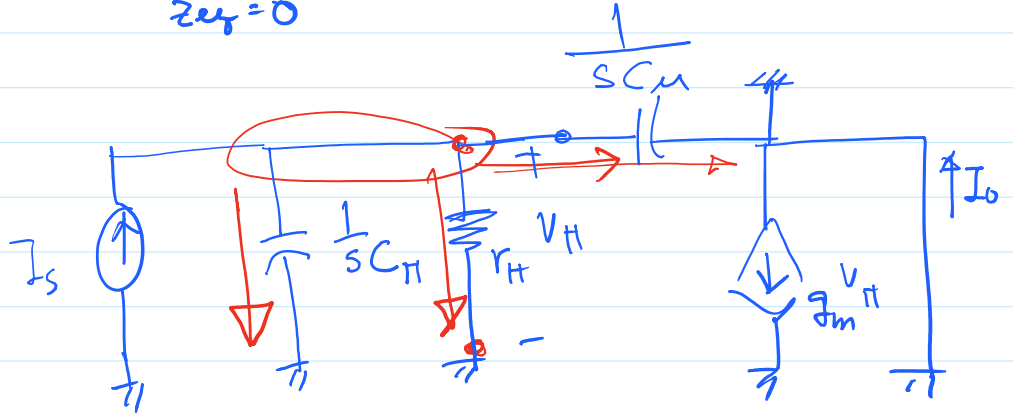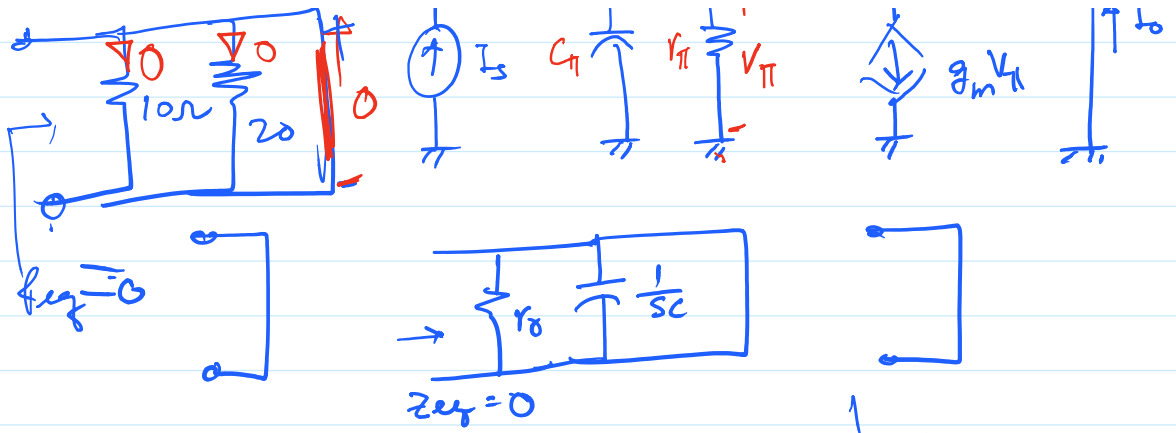

$$I_s = \frac{V_\pi}{1/sC_\pi} + \frac{V_\pi}{r_\pi} + \frac{V_\pi}{1/sC_\mu}$$

$$= sV_\pi [C_\pi + C_\mu] + \frac{V_\pi}{r_\pi}$$

$$= \frac{V_\pi}{r_\pi} \left[1 + sr_\pi (C_\pi + C_\mu) \right]$$

$$I_o = g_m V_\pi - \frac{V_\pi}{1/sC_\mu}$$

$$= V_\pi [g_m - sC_\mu]$$

$$A_I \Big|_{f=0} = \frac{I_o}{I_s} = \frac{V_\pi [g_m - sC_\mu]}{V_\pi [1 + sr_\pi (C_\pi + C_\mu)]}$$

$$A_I \Big|_{sc} = \frac{v_o}{I_s} = \frac{\cancel{v_{\pi}}}{r_{\pi}} \left[1 + s r_{\pi} (C_{\mu} + C_{\pi}) \right]$$

$$= \frac{\beta \cancel{r_{\pi}} g_m - s r_{\pi} C_{\mu}}{1 + s r_{\pi} (C_{\mu} + C_{\pi})}$$

$r_{\pi} g_m \gg s r_{\pi} C_{\mu}$


$$A_I \approx \frac{\beta}{1 + s r_{\pi} (C_{\mu} + C_{\pi})}$$


$g_m \gg C_{\mu}$

$$A_I = \frac{\beta}{1 + s \tau}$$

$$\tau = r_{\pi} (C_{\mu} + C_{\pi})$$
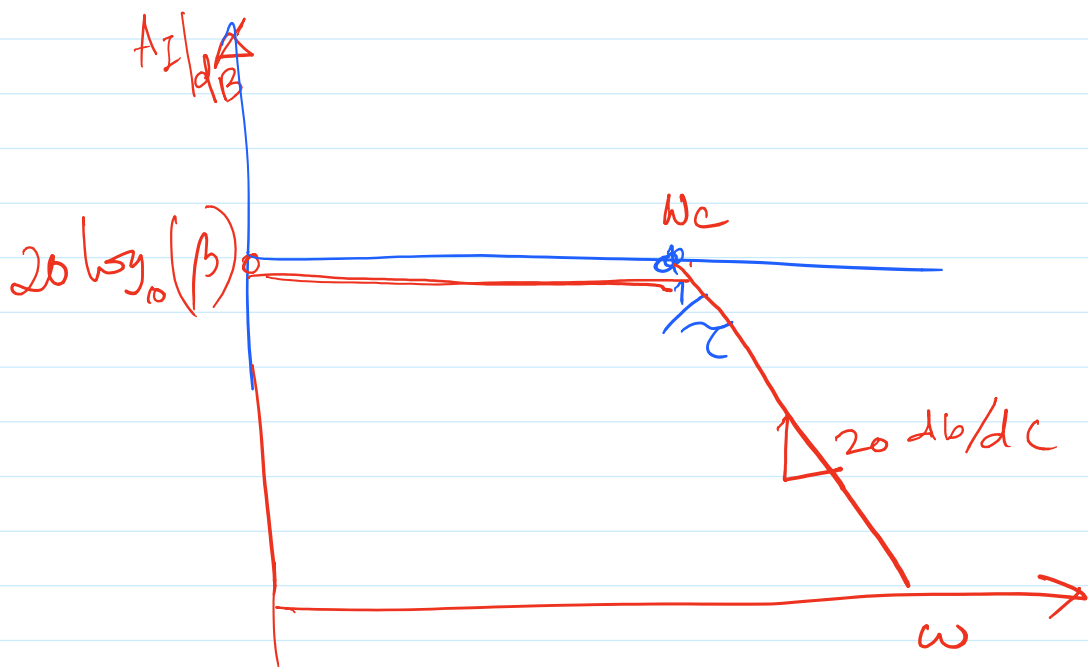
$$\omega_c = \frac{1}{\tau} = \frac{1}{r_{\pi} (C_{\mu} + C_{\pi})}$$



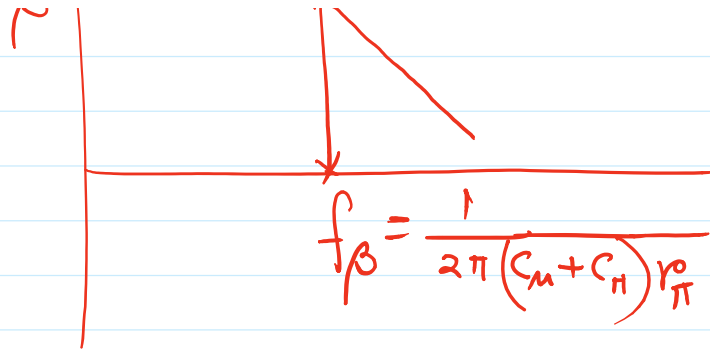
$$f_{\beta} = \frac{1}{2\pi(C_u + C_n) \frac{R_o}{\pi}}$$