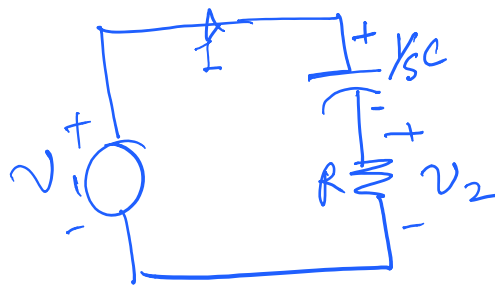


$$I = \frac{V_1}{R_1 + R_2}$$



$$I = \frac{\bar{V}_1}{R + \frac{1}{j\omega C}}$$


$$= \frac{\bar{V}}{R - j \frac{1}{\omega C}}$$

$$I = \frac{\bar{V}}{|Z| \angle -\theta_1}$$


$$= \frac{|\bar{V}| \angle \theta}{|Z| \angle -\theta_1}$$

$$I = \frac{|\bar{V}|}{|Z|} \angle \theta + \theta_1$$


$$\tan \theta = \frac{1}{\omega CR}$$

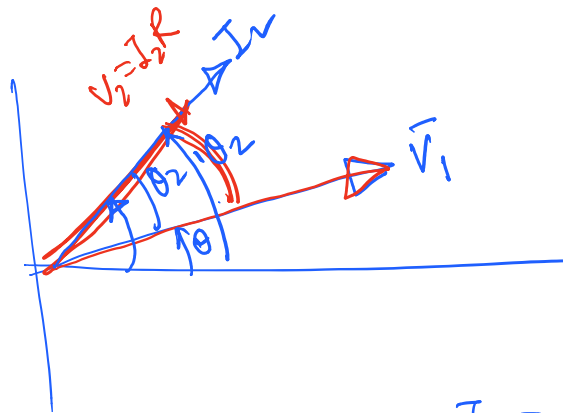




$$V_1 = 20 \angle 0$$

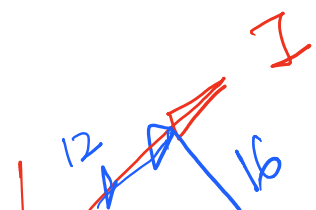

$$Z = 3 - j4 = 5 \angle -53.13^\circ$$

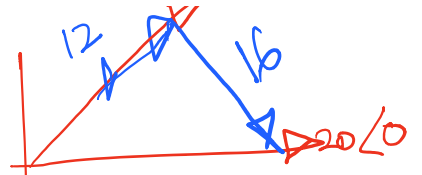

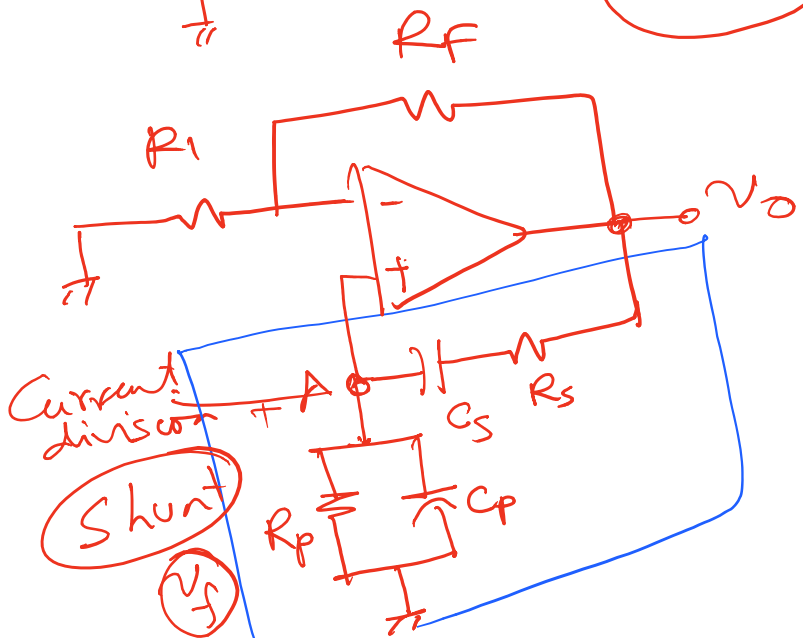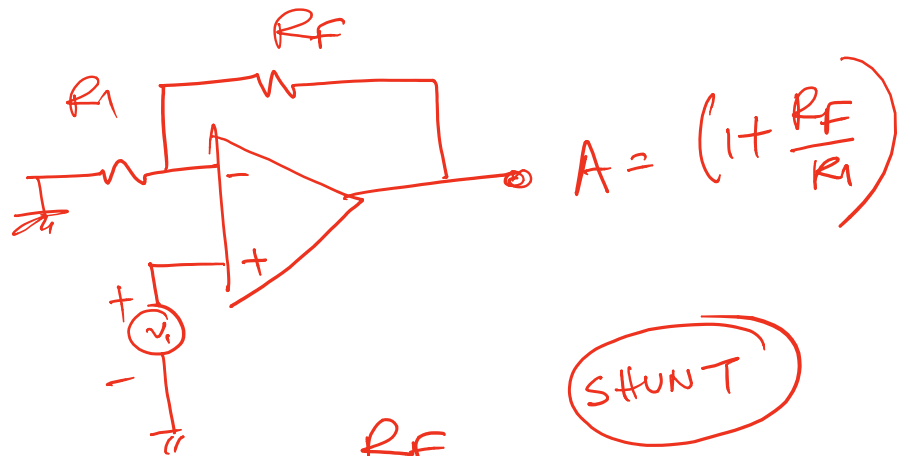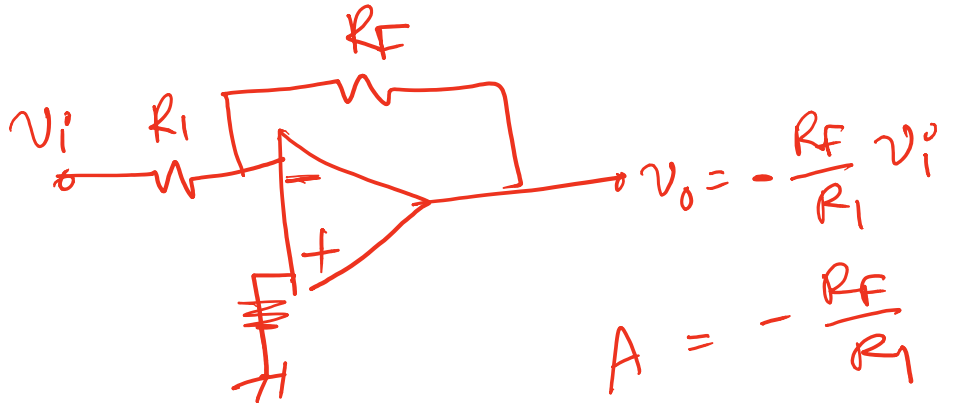
$$I = \frac{V}{Z} = 4 \angle 53.13^\circ$$



$$A\beta = 1 + j\omega$$

$$A = \left(1 + \frac{R_F}{R_1}\right)$$

$$\beta = \frac{v_f}{v_o}$$

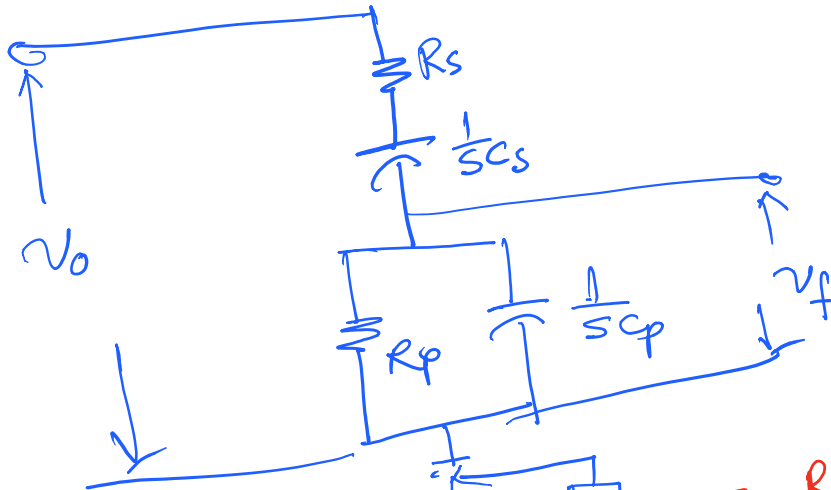

$$Z_p + Z_s$$

$$= \frac{1 + R_s C_s s}{s C_s} + \frac{R_p}{1 + s C_p R_p}$$

$$Z_s = R_s + \frac{1}{s C_s} = \frac{1 + R_s C_s s}{s C_s}$$

$$v_f = R_p \parallel \frac{1}{s C_p} = \frac{R_p \frac{1}{s C_p}}{R_p + \frac{1}{s C_p}}$$


$$= \frac{R_p}{1 + s C_p R_p}$$

$$\text{Let } R_s = R_p = R$$

$$C_s = C_p = C$$

$$Z_p + Z_s = \frac{(1 + R C s)^2 + s R C}{s C (1 + s C R)}$$

$$Z_p + Z_s =$$

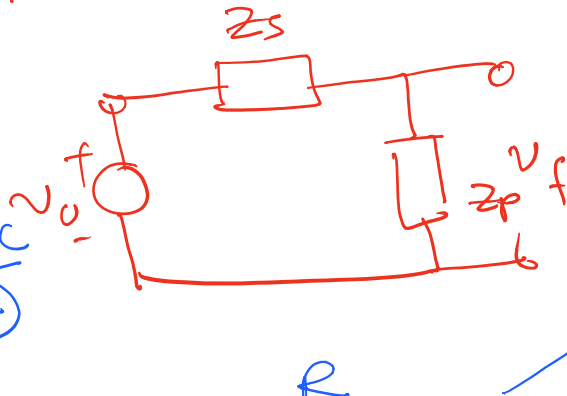

$$Z_p + Z_s = \frac{1}{sC(1+sCR)}$$

$$\beta^2 \frac{Z_p}{Z_p + Z_s} = \frac{\frac{R}{1+sCR}}{\frac{(1+RCs)^2 + sRC}{sC(1+sCR)}}$$

$$= \frac{RSC}{(1+RCs)^2 + sRC}$$

$$= \frac{RSC}{1 + R^2C^2s^2 + 2RCs + sRC}$$

$$= \frac{RSC}{1 + 3RCs + R^2C^2s^2}$$

Loop gain

$$A\beta = \left(1 + \frac{R_F}{R}\right) \left(\frac{RSC}{1 + 3RCs + R^2C^2s^2}\right)$$

$$s = j\omega$$

$$A\beta = \left(1 + \frac{R_F}{R}\right) \left[\frac{j\omega RC}{1 + 3j\omega RC - \omega^2 CR^2}\right]$$

$$= \left(1 + \frac{R_F}{R}\right) \left[\frac{j\omega RC}{(1 - \omega^2 CR^2) + j3\omega RC}\right] = 1 + j0$$

$$1 - \omega_0^2 CR^2 = 0$$

$$\omega_0 = \frac{1}{RC}$$

$$a + j(c+d) = 1 + j0$$

$$\omega_0 = \frac{1}{RC}$$
$$f_0 = \frac{1}{2\pi RC}$$

$$\frac{+j(c+d)}{B + jE} = 1 + j0$$

$$\left(1 + \frac{R_F}{R_1}\right) \left[ \frac{\cancel{3\omega_0 RC}}{(1 - \cancel{\omega_0 RC}) + j\cancel{3\omega_0 RC}} \right] = 1$$

$\downarrow$   
0

$$\left(1 + \frac{R_F}{R_1}\right) \cdot \frac{1}{3} = 1$$

$$\therefore \underline{\underline{\left(1 + \frac{R_F}{R_1}\right) = 3}}$$

Min Amplified gain is 3

1kHz,

Let  $C = 0.1 \mu F$

$$f_0 = \frac{1}{2\pi RC}$$

$$R = \frac{1}{2\pi f_0 C} = \frac{1}{2\pi \times 1k \times 0.1M}$$

$R_1, R_F$

$$\frac{R_F}{R_1} = 3 - 1 = 2$$

$$R_i = 10\text{K}, \quad R_F = 20\text{K}$$


$$T(s) = \frac{10^3 \cdot s \cdot \left(1 + \frac{s}{100}\right)}{\left(1 + \frac{s}{10}\right) \left(1 + \frac{s}{50}\right)}$$


$$\omega = 70 \text{ rad/sec}$$

$$\theta = 90^\circ + \tan^{-1} \frac{\omega}{100} - \tan^{-1} \frac{\omega}{10} - \tan^{-1} \frac{\omega}{50}$$

$$T\left(\frac{\omega}{70}\right) = \frac{10^3 \times 70}{\left(1 + \frac{70}{10}\right) \left(1 + \frac{70}{50}\right)}$$

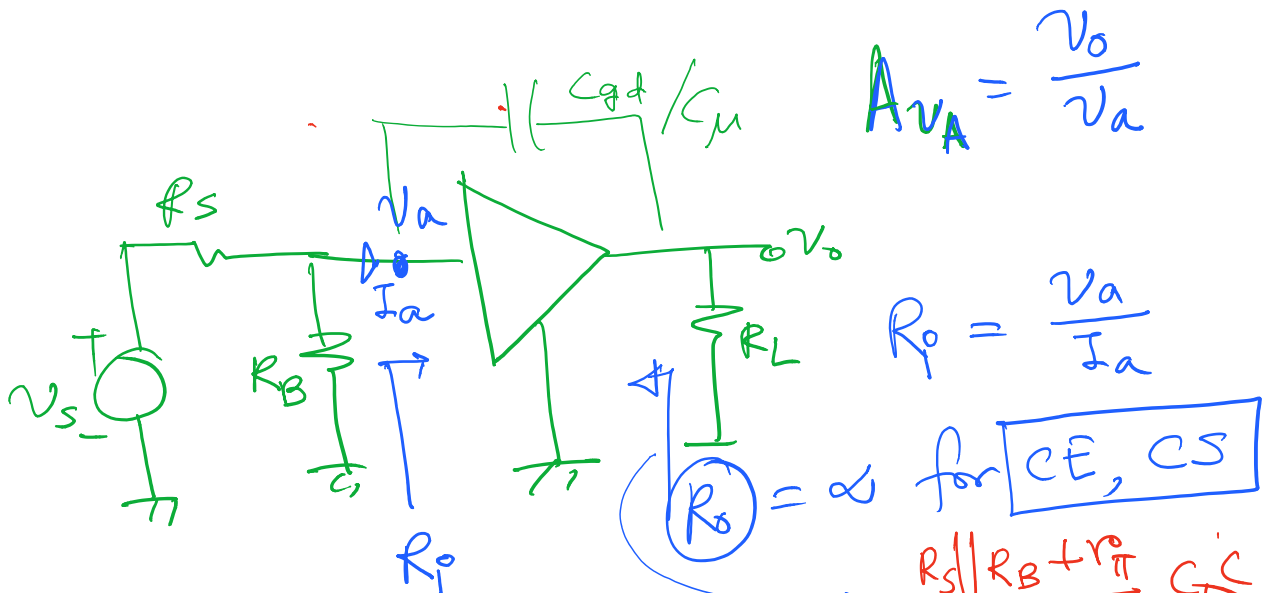
$$T(\omega = 50) = \frac{10^3 + 50}{\left(\frac{50}{10}\right)}$$



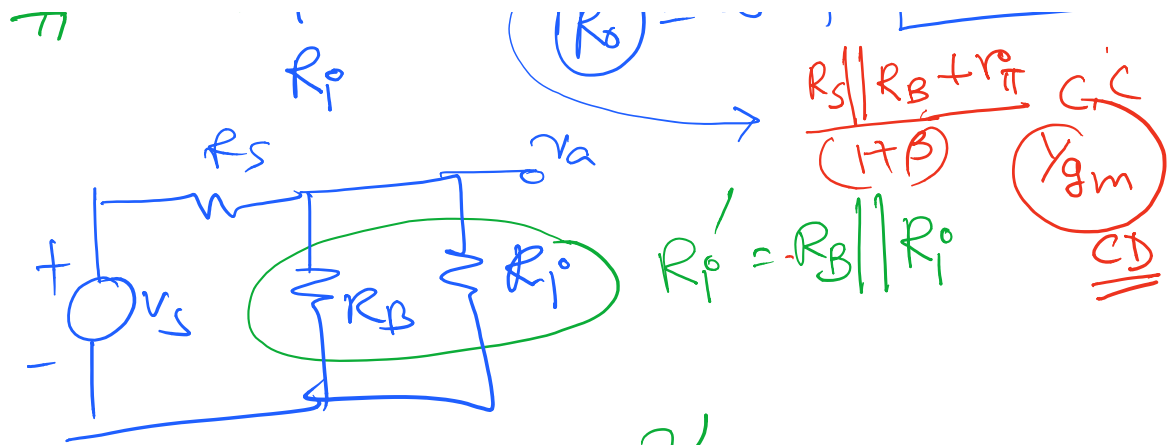

$$A_v = A_{vA} \times \frac{v_a}{v_s}$$
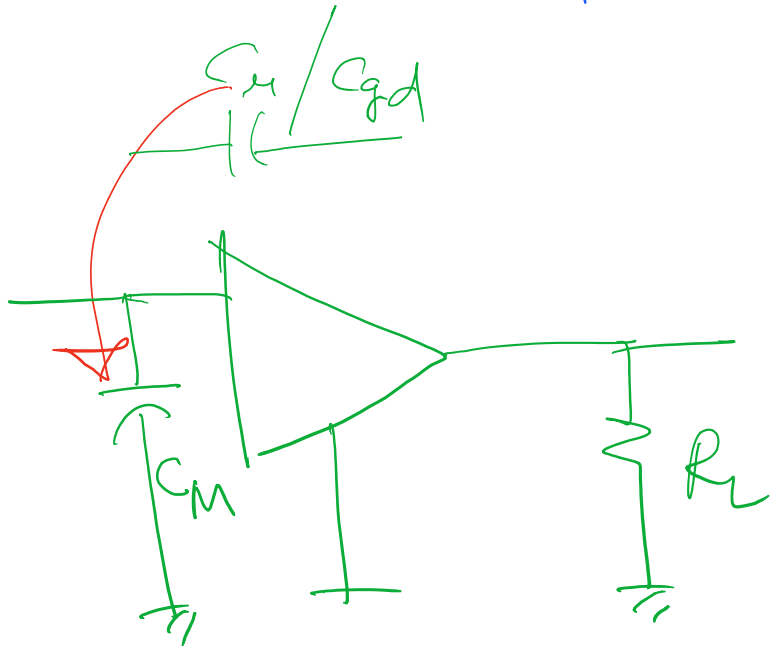
$$= A_{vA} \times \frac{R_o}{R_o + R_s}$$



$$C_M = C_M [1 + |A_{vA}|]$$

$$C_{gd} [1 + |A_{vA}|]$$

$$f_L = \frac{1}{2\pi (R_S + R_i^{\uparrow}) C_{C1}}$$

$$f_L = \frac{1}{2\pi (R_L + R_o^{\downarrow}) C_{C2}}$$

$$f_H = \frac{1}{2\pi R_L^{\downarrow} C_L} \quad R_L^{\downarrow} = R_o \parallel R_L$$

$$f_{HM} = \frac{1}{2\pi R_S \parallel R_i^{\uparrow} \times C_T} \rightarrow C_T = C_M + C_T = \underline{\underline{C_M + C_{GS}}}$$