

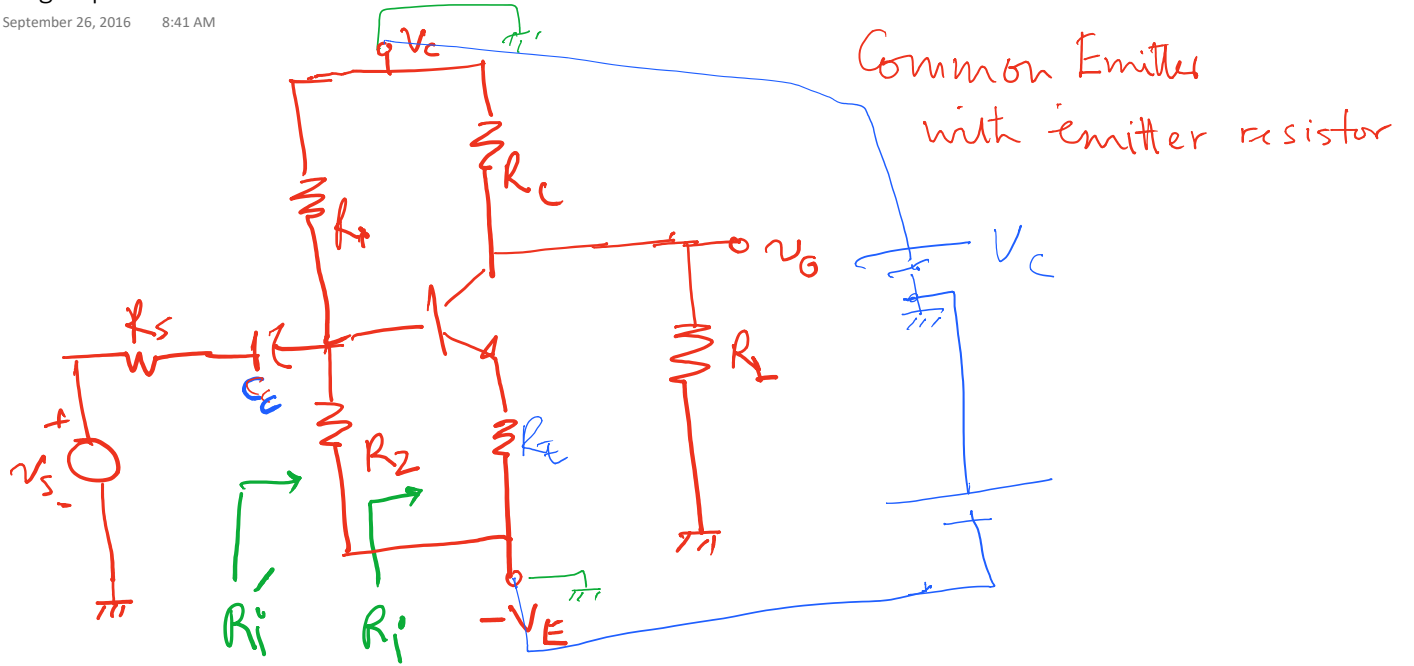


Coupling Capacitor Effects

Monday, September 26, 2016 8:41 AM

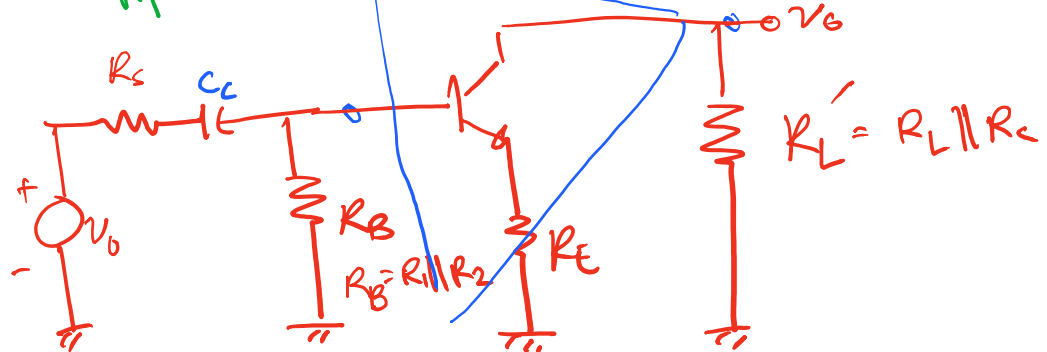


AC equivalent circuit

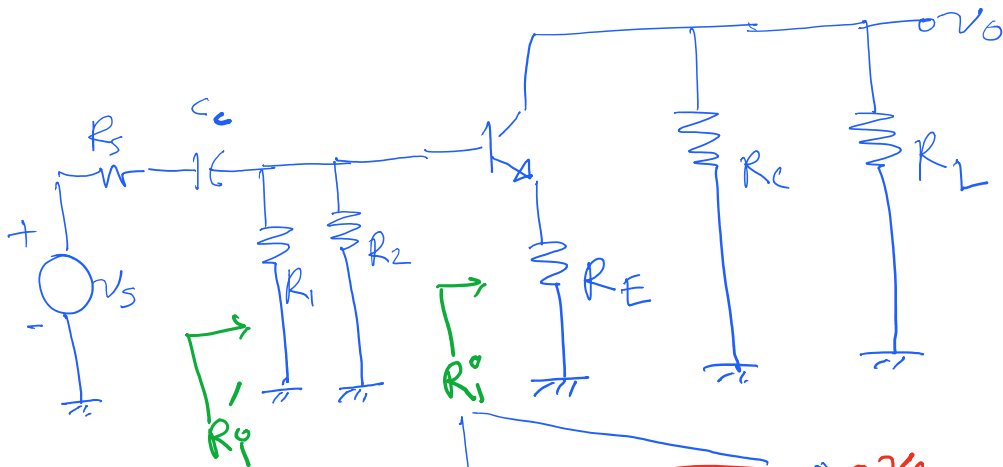


- ① Find the gain at low frequency
- ② Find the gain at midband frequency

Find the maximum gain.

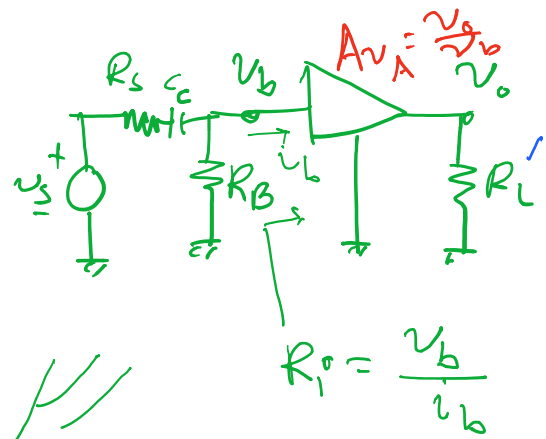

$$\tau = (R_s + R_i') C_c$$


$$f_L = \frac{1}{2\pi\tau}$$

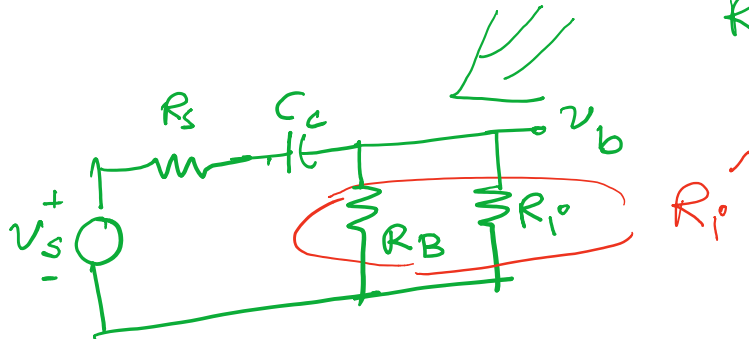


$$A_v = \frac{v_o}{v_s} = \frac{v_o}{v_b} \cdot \frac{v_b}{v_s} = A_{vA} \times \frac{v_b}{v_s}$$

$$\frac{v_b}{v_s} = \frac{R_i'}{R_s + R_i' - j\omega C_c} = \frac{R_i'}{R_s + R_i' + \frac{1}{sC_c}}$$

$$\left. \frac{v_b}{v_s} \right|_{\text{midband}} = \frac{R_i'}{R_s + R_i'}$$

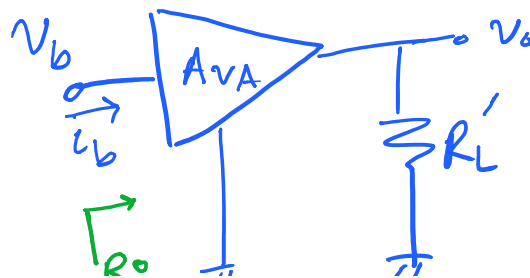

$$A_{vA} = \frac{v_o}{v_b}$$

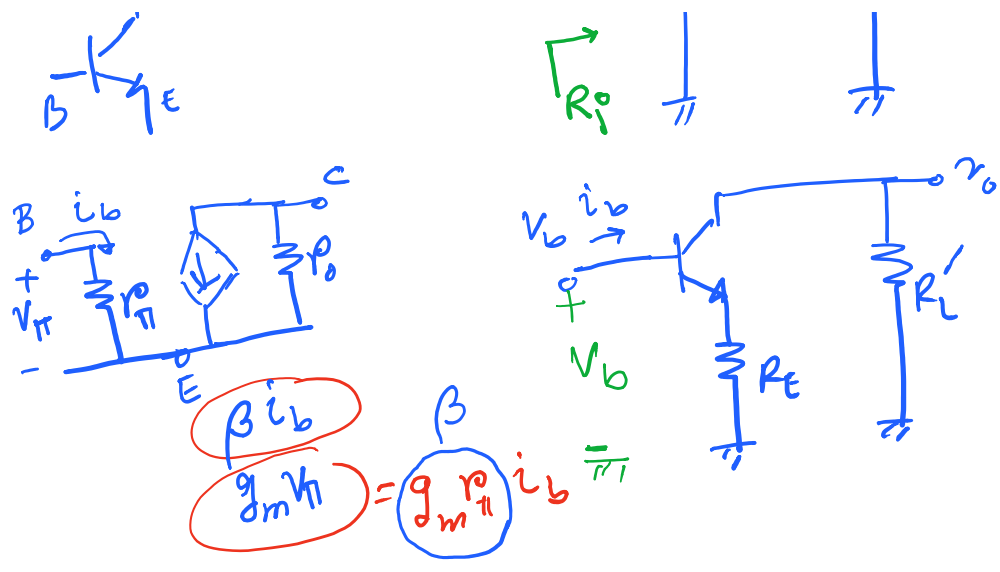

$$\beta i_b = g_{m\pi} v_{\pi} = g_{m\pi} r_{\pi} i_b$$


$$r_o = \infty$$

$$A_{vA} = \frac{v_o}{v_b}$$

$$= \frac{-\beta I_b R_L'}{[r_{\pi} + (1+\beta)R_E] I_b}$$

$$= \frac{-\beta R_L'}{r_{\pi} + (1+\beta)R_E}$$

$$A_{vA} \Big|_{R_E=0} = -\frac{\beta R_L'}{r_{\pi}}$$

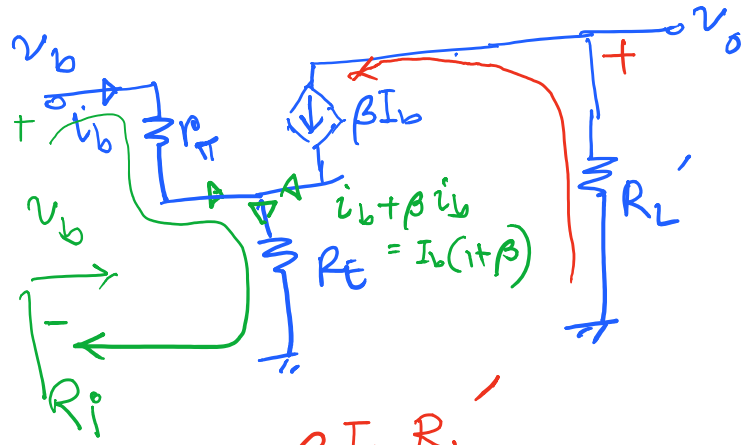

$$v_o = -\beta I_b R_L'$$

$$v_b = I_b r_{\pi} + (1+\beta) I_b R_E = (r_{\pi} + (1+\beta)R_E) I_b$$

$$R_i = \frac{v_b}{I_b} = r_{\pi} + (1+\beta)R_E$$

20.1

20.1

$$R_E = 0$$

$$A_{vA} |_{R_E \neq 0} = \frac{-\beta R_L'}{r_{\pi} + (1+\beta)R_E}$$


$$\approx \frac{-\beta R_L'}{(1+\beta)R_E} \approx \left(-\frac{R_L'}{R_E} \right) \quad \beta \gg 1$$

$$A_v = A_{vA} \cdot \frac{v_b}{v_s}$$


Lowfreq


$$= \frac{-\beta R_L'}{r_{\pi} + (1+\beta)R_E} \times \frac{R_i'}{R_i' + R_s + \frac{1}{sC_c}}$$

$$A_v |_{\text{midband}} = \frac{-\beta R_L'}{r_{\pi} + (1+\beta)R_E} \times \frac{R_i'}{R_i' + R_s}$$

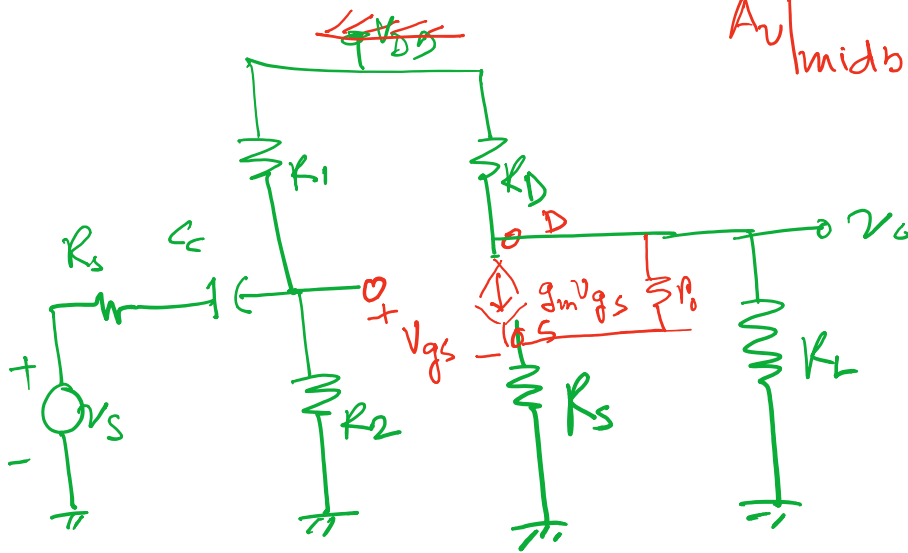

$$v_o = \infty$$

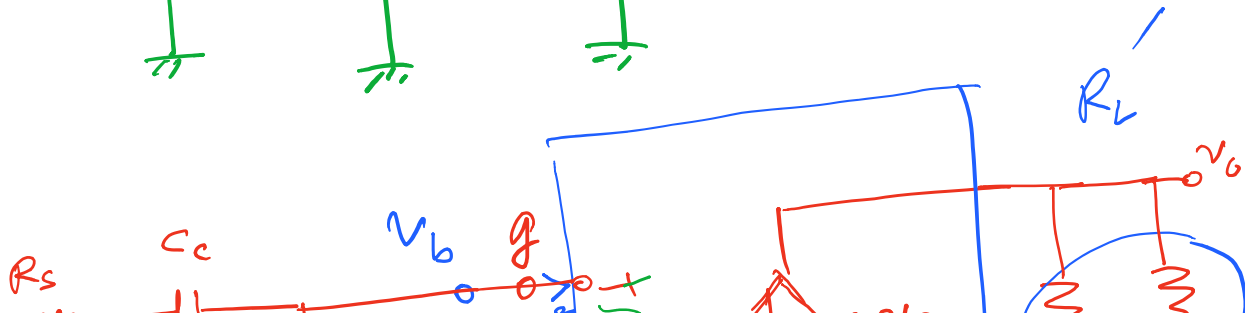

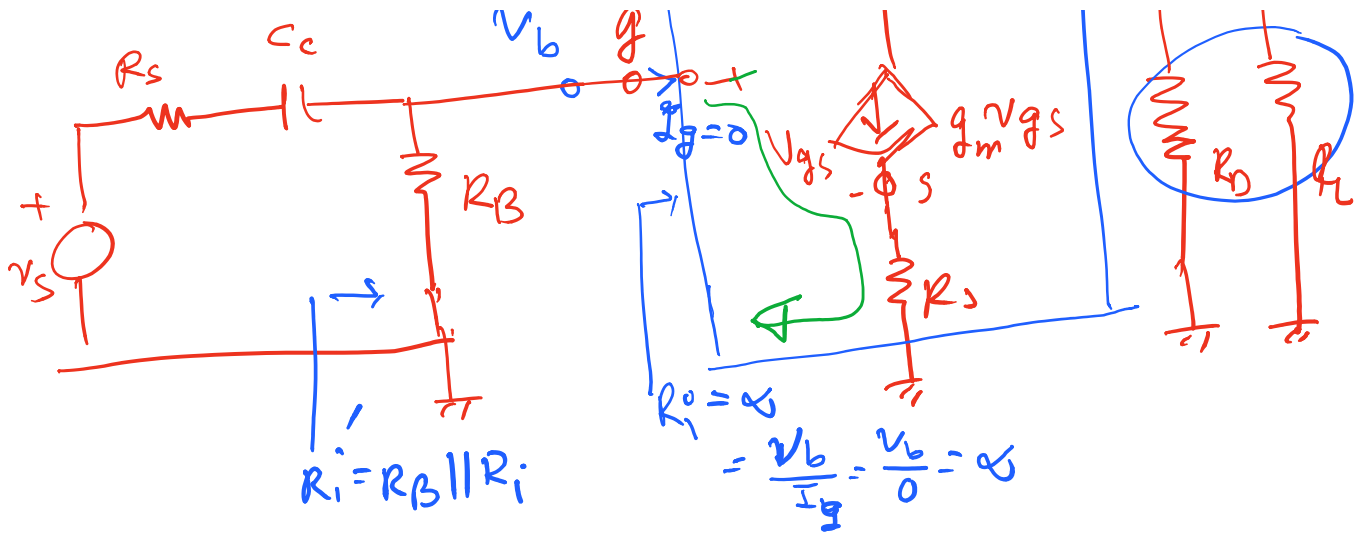

$$R_i = R_B \parallel R_i$$

$$= R_B$$

$$R_o = \infty = \frac{v_b}{i_b} = \frac{v_b}{0} = \infty$$

$$A_{vA} = \frac{v_o}{v_b} =$$

$$\frac{-g_m v_{gs} R_L'}{v_{gs} + g_m v_{gs} R_s}$$

$$[R_L' = R_D \parallel R_L]$$

$$= \frac{-g_m R_L'}{(1 + g_m R_s)}$$