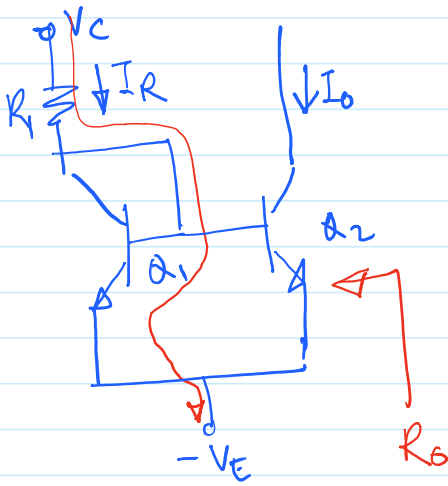


Two Transistor Biasing Circuit



$$I_o = \frac{I_R}{1 + \frac{2}{\beta}}$$


$$V_A = \infty$$

$$r_o = \infty$$

$$R_1 = \frac{V_c + V_E - V_{BE}}{I_R}$$

$V_A \neq \infty$
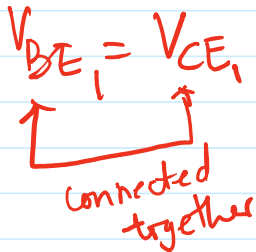
$$I_c = I_s \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$




$$\frac{I_{c2}}{I_{c1}} = \frac{1 + \frac{V_{CE2}}{V_A}}{1 + \frac{V_{BE1}}{V_A}}$$

$$R_o = r_{o2} = \frac{V_A}{I_{c2}}$$


$$I_o = 5 \mu A$$

$$I_R = 5.1 \mu A$$

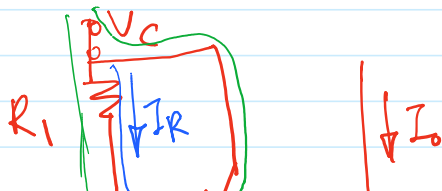Modified Circuit : 3-Transistor Biasing Circuit



Identical β

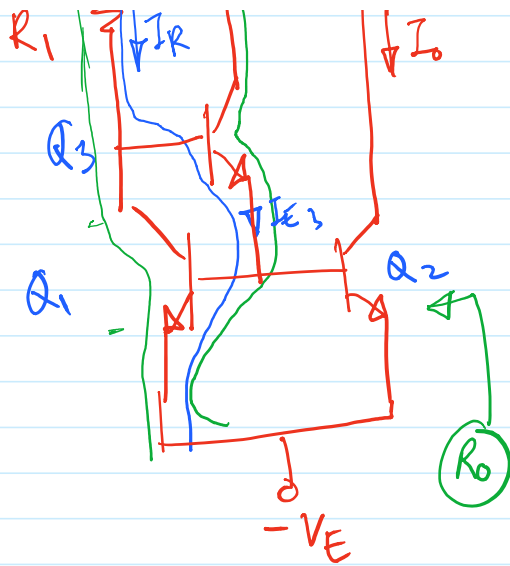

identical β

Formulate the relationship between I_R and I_O and design the circuit

$$V_C = I_R R + V_{BE} + V_{BE} - V_E$$

$$\therefore R = \frac{V_C + V_E - 2V_{BE}}{I_R}$$

$$I_{C1} = I_{C2} = I_O$$

$$[V_{BE1} = V_{BE2}, I_{B1} = I_{B2}, I_{C1} = I_{C2}]$$

$$I_R = I_{C1} + I_{B3}$$

$$I_{E3} = (1 + \beta) I_{B3}$$

$$I_{E3} = I_{B1} + I_{B2} = 2I_{B1} \\ = (1 + \beta) I_{B3}$$

$$I_{B3} = \frac{2I_{B1}}{(1 + \beta)}$$

$$I_R = I_{C1} + \frac{2I_{B1}}{(1 + \beta)}$$

$$= I_{C1} + \frac{2I_{C1}}{\beta(1 + \beta)}$$

$$= I_{C1} \left[1 + \frac{2}{\beta(1 + \beta)} \right]$$

$$= I_O \left[1 + \frac{2}{\beta(1 + \beta)} \right]$$

$$= 5\mu \left[1 + \frac{2}{100(1 + 100)} \right] \cong 5.0\mu\text{A}$$


$$\therefore I_0 = \frac{I_R}{1 + \frac{2}{\beta(1+\beta)}}$$

$$100(1+100)$$


$$R = \frac{30 - 0.7 \times 2}{5\mu}$$

⊛ $V_{CC} = 30V, V_{BE} = 0.7, \beta = 100$

$$I_0 = 5\mu A$$

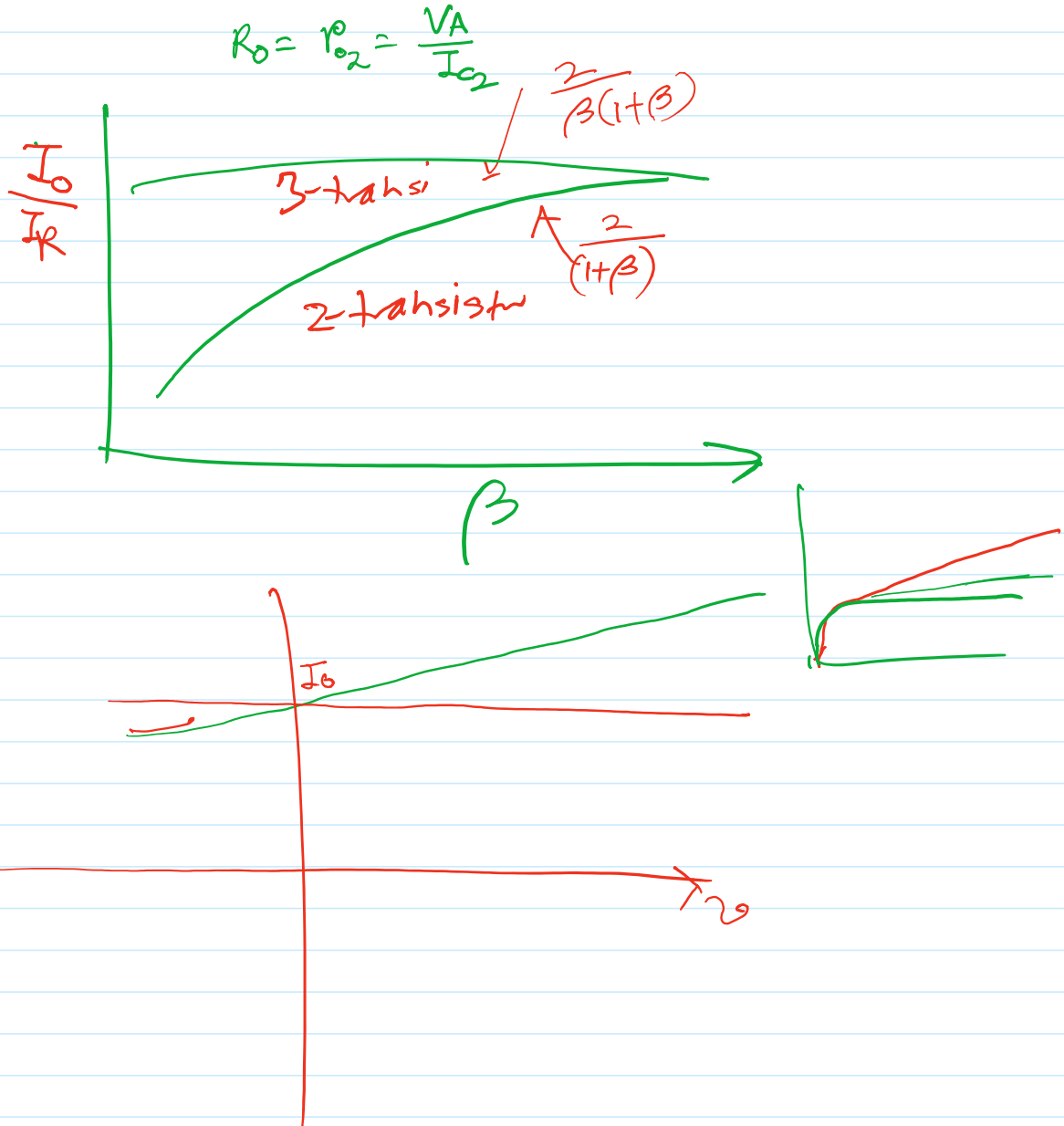

WILSON CURRENT SOURCE

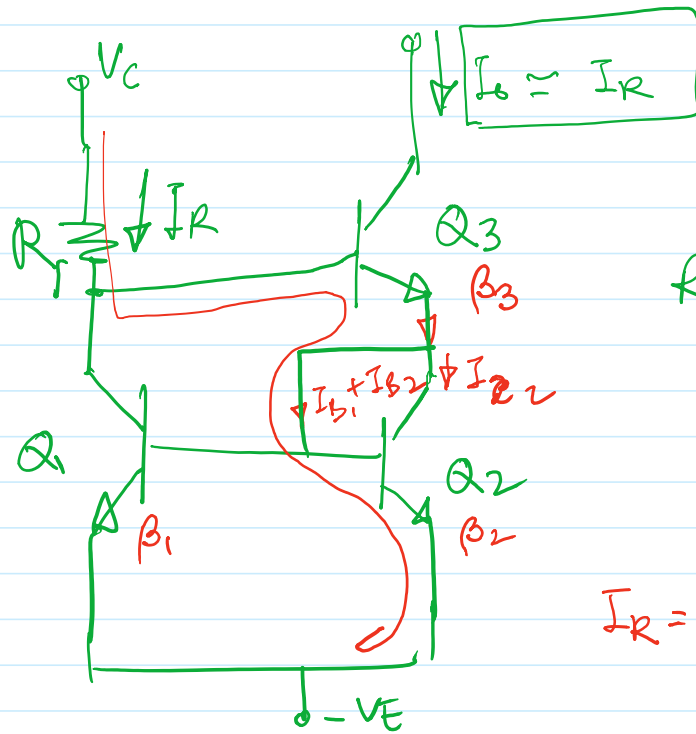

$$R_1 = \frac{V_C + V_E - 2V_{BE}}{I_R}$$

$$\beta_1 = \beta_2 = \beta_3 = \beta$$

$$I_R = I_{C1} + I_{B3} \quad (1)$$

$$I_{B1} = I_{B2} \quad [V_{BE1} = V_{BE2}]$$

$$I_{C1} = I_{C2}$$

$$I_{C3} = I_0 = \beta I_{B3}$$

$$I_{E3} = (1 + \beta) I_{B3} = I_{C2} + I_{B1} + I_{B2} \quad \text{KCL}$$

$$= I_{C1} + 2 I_{B1} = I_{C1} + \frac{2 I_{C1}}{\beta}$$

$$= I_{C1} \left[1 + \frac{2}{\beta} \right]$$

$$\therefore I_{C1} = \frac{(1 + \beta) I_{B3}}{\left[1 + \frac{2}{\beta} \right]}$$

$$I_R = I_{C1} + I_{B3}$$

$$= \frac{(1 + \beta) I_{B3}}{1 + \frac{2}{\beta}} + I_{B3} = I_{B3} \left[\frac{(1 + \beta)}{1 + \frac{2}{\beta}} + 1 \right]$$


$$= \frac{I_0}{\left[\frac{(1 + \beta)}{1 + \frac{2}{\beta}} + 1 \right]}$$

$$I_T \frac{1}{\beta}$$

$$= \frac{I_0}{\beta} \left[\frac{(1+\beta)}{1 + \frac{2}{\beta}} + 1 \right]$$

$$I_0 = 5 \text{ mA}, \quad V_C = 30 \text{ V}, \quad V_{BE} = 0.7 \text{ V}, \quad \beta = 100$$
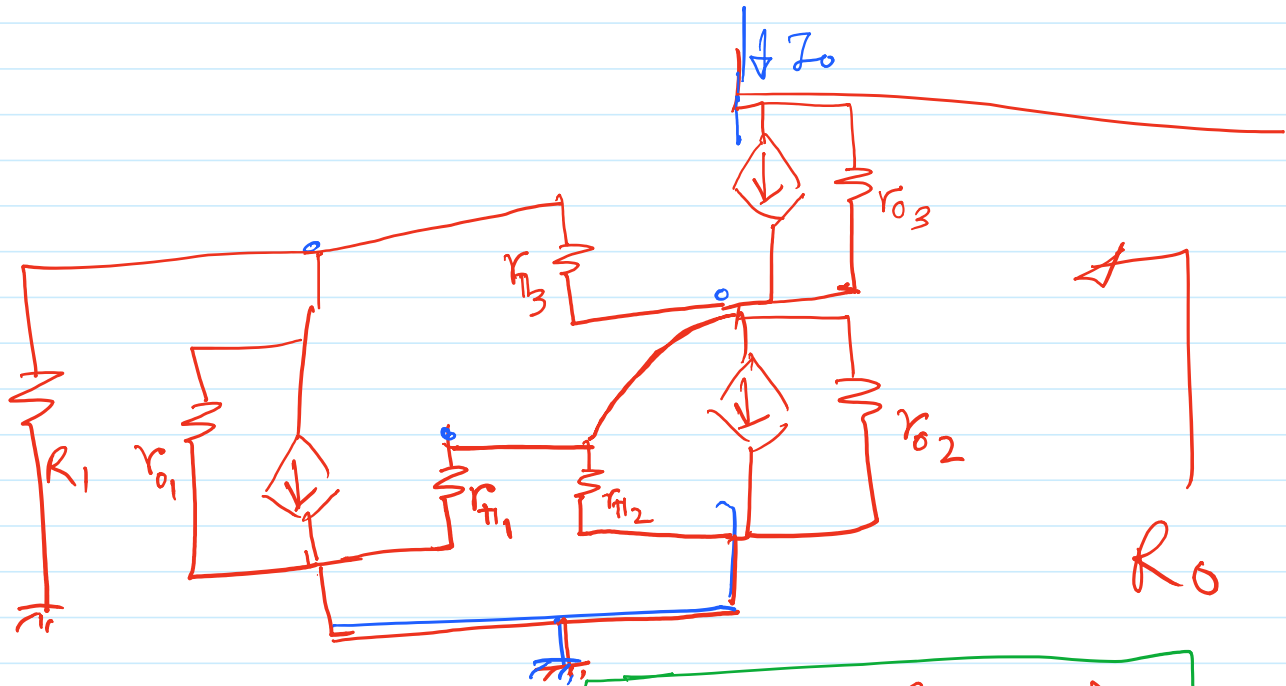
$$I_R = \frac{5 \text{ mA}}{100} \left[\frac{101}{1 + \frac{2}{100}} + 1 \right] \approx 5 \text{ mA}$$



$$R_0 = r_{o2} \left(1 + \frac{\beta}{2} \right)$$