

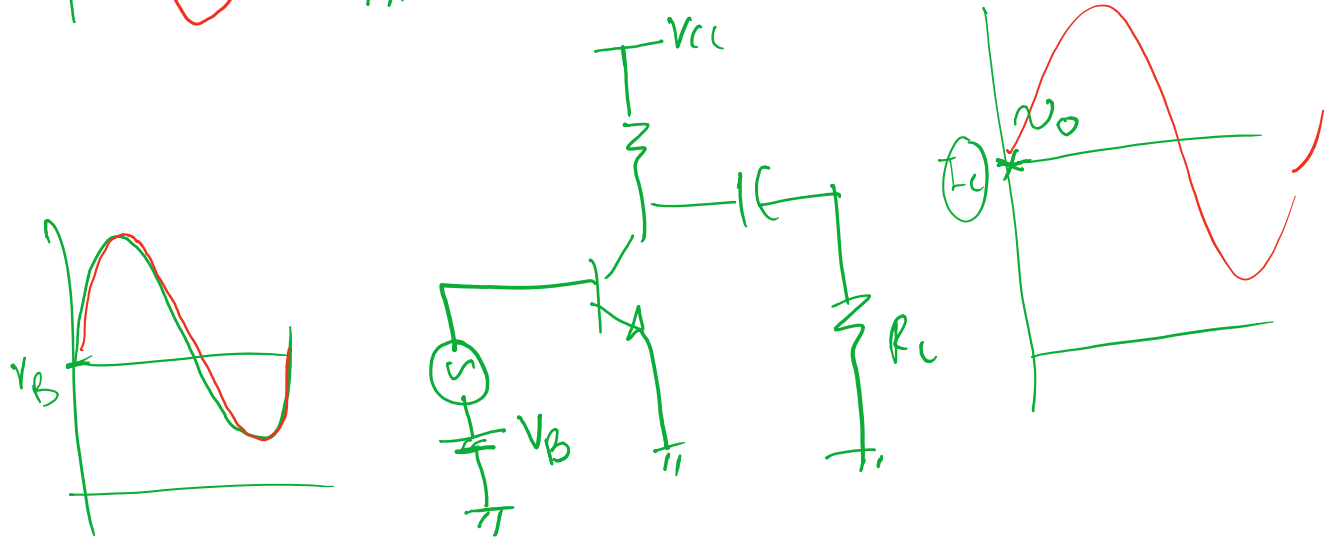
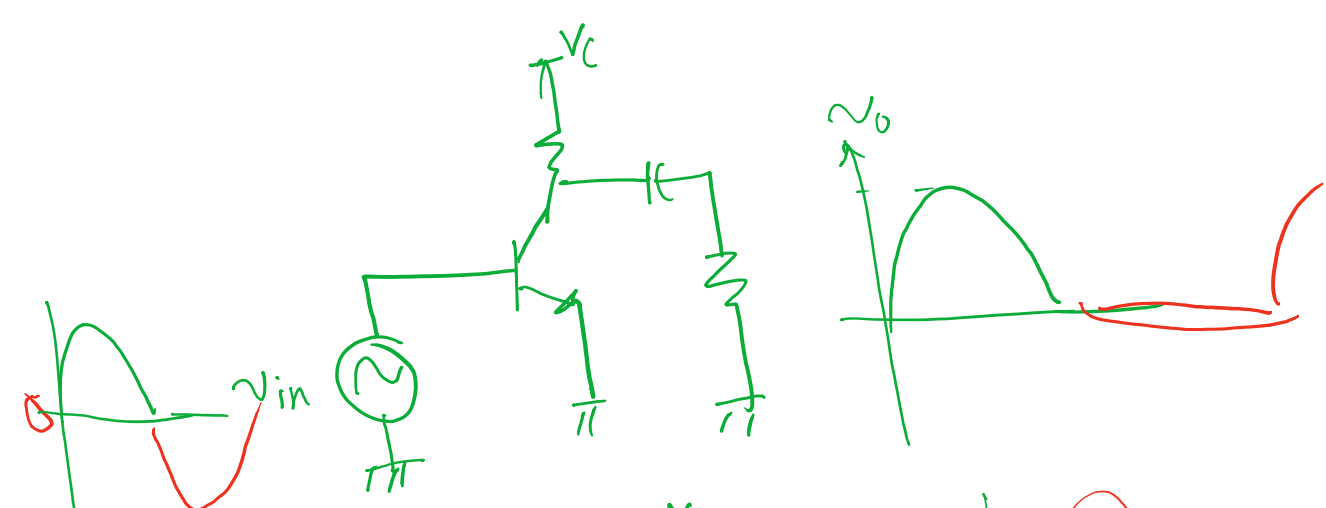
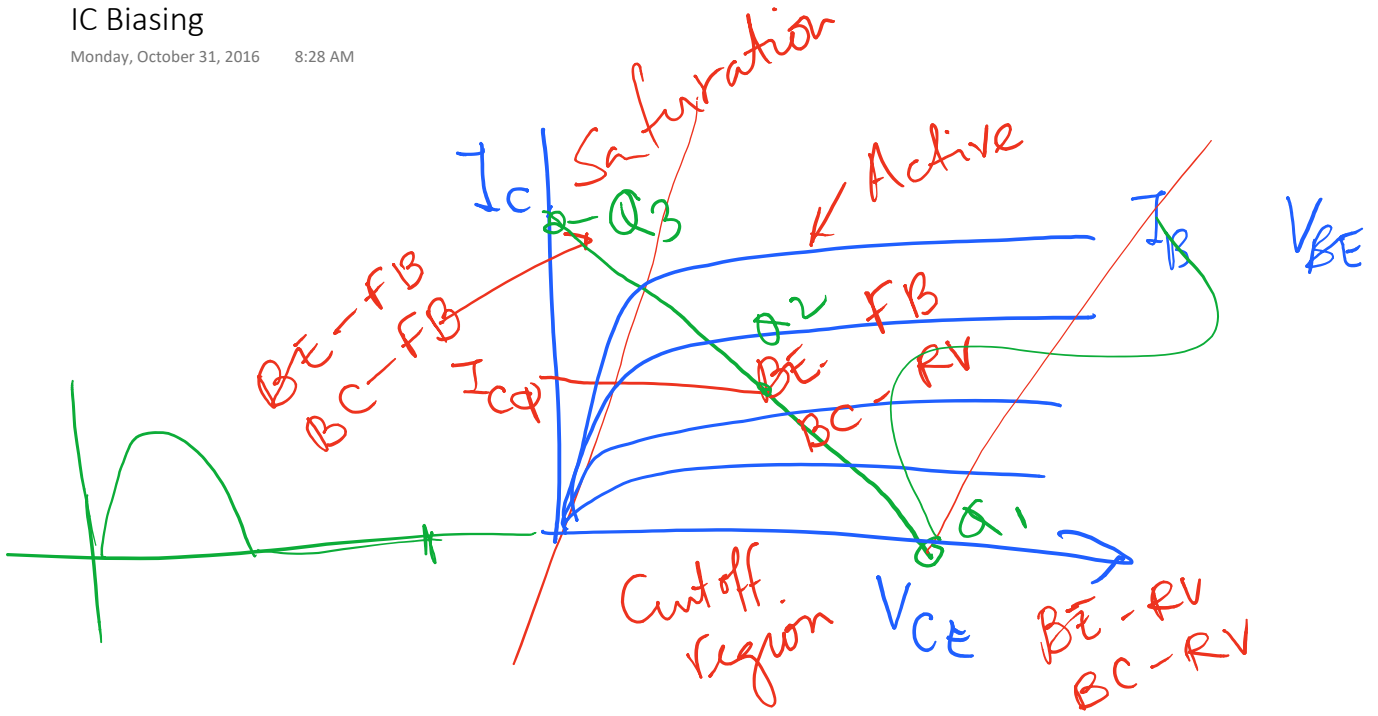
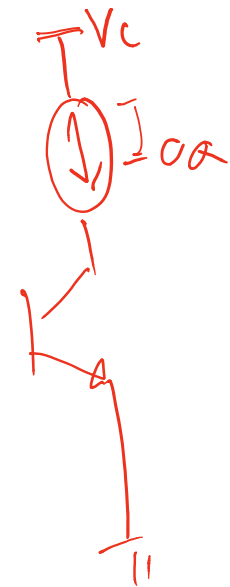
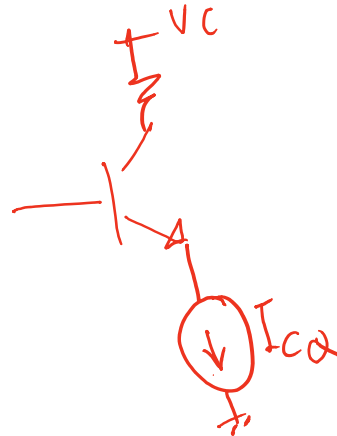
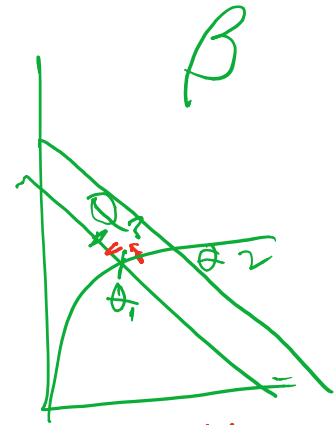


# IC Biasing


Monday, October 31, 2016 8:28 AM

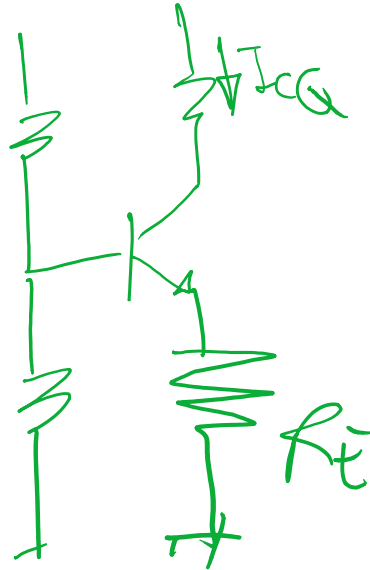

1 A B

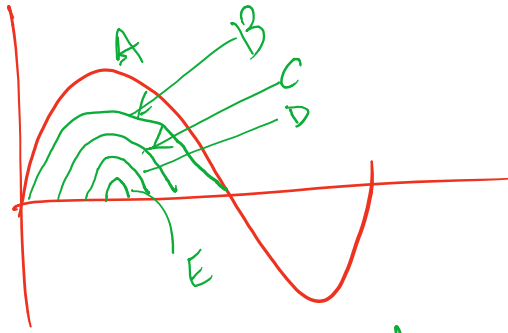


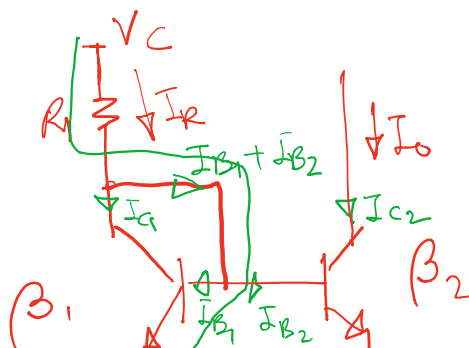\* 2 transistor current source (Basic current source)



$$\beta_1 = \beta_2 = \beta$$

$$V_A = \infty \quad r_o = \infty$$

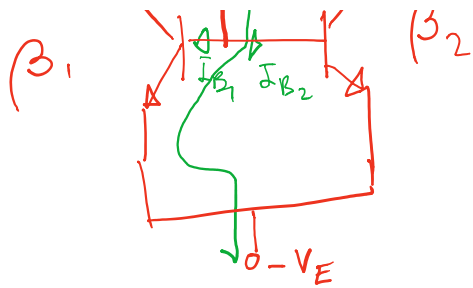

$$V_A = \infty \quad r_o = \infty$$

$$V_C = I_R R_1 + V_{BE1} - V_E$$

$$I_C = \beta I_B$$

$$\therefore R_1 = \frac{V_C + V_E - V_{BE1}}{I_R}$$


$$V_{BE1} = V_{BE2} \rightarrow I_{B1} = I_{B2} \rightarrow I_{C1} = I_{C2} = I_O$$

$$I_R = I_{C1} + I_{B1} + I_{B2} = I_{C1} + 2I_{B1}$$

$$= I_{C1} + \frac{2I_{C1}}{\beta}$$

$$= I_{C1} \left[ 1 + \frac{2}{\beta} \right] = I_O \left[ 1 + \frac{2}{\beta} \right]$$
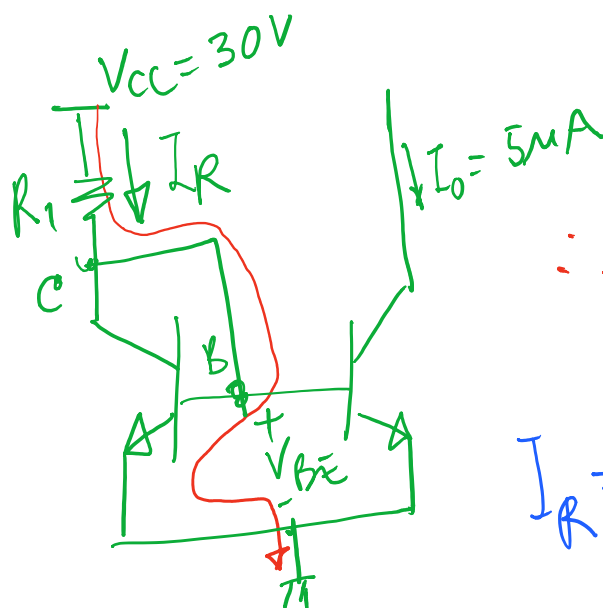
$$\therefore I_O = \frac{I_R}{1 + \frac{2}{\beta}}$$



$$V_{CC} = I_R R_1 + V_{BE1}$$

$$\therefore R_1 = \frac{V_{CC} - V_{BE1}}{I_R}$$

$$I_R = I_O \left[ 1 + \frac{2}{\beta} \right]$$

$$= 5m \left[ 1 + \frac{2}{100} \right]$$

$$30 - 0.7 = 5.745m R_1$$

$$R_1 = \frac{30 - 0.7}{5.1 \mu} = 5.745 \text{ M}\Omega$$

$$= 5 \text{ m} \left[ 1 + \frac{100}{1} \right] = 5.1 \mu$$


$$I_c = I_s \left[ e^{\frac{V_{BE}}{V_T}} - 1 \right] \left[ 1 + \frac{V_{CE}}{V_A} \right]$$

$$\frac{I_{c2}}{I_{c1}} = \frac{I_s \left[ e^{\frac{V_{BE2}}{V_T}} - 1 \right] \left[ 1 + \frac{V_{CE2}}{V_A} \right]}{I_s \left[ e^{\frac{V_{BE1}}{V_T}} - 1 \right] \left[ 1 + \frac{V_{CE1}}{V_A} \right]}$$

$$\left[ V_{BE1} = V_{BE2} \right]$$


$$= \frac{1 + \frac{V_{CE2}}{V_A}}{1 + \frac{V_{CE1}}{V_A}} = \frac{1 + \frac{V_{CE2}}{V_A}}{1 + \frac{V_{BE1}}{V_A}}$$

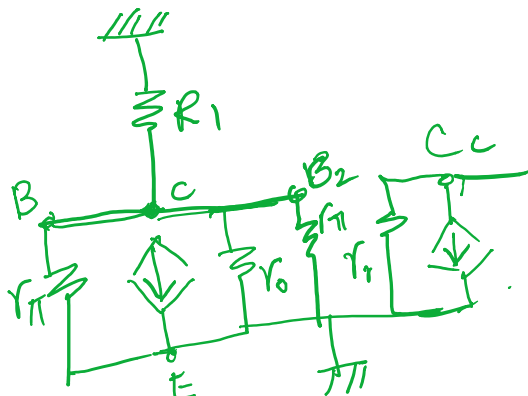$V_{CE1} = V_{BE1}$   
 Connected together



↑ a v v - a V v
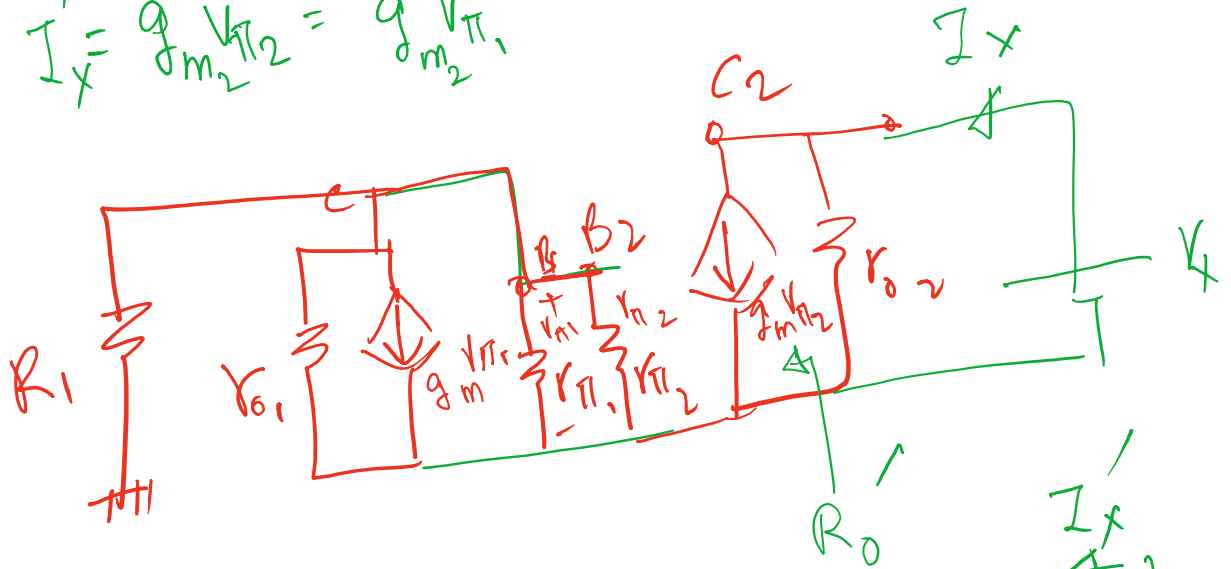
$$I'_x = g_{m2} V_{\pi 2} = g_{m2} V_{\pi 1}$$



$$I'_x = g_{m2} V_{\pi 2} = 0$$

$$R'_x = \infty$$



$$V_{\pi 1} = -g_{m1} V_{\pi 1} (R_{SS})$$

$$V_{\pi 1} [1 + g_{m1} R_{SS}] = 0 \quad V_{\pi 1} = 0$$

$$R_x = r_{o2} = \frac{V_A}{I_{C2}}$$