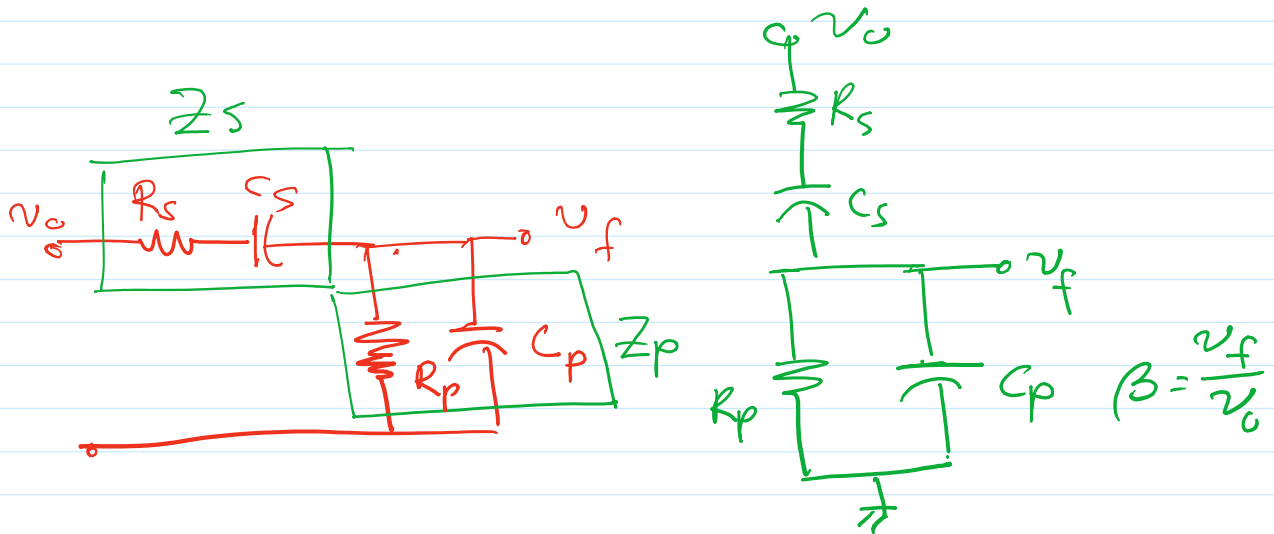


Oscillator

Wednesday, November 30, 2016 9:12 AM



$$\frac{v_f}{v_0} = T(s) = \frac{Z_p}{Z_p + Z_s}$$

$$Z_s = R_s + \frac{1}{sC_s} = \frac{1 + sR_sC_s}{sC_s}$$

$$Z_p = R_p \parallel \left(\frac{1}{sC_p} \right) = \frac{R_p \times \frac{1}{sC_p}}{R_p + \frac{1}{sC_p}}$$

$$= \frac{R_p}{1 + sC_p R_p}$$

$$Z_p + Z_s = \frac{R_p}{1 + sC_p R_p} + \frac{1 + sR_s C_s}{sC_s}$$

$$= \frac{R_p s C_s + (1 + sC_p R_p)(1 + sR_s C_s)}{(1 + sC_p R_p) s C_s}$$

$$T(s) = \frac{Z_p}{Z_p + Z_s} = \frac{\frac{R_p}{1 + sR_pC_p}}{R_p s C_s + (1 + sC_p R_p)(1 + sR_s C_s)}$$

$$= \frac{s C_s R_p}{s R_p C_s + (1 + sC_p R_p)(1 + sR_s C_s)}$$

$$\left. \begin{array}{l} R_p = R_s = R \\ C_s = C_p = C \end{array} \right\|$$

$$T(s) = \beta(s) = \frac{CR}{sCR + (1 + sCR)^2}$$

$$= \frac{sCR}{sCR + 1 + 2sCR + s^2 C^2 R^2}$$

$$\beta(s) = \frac{sCR}{1 + 3sCR + s^2 C^2 R^2}$$

$$s = j\omega$$


$$\beta(\omega) = \frac{j\omega CR}{1 + j3\omega CR - \omega^2 C^2 R^2}$$

$$= \frac{j\omega CR}{(1 - \omega^2 C^2 R^2) + j\omega 3CR}$$

Loop gain $A\beta$

for oscillation $|A\beta| = 1$

Non-inverting Amplifier gain

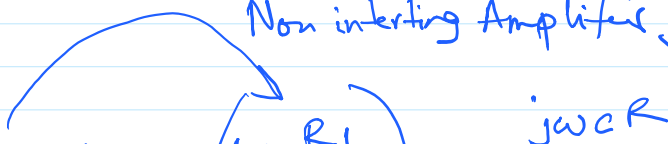

$$A\beta(\omega) = \left(1 + \frac{R_1}{R_2}\right) \frac{j\omega CR}{(1 - \omega^2 R^2 C^2) + j\omega 3CR}$$


Real part

$$1 - \omega_0^2 R^2 C^2 = 0$$

$$\omega_0 = \frac{1}{RC}$$



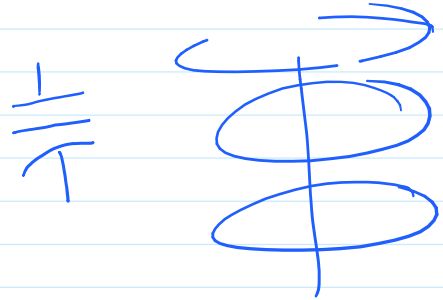Frequency of oscillation is $f_0 = \frac{1}{2\pi RC}$



for oscillation

$$A\beta = \left(1 + \frac{R_1}{R_2}\right) \frac{j\omega CR}{j3\omega CR} = 1$$

$$= \left(1 + \frac{R_1}{R_2}\right) \frac{1}{3} = 1$$

$$\therefore \left(1 + \frac{R_1}{R_2}\right) = 3$$

$$A = 3$$

$$\frac{R_1}{R_2} = 2$$