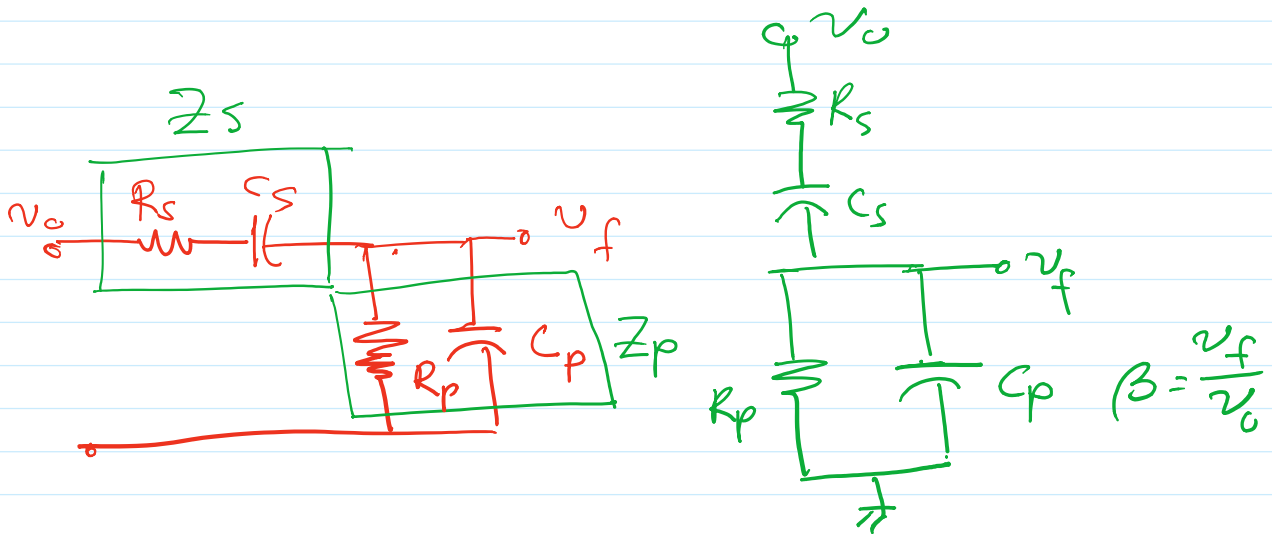


Oscillator

Wednesday, November 30, 2016 9:12 AM



$$\frac{v_f}{v_0} = T(s) = \frac{Z_p}{Z_p + Z_s}$$

$$Z_s = R_s + \frac{1}{sC_s} = \frac{1 + sR_sC_s}{sC_s}$$

$$Z_p = R_p \parallel \left(\frac{1}{sC_p} \right) = \frac{R_p \times \frac{1}{sC_p}}{R_p + \frac{1}{sC_p}}$$

$$= \frac{R_p}{1 + sC_p R_p}$$

$$Z_p + Z_s = \frac{R_p}{1 + sC_p R_p} + \frac{1 + sR_sC_s}{sC_s}$$

$$= \frac{R_p s C_s + (1 + s C_p R_p)(1 + s R_s C_s)}{(1 + s C_p R_p) s C_s}$$

$$T(s) = \frac{Z_p}{Z_p + Z_s} = \frac{\frac{R_p}{1 + sR_pC_p}}{R_p s C_s + (1 + sC_p R_p)(1 + sR_s C_s)}$$

$$= \frac{s C_s R_p}{s R_p C_s + (1 + sC_p R_p)(1 + sR_s C_s)}$$

$$\left. \begin{array}{l} R_p = R_s = R \\ C_s = C_p = C \end{array} \right\}$$

$$T(s) = \beta(s) = \frac{CR}{sCR + (1 + sCR)^2}$$

$$= \frac{sCR}{sCR + 1 + 2sCR + s^2 C^2 R^2}$$

$$\beta(s) = \frac{sCR}{1 + 3sCR + s^2 C^2 R^2}$$


$$s = j\omega$$

$$\beta(\omega) = \frac{j\omega CR}{1 + j3\omega CR - \omega^2 C^2 R^2}$$

$$= \frac{j\omega CR}{(1 - \omega^2 C^2 R^2) + j\omega 3CR}$$

Loop gain $A\beta$

for oscillation $|A\beta| = 1$

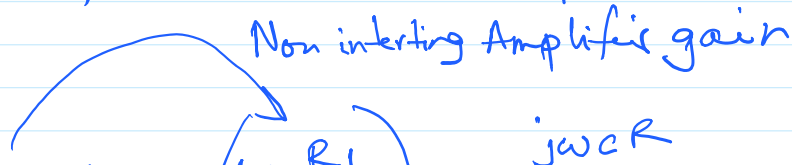

$$A\beta(\omega) = \left(1 + \frac{R_1}{R_2}\right) \frac{j\omega CR}{(1 - \omega^2 R^2 C^2) + j\omega 3CR}$$


Real part.

$$1 - \omega_0^2 R^2 C^2 = 0$$

$$\omega_0 = \frac{1}{RC}$$



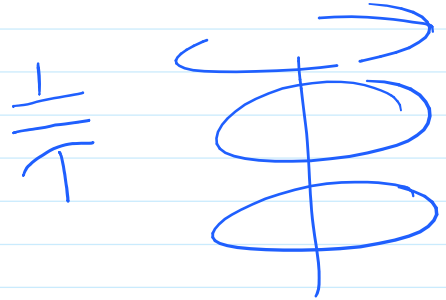Frequency of oscillation is $f_0 = \frac{1}{2\pi RC}$



for oscillation


$$A\beta = \left(1 + \frac{R_1}{R_2}\right) \frac{j\omega CR}{j3\omega CR} = 1$$

$$= \left(1 + \frac{R_1}{R_2}\right) \frac{1}{3} = 1$$

$$\therefore \left(1 + \frac{R_1}{R_2}\right) = 3$$

$$A = 3$$


$$\frac{R_1}{R_2} = 2$$

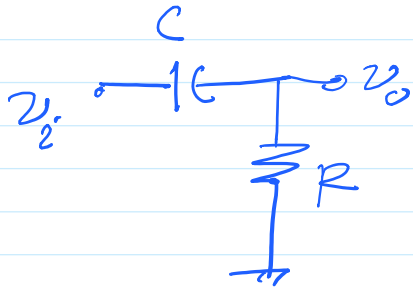

$$\frac{R}{R + \frac{1}{sC}} = \frac{sRC}{1 + sRC}$$


$$= \frac{j\omega RC}{1 + j\omega RC}$$
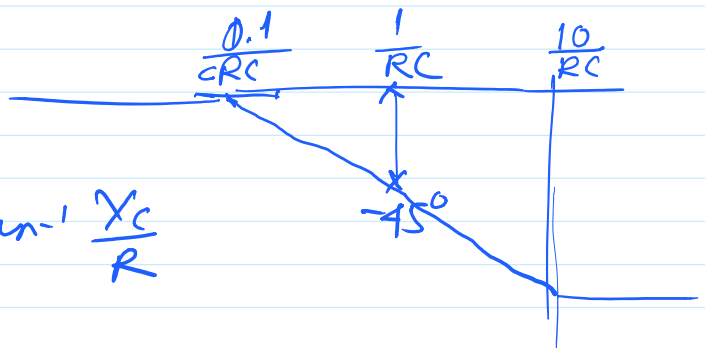
$$= \frac{\omega RC \angle 90^\circ}{\sqrt{1 + (\omega RC)^2} \tan^{-1} \omega RC}$$




$$R + jX_c \Rightarrow \tan^{-1} \frac{X_c}{R}$$

RC-phase-shift oscillator

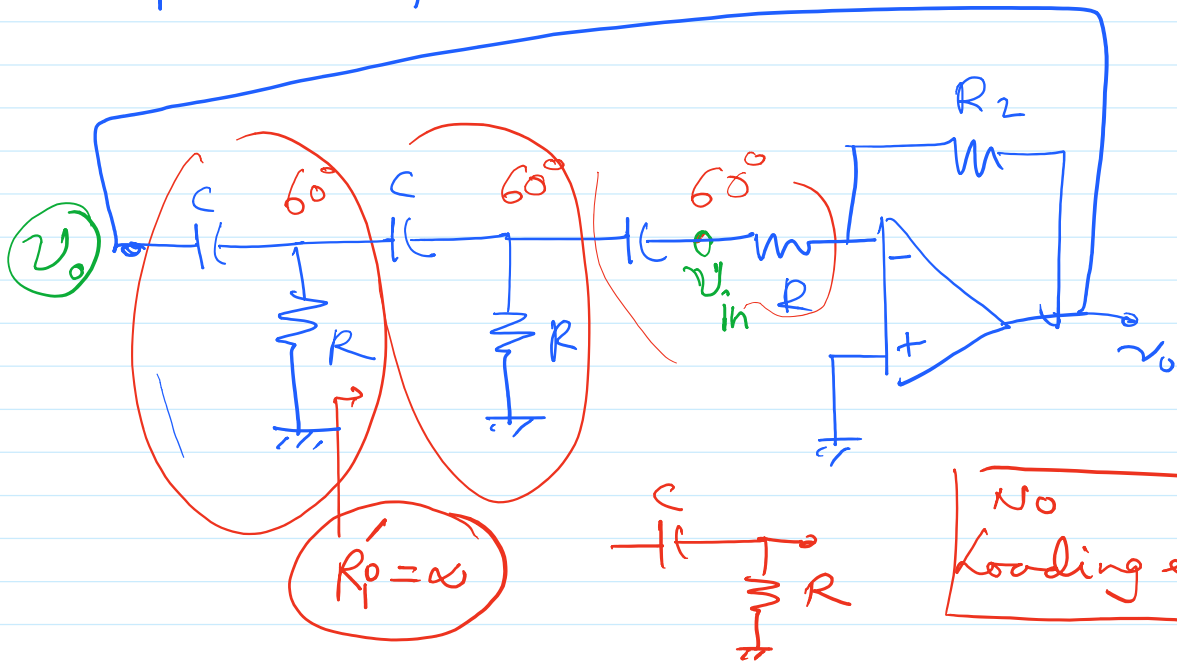


$$R_1 = \infty$$

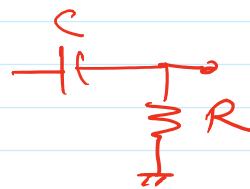

No loading effect

Buffer Amplifier

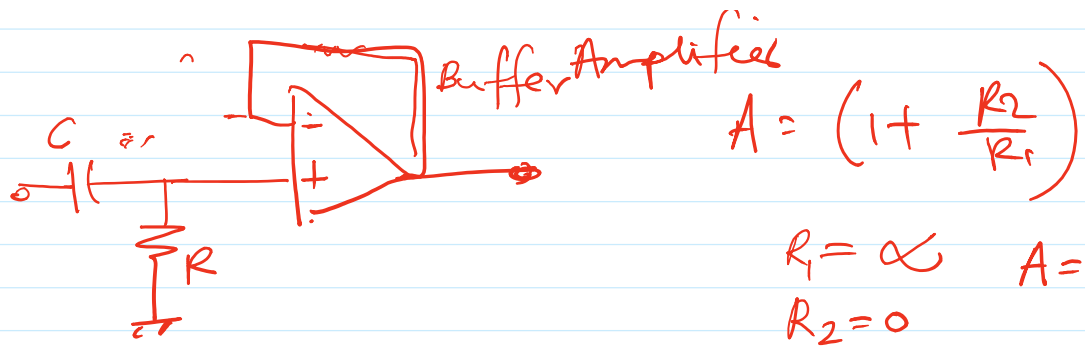


$$A = \left(1 + \frac{R_2}{R_1}\right)$$

$$R_1 = \infty \quad A = 1$$

$$R_2 = 0$$

$$\beta = \frac{v_o}{v_i}$$

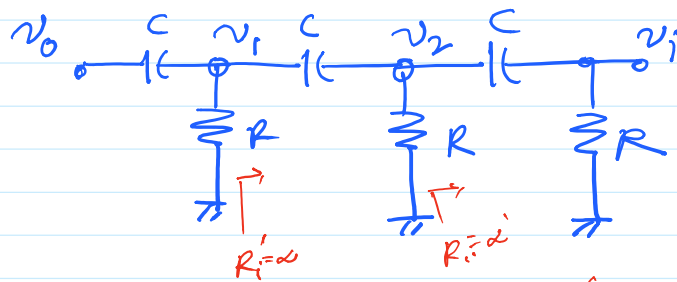

$$\beta = \frac{v_i}{v_o} = \left(\frac{v_1}{v_o}\right) \cdot \left(\frac{v_2}{v_1}\right) \cdot \left(\frac{v_i}{v_2}\right) = \left(\frac{v_1}{v_o}\right)^3$$

$$\frac{v_1}{v_o} = \frac{R}{R + \frac{1}{sC}} = \frac{sRC}{1 + sRC}$$

$$(a+b)(a+b)^2 = (a+b)(a^2 + 2ab + b^2)$$

$$(a+b)^3 = a^3 + 3ab^2 + 3a^2b + b^3$$

$$\beta = \left(\frac{v_1}{v_o}\right)^3 = \frac{(sRC)^3}{(1 + sRC)^3}$$

$$\beta(s) = \frac{s^3 R^3 C^3}{1 + 3s^2 R^2 C^2 + 3sRC + s^3 R^3 C^3}$$

$$s = j\omega$$

$$\beta(\omega) = \frac{-jR^3 C^3 \omega^3}{1 - 3\omega^2 R^2 C^2 + j3\omega RC - j\omega^3 R^3 C^3}$$

$$= \frac{-jR^3 C^3 \omega^3}{(1 - 3\omega^2 R^2 C^2) + j\omega RC [3 - \omega^2 R^2 C^2]}$$

$$\text{Loop gain } A\beta = -\frac{R_2}{R} \frac{-jR^3 C^3 \omega^3}{(1 - 3\omega^2 R^2 C^2) + j\omega RC [3 - \omega^2 R^2 C^2]}$$

$$|A\beta| = 1 \Rightarrow 1 - 3\omega_0^2 R^2 C^2 = 0$$

$$\omega_0^2 = \frac{1}{3R^2 C^2}$$

$$\omega_0 = \frac{1}{\sqrt{3}RC}$$

frequency of oscillation

$$|A\beta| = 1 = \frac{R_2}{R} \cdot \frac{\omega_0^3 R^3 C^3}{\omega_0 RC [3 - \omega_0^2 R^2 C^2]} = \frac{\omega_0^2 R^2 C^2}{[3 - \omega_0^2 R^2 C^2]}$$

$$= \frac{R_2}{R} \cdot \frac{\frac{1}{3}}{[3 - \frac{1}{3}]} = \frac{\frac{1}{3}}{\frac{9-1}{3}} = \frac{1}{8}$$

$$\therefore \frac{R_2}{R} = 8$$

Considering the loading effect:

$$\omega = \frac{1}{\sqrt{6} RC}$$

$$\frac{R_2}{R} = 29$$