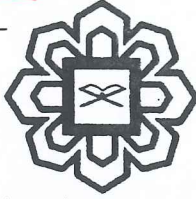


Name:

MODEL ANSWER

Matric No: \_\_\_\_\_

Section: \_\_\_\_\_



الجامعة الإسلامية العالمية ماليزيا

INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA

MID-TERM EXAMINATION

SEMESTER II, 2014/2015 SESSION

KULLIYAH OF ENGINEERING

Programme : ENGINEERING

Level of Study : UG 2

Time : 8:00pm-10:00 pm

Date : 19/03/2015

Duration : 2 Hours

Course Code : ECE 2133

Section(s) : 1 & 2

Course Title : **Electronic Circuits**

This Question Paper consists of Seven (7) Printed Pages (Including Cover and a blank page) with Three (3) Questions.

**INSTRUCTION(S) TO CANDIDATES**

DO NOT OPEN UNTIL YOU ARE ASKED TO DO SO

- Use only pen for writing answer.
- Do not use your own sheet.
- Useful formulas and values are given in page 7.
- A total mark of this examination is 60.
- This examination is worth 30% of the total assessment.
- For drawing you may use pencil
- Answer ALL questions.

**Any form of cheating or attempt to cheat is a serious offence which may lead to dismissal.**

	Q 1a	Q 1b	Q 2a	Q 2b	Q 3	Total Marks
Marks	8	12	10	10	20	60
Marks Obtained						

## Q.1 [30 marks]

- (a) Define transfer function. Find the transfer function of the following circuit. What should be maximum gain? (8 marks)


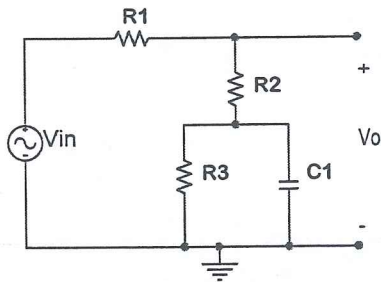


Fig. 1(a)

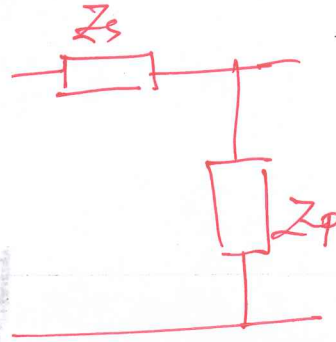

$$T(s) = \frac{Z_p}{Z_s + Z_p}$$

$$Z_s = R_1$$

$$Z_p = R_2 + R_3 \parallel \frac{1}{sC_1}$$

$$= R_2 + \frac{R_3 \frac{1}{sC_1}}{R_3 + \frac{1}{sC_1}} = R_2 + \frac{R_3}{1 + \frac{1}{sC_1} R_3 s}$$

$$= \frac{(R_2 + R_3) + R_2 R_3 C_1 s}{1 + R_3 C_1 s}$$

$$Z_p + Z_s = R_1 + R_2 + \frac{R_3}{1 + R_3 C_1 s} = \frac{(R_1 + R_2 + R_3) + (R_2 + R_3) R_3 C_1 s}{1 + R_3 C_1 s}$$

$$\therefore T(s) = \frac{Z_p}{Z_s + Z_p} = \frac{(R_2 + R_3) + R_2 R_3 C_1 s}{(R_1 + R_2 + R_3) + (R_2 + R_3) R_3 C_1 s}$$

$$|T(s)|_{\max} = \frac{R_2 R_3}{R_1 + R_2 + R_3} = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$


(b) Draw the Bode magnitude and phase plots of the following transfer function:

$$T(s) = 5000 \frac{s(s+50)}{(s+5)(s+500)}$$



(12 marks)

$$= \frac{100 \cancel{s} \times s \cancel{s} \left(1 + \frac{s}{50}\right)}{5 \left(1 + \frac{s}{5}\right) \cdot 500 \cancel{s} \left[1 + \frac{s}{500}\right]}$$
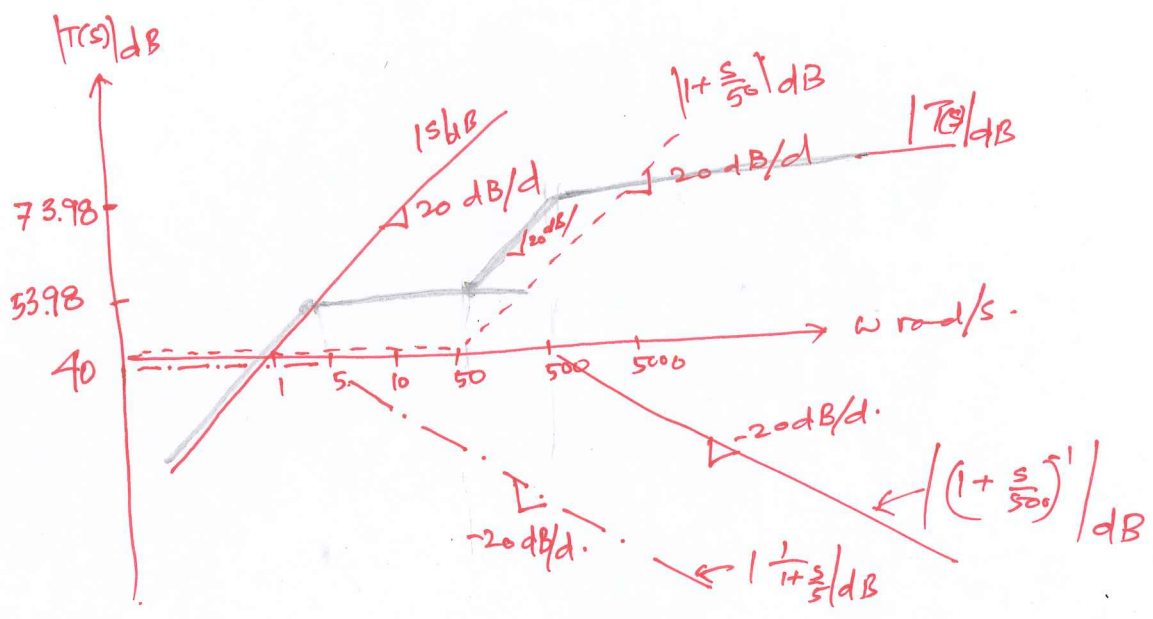
$$= \frac{100 s \left(1 + \frac{s}{50}\right)}{\left(1 + \frac{s}{5}\right) \left(1 + \frac{s}{500}\right)}$$



Magnitude.

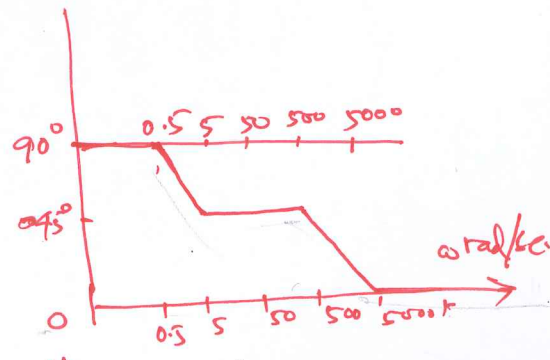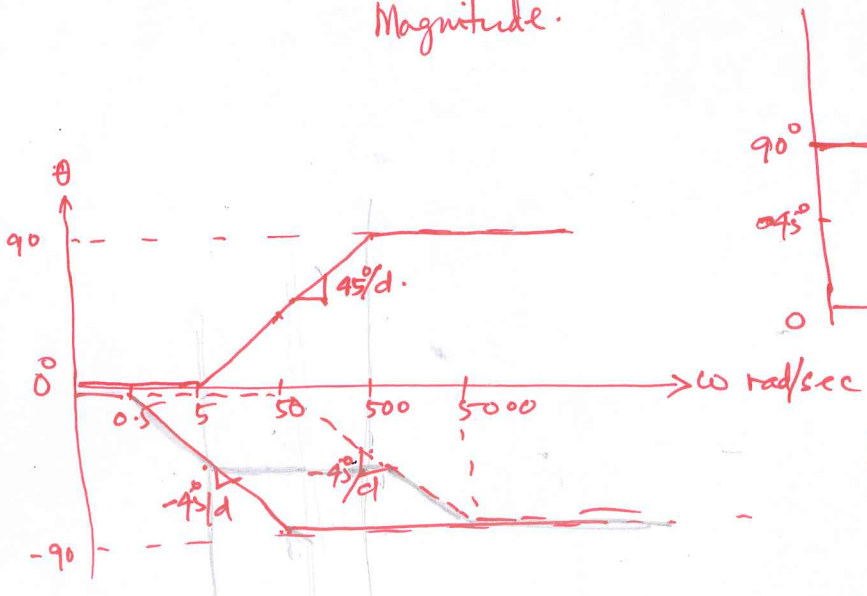

Phase.

**Q.2 [20 marks]**

(a) Draw the small signal equivalent circuit diagram of the MOSFET amplifier circuit shown in Fig. 2(a) and find the midband voltage gain  $A_v = \frac{v_o}{v_i}$  of the amplifier. If  $C_C = 10\mu\text{F}$  and  $C_{C2} = \infty$  then find the corner frequency due to  $C_C$ . The transistor parameters are  $g_m = 0.5 \text{ mA/V}$  and  $r_o = \infty$ . **(10 marks)**


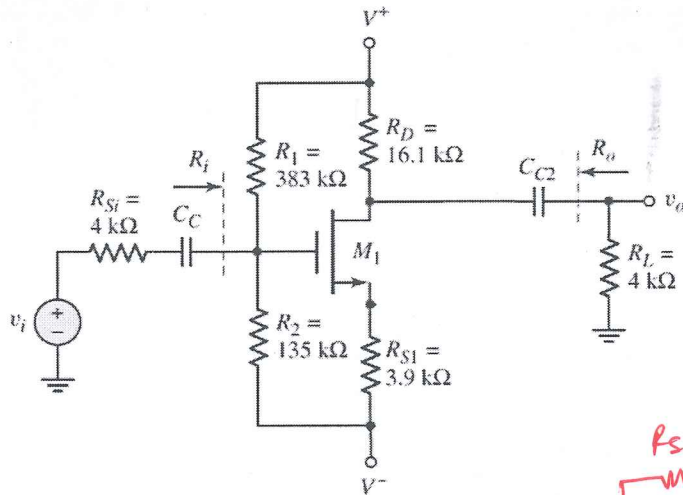


Fig. 2(a)

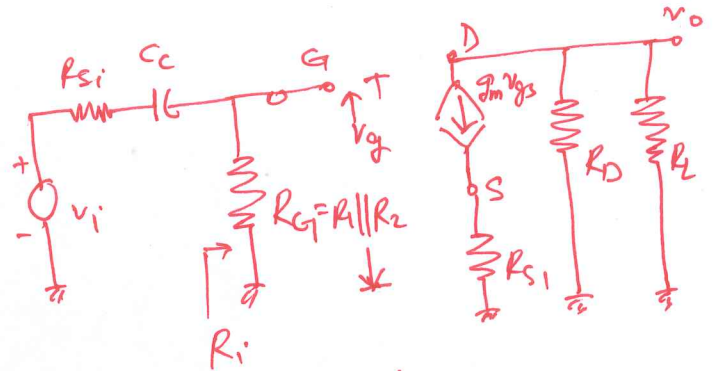

$$v_o = -g_m v_{gs} R'_L$$

$$v_{gs} = v_{gs} + g_m v_{gs} R_{S1}$$

$$= v_{gs} (1 + g_m R_{S1})$$

$$\therefore A_{vA} = \frac{v_o}{v_{gs}} = \frac{-g_m R'_L}{1 + g_m R_{S1}}$$

$$= \frac{-0.5 \times 3.2}{1 + 0.5 \times 3.9} = -0.5423$$

$$R'_L = R_D || R_L$$


$$= 3.2 \text{ k}\Omega$$

$$R_i = R_G = 99.817 \text{ k}\Omega$$

$$\therefore A_v = A_{vA} \times \frac{R_i}{R_i + R_{S1}} = -0.5423 \times \frac{99.817}{99.817 + 4}$$

$$= -0.521 \text{ V/V}$$
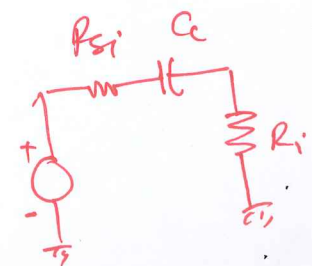
$$\tau = (R_{S1} + R_i) C_C = \frac{(99.817 + 4) \times 10^{-6}}{1} = 1.0387$$



$$\therefore f_L = \frac{1}{2\pi\tau} = 0.153 \text{ Hz} = 153.3 \text{ MHz}$$

(b) Draw the small signal equivalent circuit diagram of the BJT amplifier circuit shown in Fig. 2(b) and find the output resistance,  $R_o$ . Given that  $R_1 = 300 \text{ k}\Omega$ ,  $R_2 = 500 \text{ k}\Omega$ ,  $R_E = 20.0 \text{ k}\Omega$ ,  $R_L = 10.0 \text{ k}\Omega$ ,  $C_{C1} = \infty$ ,  $C_{C2} = 1\mu\text{F}$  and  $C_L = 10\text{pF}$ .

Also find the corner frequency due to  $C_{C2}$  and  $C_L$  and hence determine the bandwidth of the amplifier.

The transistor parameters are  $\beta = 120$ ,  $r_{\pi} = 3 \text{ k}\Omega$  and  $r_o = 100 \text{ k}\Omega$ .

(10 marks)



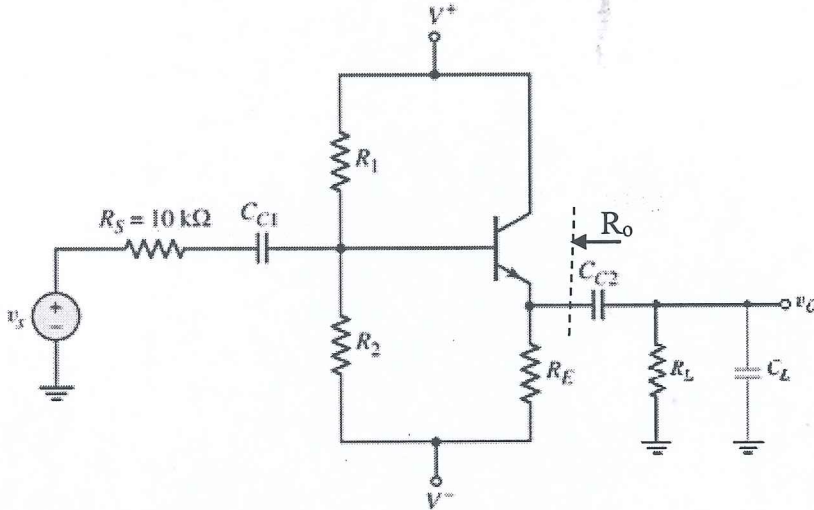


Fig. 2(b)

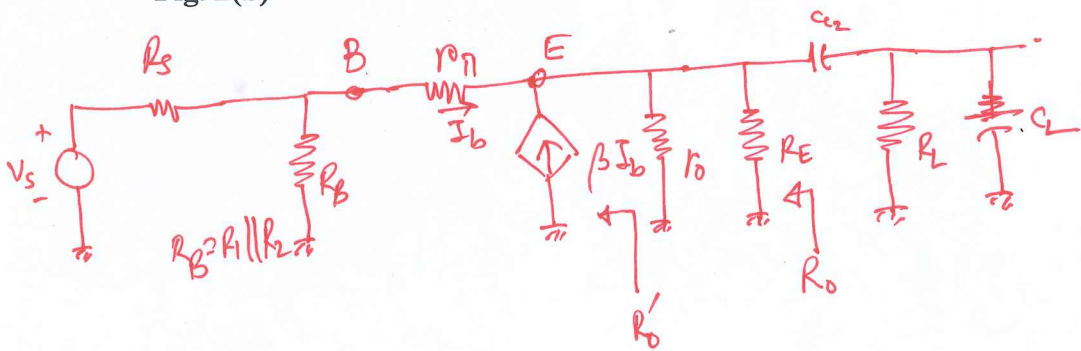

$R_o = ?$

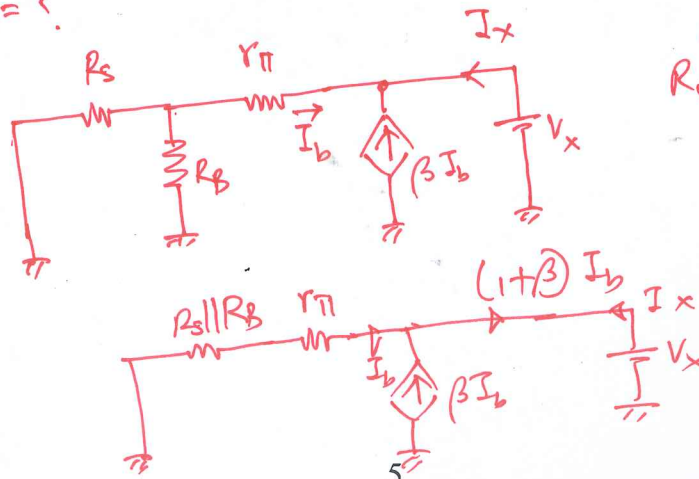

$$R_o = \frac{V_x}{I_x}$$

$$I_x = -(1+\beta)I_b$$

$$(R_s || R_B + r_{\pi}) I_b + V_x = 0$$

$$\therefore I_b = -\frac{V_x}{R_s || R_B + r_{\pi}}$$


$$I_x = \frac{(1+\beta) V_x}{R_s || R_B + r_{\pi}}$$

$$\therefore R_o = \frac{V_x}{I_x} = \frac{R_s || R_B + r_{\pi}}{(1+\beta)}$$

$$R_S \parallel R_B = R_S \parallel R_1 \parallel R_2 = 10 \parallel 800 \parallel 500 = 9.494 \text{ k}\Omega.$$

$$\therefore R_o' = \frac{9.494 + \beta}{(1 + \beta)} = 0.1032 \text{ k}\Omega = \underline{\underline{103.2534 \Omega}}.$$
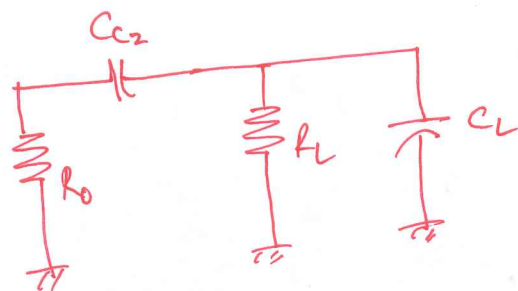
$$R_o = R_o' \parallel r_o \parallel R_E = 0.10325 \parallel 100 \parallel 20 = 102.62 \Omega \swarrow$$



$$\tau_{C_{c2}} = (R_o + R_L) C_{c2} = 10.1026 \text{ ns}.$$

$$\therefore f_{H_{C_{c2}}} = \frac{1}{2\pi \tau_{C_{c2}}} = 15.754 \text{ Hz} \swarrow$$

$$\tau_{C_L} = R_o \parallel R_L \times C_L = 1.01577 \text{ ns}$$


$$\therefore f_{H_{C_L}} = \frac{1}{2\pi \tau_{C_L}} = 156.683 \text{ MHz} \swarrow$$

$$BW = f_{H_{C_L}} \rightarrow f_{C_{c2}} \approx f_{H_{C_L}} = 156.683 \text{ MHz} \leftarrow$$


**Q.3 [20 marks]**

The common emitter amplifier is shown in **Fig. 3** that operated at high frequencies. The transistor parameters are:  $g_m = 40 \text{ mA/V}$ ,  $r_\pi = 4 \text{ k}\Omega$ ,  $r_o = 100 \text{ k}\Omega$ ,  $C_\pi = 10 \text{ pF}$ , and  $f_T = 500 \text{ MHz}$ .

- (i) Draw the simplified high-frequency small signal equivalent circuit diagram. (3 marks)
- (ii) Find the value of  $C_\mu$ . (3 marks)
- (iii) Find the value of Miller capacitance. (4 marks)
- (iv) Evaluate the upper 3dB frequency ( $f_H$ ) considering Miller capacitance (4 marks)
- (v) Evaluate the upper 3dB frequency ( $f_H$ ) without considering Miller capacitance. (4 marks)
- (vi) How do you evaluate the the upper 3dB frequency? (2 mark)

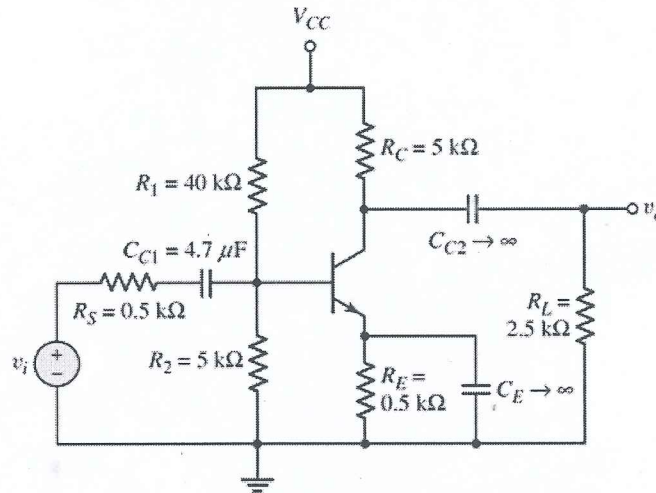

**Fig. 3**

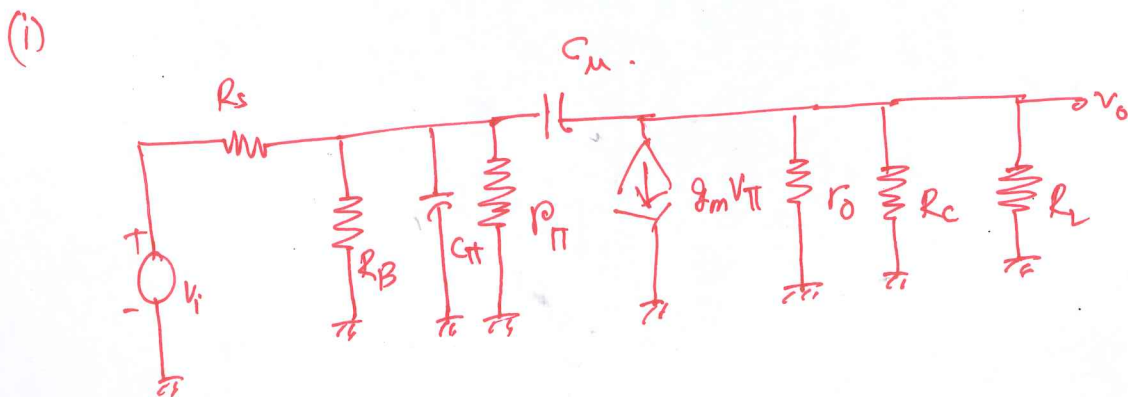

(ii)

$$f_T = \beta f_\beta = \frac{\beta}{2\pi r_\pi (C_\mu + C_\pi)} = \frac{g_m r_\pi}{2\pi r_\pi (C_\mu + C_\pi)}$$
$$= \frac{g_m}{2\pi (C_\mu + C_\pi)}$$

$$C_\mu + C_\pi = \frac{g_m}{2\pi f_T} = \frac{40 \text{ m}}{2\pi \times 500 \text{ m}} = 12.73 \text{ pF}$$

$$C_\mu = 12.73 - C_\pi = 12.73 - 10 = 2.73 \text{ pF} \leftarrow$$

(iii)

$$A_{vM} = - \frac{g_m V_{\pi} \times r_o \parallel R_c \parallel R_L}{V_{\pi}} = - g_m r_o \parallel R_c \parallel R_L$$
$$= - 40 \times 5 \parallel 100 \parallel 2.5$$
$$= - 65.57$$

$$C_M = C_\pi [1 + |A_{vM}|] = 2.73 \text{ pF} \times [1 + 65.57]$$
$$= 181.746 \text{ pF} \leftarrow$$

$$(iv) C_T = C_\pi + C_M = 191.746 \text{ pF}$$

$$\tau_M = C_T \times R_{eq}$$

$$= 191.746 \text{ p} \times 0.4040$$
$$= 77.47 \text{ ns}$$

$$R_{eq} = R_s \parallel R_i \parallel R_c \parallel R_L \parallel r_o$$
$$= 0.5 \parallel 40 \parallel 5 \parallel 4$$
$$= 0.404 \text{ k}\Omega$$

$$\therefore f_{H_M} = \frac{1}{2\pi \tau_M} = 2.054 \text{ MHz}$$

$$(v) C_T = C_\pi = 10 \text{ pF}$$

$$\therefore f_H = \frac{1}{2\pi \tau} = 39.39 \text{ MHz}$$

$$\tau = C_\pi \times R_{eq} = 4.04 \text{ ns}$$

(vi) Upper dB freq is 2.054 MHz due to Miller effect,