

Name: _____

Matric No: _____ Section: _____

Lecturer's Name: _____



الجامعة الإسلامية العالمية ماليزيا

INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA

**MID-TERM EXAMINATION
SEMESTER 1, 2019/2020 SESSION
KULLIYAH OF ENGINEERING**

Programme : ENGINEERING Level of Study : UG 2
Time : 5:20 pm-6:50 pm Date : 23/10/2019
Duration : 1 Hour 30 Minutes
Course Code : EECE 2313 Section(s) : 1, 2
Course Title : **Electronic Circuits**

This Question Paper consists of **Eight (8)** Printed Pages (including cover and two blank pages) with **Three (3)** Questions.

INSTRUCTION(S) TO CANDIDATES

DO NOT OPEN UNTIL YOU ARE ASKED TO DO SO

- Use only pen for writing the answer
- Do not use your own paper sheet and no extra paper will be provided
- A total mark of this examination is 50
- This examination is worth 30% of the total assessment
- For drawing, you may use a pencil
- Answer **ALL THREE (3)** questions
- Answer on the question paper

Any form of cheating or attempt to cheat is a serious offence which may lead to dismissal.

	Question 1	Question 2	Question 3	Total Marks
Marks	20	20	10	50
Marks Obtained				

Q.1 [20 marks]

(a) An RC-circuit circuit as shown in Fig. 1(a), derive the expression (step by step) for the voltage transfer function $T(s) = v_o(s)/v_i(s)$. Find the corner frequencies of the circuit if $R_s = 4.5 \text{ k}\Omega$, $R_p = 1.5 \text{ k}\Omega$, $C_1 = 80 \text{ pF}$ and $C_2 = 20 \text{ pF}$. (6+2 marks)

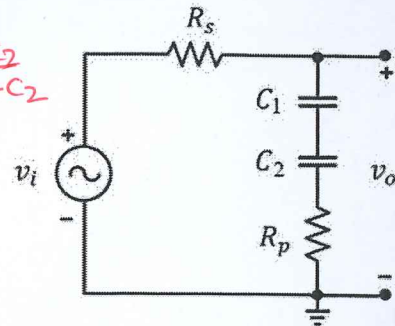
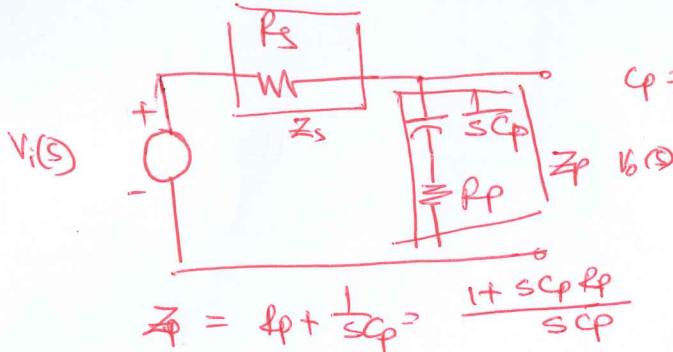


Fig. 1(a)

$$Z_p = R_p + \frac{1}{sC_p} = \frac{1 + sC_p R_p}{sC_p}$$

$$Z_s + Z_p = R_s + R_p + \frac{1}{sC_p} = \frac{1 + sC_p(R_p + R_s)}{sC_p}$$

$$T(s) = \frac{v_o}{v_i} = \frac{Z_p}{Z_s + Z_p} = \frac{\frac{1 + sC_p R_p}{sC_p}}{\frac{1 + sC_p(R_p + R_s)}{sC_p}} = \frac{1 + sC_p R_p}{1 + sC_p(R_p + R_s)} = \frac{1 + s\tau_1}{1 + s\tau_2}$$

$$\tau_1 = C_p R_p \quad \tau_2 = C_p(R_p + R_s)$$

$$f_1 = \frac{1}{2\pi C_p R_p} = \frac{1}{2\pi \cdot 16 \text{ pF} \cdot 1.5 \text{ k}\Omega} = 6.631 \text{ MHz}$$

$$f_2 = \frac{1}{2\pi C_p (R_p + R_s)} = \frac{1}{2\pi \cdot 16 \text{ pF} \cdot (1.5 + 4.5) \text{ k}\Omega} = 1.657 \text{ MHz}$$


(b) Draw the Bode plots (magnitude and phase) of the following transfer function.

(8 marks)

$$T(s) = \frac{10^{-5}s(s + 250)}{(s + 150)(s + 400)}$$

Determine the magnitude and phase at $s = 550$ rad/Sec, using the solution from the graph of the question Q1.(b). (4 marks)
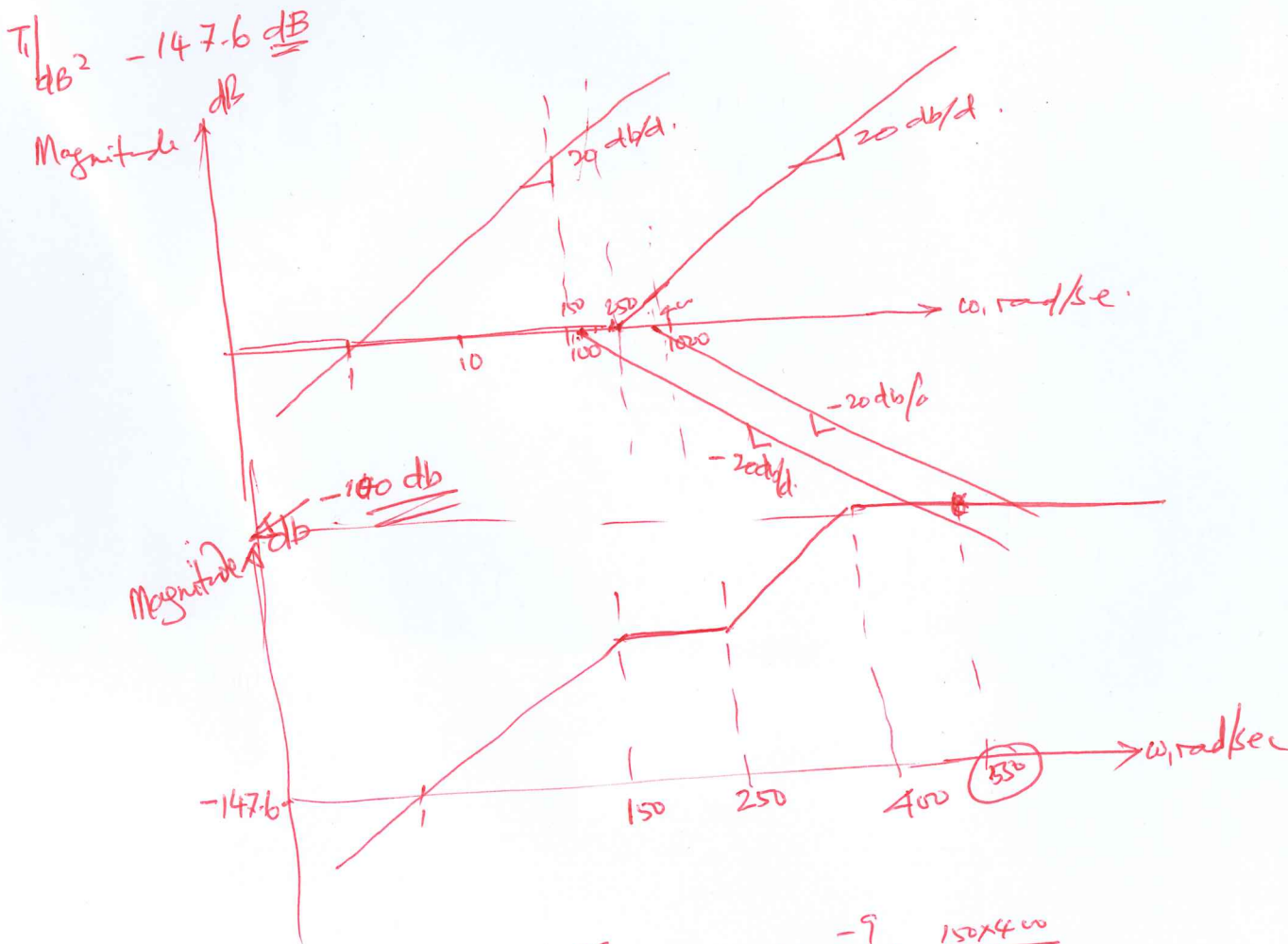
$$T(s) = \frac{10^{-5} \cdot 250 \cdot s \left(1 + \frac{s}{250}\right)}{150 \times 400 \left(1 + \frac{s}{150}\right) \left(1 + \frac{s}{400}\right)} = 41.67 \times 10^{-9} \frac{s \left(1 + \frac{s}{250}\right)}{\left(1 + \frac{s}{150}\right) \left(1 + \frac{s}{400}\right)}$$





$$T(s) \Big|_{550} = 41.67 \times 10^{-9} \cdot \frac{s \times \frac{s}{250}}{\frac{s}{150} \times \frac{s}{400}} = 41.67 \times 10^{-9} \times \frac{150 \times 400}{250}$$

$$= 41.67 \times 10^{-9} \times 240$$

$$T(s) \Big|_{db} = \cancel{-147.6} + \cancel{47.6} = \cancel{100} \text{ dB}$$


$$= -100 \text{ dB}$$

Q1(b)

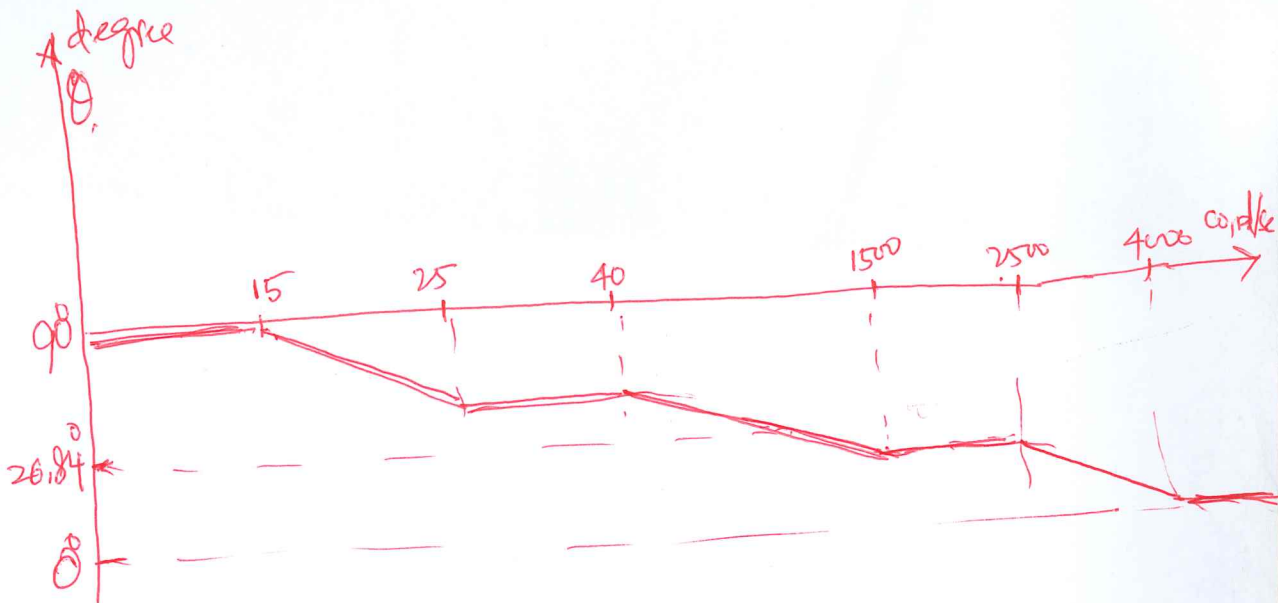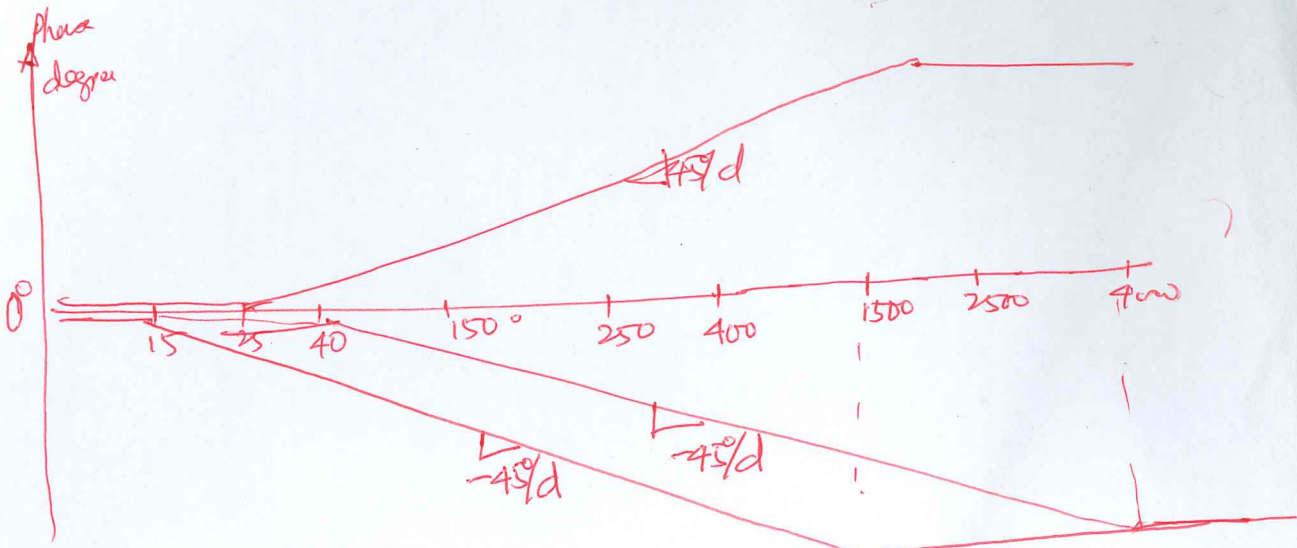


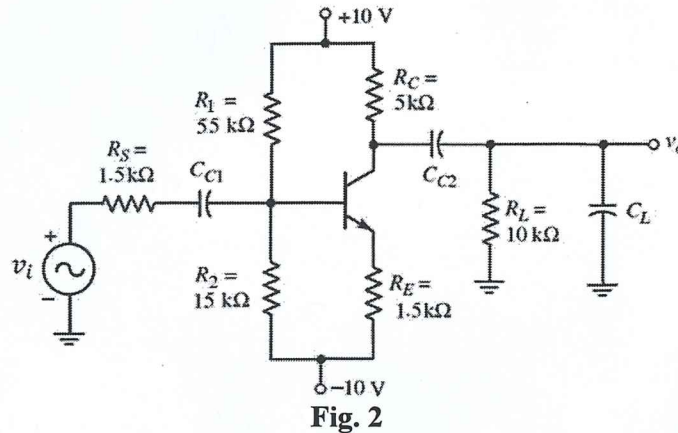Q.2 [20 marks]

A common emitter amplifier circuit as shown in Fig. 2, with the following circuit component values are, $R_S = 1.5\text{ k}\Omega$, $R_1 = 55\text{ k}\Omega$, $R_2 = 15\text{ k}\Omega$, $R_E = 1.5\text{ k}\Omega$, $R_C = 5\text{ k}\Omega$ and $R_L = 10\text{ k}\Omega$. The transistor has a small-signal parameters, $\beta = 120$, $r_\pi = 1.5\text{ k}\Omega$ and $r_o = \infty$. Assume that, C_{C2} is infinity.



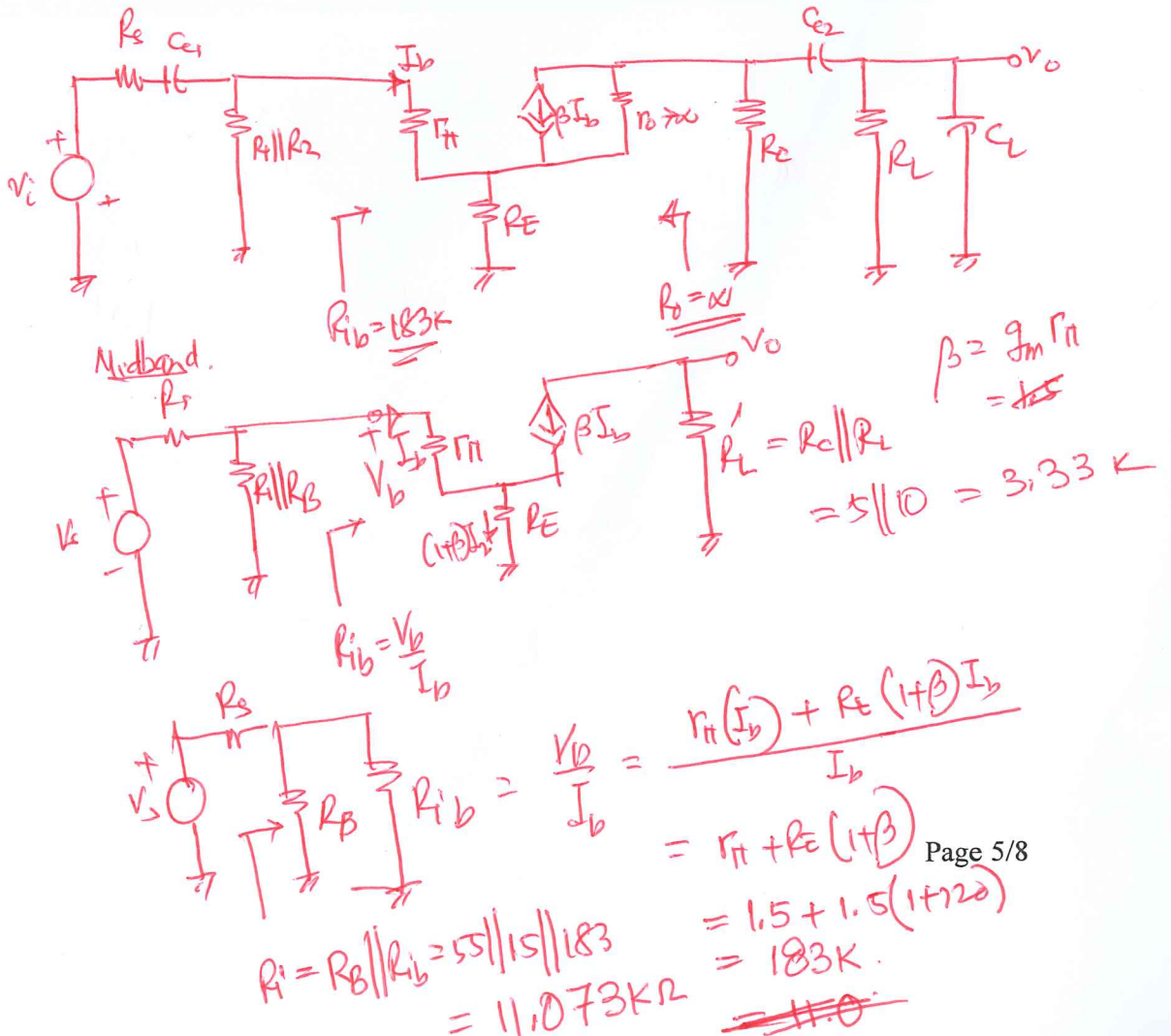- i. Draw the small-signal equivalent circuit (3 marks)
- ii. Evaluate the midband voltage gain, $A_v = \frac{v_o}{v_i}$ in dB scale. (6 marks)
- iii. Design the circuit so that the -3dB lower corner frequency, $f_L = 200\text{Hz}$. (7 marks)
- iv. If, $C_L = 10\text{ nF}$ determine the -3dB upper corner frequency, f_H . (4 marks)



(Space for answer to the question Q.2)

$$\begin{aligned}
 A_{vA} &= \frac{v_b}{v_b} = \frac{-\beta I_b R_L'}{r_{\pi} I_b + R_E (1+\beta) I_b} \\
 &= \frac{-\beta R_L'}{r_{\pi} + R_E (1+\beta)} = -\frac{120 \times 3.33 \text{ K}}{1.83 \text{ K}} \\
 &= -2.186
 \end{aligned}$$

$$\begin{aligned}
 A_v &= A_{vA} \frac{R_i}{R_i + R_s} = -2.186 \times \frac{11.073 \text{ K}}{(11.073 + 1.5) \text{ K}} \\
 &= -1.925 \text{ V/V} \\
 &= \underline{5.689 \text{ dB}} \quad \blacktriangleleft
 \end{aligned}$$

$$f_L = \frac{1}{2\pi C_C (R_s + R_i)}$$

$$\begin{aligned}
 \therefore C_C &= \frac{1}{2\pi f_L (R_s + R_i)} = \frac{1}{2\pi \times 200 \times (1.5 + 11.073) \text{ K}} \\
 &= 63.29 \text{ nF} \quad \blacktriangleleft
 \end{aligned}$$

$$f_H = \frac{1}{2\pi C_C R_L'} = \frac{1}{2\pi \times 10 \text{ n} \times 3.33 \text{ K}}$$

$$= 4.78 \text{ kHz} \quad \blacktriangleleft$$

Q.3 [10 marks]

(a) Draw the detail high-frequency model of a MOSFET and mention the name of each parameter. (2 marks)

(b) A short-circuit MOSFET current amplifier as shown in Fig. 3(b).

i) Determine step by step the unity gain bandwidth or f_T of the MOSTET. (6 marks)


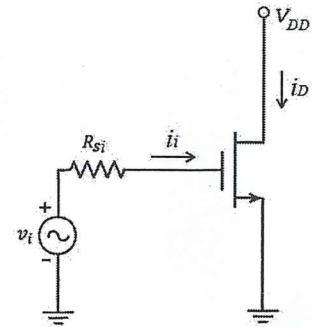
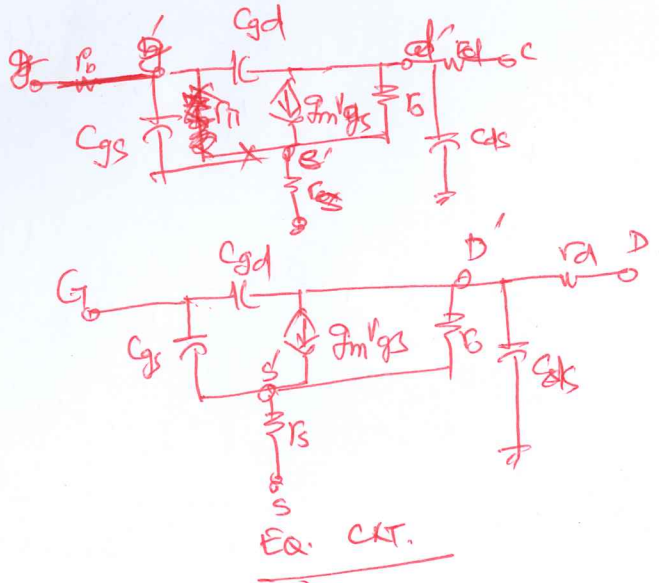


Fig. 3(b)

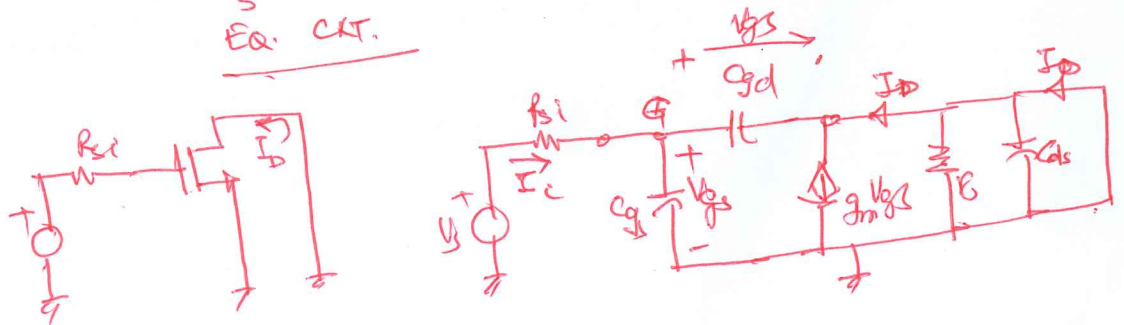

$$I_i = sC_{gs}V_{gs} + sC_{gd}V_{gd}$$

$$I_D = g_m V_{gs} - sC_{gd}V_{gs}$$

$$\therefore A_2 = \frac{I_D}{I_i} = \frac{g_m V_{gs} - sC_{gd}V_{gs}}{sV_{gs}(C_{gs} + C_{gd})} = \frac{g_m - sC_{gd}}{s(C_{gs} + C_{gd})}$$

$$\approx \frac{g_m}{s(C_{gs} + C_{gd})} = \frac{g_m}{j\omega(C_{gs} + C_{gd})}$$

$$A_2 = 1 = \left| \frac{g_m}{\omega_T(C_{gs} + C_{gd})} \right| \Rightarrow \therefore \omega_T = \frac{g_m}{C_{gs} + C_{gd}}$$

$$\therefore f_T = \frac{1 \cdot g_m}{2\pi(C_{gs} + C_{gd})}$$

- ii) Calculate the bandwidth of the amplifier for current gain equal 15. Assume that, the MOSFET parameter are, $g_m = \frac{15mA}{V}$, $C_{gs} = 12pF$ and $C_{gd} = 5pF$ (2 marks)

$$\frac{1}{s} + \frac{1}{s} + R_p$$

$$= \frac{1}{s} + \frac{1}{s} + R_p$$

$$f_T = BW \cdot Gain$$

$$f_T = \frac{g_m}{2\pi(C_{gd} + C_{gs})} = \frac{15m}{2\pi(12+5)p} = 140,43 \text{ MHz}$$

$$\therefore f_T = BW \times Gain \Rightarrow BW = \frac{f_T}{Gain} = \frac{140,43 \text{ MHz}}{15} = \underline{\underline{9,362 \text{ MHz}}}$$

END OF QUESTION