

الجامعة الإسلامية العالمية ماليزيا  
INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA  
يُونِيسْتِي اِسْلَامْ اِنْتَار اَبْحَسَا مَلِيسِيَا

## KULLIYAH OF ENGINEERING

### END OF SEMESTER EXAMINATION SEMESTER I, 2020/2021 SESSION

Programme	: Engineering	Level of Study	: UG 2
Time	: 2:30 pm - 5:30 pm	Date	: 14/01/2021
Duration	: 3 Hrs		
Course Code	: EECE 2312	Section(s)	: 1-2
Course Title	: Electronic Circuits		

This Question Paper Consists of **5 (Five)** Printed Pages (Including Cover Page) with **4 (Four)** Questions.

#### INSTRUCTION(S) TO CANDIDATES

- Total mark of this examination is **80**.
- This examination is worth **60%** of the total course assessment.
- Answer **ALL QUESTIONS**.
- Marks assigned to each problem are listed in the margins.
- Online exam
- **Note that one of the conditions to pass the course is to obtain at least 50 % of this examination.**

#### **DECLARATION**

By answering this final examination, I hereby declare that:


- The whole answer of this final examination is my own work.
- I do not receive any help from any other parties in answering on any part of this final examination.
- I do not give any clue, hint or work to other students in answering on any part of this final examination.
- I understand that any form of cheating or attempt to cheat is a serious offence, which may lead to dismissal.

**Question 1 [20 marks]**


- (a) Derive the transfer function step by step for the RC-circuit shown in **Fig. 1 (a)** the following standard format:

$$T(s) = k \frac{1 + s\tau_1}{1 + s\tau_2}$$

where,  $\tau_1$  and  $\tau_2$  are the two different time constants, and  $k$  is a frequency independent constant. **(7 marks)**

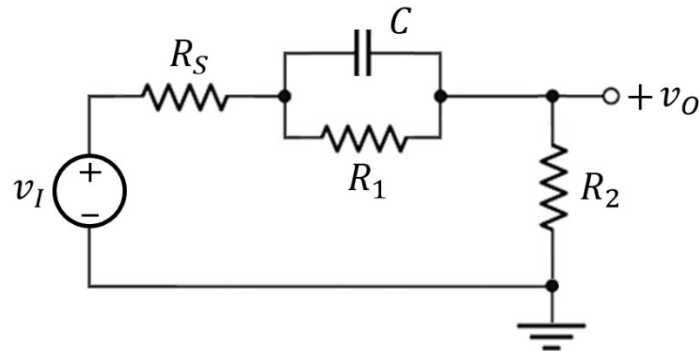**Fig. 1(a)**

- (b) Determine the  $-3$  dB lower corner, upper frequencies and bandwidth of the circuit as shown in **Fig. 1(b)**. The circuit components are  $R_1 = 2.5$  k $\Omega$ ,  $R_2 = 4.0$  k $\Omega$ ,  $C_1 = 150$  pF and  $C_2 = 80$  nF respectively. **(3 marks)**

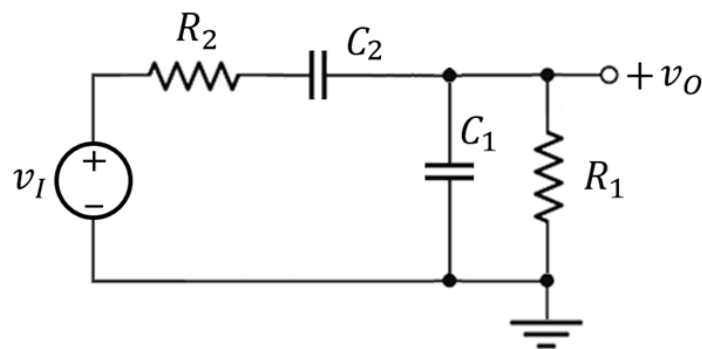**Fig. 1(b)**


- (c) Plot the Bode magnitude and phase for the following transfer function and determine the magnitude and phase at angular frequency 80 rad/sec. **(6+4 marks)**

$$T(s) = \frac{1.25 \times 10^{-3} s(s + 50)}{(s + 20)(s + 90)}$$

**Question 2 [20 marks]**


(a) The common emitter amplifier is shown in **Fig. 2(a)** with the following circuit component values  $R_S = 5 \text{ k}\Omega$ ,  $C_{C1} = 0.1 \text{ }\mu\text{F}$ ,  $R_1 = 180 \text{ k}\Omega$ ,  $R_2 = 85 \text{ k}\Omega$ ,  $R_E = 0.5 \text{ k}\Omega$ ,  $R_C = 3 \text{ k}\Omega$ , and  $R_L = 10 \text{ k}\Omega$ . The BJT has AC small-signal hybrid- $\pi$  parameters,  $g_m = 50 \text{ mA/V}$ ,  $r_\pi = 1.5 \text{ k}\Omega$  and  $r_o = \infty$ . **(14 marks)**

- i. Find the lower corner frequency due to  $C_{C1}$ .
- ii. Design the amplifier circuit by considering the lower corner frequency is same due to  $C_{C1}$  and upper corner frequency,  $f_H = 300 \text{ kHz}$ .
- iii. What is the bandwidth of the amplifier?
- iv. Determine the maximum gain of the designed amplifier in dB.
- v. What is the amplifier gain if  $R_S$  is bypassed by a large capacitance?

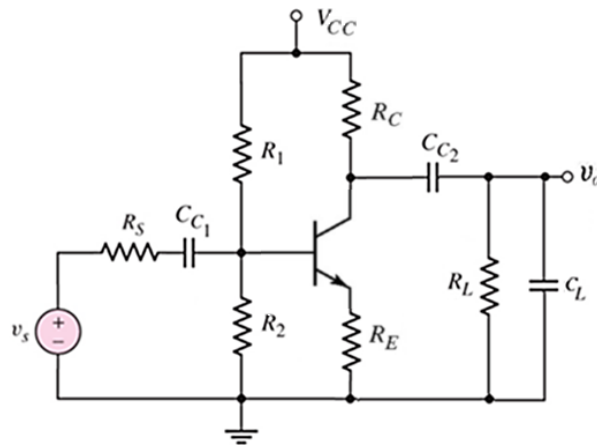

**Fig. 2(a)**

(b) The common source amplifier is shown in **Fig. 2(b)**. Assume that the MOSFET has small-signal high frequency parameters,  $g_m = 2 \text{ mA/V}$ ,  $r_o = 25 \text{ k}\Omega$ ,  $C_{gs} = 20 \text{ pF}$  and  $C_{ds} = 12 \text{ pF}$ . Draw the Miller equivalent circuit and determine the Miller capacitance,  $C_M$ . **(6 marks)**

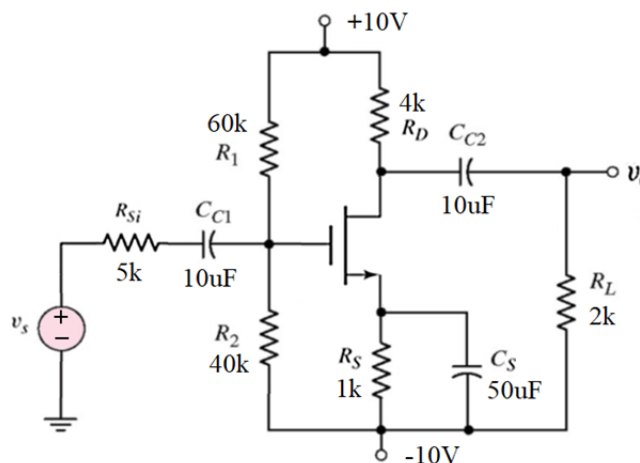

**Fig. 2(b)**



**Question 4 [20 marks]**

- (a) The feedback current  $i_{fb}$  and error current  $i_e$  of a feedback amplifier are 0.5 mA and 85  $\mu$ A respectively. Determine the gain of the feedback amplifier. Assume that the open-loop gain of the amplifier is  $2.5 \times 10^4$ . **(5 marks)**
- (b) The change of gain is 55% of a voltage amplifier without feedback. Design a feedback amplifier to determine the feedback factor  $\beta_v$  so that the change of gain would be reduced to 5%. Assume that the open-loop gain of the amplifier is 60 dB. **(5 marks)**
- (c) The bandwidth of a voltage amplifier is extended 175 times after feedback. Determine the input and output resistances  $R_{if}$ ,  $R_{of}$  and voltage gain  $A_{vf}$  after feedback. Assume that the input resistance, output resistance and voltage gain without feedback of the amplifier are,  $R_i = 10 \text{ k}\Omega$ ,  $R_o = 5 \text{ k}\Omega$ ,  $A_v = 1500$  respectively and bandwidth of the amplifier without feedback is 5 kHz. **(5 marks)**
- (d) Draw the schematic and design an Op-amp based phase-shift oscillator for generating frequency of 5.0 kHz. **(5 marks)**

**END OF QUESTIONS**