



الجامعة الإسلامية العالمية ماليزيا

**INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA
END OF SEMESTER EXAMINATION
SEMESTER I, 2014/2015 SESSION
KULLI YAH OF ENGINEERING**

Programme : ENGINEERING Level of Study : UG 2
Time : 2:30 pm-5:30 pm Date : 30/12/2014
Duration : 3 Hrs
Course Code : ECE 2133 Section(s) : 1-2
Course Title : **Electronic Circuits**

This Question Paper consists of Six (6) Printed Pages with Five (5) Questions.

INSTRUCTION(S) TO CANDIDATES

DO NOT OPEN UNTIL YOU ARE ASKED TO DO SO

- A total mark of this examination is **100**.
- This examination is worth **50%** of the total assessment.
- Answer **ALL FIVE (5)** questions.
- Useful formula and necessary parameters are given in page 6.

**Any form of cheating or attempt to cheat is a serious offence
which may lead to dismissal.**

Q.1 [20 marks]

- (a) Describe the effect of C_S and C_P of the circuit shown in **Fig. 1(a)** on the frequency response shown in **Fig. 1(b)**. **(10 marks)**

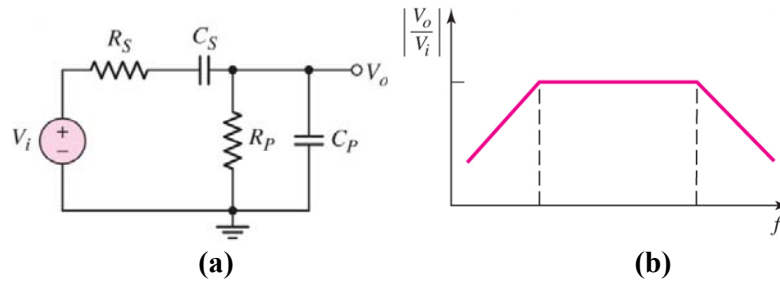


Fig. 1

- (b) Draw the frequency response curves, magnitude and phase of the following transfer function by applying Bode plot. **(10 marks)**

$$H(s) = \frac{10^6 s(s+10)}{(s+100)(s+1)}$$

Q.2 [20 marks]

Draw the small signal equivalent circuit diagram in the midband frequency region of the circuit shown in **Fig. 2**. The circuit parameters are: $R_{Si} = 0.1 \text{ k}\Omega$, $R_1 = 60 \text{ k}\Omega$, $R_2 = 40 \text{ k}\Omega$, $R_E = 0.4 \text{ k}\Omega$, $R_C = 10 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$ and neglecting the effect of C_L . The transistor has small-signal hybrid- π parameters, $r_\pi = 3 \text{ k}\Omega$, $g_m = 40\text{mA/V}$ and $r_o = \infty \text{ k}\Omega$.

Analyze the circuit by finding the followings:

- (i) The small signal voltage gain, $A_v = \frac{v_o}{v_i}$ in midband range. **(4 marks)**
- (ii) The input resistance, R_i . **(4 marks)**
- (iii) The equivalent output resistance, R_o . **(5 marks)**
- (iv) The lower corner frequency due to $C_C = 10 \mu\text{F}$. **(5 marks)**

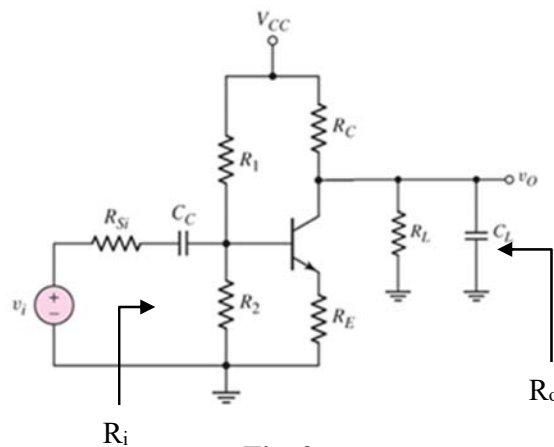



Fig. 2

What will be the midband voltage gain if R_E is short circuited of the circuit of **Fig. 2**? **(2 marks)**

Q.3 [20 marks]


The common source amplifier is shown in **Fig. 3** that operated at high frequencies. The transistor parameters are: $g_m = 40 \text{ mA/V}$ and $r_o = \infty$, $C_{gd} = 35 \text{ pF}$, and $C_{gs} = 4 \text{ pF}$ and $C_L = 5 \text{ pF}$.

- (i) Draw the simplified high-frequency small signal equivalent circuit diagram. **(3 marks)**
- (ii) How do you find Miller capacitance? What is the value of Miller capacitance. **(6 marks)**
- (iii) Evaluate the upper 3dB frequency (f_H) considering Miller capacitance **(3 marks)**
- (iv) Evaluate the upper 3dB frequency (f_H) without considering Miller capacitance. **(3 marks)**
- (v) Evaluate the upper 3dB frequency (f_H) considering load capacitance $C_L = 5 \text{ pF}$. **(4 marks)**
- (vi) How do you evaluate the the upper 3dB frequency? **(1 mark)**

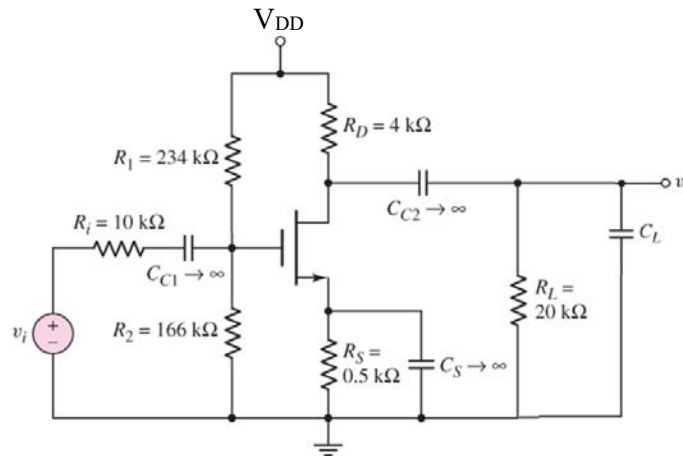**Fig. 3**

Q.4 [20 marks]

- (a) The circuit diagram of a Wildar current source is shown in **Fig. 4(a)**. Design the circuit such that $I_o = 20\mu\text{A}$ and $I_{\text{REF}} = 100\mu\text{A}$ neglecting the base current. Also determine the $V_{\text{BE}2}$. [Given that $V^+ = 3.3\text{ V}$, $V^- = -3.3\text{ V}$, $V_{\text{BE}1} = 0.7\text{ V}$ and $V_A = \infty$] **(10 marks)**

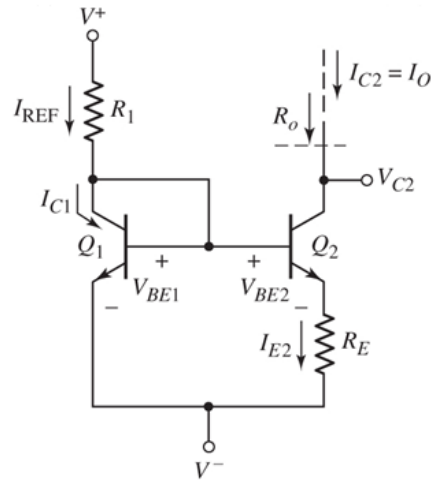**Fig. 4(a)**

- (b) Define feedback amplifier and describe its advantages and disadvantages of the negative feedback amplifier. **(5 marks)**
- (c) The open-loop low-frequency gain of a series shunt amplifier is $A_v = 5 \times 10^4$ and the open loop 3 dB frequency is $f_H = 10\text{ kHz}$. If the closed-loop gain is $A_{vf} = 25$, what is the closed loop bandwidth? If the open-loop amplifier $R_i = 10\text{ K}\Omega$ and $R_o = 100\ \Omega$, what is the value of input resistance, R_{if} and output resistance R_{of} of the feedback amplifier? **(5 marks)**

Q.5 [20 marks]

- (a) The ideal feedback amplifier topology is shown **Fig. 5(a)**. Identify the type of feedback and derive step by step the closed loop gain, A_{gf} , the input resistance, R_{if} and output resistance R_{of} . **(10 marks)**

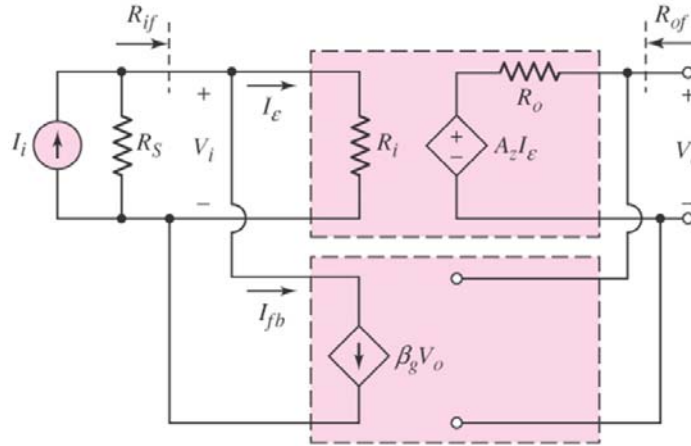


Fig. 5(a)

- (b) Derive step by step the DC transfer characteristic equations (i_c as a function of v_d) for the differential amplifier shown in **Fig. 5(b)** and draw the transfer characteristics curve (i_c versus v_d) **(10 marks)**

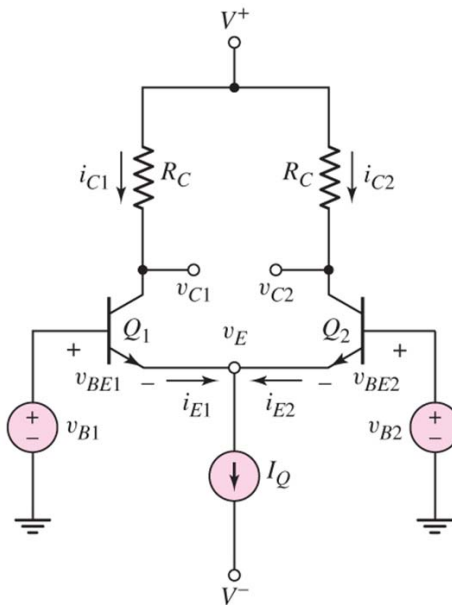


Fig. 5(b)

USEFUL FORMULA

BJT	MOSFET
$i_C = I_S e^{v_{BE}/V_T} \cdot \left(1 + \frac{v_{CE}}{V_A}\right)$ $g_m = \frac{I_{CQ}}{V_T}$ $r_\pi = \frac{\beta V_T}{I_{CQ}}$ $r_o = \frac{V_A}{I_{CQ}}$ $V_T = 26 \text{ mV}$ $V_{BE}(\text{on}) = 0.7 \text{ V}$	$I_D = \frac{1}{2} k'_n \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$ $g_m = 2\sqrt{K_n I_{DQ}}$ $r_o = \frac{1}{\lambda I_{DQ}}$ $K_n = \frac{k'_n}{2} \left(\frac{W}{L}\right)$