

الجامعة الإسلامية العالمية ماليزيا
INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA
يُونَيْتِي إِسْلَامًا، إِنْتَارَا إِجْسَابًا مَلَيْسِيَا

KULLIYAH OF ENGINEERING

**END OF SEMESTER EXAMINATION
SEMESTER I, 2015/2016 SESSION**

Programme	: Engineering	Level of Study	: UG 2
Time	: 9:00 am -12:00 pm	Date	: 30/12/2015
Duration	: 3 Hrs		
Course Code	: ECE 2133	Section(s)	: 1-2
Course Title	: Electronic Circuits		

This Question Paper Consists of **6 (Six)** Printed Pages (Including Cover Page) with **5 (Five)** Questions.

INSTRUCTION(S) TO CANDIDATES

DO NOT OPEN UNTIL YOU ARE ASKED TO DO SO

- Total mark of this examination is **100**.
- This examination is worth **50 %** of the total course assessment.
- Answer **ALL QUESTIONS**.
- Only approved calculator with 'KoE approved' sticker is allowed (non-programmable and non-graphical).
- Marks assigned to each problem are listed in the margins.

Any form of cheating or attempt to cheat is a serious offence which may lead to dismissal.

***All electronics gadgets are prohibited in the exam hall / venue.
(e.g. mobile / smart phones, smart watches, and smart glasses)***

QUESTION 1 (20 marks)

- (a) Find the transfer function of the circuit shown in **Fig. 1(a)** and its the corner frequency. What should be the maximum gain of the circuit? (8 marks)

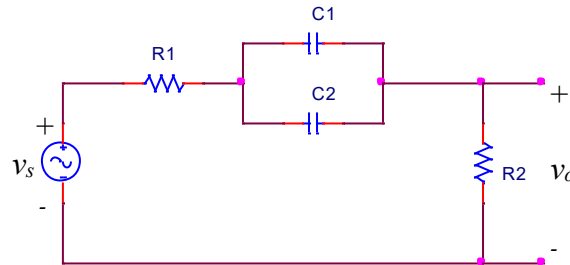


Fig. 1(a)

- (b) Draw the frequency response curves, magnitude and phase of the following transfer function by applying Bode plot. (12 marks)

$$H(s) = \frac{10^6 s(s + 5)(s + 50)}{(s + 500)}$$

QUESTION 2 (20 marks)

Design an audio amplifier as shown in **Fig. 2** such that the lower corner frequency is 20 Hz and upper frequency is 20 kHz. The transistor has small-signal hybrid- π parameters, $r_\pi = 3 \text{ k}\Omega$, $g_m = 40\text{mA/V}$ and $r_o = \infty$. (10 marks)

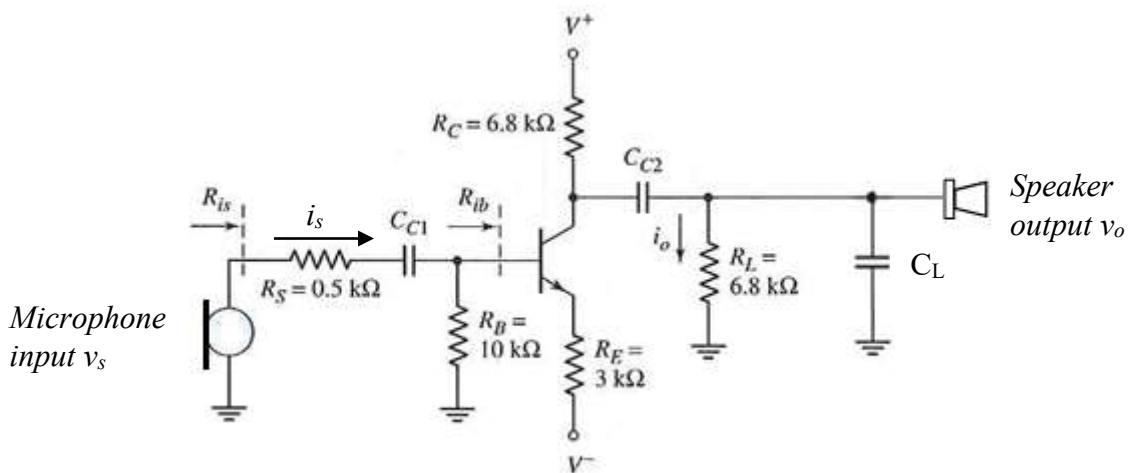


Fig. 2

What should be the output voltage of the speaker, if the microphone input voltage is 20 mV? (5 marks)

Find the current gain, $A_i = \frac{i_o}{i_s}$ of the audio amplifier. (5 marks)

QUESTION 3 (20 marks)

- a) Draw a small signal high frequency equivalent circuit diagram of a short circuited BJT amplifier shown in **Fig. 3(a)**. Analyze the circuit step by step to find the short circuit current gain, $A_i = \frac{i_o}{i_i}$. Find the beta frequency, f_{β} of the amplifier. What should be the unity gain frequency, f_T of the amplifier? (10 marks)

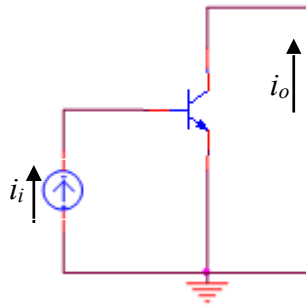


Fig. 3 (a)

- b) A common source amplifier is shown in **Fig. 3 (b)** that operates at high frequencies. The transistor parameters are: $g_m = 40 \text{ mA/V}$ and $r_o = 100 \text{ K}\Omega$, $C_{gs} = 15 \text{ pF}$ and $C_{gd} = 3 \text{ pF}$.
- (i) Draw the simplified high-frequency small signal equivalent circuit diagram. (2 marks)
 - (ii) What is the equivalent Miller capacitance? (3 marks)
 - (iii) Determine the upper 3 dB frequency. (2 marks)
 - (iv) Find the midband voltage gain in dB. (3 marks)

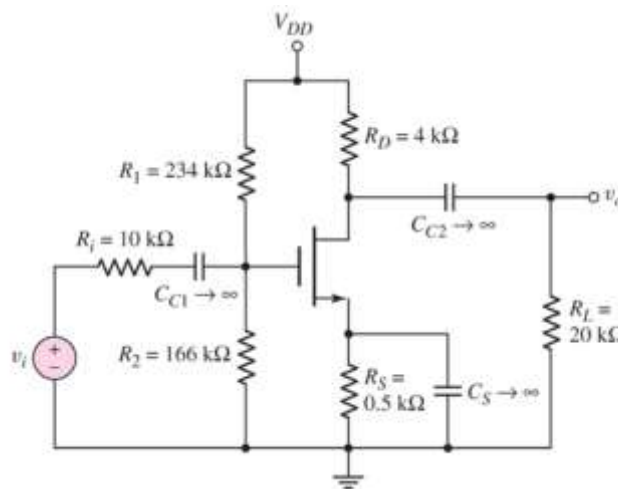


Fig. 3(b)

QUESTION 4 (20 marks)

- a) The circuit diagram of a Wildar current source is shown in **Fig. 4(a)**. Design the circuit such that $I_o = 10\mu\text{A}$ and $I_{\text{REF}} = 150\mu\text{A}$ by neglecting base current. Also determine $V_{\text{BE}2}$ for the circuit [Given that $V^+ = 5\text{ V}$, $V^- = -5\text{ V}$, $V_{\text{BE}1} = 0.7\text{ V}$ and $V_A = \infty$] (5 marks)

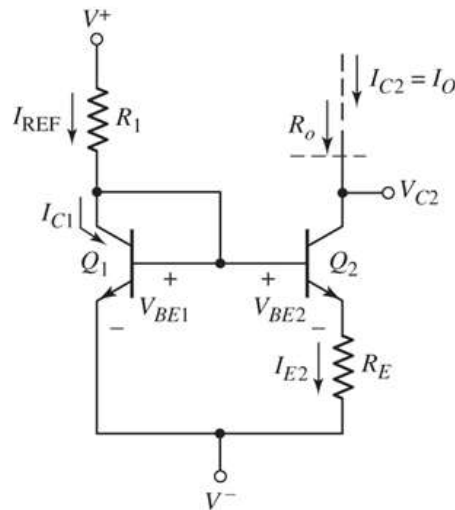


Fig. 4(a)

- b) (i) Design a MOSFET current source as shown in **Fig. 4(b)** such that $I_R = 25\text{ mA}$, $I_o = 50\text{ mA}$, and $V_{\text{DS}2(\text{sat})} = 0.3\text{ V}$. The biasing voltages $V^+ = 5\text{ V}$. The transistors are available with parameters: $k'_n = 60\mu\text{A}/\text{V}^2$, $V_{\text{TN}} = 0.4\text{ V}$ and $\lambda = 0$. (4 marks)

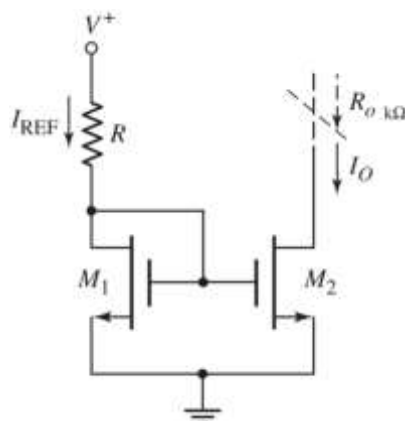


Fig. 4(b)

- (ii) Draw a new current source by using only BJTs with replacing the MOSFETs in **Fig. 4(b)** (1 marks)

- c) Define negative feedback and state its advantages and disadvantages for the amplifier. (5 marks)
- d) A negative feedback amplifier has a closed loop gain of $A_f = 100$ and an open loop gain of $A = 5 \times 10^4$. (i) Determine the feedback transfer function β . (ii) What should be the closed loop bandwidth if the open loop bandwidth is 5 kHz (5 marks)

QUESTION 5 (20 marks)

- a) Draw the block diagram and small signal equivalent circuit diagram of a shunt-shunt ideal feedback amplifier and identify the type of amplifiers used in the feedback amplifier. Analyze step by step the feedback amplifier to find the closed loop gain, A_f , the input resistance, R_{if} and the output resistance R_{of} in terms of open-loop amplifier parameters. (10 marks)
- b) Define differential input voltage, v_d and common mode input voltage, v_{cm} of a differential amplifier. Derive step by step the DC transfer characteristic equations (i_c as a function of v_d) for the differential amplifier shown in **Fig. 5(b)** and draw its transfer characteristics curve (i_c versus v_d). (10 marks)

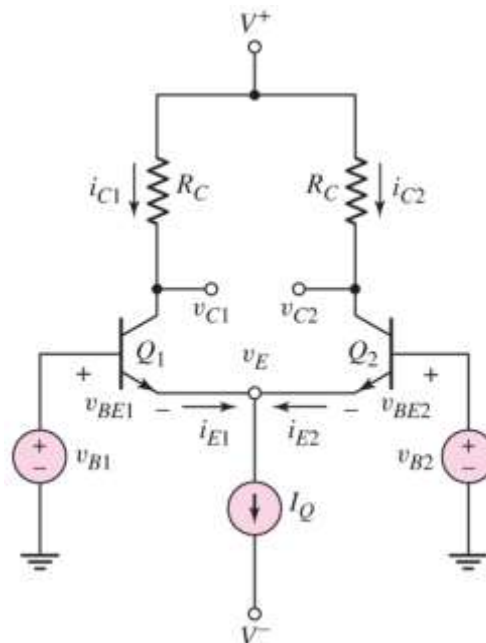


Fig. 5(b)

USEFUL FORMULA

BJT	MOSFET
$i_C = I_S e^{v_{BE}/V_T} \cdot \left(1 + \frac{v_{CE}}{V_A}\right)$ $g_m = \frac{I_{CQ}}{V_T}$ $r_\pi = \frac{\beta V_T}{I_{CQ}}$ $r_o = \frac{V_A}{I_{CQ}}$ $V_T = 26 \text{ mV}$ $V_{BE}(\text{on}) = 0.7 \text{ V}$	$I_D = \frac{1}{2} k'_n \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$ $g_m = 2\sqrt{K_n I_{DQ}}$ $r_o = \frac{1}{\lambda I_{DQ}}$ $K_n = \frac{k'_n}{2} \left(\frac{W}{L}\right)$

END OF PAPER