

الجامعة الإسلامية العالمية ماليزيا
INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA
يُونَيْتِي سَلَامٌ، أَنْتَ رَابِعٌ مَلِيْسِيَا

KULLIYAH OF ENGINEERING

**END OF SEMESTER EXAMINATION
SEMESTER 1, 2018/2019 SESSION**

Programme	: Engineering	Level of Study	: UG 2
Time	: 2:30 pm -5:30 pm	Date	: 31/12/2018
Duration	: 3 Hrs		
Course Code	: EECE 2313/ECE 2133	Section(s)	: 1-2
Course Title	: Electronic Circuits		

This Question Paper Consists of **6 (Six)** Printed Pages (Including Cover Page) with **5 (Five)** Questions.

INSTRUCTION(S) TO CANDIDATES

DO NOT OPEN UNTIL YOU ARE ASKED TO DO SO

- Total mark of this examination is **100**.
- This examination is worth **50 %** of the total course assessment.
- Answer **ALL QUESTIONS**.
- Only approved calculator with 'KoE approved' sticker is allowed (non-programmable and non-graphical).
- Marks assigned to each problem are listed in the margins.

Any form of cheating or attempt to cheat is a serious offence which may lead to dismissal.

***All electronics gadgets are prohibited in the exam hall / venue.
(e.g. mobile / smart phones, smart watches, and smart glasses)***

Q.1 [20 marks]

- (a) Consider the circuit shown in **Fig. 1(a)**, derive the expression (step by step) for the voltage transfer function, $T(s) = v_o(s)/v_i(s)$. Find the corner frequency of the circuit if $R = 3 \text{ k}\Omega$, $R_1 = 6 \text{ k}\Omega$, $C_1 = 0.05 \text{ }\mu\text{F}$ and $R_2 = 8 \text{ k}\Omega$. **(8 marks)**

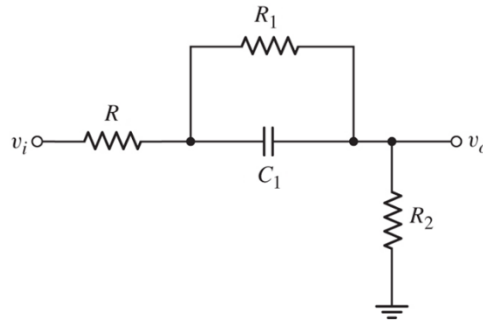


Fig. 1(a)

- (b) Draw the Bode plot (magnitude and phase) of the following transfer function. **(8 marks)**

$$T(s) = 10^7 \frac{(s + 1)(s + 100)}{(s + 1000)}$$

- (c) Determine the magnitude and phase of the transfer function from the plots drawn for **Q1(b)** at frequency $\omega = 700 \text{ radian/sec}$. **(4 marks)**

Q.2 [20 marks]

- (a) The common emitter amplifier is shown in **Fig. 2(a)** with the following circuit component values, $R_s = 0.5 \text{ k}\Omega$, $R_B = 60 \text{ k}\Omega$, $R_E = 3 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$. The BJT has small-signal hybrid- π parameters, $g_m = 40 \text{ mA/V}$, $r_\pi = 3 \text{ k}\Omega$ and $r_o = 100 \text{ k}\Omega$.

Design the amplifier circuit that operates at lower corner frequency, $f_L = 60 \text{ Hz}$ and the bandwidth of the amplifier, $BW = 40 \text{ kHz}$. Determine the midband voltage and current gain of the designed amplifier in dB. **(14 Marks)**

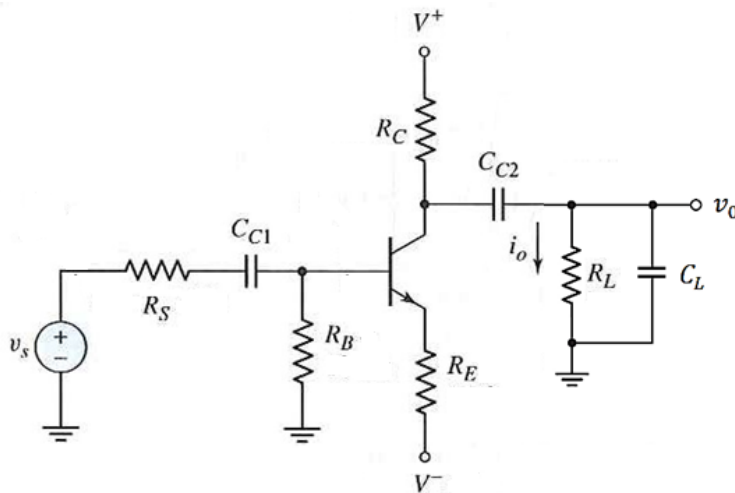


Fig. 2(a)

(b) Draw a small signal high frequency equivalent circuit diagram of a short circuited BJT amplifier as shown in **Fig. 3(a)**. Analyze the circuit step by step to find the short circuit current gain, $A_i = \frac{i_o}{i_i}$. Evaluate the unity gain bandwidth, f_T of the BJT if the transistor parameters are given as $g_m = 2 \text{ mA/V}$, $C_{gd} = 10 \text{ fF}$ and $C_{gs} = 50 \text{ fF}$.

(10 marks)

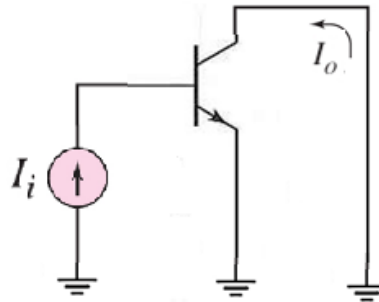


Fig. 2(b)

Q.3 [20 marks]

(a) Derive step by step the relation between I_{REF} and I_o a three-transistor current source as shown in **Fig. 3(a)** and design the current source such that $I_o = 5 \text{ mA}$. The transistor parameters are: $V_{BE(on)} = 0.7 \text{ V}$, $\beta = 100$ and $V_A = \infty$. (10 marks)

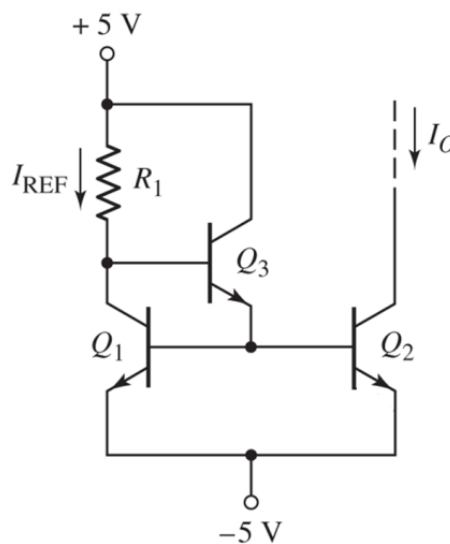


Fig. 3(a)

(b) Draw the small signal equivalent circuit diagram of the current source shown in **Fig. 3(a)**. (2 marks)

- (c) Design a MOSFET current source as shown in Fig. 3(c) such that $I_{REF} = 0.1\text{mA}$, $I_{O1} = 0.2\text{mA}$, $I_{O2} = 0.3\text{mA}$ assuming M_3 , M_4 and M_5 are identical. The transistors are available with parameters $k'_n = 80\ \mu\text{A}/\text{V}^2$, $V_{TN} = 0.7\text{V}$ and $\lambda = 0$. **(8 marks)**

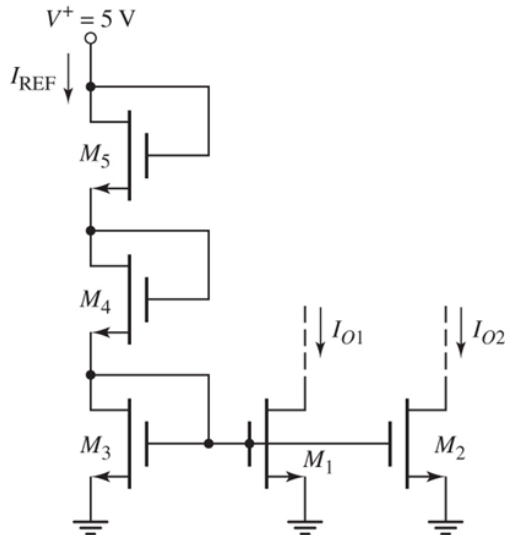


Fig. 3(c)

Q.4 [20 marks]

- (a) Draw a basic configuration of a feedback amplifier and show step by step that the gain sensitivity is reduced by a factor of $(1 + \beta A)$. **(5 marks)**
- (b) Draw the block diagram and small signal equivalent circuit diagram of a Shunt-Shunt ideal feedback amplifier. Analyze step by step the feedback amplifier to find the expression of the closed loop gain, A_f , the input resistance, R_{if} and the output resistance, R_{of} in terms of open-loop amplifier gain, A and feedback amplifier gain, β . **(10 marks)**
- (c) For a series shunt feedback system, the open-loop gain A_v and closed loop gain A_{vf} of the amplifier are 10^5 and 60 respectively. Find the input resistance and output resistance of the amplifier if the input and output resistances of the basic amplifier are $R_i = 15\text{ k}\Omega$ and $R_o = 35\text{ k}\Omega$ respectively. Also find the closed loop bandwidth if the open loop amplifier bandwidth is 10 kHz. **(5 marks)**

Q.5 [20 marks]

- (a) What are the conditions for oscillation? **(2 marks)**
- (b) A wine bridge oscillator circuit is shown in **Fig. 5**. Derive the transfer function of the feedback network and derive the frequency of oscillation, f_o . Find the minimum amplifier gain for sustained oscillations. **(12 marks)**

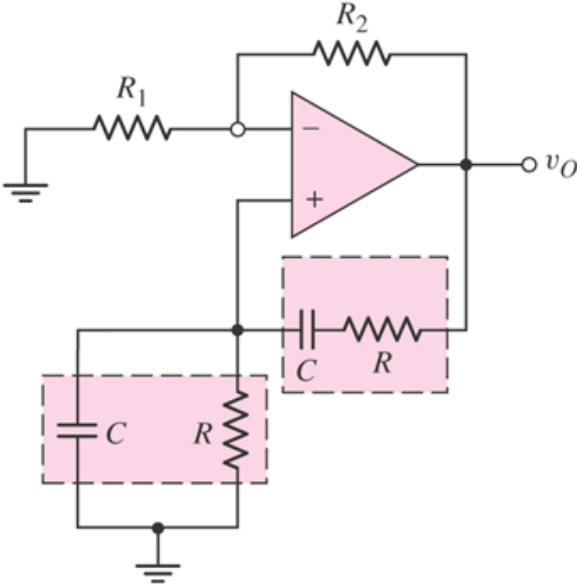


Fig. 5

- (c) Design a wine bridge oscillator for generating 10 kHz. **(4 marks)**

USEFUL FORMULA

BJT	MOSFET
$i_C = I_S e^{v_{BE}/V_T} \cdot \left(1 + \frac{v_{CE}}{V_A}\right)$ $g_m = \frac{I_{CQ}}{V_T}$ $r_\pi = \frac{\beta V_T}{I_{CQ}}$ $r_o = \frac{V_A}{I_{CQ}}$ $V_T = 26 \text{ mV}$ $V_{BE(on)} = 0.7 \text{ V}$	$I_D = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$ $g_m = 2\sqrt{K_n I_{DQ}}$ $r_o = \frac{1}{\lambda I_{DQ}}$

END OF PAPER