

الجامعة الإسلامية العالمية ماليزيا  
INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA  
يُونَيْتِي سَلَامٌ، أَنْتَ رَابِعِيَا مَلِيْسِيَا

**KULLIYAH OF ENGINEERING**

**END OF SEMESTER EXAMINATION  
SEMESTER II, 2016/2017 SESSION**

Programme	: <b>Engineering</b>	Level of Study	: <b>UG 2</b>
Time	: <b>2:30 pm -5:30 pm</b>	Date	: <b>23/05/2017</b>
Duration	: <b>3 Hrs</b>		
Course Code	: <b>EECE 2313/ECE 2133</b>	Section(s)	: <b>1-3</b>
Course Title	: <b>Electronic Circuits</b>		

This Question Paper Consists of **6 (Six)** Printed Pages (Including Cover Page) with **5 (Five)** Questions.

**INSTRUCTION(S) TO CANDIDATES**

**DO NOT OPEN UNTIL YOU ARE ASKED TO DO SO**


- Total mark of this examination is **100**.
- This examination is worth **50 %** of the total course assessment.
- Answer **ALL QUESTIONS**.
- Only approved calculator with 'KoE approved' sticker is allowed (non-programmable and non-graphical).
- Marks assigned to each problem are listed in the margins.

***Any form of cheating or attempt to cheat is a serious offence which may lead to dismissal.***

***All electronics gadgets are prohibited in the exam hall / venue.  
(e.g. mobile / smart phones, smart watches, and smart glasses)***

**Q.1 [20 marks]**

- (a) Consider the circuit shown in **Fig. 1(a)**, derive the expression (step by step) for the voltage transfer function,  $T(s) = v_o(s)/v_i(s)$ . Find the corner frequency of the circuit if  $C_{S1} = 30 \mu\text{F}$ ,  $C_{S2} = 60 \mu\text{F}$  and  $R_p = 60 \text{ k}\Omega$ . (8 Marks)

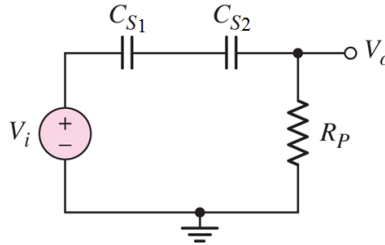

**Fig. 1(a)**

- (b) Draw the Bode plot (magnitude and phase) of the following transfer function. (8 Marks)


$$T(s) = 10^6 \frac{s(s + 50)(s + 500)}{(s + 100)}$$

- (c) Determine the magnitude and phase of the transfer function from the plots drawn for **Q1(b)** at frequency  $\omega = 200$  radian/sec. (4 Marks)

**Q.2 [20 marks]**

- (a) The common source amplifier as shown in **Fig. 2(a)** with the following circuit component values  $R_{si} = 10 \text{ k}\Omega$ ,  $R_1 = 234 \text{ k}\Omega$ ,  $R_2 = 166 \text{ k}\Omega$ ,  $R_s = 0.5 \text{ k}\Omega$ ,  $R_D = 4 \text{ k}\Omega$ ,  $R_L = 20 \text{ k}\Omega$ . The MOSFET has small-signal hybrid- $\pi$  parameters,  $g_m = 2 \text{ mA/V}$  and  $r_o = \infty$ .

Design the amplifier circuit that operate at lower corner frequency,  $f_L = 300 \text{ Hz}$  and upper corner frequency,  $f_H = 300 \text{ kHz}$ . Determine the maximum gain of the designed amplifier in dB? (10 Marks)

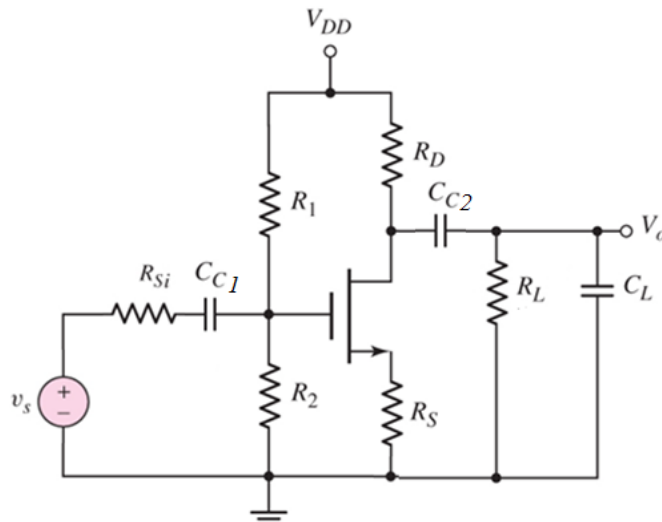

**Fig. 2(a)**

- (b) A common emitter amplifier is shown in Fig. 2 (b). It operates at very high frequencies. Consider the transistor parameters of the transistor are:  $g_m = 40 \text{ mA/V}$ ,  $r_\pi = 3 \text{ k}\Omega$  and  $r_o = 100 \text{ K}\Omega$ ,  $C_\pi = 8 \text{ pF}$  and  $C_\mu = 2 \text{ pF}$ .
- (i) Draw the simplified high-frequency small signal equivalent circuit diagram and Miller equivalent circuit diagram. (3 marks)
  - (ii) Write the expression of Miller capacitance and find its value. (3 marks)
  - (iii) Evaluate the upper 3dB frequency ( $f_H$ ) by considering Miller capacitance. (2 marks)
  - (iv) Evaluate the upper 3dB frequency ( $f_H$ ) without considering Miller capacitance. (2 marks)

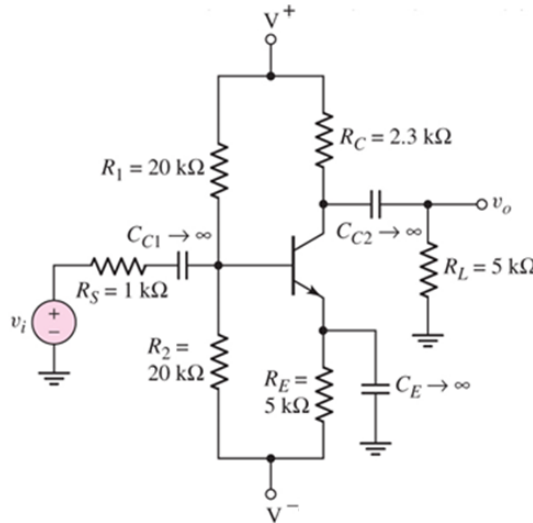


Fig. 2(b)

**Q.3 [20 marks]**

- (a) (i) The circuit diagram of a Wildar current source is shown in Fig. 3(a). Step by step derive the relationship between  $I_{REF}$  and  $I_o$  by neglecting base currents. (9 marks)
- (ii) Design the Wildar current source to produce  $I_o = 20\mu\text{A}$  for  $I_{REF} = 100\mu\text{A}$  by neglecting the base currents. Also determine the  $V_{BE2}$
- [Given that  $V^+ = 3.3 \text{ V}$ ,  $V^- = -3.3 \text{ V}$ ,  $V_{BE1} = 0.7 \text{ V}$  and  $V_A = \infty$ ] (3 marks)


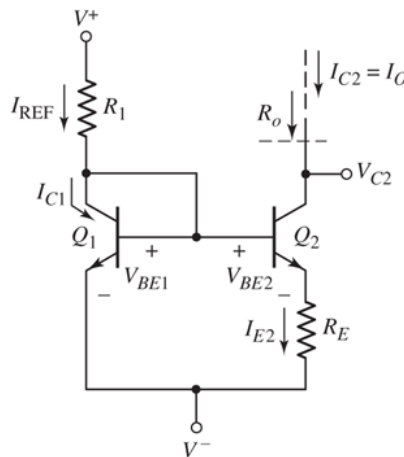


Fig. 3(a)

- (b) A multitransistor current source is shown in **Fig. 3(b)**. Design a current source such that  $I_R = 10 \text{ mA}$  and  $I_{O1} = 5 \text{ mA}$  and  $I_{O2} = 20 \text{ mA}$  by assuming  $M_3, M_4$  and  $M_5$  are identical. The transistor parameters are  $k'_n = 100 \mu\text{A}/V^2$ ,  $V_{TN} = 0.8 \text{ V}$  and  $\lambda = 0$ . (6 marks)

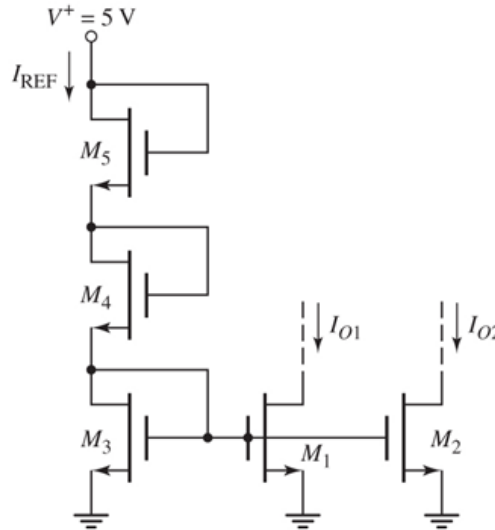

**Fig. 3(b)**

- (ii) Draw the small signal equivalent circuit diagram of the current source shown in **Fig. 3(b)**. (2 marks)

**Q.4 [20 marks]**

- (a) Define feedback system with a schematic diagram. (2 marks)


A negative feedback amplifier has a closed loop gain of  $A_f = 100$  and an open loop gain of  $A = 5 \times 10^4$ . (6 marks)

- (i) Determine the feedback transfer function  $\beta$ .  
 (ii) What should be the closed loop bandwidth if the open loop bandwidth is 5 kHz?

- (b) Draw the block diagram and small signal equivalent circuit diagram of a series-series ideal feedback amplifier. Analyze step by step the feedback amplifier to find the expression of the closed loop gain,  $A_f$ , the input resistance,  $R_{if}$  and the output resistance,  $R_{of}$  in terms of open-loop amplifier gain,  $A$  and feedback amplifier gain,  $\beta$ . (12 marks)

**Q.5 [20 marks]**

- (a) A phase-shift RC oscillator is shown in **Fig. 5(a)**. Derive the transfer function of the feedback network,  $\beta(s) = \frac{v_f(s)}{v_o(s)}$ . Derive the frequency of oscillation,  $f_o$ . Also find the minimum amplifier gain for sustained oscillations. (16 Marks)

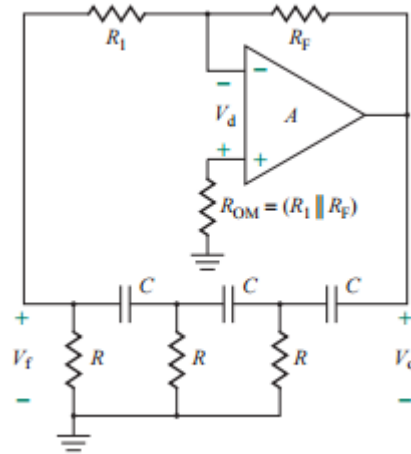**Fig. 5(a)**

- (b) Design the phase shift oscillator as shown in **Fig. 5(a)** so that the oscillation frequency is  $f_o = 1$  kHz. (4 Marks)

## USEFUL FORMULA

BJT	MOSFET
$i_C = I_S e^{v_{BE}/V_T} \cdot \left(1 + \frac{v_{CE}}{V_A}\right)$ $g_m = \frac{I_{CQ}}{V_T}$ $r_\pi = \frac{\beta V_T}{I_{CQ}}$ $r_o = \frac{V_A}{I_{CQ}}$ $V_T = 26 \text{ mV}$ $V_{BE}(\text{on}) = 0.7 \text{ V}$	$I_D = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$ $g_m = 2\sqrt{K_n I_{DQ}}$ $r_o = \frac{1}{\lambda I_{DQ}}$ $K_n = \frac{k_n'}{2} \left(\frac{W}{L}\right)$

END OF PAPER