



الجامعة الإسلامية العالمية ماليزيا

**INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA
END OF SEMESTER EXAMINATION
SEMESTER II, 2012/2013 SESSION
KULLI YAH OF ENGINEERING**

Programme : ENGINEERING Level of Study : UG 2
Time : 2:30 pm-5:30 pm Date : 26/05/2013
Duration : 3 Hrs
Course Code : ECE 2133 Section(s) : 1-2
Course Title : **Electronic Circuits**

This Question Paper consists of **Six (6)** Printed Pages (Including cover and a blank page) with **Five (5)** Questions.

INSTRUCTION(S) TO CANDIDATES

DO NOT OPEN UNTIL YOU ARE ASKED TO DO SO

- A total mark of this examination is **100**.
- This examination is worth **50%** of the total assessment.
- Answer **ALL FIVE (5)** questions.
- Useful formula and necessary parameters are given in page 6.

Any form of cheating or attempt to cheat is a serious offence which may lead to dismissal.

Q.1 [20 marks]

- (a) The MOSFET circuit is shown in **Fig. 1**, the transistor parameters are $K_n = 0.5 \text{ mA/V}^2$, $V_{TN} = 0.8\text{V}$ and $\lambda = 0$. Find V_{GS} , I_D , and V_{DS} . Also calculate the small-signal hybrid- π parameters g_m and r_o . **(10 marks)**

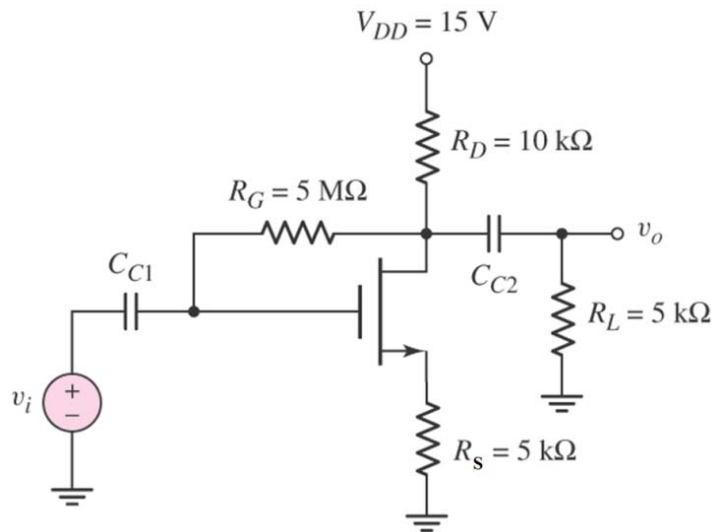


Fig. 1(a)

- (b) The BJT amplifier circuit is shown in **Fig. 1(b)**, the transistor parameters are $\beta=100$ and $V_A=100$. (i) Determine I_{CQ} and V_{CEQ} (ii) find the small-signal hybrid- π parameters r_π , g_m and r_o . **(10 marks)**

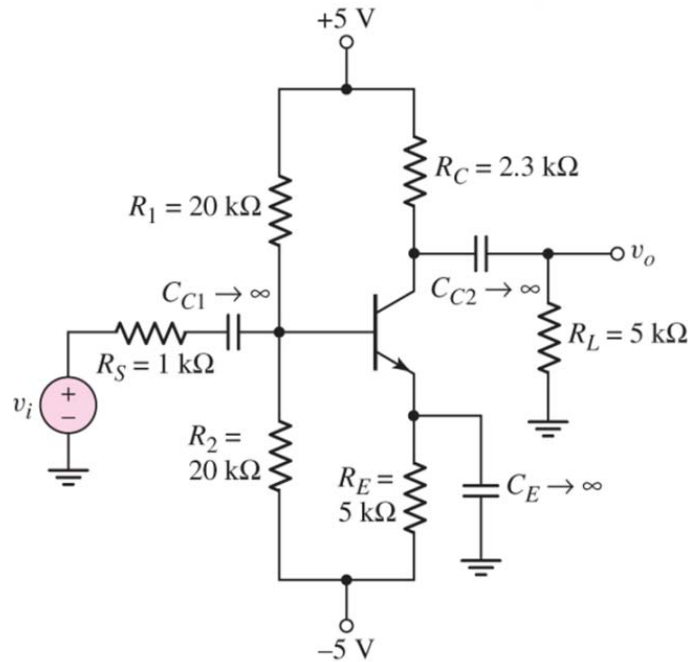


Fig. 1(b)

Q.2 [20 marks]

Draw the small signal equivalent circuit diagram of the MOSFET amplifier which is shown in **Fig. 2** and find followings; **(20 marks)**

- (i) the input resistance R_i ,
- (ii) the voltage gain $A_v = \frac{v_o}{v_s}$ and
- (iii) the output resistance R_o of the amplifier at midband frequencies . The transistor parameters are $g_m=0.65 \text{ mA/V}$ and $r_o = 100 \text{ k}\Omega$.

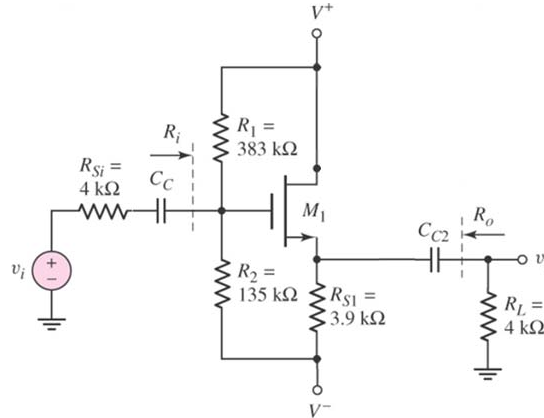


Fig. 2

Q.3 [20 marks]

(a) Draw the Bode plot (magnitude and phase) of the following transfer function.

$$H(s) = \frac{10^6 s(s+10)}{(s+100)(s+1000)} \quad \text{(8 marks)}$$

(b) The common emitter transistor amplifier is shown in **Fig. 3(b)** and the transistor has small signal hybrid- π parameters, $r_\pi = 2.5 \text{ k}\Omega$, $g_m = 40 \text{ mA/V}$ and $r_o = \infty$.

- (i) Determine the value of C_C such that the lower 3dB/corner frequency is 15Hz.
- (ii) Find the maximum current gain $|A_i|_{dB}$ in dB, where $A_i = \frac{i_o}{i_s}$. **(12 marks)**

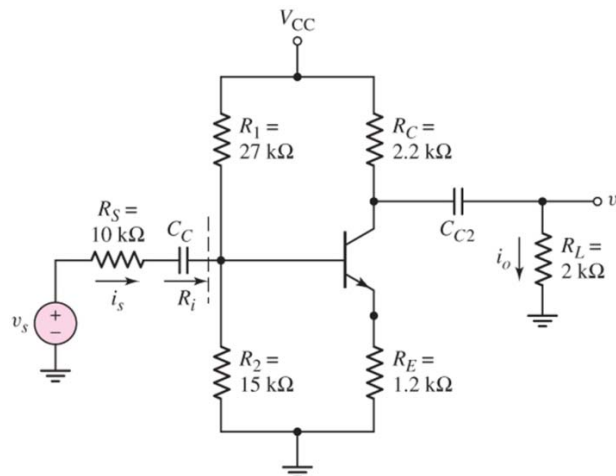



Fig. 3(b)

Q.4 [20 marks]

- (a) A BJT is biased at $I_C = 0.15 \text{ mA}$, and has parameters $\beta_o = 150$, $C_\pi = 0.8 \text{ pF}$ and $C_\mu = 0.12 \text{ pF}$. Determine beta cutoff frequency f_β and cutoff frequency f_T .

(5 marks)

- (b) The common emitter amplifier is shown in **Fig. 4(b)** which is operated at high frequencies. The transistor parameters are: $r_\pi = 3 \text{ k}\Omega$, $g_m = 40 \text{ mA/V}$ and $r_o = \infty$, $C_\pi = 25 \text{ pF}$, and $C_\mu = 2 \text{ pF}$.

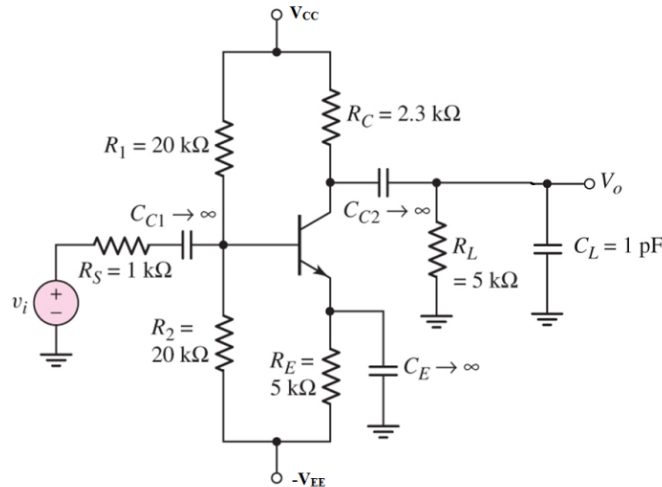(15 marks)**Fig. 4(b)**

- (i) Draw the high-frequency equivalent circuit diagram.
- (ii) Draw the Miller equivalent circuit diagram.
- (iii) Find the Miller capacitance.
- (iv) Find the upper 3 dB/corner frequency (f_H) without Miller capacitance,
- (v) Find the upper 3 dB/corner frequency (f_H) with Miller capacitance,
- (vi) Find the upper 3 dB/corner frequency (f_H) with load capacitance, C_L and
- (vii) Find the midband voltage gain.

Q.5 [20 marks]

- (a) State 5 advantages and 2 disadvantages of a negative feedback amplifier.

(5 marks)

- (b) The open-loop low-frequency voltage gain of an amplifier is $A_v = 5 \times 10^4$ and the open-loop 3 dB frequency is $f_H = 10 \text{ Hz}$. If the closed-loop gain is $A_{vf} = 25$, what is the closed-loop bandwidth?

(5 marks)

- (c) A series-series feedback amplifier topology is shown **Fig. 5(c)**. Draw the ideal equivalent circuit diagram and find the closed loop transconductance gain, A_{gf} , the input resistance, R_{if} and output resistance R_{of} .

(10 marks)

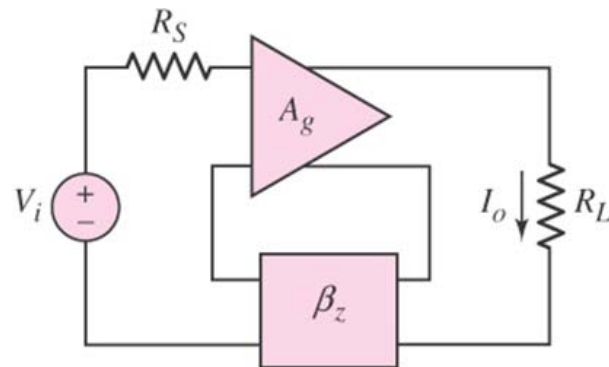


Fig. 5(c)

USEFUL FORMULA

BJT	MOSFET
$i_C = I_S e^{v_{BE}/V_T} \cdot \left(1 + \frac{v_{CE}}{V_A}\right)$ $g_m = \frac{I_{CQ}}{V_T}$ $r_\pi = \frac{\beta V_T}{I_{CQ}}$ $r_o = \frac{V_A}{I_{CQ}}$ $V_T = 26 \text{ mV}$ $V_{BE}(\text{on}) = 0.7 \text{ V}$	$g_m = 2\sqrt{K_n I_{DQ}}$ $r_o = \frac{1}{\lambda I_{DQ}}$ $K_n = \frac{k'_n}{2} \left(\frac{W}{L}\right)$