

الجامعة الإسلامية العالمية ماليزيا
INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA
يُونَيْتِي إِسْلَامُ، أَنْتَارِ ابْحَسِبَا مَلِدْسِيَا

KULLIYAH OF ENGINEERING

**END OF SEMESTER EXAMINATION
SEMESTER I, 2016/2017 SESSION**

Programme	: Engineering	Level of Study	: UG 2
Time	: 2:30 pm -5:30 pm	Date	: 23/05/2016
Duration	: 3 Hrs		
Course Code	: ECE 2133	Section(s)	: 1
Course Title	: Electronic Circuits		

This Question Paper Consists of **7 (Six)** Printed Pages (Including Cover Page) with **5 (Five)** Questions.

INSTRUCTION(S) TO CANDIDATES

DO NOT OPEN UNTIL YOU ARE ASKED TO DO SO

- Total mark of this examination is **100**.
- This examination is worth **50 %** of the total course assessment.
- Answer **ALL QUESTIONS**.
- Only approved calculator with 'KoE approved' sticker is allowed (non-programmable and non-graphical).
- Marks assigned to each problem are listed in the margins.

Any form of cheating or attempt to cheat is a serious offence which may lead to dismissal.

***All electronics gadgets are prohibited in the exam hall / venue.
(e.g. mobile / smart phones, smart watches, and smart glasses)***

Q.1 [20 marks]

(a) Draw the Bode plot (magnitude and phase) of the following transfer function. (marks 3+3)

$$T(s) = \frac{1}{150} \frac{(s+15)(s+400)}{s(s+250)}$$

(b) Determine the magnitude and phase of the transfer function from the plots drawn in Q.1(a) at a frequency, $s = 300$ radian/sec. (marks 2+2)

(c) A common emitter amplifier circuit as shown in **Fig. 1(c)** has $\beta = 90$ and $r_{\pi} = 1.5 \text{ k}\Omega$

- i. Draw the small-signal AC equivalent circuit. (marks 2)
- ii. Determine the input and output resistances of the amplifier (marks 3+2)
- iii. Calculate the corner frequencies (marks 3)

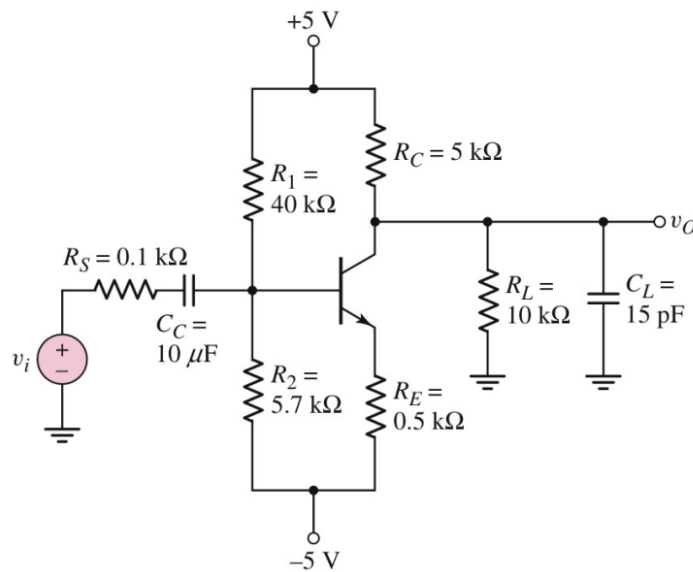


Fig. 1(c)

Q.2 [20 marks]

(a) Draw the simplified small-signal high-frequency equivalent circuit of **Fig. 1(a)**.

(marks 2)

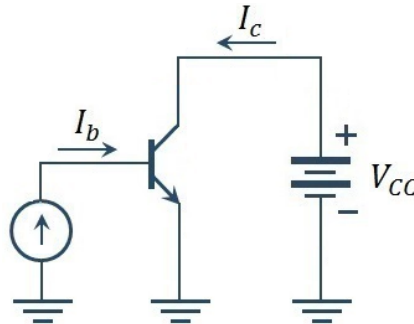


Fig. 1(a)

(b) Determine the transistor short-circuit beta frequency, f_β and cutoff frequency, f_T using the simplified small-signal high-frequency equivalent circuit of **Fig. 1(a)**.

(marks 8)

(c) A simplified small signal high-frequency transistor amplifier model is shown in **Fig. 2(c)**. The transistor parameters are, $r_\pi = 1.5\text{ k}\Omega$, $\beta = 150$, $r_o = 80\text{ k}\Omega$, $C_\pi = 20\text{ pF}$ and $C_\mu = 10\text{ pF}$. If the circuit parameters are, $R_S = 1.5\text{ k}\Omega$, $R_B = 15\text{ k}\Omega$, $R_C = 15\text{ k}\Omega$ and $R_L = 10\text{ k}\Omega$ then determine the followings:

- i. The Miller capacitor value (marks 6)
- ii. -3dB higher corner frequency (marks 4)

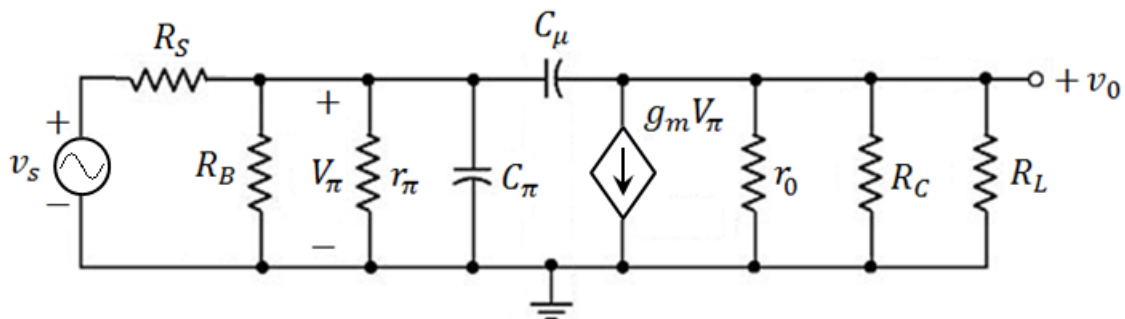


Fig. 2(c)

Q.3 [20 marks]

(a)

- i. Design a modified basic current source as shown in **Fig. 3(a)** to give an output resistance $R_0 = 45\text{ M}\Omega$. All the transistors are identical and their parameters are, $g_m = 60\text{ mA/V}$, $r_{\pi} = 2.5\text{ k}\Omega$, and $V_A = 150\text{ V}$ respectively. The circuit parameters are, $V_{CC} = 40\text{ V}$, $V_{BE1} = V_{BE2} = V_{BE3} = 0.7\text{ V}$ and $V_{CE2} = 25\text{ V}$ respectively.

(marks 3)

- ii. Determine the collector current ratio of the circuit, $\frac{I_{C2}}{I_{C1}}$.

(marks 3)

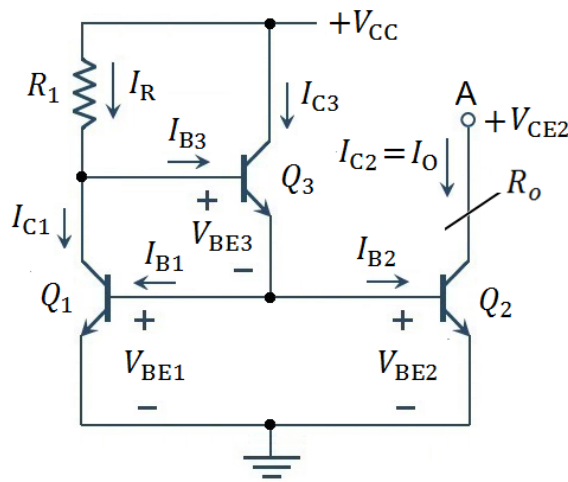


Fig. 3(a)

(b) Deduce the following expressions step by step for MOSFET current source as shown in **Fig. 3(b)**. Assuming all the MOSFETs are identical.

- i. MOSFETs parameter ratio, K_{n3}/K_{n2}

(marks 2.5)

- ii. Output resistance, R_0

(marks 2.5)

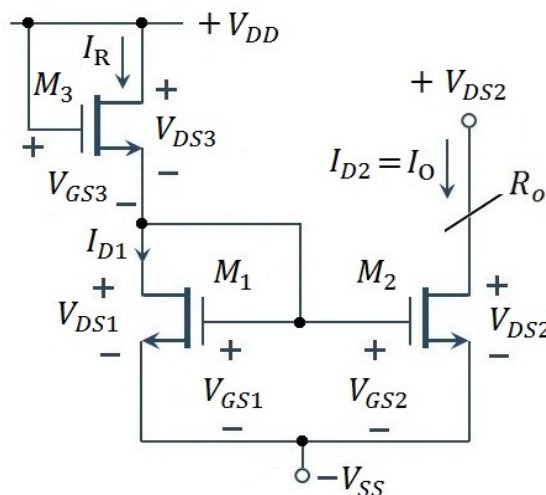


Fig. 3(b)

- iii. Design an integrated MOSFET current source as shown in **Fig. 3(b)** for output current $I_0 = I_{D1} = I_{D2} = 10 \mu\text{A}$ and output resistance $R_0 = 30 \text{ M}\Omega$. All the MOSFETs are identical and their threshold voltage $V_{t1} = V_{t2} = V_{t3} = 0.5 \text{ V}$. Assume that the supply voltage, $V_{DD} = 30 \text{ V}$, $V_{DS1} = 15 \text{ V}$ and $V_{GS1} = 10 \text{ V}$. (marks 3+3+3)

Q.4 [20 marks]

- (a) What are the merits and demerits of the negative feedback amplifier? (marks 4)
- (b) Prove that gain sensitivity of an amplifier is improved with negative feedback. (marks 4)
- (c) The open loop gain of a voltage amplifier is changed from 1000 to 850 due to temperature effects. Design a negative feedback system to improve the gain stability 1.5% by determining the feedback factor β . (marks 4)
- (d) The feedback voltage, v_{fb} and the error voltage v_e of a series-shunt amplifier are 1.5 V and 100 μV respectively. The close-loop voltage gain of the amplifier is, $A_{v_f} = -300$ and the input and output resistances of the original amplifier are $R_i = 10 \text{ k}\Omega$ and $R_o = 1.5 \text{ k}\Omega$ respectively.
- i. Determine the open-loop gain and feedback factors of the circuit. (marks 4)
 - ii. Determine the input and output resistances of the amplifier after feedback. (marks 4)

Q.5 [20 marks]

- (a) What are the conditions for oscillation? (marks 2)
- (b) A wine bridge oscillator circuit as shown in **Fig. 5(b)**, derive the equations
- i. The loop gain of the circuit for sustaining oscillation (marks 7)
 - ii. Frequency of oscillation (marks 7)

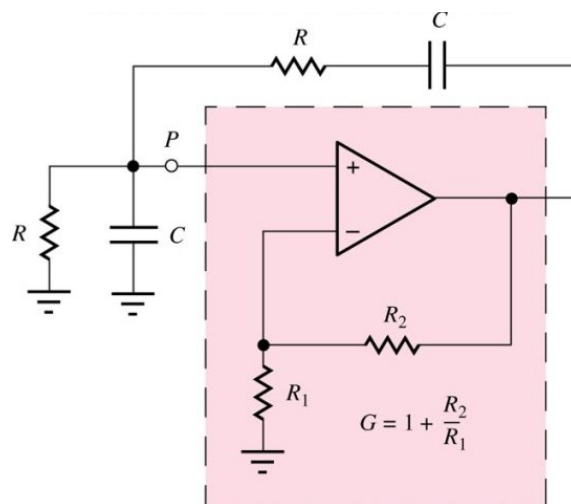


Fig. 5(b)

- (c) Design a wine bridge oscillator for generating 1.5 kHz. Assume that the capacitor value is $0.22\mu\text{F}$. (marks 4)

USEFUL FORMULA

BJT	MOSFET
$i_C = I_S e^{v_{BE}/V_T} \cdot \left(1 + \frac{v_{CE}}{V_A}\right)$ $g_m = \frac{I_{CQ}}{V_T}$ $r_\pi = \frac{\beta V_T}{I_{CQ}}$ $r_o = \frac{V_A}{I_{CQ}}$ $V_T = 26 \text{ mV}$ $V_{BE}(\text{on}) = 0.7\text{V}$	$I_D = \frac{1}{2} k'_n \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$ $g_m = 2\sqrt{K_n I_{DQ}}$ $r_o = \frac{1}{\lambda I_{DQ}}$ $K_n = \frac{k'_n}{2} \left(\frac{W}{L}\right)$

END OF PAPER