

الجامعة الإسلامية العالمية ماليزيا  
INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA  
يونسريستي إسلام انتارا نجسيا ملديسيا

**KULLIYAH OF ENGINEERING**

**END OF SEMESTER EXAMINATION  
SEMESTER I, 2022/2023 SESSION**

Programme	: Engineering	Level of Study	: UG 2
Time	: 3:00 pm - 6:00 pm	Date	: 27/01/2023
Duration	: 3 Hrs		
Course Code	: EECE 2313	Section(s)	: 1-3
Course Title	: Electronic Circuits		

This Question Paper Consists of 5 (Five) Pages (Including Cover Page)  
with 4 (Four) Questions.

**INSTRUCTION(S) TO CANDIDATES**

- Total mark of this examination is 60.
- This examination is worth 60% of the total course assessment.
- Answer ALL QUESTIONS.
- Marks assigned to each problem are listed in the margins.
- Only approved calculator with 'KoE approved' sticker is allowed (non-programmable and non-graphical).
- Note that one of the conditions to pass the course is to obtain at least 50 % of this examination.

**Any form of cheating or attempt to cheat is a serious offence which may lead to dismissal.**

DR. MD RAFIQL ISLAM  
Professor & Head  
Department of Electrical and Computer Engineering  
Kulliyah of Engineering  
International Islamic University Malaysia

**Question 1 [15 marks]**

- (a) Derive the transfer function step by step for the RC-circuit as shown in Fig. 1 (a) with following standard format:

$$T(s) = k \frac{1 + s\tau_1}{1 + s\tau_2}$$

where,  $\tau_1$  and  $\tau_2$  are the two different time constants, and  $k$  is a frequency independent constant. (5 marks)

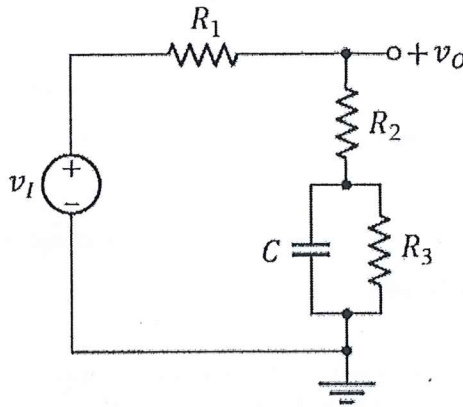


Fig. 1(a)

- (b) Determine the -3 dB lower corner frequency, upper corner frequency and bandwidth of the circuit as shown in Fig. 1(b). Consider that the circuit components are  $R_1 = 4 \text{ k}\Omega$ ,  $R_2 = 2 \text{ k}\Omega$ ,  $C_1 = 10 \text{ nF}$  and  $C_2 = 100 \text{ pF}$  respectively. (4 marks)

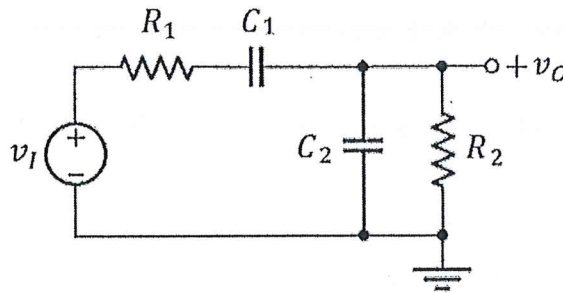


Fig. 1(b)

- (c) Plot the Bode magnitude and phase for the following transfer function and determine the magnitude and phase at angular frequency 1500 rad/sec. (4+2 marks)

$$T(s) = \frac{10^{-5} s(s + 300)}{(s + 30)}$$

**Question 2 [15 marks]**

(a) The common emitter amplifier is shown in Fig. 2(a) with the following circuit component values  $R_S = 2\text{ k}\Omega$ ,  $R_1 = 60\text{ k}\Omega$ ,  $R_2 = 30\text{ k}\Omega$ ,  $R_E = 0.5\text{ k}\Omega$ ,  $R_C = 5\text{ k}\Omega$ , and  $R_L = 4.5\text{ k}\Omega$ . The BJT has AC small-signal hybrid- $\pi$  parameters,  $g_m = 150\text{ mA/V}$ ,  $r_\pi = 5\text{ k}\Omega$  and  $r_o = 45\text{ k}\Omega$ . Assume that,  $C_E = C_{C2} = \infty$ . (4+6 marks)

- i. Draw the small-signal equivalent circuit and determine the maximum gain of the amplifier in dB scale.
- ii. Design the amplifier circuit for -3dB lower-corner frequency,  $f_L = 20\text{ Hz}$  and higher-corner frequency,  $f_H = 20\text{ kHz}$ .

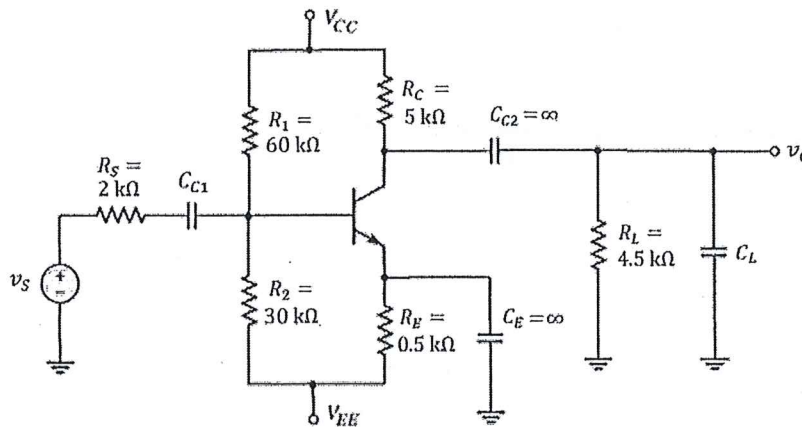


Fig. 2(a)

(b) The common emitter amplifier is shown in Fig. 2(b). Assume that the transistor has small-signal high-frequency parameters,  $g_m = 75\text{ mA/V}$ ,  $r_o = \infty$ ,  $r_\pi = 3\text{ k}\Omega$ ,  $C_\pi = 10\text{ pF}$  and  $C_\mu = 1.5\text{ pF}$ . Draw the simplified Miller high-frequency equivalent circuit and determine the -3dB higher corner frequency considering the miller capacitance effect. (5 marks)


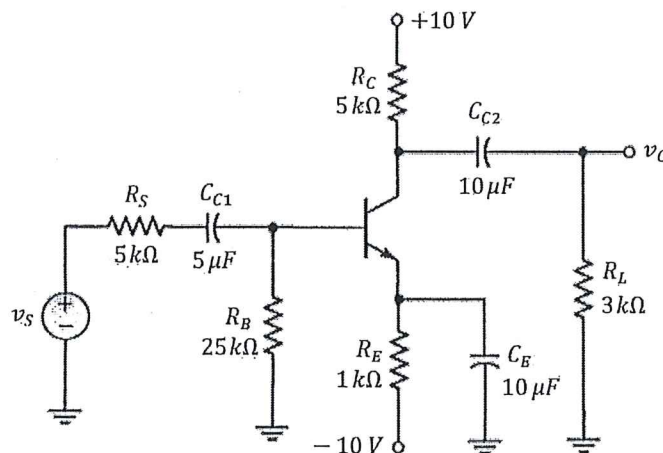


Fig. 2(b)

**Question 3 [15 marks]**

- (a) Derive the expression for the BJT Wilson current source step by step as shown in Fig. 3(a). (5 marks)

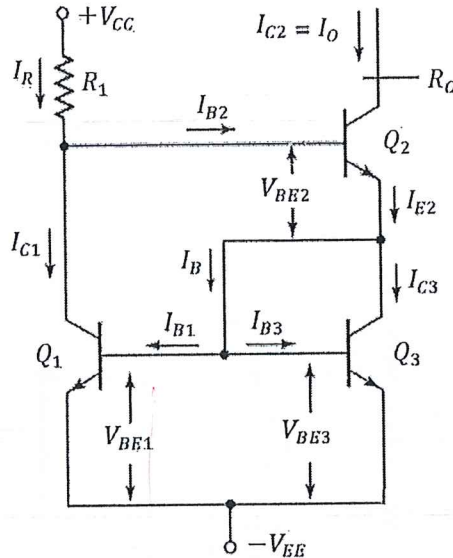

**Fig. 3(a)**

- (b) Design the current source as shown in Fig. 3(a) for output current  $I_0 = 10 \mu\text{A}$  and determine its output resistance  $R_O$ . Assume that all the transistors are identical,  $V_{CC} = +10\text{V}$ ,  $V_{EE} = -10\text{V}$ ,  $V_{BE1} = V_{BE2} = V_{BE3} = 0.7\text{V}$ ,  $\beta = 10$ ,  $V_A = 100\text{V}$  and  $r_{\pi} = 5\text{k}\Omega$ . (4 marks)


- (c) An oscillator is an electronic circuit which produces a continuous, repeated, alternating waveform without any input.

- i. What are the conditions for sustainable oscillation of a sine wave oscillator? (2 marks)

- ii. Draw the schematic design of an Op-amp based Wien Bridge oscillator and design the circuit for generating a sine wave frequency of 2 kHz. (4 marks)

**Question 4 [15 marks]**

- (a) Draw the equivalent circuit for the series-shunt feedback amplifier as shown in Fig. 4(a), and derive the expression step by step for  $A_{vf}$ ,  $R_{if}$  and  $R_{of}$  of the amplifier. **(8 marks)**

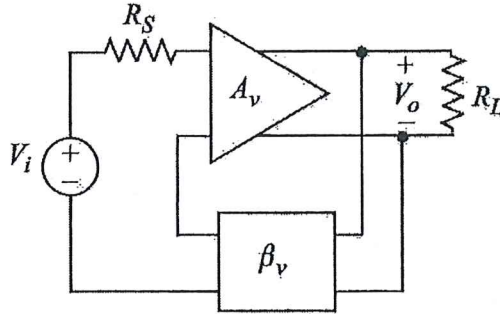**Fig. 4(a)**

- (b) The feedback voltage  $v_{fb}$  and error voltage,  $v_e$  of a feedback amplifier are, 5.0 mV and 10  $\mu$ V, respectively. Determine the gain,  $A_{vf}$ , input resistance,  $R_{if}$ , and output resistance,  $R_{of}$  after feedback of the amplifier. Assume that the gain of the amplifier without feedback is,  $2.5 \times 10^4$ . **(4 marks)**
- (c) The change of gain is 26% of a current amplifier without feedback. Design the feedback amplifier to determine the feedback factor  $\beta_i$  so that the change of gain would be reduced to 2%. Assume that the open-loop gain of the amplifier is,  $A_i = 1.3 \times 10^3$ . **(3 marks)**

**END OF QUESTION**

