



الجامعة الإسلامية العالمية ماليزيا
INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA
يُونَيْتِي إِسْلَامِيَّةٌ اِبْتَدَائِيَّةٌ مَلَيْسِيَا

KULLIYAH OF ENGINEERING

END OF SEMESTER EXAMINATION SEMESTER 1, 2019/2020 SESSION

Programme : **Electrical and Computer Engineering** Level of Study : **UG 2**
Time : **2:30 pm - 5:30 pm** Date : **09/01/2020**
Duration : **3.0 hours**
Course Code : **EECE 2313** Section(s) : **1-2**
Course Title : **Electronic Circuits**

This Question Paper Consists of **6 (Six)** Printed Pages (Including Cover Page) with **5 (Five)** Questions.


INSTRUCTION(S) TO CANDIDATES

DO NOT OPEN UNTIL YOU ARE ASKED TO DO SO

- Total mark of this examination is **100**.
- This examination is worth **50 %** of the total course assessment.
- Answer **ALL QUESTIONS**
- Only approved calculator with '**KoE approved**' sticker is allowed (non-programmable and non-graphical).
- Marks assigned to each question are listed in the margin.
- Note that one of the conditions to pass the course is to obtain at least **50%** of this examination.


Any form of cheating or attempt to cheat is a serious offence which may lead to dismissal.

All electronics gadgets are prohibited in the exam hall / venue.
(e.g. mobile / smart phones, smart watches, and smart glasses)


PROF. DR. MOHAMED HADI HABAEBI
Head
Department of Electrical and Computer Engineering
Kulliyah of Engineering
International Islamic University Malaysia

Question 1 (20 marks)

- a) Consider the circuit shown in **Fig. 1**, derive the expression (step by step) for the voltage transfer function, $T(s) = v_o(s)/v_i(s)$. Determine the -3 dB corner frequencies of the circuit, considering, $R_1 = 1 \text{ k}\Omega$, $C = 0.1 \text{ }\mu\text{F}$, $R_2 = 2 \text{ k}\Omega$ and $R_3 = 4 \text{ k}\Omega$. (8+2)

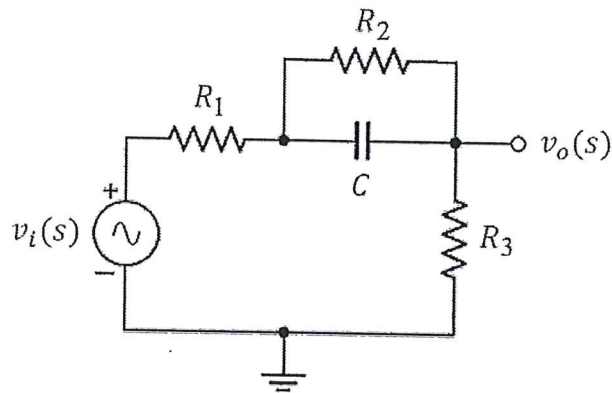**Fig. 1**

- b) Draw the Bode plots (magnitude and phase) of the following transfer function. (6)

$$T(s) = 10^{-3} \frac{(s + 50)(s + 300)}{s(s + 500)}$$

- c) Determine the magnitude and phase of the transfer function from the plots drawn for **Question 1(b)** at frequency $\omega = 450$ radian/sec. (4)

Question 2 (20 marks)

- a) Derive the expression for a short circuit high frequency current gain of a BJT (step by step) and prove that the beta frequency expression can be represented by the following expression. (7)

$$f_\beta = \frac{1}{2\pi r_\pi (C_\pi + C_\mu)}$$

- b) If the small-signal and high frequency parameters of the BJT are, $r_\pi = 1.5 \text{ k}\Omega$, $\beta = 80$, $C_\pi = 15 \text{ pF}$ and $C_\mu = 10 \text{ pF}$, determine the value of the cutoff frequency, f_T of the transistor. (2)

c) A common source amplifier is shown in **Fig. 2** that operates at very high frequencies. The coupling and bypass capacitors have very large values. The transistor parameters are as follows: $g_m = 20 \text{ mA/V}$, $r_o = 50 \text{ k}\Omega$, $C_{gs} = 50 \text{ fF}$ and $C_{gd} = 8 \text{ fF}$.

- i. Draw the simplified high-frequency small signal equivalent circuit diagram and Miller equivalent circuit diagram. (2)
- ii. Compute the maximum voltage gain in dB (4)
- iii. Determine the Millar capacitance. (2)
- iv. Evaluate the upper -3dB higher corner frequency f_H with and without considering the Miller capacitance. (3)

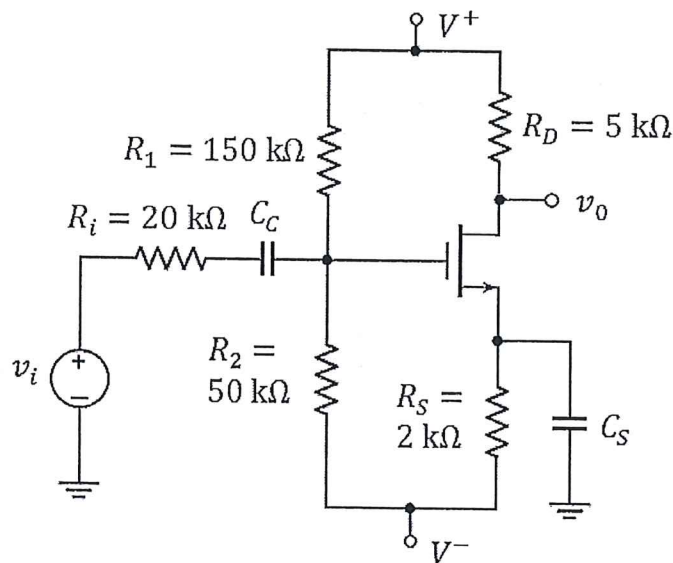


Fig. 2

Question 3 (20 marks)

- a) Draw the small-signal equivalent circuit of the Wilson current source as shown in **Fig. 3**. (3)

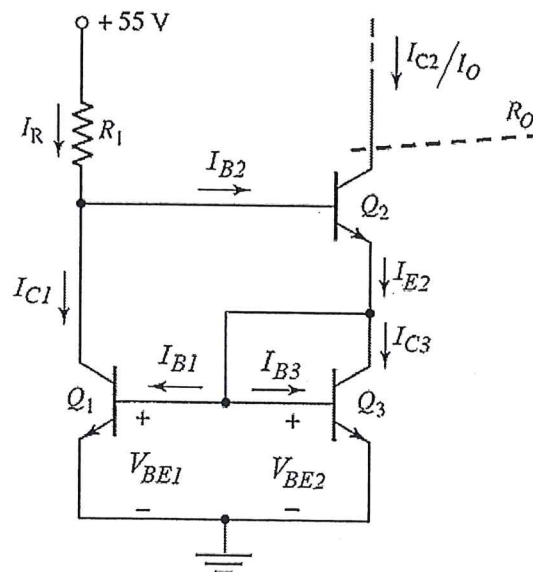


Fig. 3

- b) Derive the expression (step by step) for Wilson current source as shown in Fig. 3 for output current, I_O in terms of I_R and β , assume that all transistors are identical. (6)
- c) Design the Wilson current source circuit as shown in Fig. 3 such that, $I_O = 2.0$ mA. Assume that the transistor parameters are: $V_{BE}(on) = 0.7$ V, $\beta = 50$ and $V_A = \infty$. (3)
- d) Design a MOSFET current source shown in Fig. 4 such that, $I_{REF} = 1.0$ mA, $I_{O1} = 4.5$ mA, $I_{O2} = 15.0$ mA and $V_{DS4}(sat) = 3.0$ V. The transistors are available with parameters, $k'_n = 40$ μ A/V², $V_{TN} = 1.5$ V and $\lambda = 0$. (8)

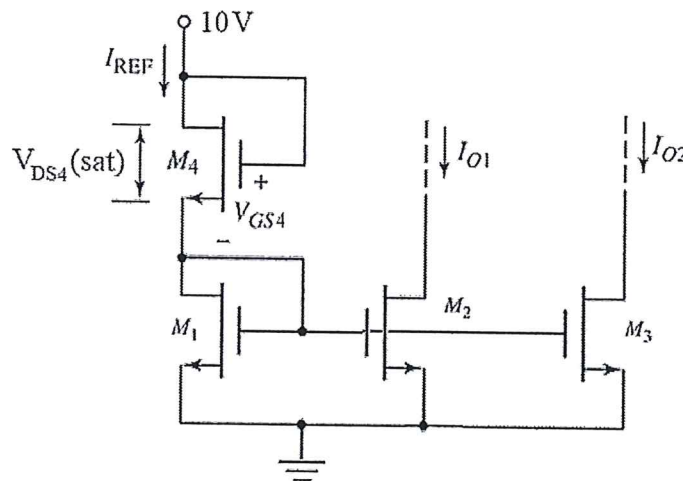



Fig. 4

Question 4 (20 marks)

- a) Draw the block diagram and small signal equivalent circuit diagram of a shunt-series ideal feedback amplifier. Analyze the feedback amplifier step by step to find the expression of the closed loop gain, A_f , the input resistance, R_{if} and the output resistance, R_{of} in terms of the open-loop amplifier gain, A and feedback factor, β . (8)
- b) The open-loop and closed loop gains of the shunt-series feedback amplifier are, $A = 5 \times 10^3$ and $A_f = 2 \times 10^2$ respectively.
- i. Determine the feedback amplifier input resistance, R_{if} and output resistance, R_{of} . Assume that the input and output resistances of the amplifier without feedback are, $R_i = 15$ k Ω and $R_o = 50$ k Ω respectively. (3)
 - ii. Determine the bandwidth of the amplifier with feedback, given that bandwidth without feedback, $f_{BW} = 20$ kHz. (2)
- c) Prove that, the gain sensitivity is improved by using negative feedback. (4)
- d) The open loop gain changes of a voltage amplifier is 30%. Calculate the percentage of gain changed when there is a negative feedback. Assume that, the open loop gain and closed loop gain of the amplifier are 4.5×10^5 and 1.5×10^2 respectively. (3)

Question 5 (20 marks)

- a) What are the conditions for a sustainable oscillation of an oscillator circuit? (2)
- b) A Wien-Bridge oscillator is shown in **Fig. 5**. Derive the equation for the frequency of oscillation, f_o and the minimum gain of the amplifier for sustained oscillation. (14)

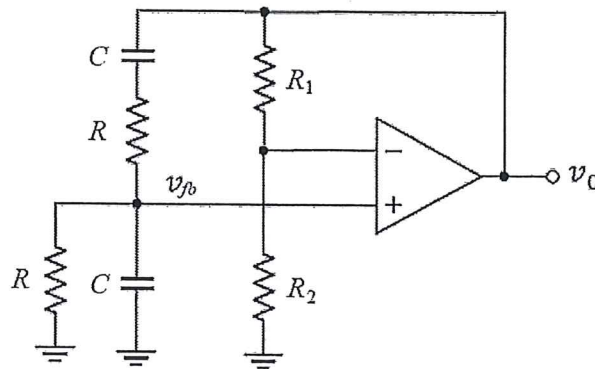**Fig. 5**

- c) Design a Wien-Bridge oscillator as shown in **Fig. 5**, with oscillation frequency of $f_o = 10$ kHz. (4)

END OF PAPER

APPENDIX

Some Useful Formulas

BJT	MOSFET
$i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A} \right)$ $g_m = \frac{I_{CQ}}{V_T}$ $r_\pi = \frac{\beta V_T}{I_{CQ}}$ $r_o = \frac{V_A}{I_{CQ}}$ $V_T = 26 \text{ mV}$ $V_{BE(on)} = 0.7 \text{ V}$	$I_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$ $g_m = 2 \sqrt{K_n I_{DQ}}$ $r_o = \frac{1}{\lambda I_{DQ}}$ $K_n = \frac{k_n'}{2} \left(\frac{W}{L} \right)$