



ECE 2133

Electronic Circuits

Dept. of Electrical and Computer Engineering
International Islamic University Malaysia



Chapter 10



Integrated Circuit Biasing



BJT Current Sources

Transistor Current Mirrors, Source, and Sink

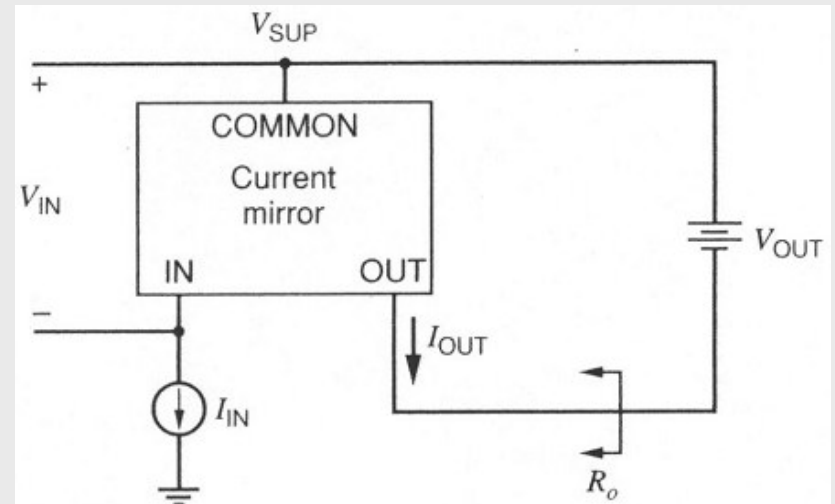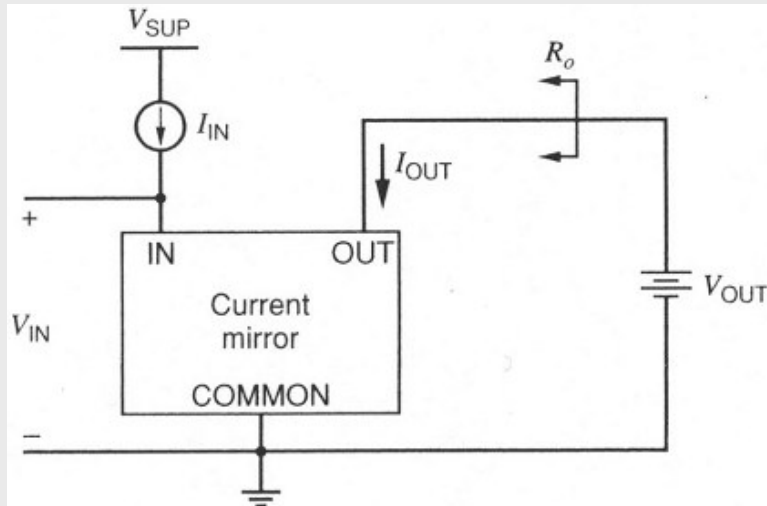- A current source/mirror have three terminals. The common terminal is connected to a power supply or ground, and the input current source is connected to the input terminal.
- The output current is equal to the input current multiplied by a desired current gain.
- If the gain is unity, then the input current is reflected to the output and named as current mirror.



BJT Current Sources

- ◆ Current sink
- ◆ Current source

Function:


Its maintain a constant current at an infinite output resistance under all operating conditions.

Uses:


- ◆ as biasing elements
- ◆ as loads for amplifying stages
- ◆ more economical than resistor in IC

Types of current sources:

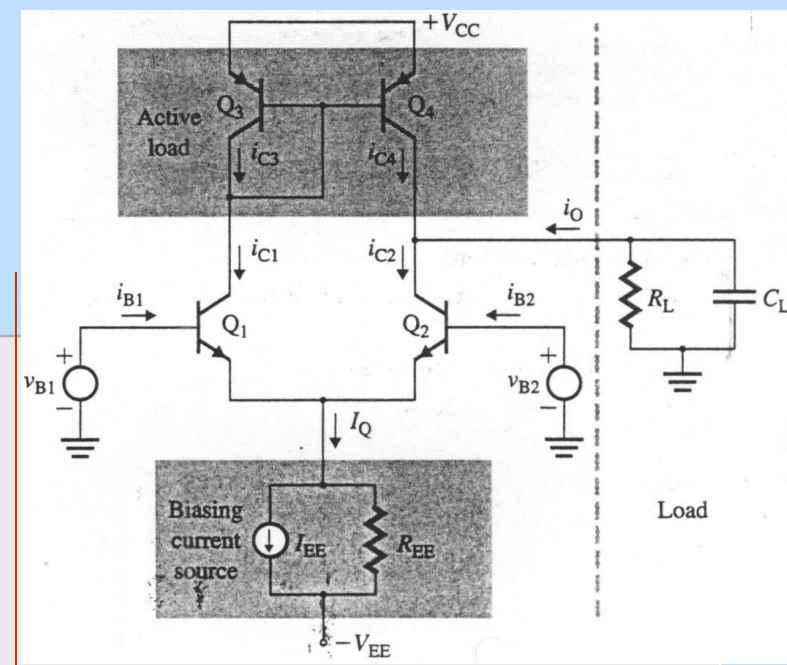- ◆ the basic current source
- ◆ the modified basic current source
- ◆ the Widlar current source
- ◆ the Wilson current source



Basic Current Source

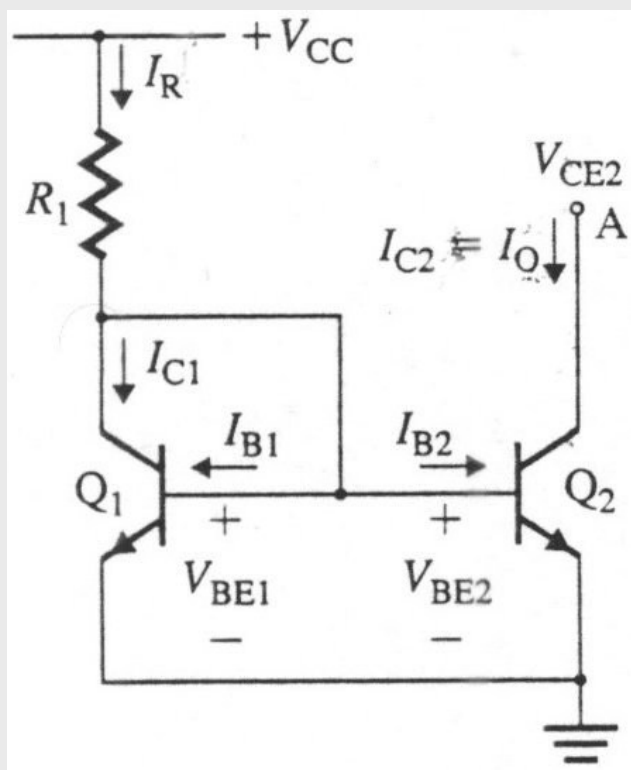

Assume Q_1 and Q_2 are identical

$$I_R = I_{C1} + I_{B1} + I_{B2} = I_{C1} + 2I_{B1}$$

$$I_R = I_{C1} + 2I_{B1} = I_{C1} + \frac{2I_{C1}}{\beta}$$

$$I_{C1} = I_{C2} = \frac{I_R}{1 + \frac{2}{\beta}} = \frac{V_{CC} - V_{BE1}}{R_1} \times \frac{1}{1 + \frac{2}{\beta}}$$



If the current gain $\beta \gg 2$, then,

$$I_{C1} = I_{C2} \approx I_R$$

I_{C2} is the mirror current of I_{C1}



Basic Current Source (contd.)

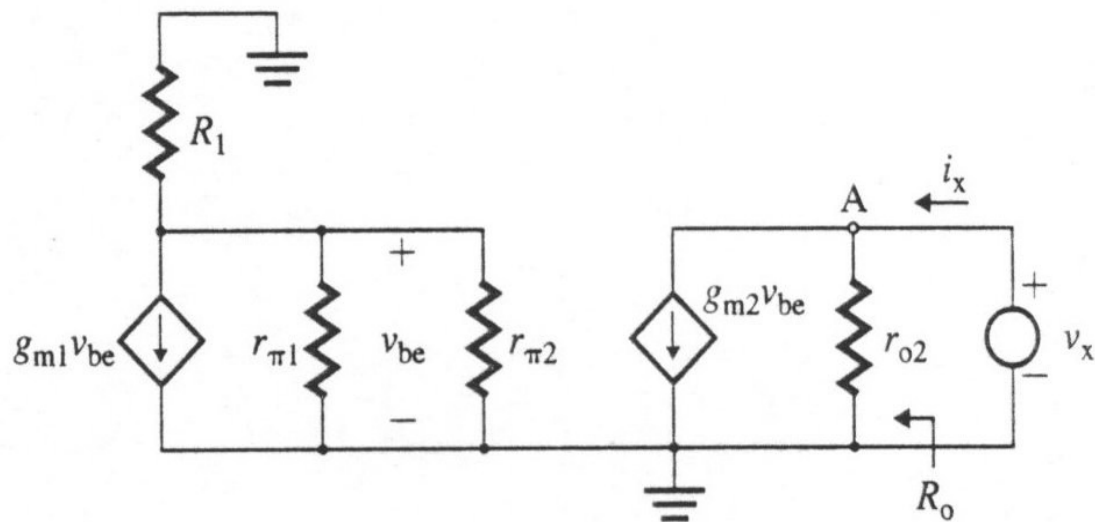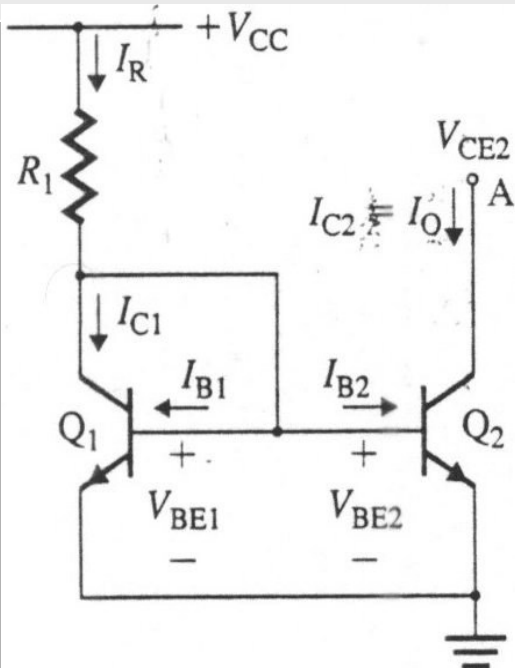

$$\diamond I_C = I_S \left[\exp \frac{v_{BE}}{V_T} - 1 \right] \left(1 + \frac{V_{CE}}{V_A} \right)$$




Basic Current Source

Collector current ratio:

$$\frac{I_{C2}}{I_{C1}} = \frac{1 + \frac{V_{CE2}}{V_A}}{1 + \frac{V_{CE1}}{V_A}}$$

Output resistance R_O :

$$R_O = \frac{v_x}{i_x} = r_{o2} = \frac{V_A}{I_{C2}}$$

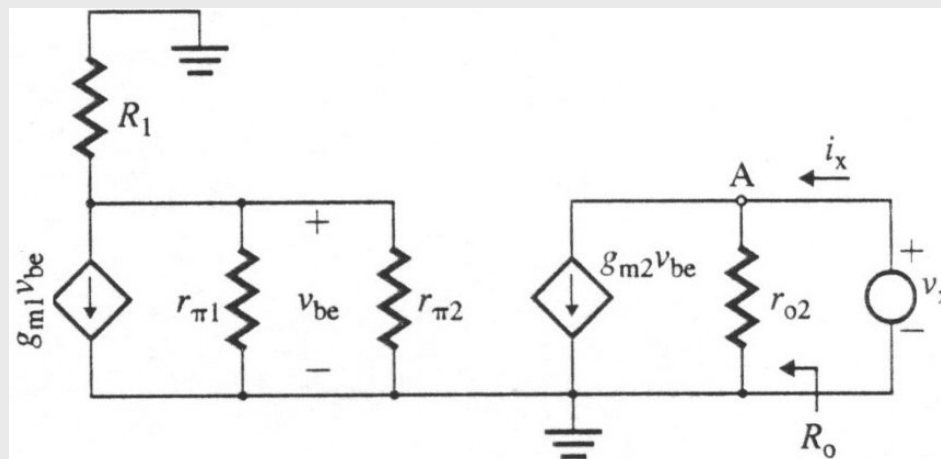

Example 4.2.1

(a) Design the basic current source in Fig. 4.2.1 to give an output current of $I_O = 5\mu A$. The transistor parameters are $\beta = 100$, $V_{CC} = 30V$, $V_{BE1} = V_{BE2} = V_{CE1} = 0.7V$, and $V_A = 150$.

(b) Calculate the output resistance R_O , and the collector current ratio if $V_{CE2} = 20V$.

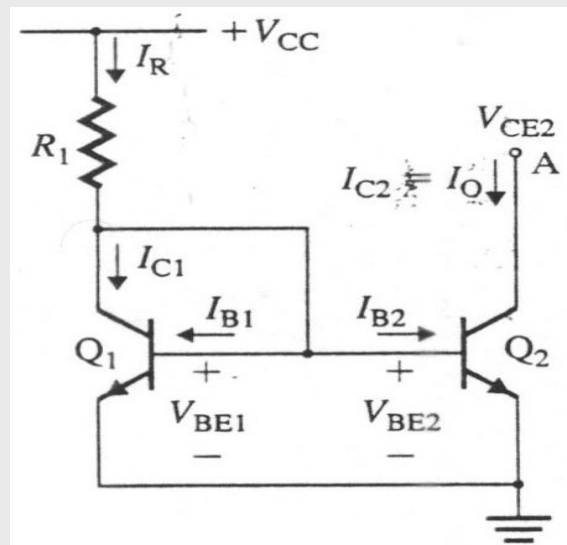


Figure 4.2.1



Example 4.2.1 (contd.)

(a)

We know,


$$I_O = I_{C1} = I_{C2} = \frac{I_R}{1 + \frac{2}{\beta}}$$

$$\Rightarrow I_R = I_O \left(1 + \frac{2}{\beta} \right) = 5 \mu A \left(1 + \frac{2}{100} \right) = 5.1 \mu A$$

Now,

$$I_R = \frac{V_{CC} - V_{BE1}}{R_1}$$

$$\Rightarrow R_1 = \frac{V_{CC} - V_{BE1}}{I_R} = \frac{30 - 0.7}{5.1 \mu A} = 5.75 M\Omega$$

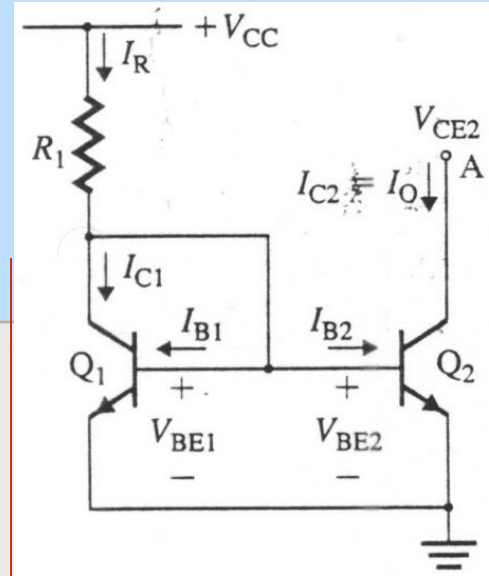

Example 4.2.1 (contd.)


(b)

Again,


$$R_O = \frac{V_A}{I_{C2}} = \frac{150}{5\mu A} = 30M\Omega$$

The collector current ratio is,
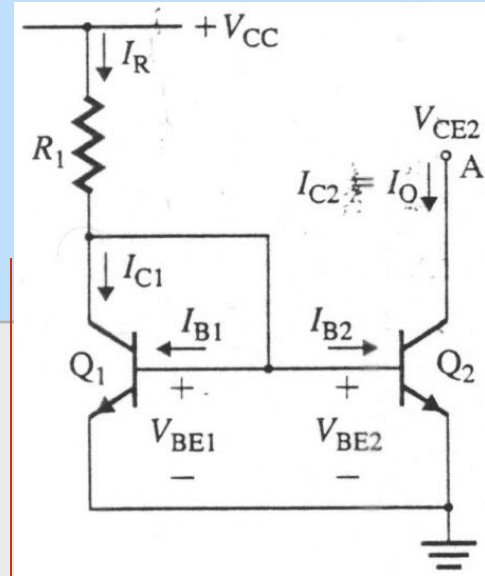
$$\frac{I_{C2}}{I_{C1}} = \frac{1 + \frac{V_{CE2}}{V_A}}{1 + \frac{V_{CE1}}{V_A}} = \frac{1 + \frac{20}{150}}{1 + \frac{0.7}{150}} = 1.128$$



Modified Basic Current Source

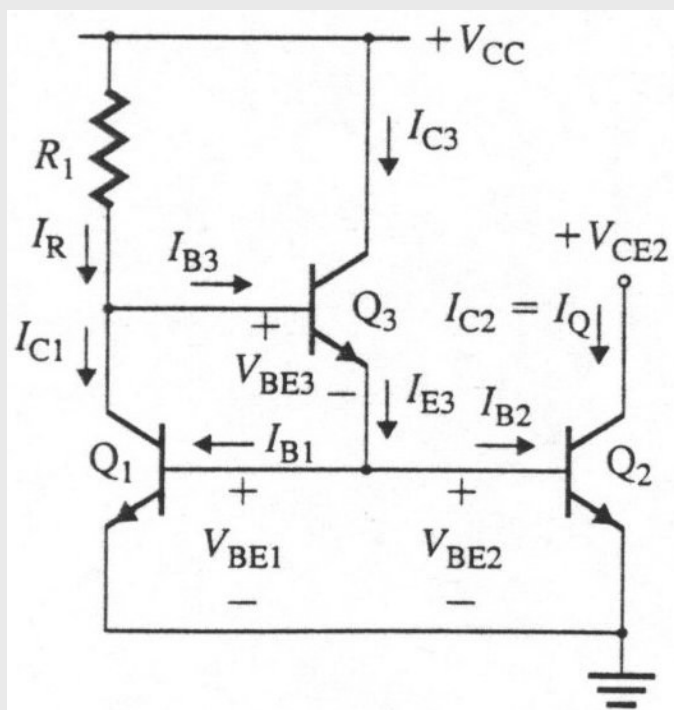

$$I_{C1} = I_{C2} = \frac{I_R}{1 + \frac{2}{\beta}}$$

Basic
current
source

Applying KCL at the emitter of Q_3

- ◆ $I_{E3} = I_{B1} + I_{B2} = \frac{I_{C1}}{\beta} + \frac{I_{C2}}{\beta} = \frac{2I_{C2}}{\beta}$
- ◆ $I_{B3} = \frac{I_{E3}}{1 + \beta} = \frac{2I_{C2}}{\beta(1 + \beta)}$



Modified Basic Current Source

Applying KCL at the collector of Q_1



$$I_R = I_{C1} + I_{B3} = I_{C1} + \frac{2I_{C2}}{\beta(1+\beta)}$$

$$I_O = I_{C2} = \frac{I_R}{1 + \frac{2}{\beta^2 + \beta}}$$

$$I_R = \frac{V_{CC} - V_{BE1} - V_{BE3}}{R_1}$$

Output resistance R_O :

$$R_O = \frac{v_x}{i_x} = r_{o2} = \frac{V_A}{I_{C2}}$$

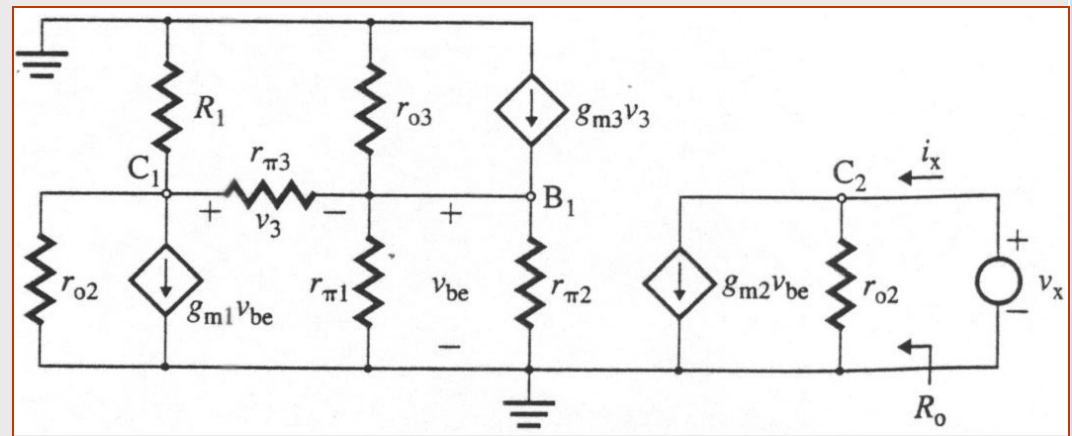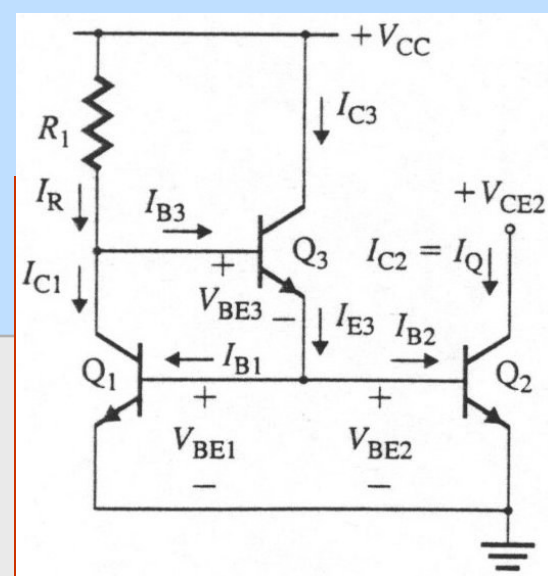

Example 4.2.2

- (a) Design the modified basic current source in Fig. 4.2.2 to give an output current of $I_O = 5\mu A$. The transistor parameters are $\beta = 100$, $V_{CC} = 30V$, $V_{BE1} = V_{BE2} = V_{BE3} = 0.7V$, and $V_A = 150$.
- (b) Calculate the output resistance R_O , and the collector current ratio if $V_{CE2} = 20V$.


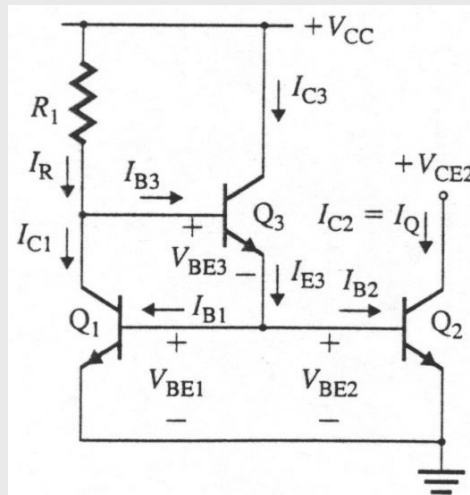


Figure 4.2.2

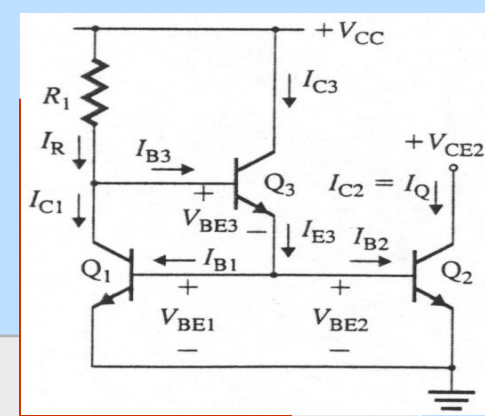

Example 4.2.2 (contd.)



(a)

$$I_O = I_{C2} = 5\mu A, V_{BE1} = V_{BE2} = V_{BE3} = 0.7V, \text{ and } V_A = 150V$$

The output current of modified basic current source can be given as,

$$I_O = I_{C2} = \frac{I_R}{1 + \frac{2}{\beta^2 + \beta}}$$

$$\Rightarrow I_R = I_O \left(1 + \frac{2}{\beta^2 + \beta} \right) = 5\mu A \left(1 + \frac{2}{100^2 + 100} \right) \approx 5\mu A$$


Now,

$$I_R = \frac{V_{CC} - V_{BE1} - V_{BE3}}{R_1}$$

$$\Rightarrow R_1 = \frac{V_{CC} - V_{BE1} - V_{BE3}}{I_R} = \frac{30 - 0.7 - 0.7}{5\mu A} = 5.72k\Omega$$



Example 4.2.2 (contd.)

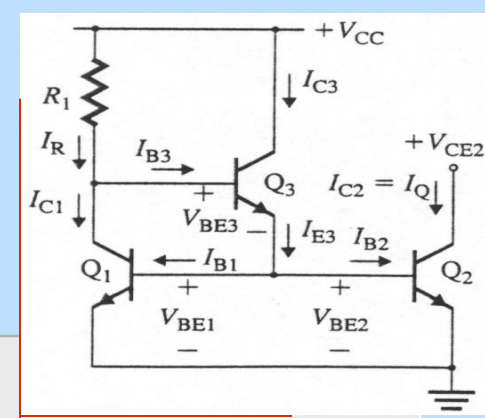

(b)

Output resistance,


$$R_O = \frac{V_A}{I_{C2}} = \frac{100}{5\mu A} = 30M\Omega$$

The ratio of two collector currents,

$$\frac{I_{C2}}{I_{C1}} = \frac{1 + \frac{V_{CE2}}{V_A}}{1 + \frac{V_{BE1} + V_{BE3}}{V_A}} = \frac{1 + \frac{20}{150}}{1 + \frac{0.7 + 0.7}{150}} = 1.123$$




Wilson Current Source

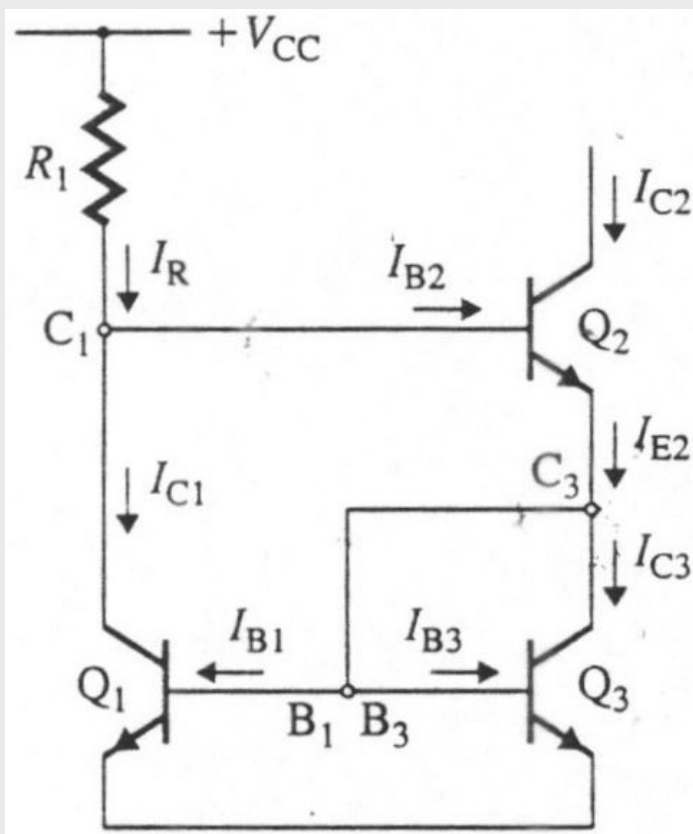

- ◆ $I_{B2} = I_R - I_{C1}$
- ◆ $I_{E2} = (1 + \beta)(I_R - I_{C1})$
- ◆ $I_{C1} = I_{C3}$
- ◆ $I_{E2} \approx I_{C2}$
- ◆ $I_{C1} \approx I_{C2}$



Wilson Current Source

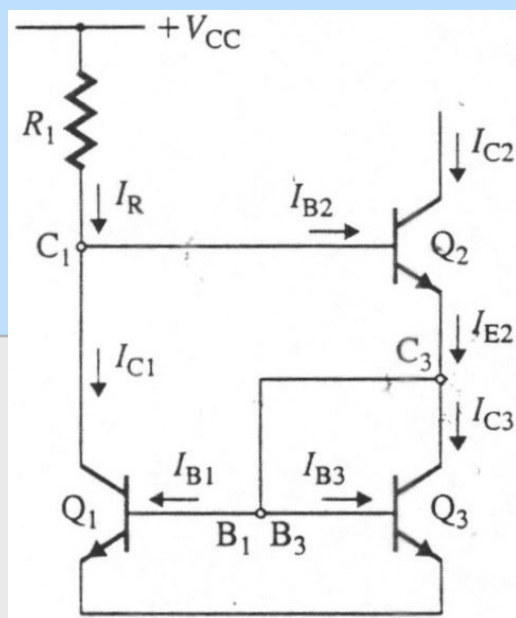

$$\diamond I_{E2} = (1 + \beta)I_{B2} = (I_R - I_{C1})(1 + \beta)$$

Assume $R_O = \alpha$, $V_A = \alpha$ and $I_{C1} = I_{C3}$

$$\diamond I_{E2} = I_{C3} + I_{B3} + I_{B1} = I_{C3} \left(1 + \frac{1}{\beta} \right) + \frac{I_{C1}}{\beta} = I_{C3} \left(1 + \frac{2}{\beta} \right)$$

$$\diamond I_{C2} = I_{E2} \frac{\beta}{1 + \beta} = I_{C3} \left(1 + \frac{2}{\beta} \right) \frac{\beta}{1 + \beta} = I_{C3} \frac{2 + \beta}{1 + \beta}$$

$$\diamond I_{C1} = I_R - I_{B2} = I_R - \frac{I_{C2}}{\beta}$$

$$\diamond I_{C1} = I_{C3} = I_{C2} \frac{1 + \beta}{2 + \beta} = I_R - \frac{I_{C2}}{\beta}$$


$$\diamond I_O = I_{C2} = I_R \left[\frac{(2 + \beta)\beta}{\beta^2 + 2\beta + 2} \right] = I_R \left[1 - \frac{2}{\beta^2 + 2\beta + 2} \right] \approx I_R \quad \because \beta \gg 1$$



Wilson Current Source

Output resistance R_o :

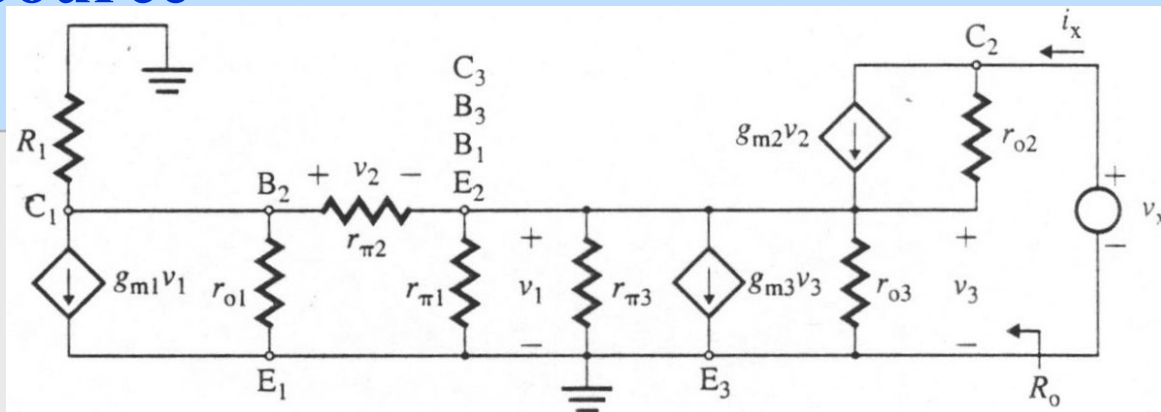- ◆ $R_e = r_{o1} \parallel R_1$
- ◆ $R_3 = r_{\pi1} \parallel r_{\pi3} \parallel r_{o3}$



Small-signal ac equivalent circuit


Applying KVL to the circuit left of $r_{\pi1}$

- ◆ $v_1 = ir_{\pi2} + (r_o \parallel R_1)(i - g_{m1}v_1)$

- ◆ $R'_e = \frac{v_1}{i} = \frac{r_{\pi2} + (r_{o1} \parallel R_1)}{1 + (r_{o1} \parallel R_1)g_{m1}}$

- ◆ $R'_e = \frac{r_{\pi2} + R_1}{1 + R_1g_{m1}} \quad \because r_{o1} \gg R_1$

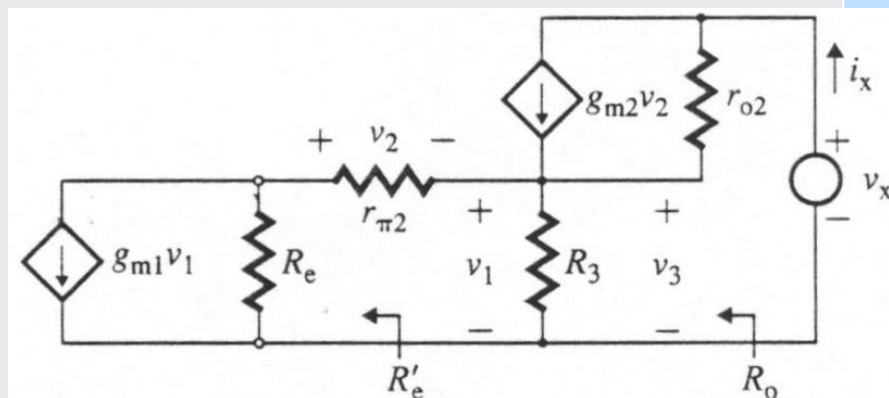
- ◆ $R'_e \approx \frac{1}{g_{m1}} \quad (\text{For } R_1 \gg r_{\pi2} \text{ and } g_{m1}R_1 \gg 1)$



Equivalent circuit



Wilson Current Source

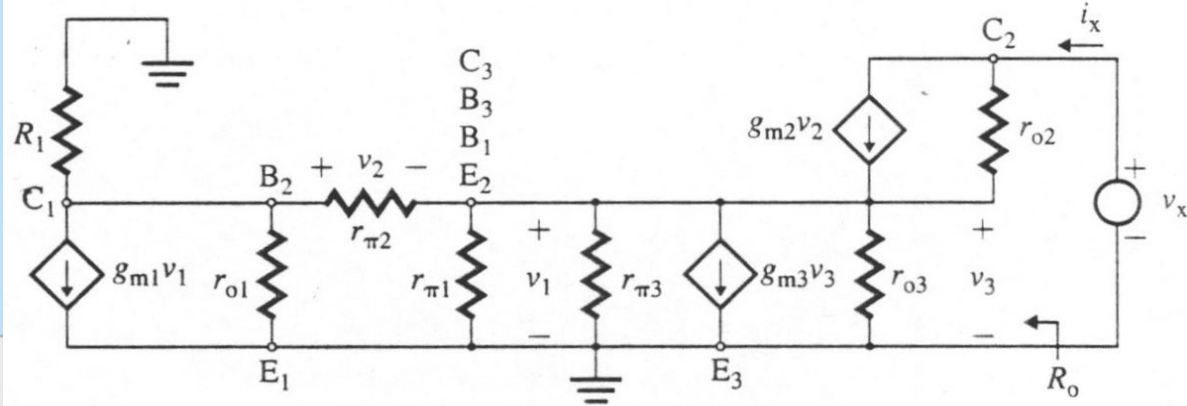


Small-signal ac equivalent circuit

$$\diamond R_O = \frac{v_x}{i_x} = R_3 \parallel R'_e + r_{o2} \left[1 + \frac{g_{m2} r_{\pi 2}}{R'_e} R_3 \parallel R'_e \right]$$

$$\diamond R_O \approx r_{o2} \left[1 + \frac{g_{m2} r_{\pi 2}}{R'_e} R_3 \parallel R'_e \right]$$

Assume $\frac{(R_3 \parallel R'_e)}{R'_e} = \frac{1}{2}$
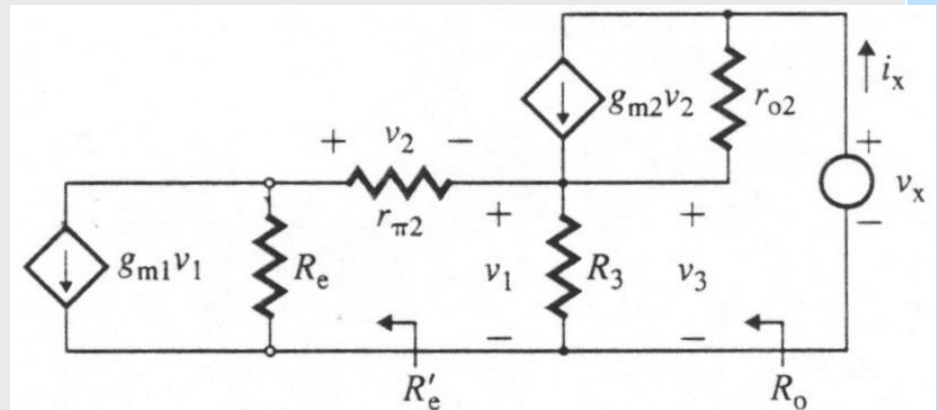
$$\diamond R_O \approx r_{o2} \left[1 + \frac{g_{m2} r_{\pi 2}}{2} \right] \approx r_{o2} \left[1 + \frac{\beta}{2} \right]$$



Equivalent circuit



Example 4.2.4

(a) Design the Wilson current source in Fig. 4.2.4 to give an output current of $I_O = 10\mu A$. The transistor parameters are $V_{CC} = 30V$, $V_{BE1} = V_{BE2} = V_{CE1} = 0.7V$, $V_T = 26mV$, $V_A = 100$ and $\beta = 150$. Assume all transistors are identical.

(b) Calculate the output resistance R_O .

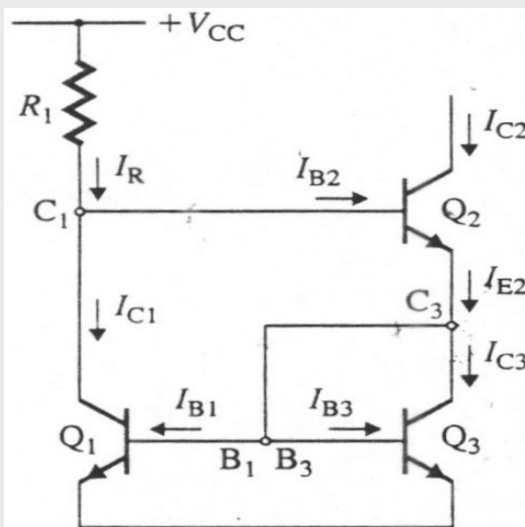


Figure 4.2.4



Example 4.2.4 (contd.)

(a)

$$I_O = I_{C2} = 10\mu A$$

The output current,


$$I_O = I_R \left[1 - \frac{2}{\beta^2 + 2\beta + 2} \right]$$

$$10\mu A = I_R \left[1 - \frac{2}{150^2 + 2 \times 150 + 2} \right] \Rightarrow I_R = 10\mu A$$

The reference current can be found from,

$$I_R = \frac{V_{CC} - V_{BE1} - V_{BE2}}{R_1}$$

$$\Rightarrow R_1 = \frac{V_{CC} - V_{BE1} - V_{BE2}}{I_R} = \frac{30 - 0.7 - 0.7}{10\mu A} = 2.86 M\Omega$$

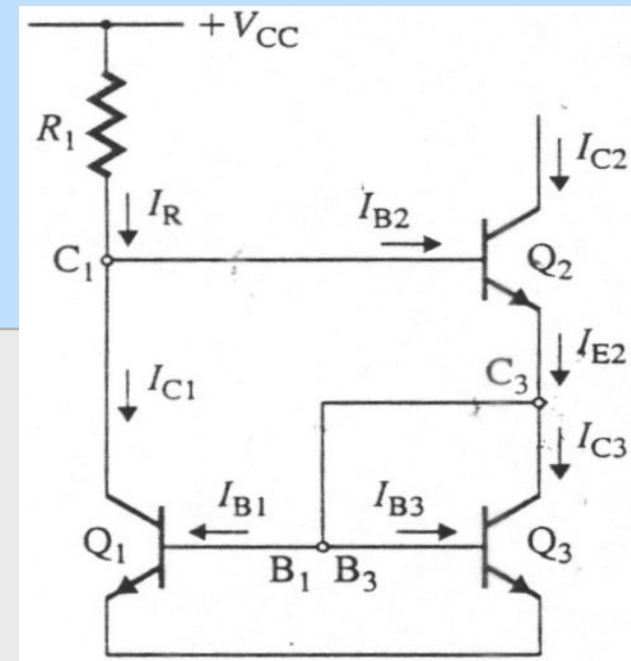

Example 4.2.4 (contd.)

(b)


$$I_{C1} = I_{C3} = I_{C2} \frac{1 + \beta}{2 + \beta} = 10 \mu A \frac{1 + 150}{2 + 150} = 9.93 \mu A$$

$$r_{o1} = r_{o3} = \frac{V_A}{I_{C1}} = \frac{100}{9.93 \mu A} = 10.07 M\Omega$$

$$r_{o2} = \frac{V_A}{I_{C2}} = \frac{100}{10 \mu A} = 10 M\Omega$$

$$g_{m1} = g_{m3} = \frac{I_{C1}}{V_T} = \frac{9.93 \mu A}{26 mV} = 381.9 \mu A/V$$

$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{10 \mu A}{26 mV} = 384.6 \mu A/V$$

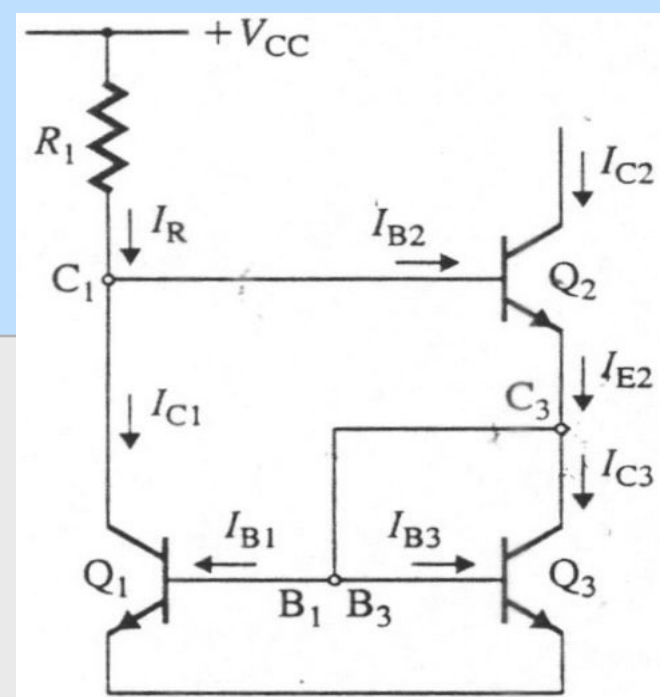


Example 4.2.4 (contd.)

Then,

$$r_{\pi 1} = r_{\pi 3} = \frac{\beta}{g_{m1}} = \frac{150}{381.9} = 393k\Omega$$


$$r_{\pi 2} = \frac{\beta}{g_{m2}} = \frac{150}{384.6} = 390k\Omega$$
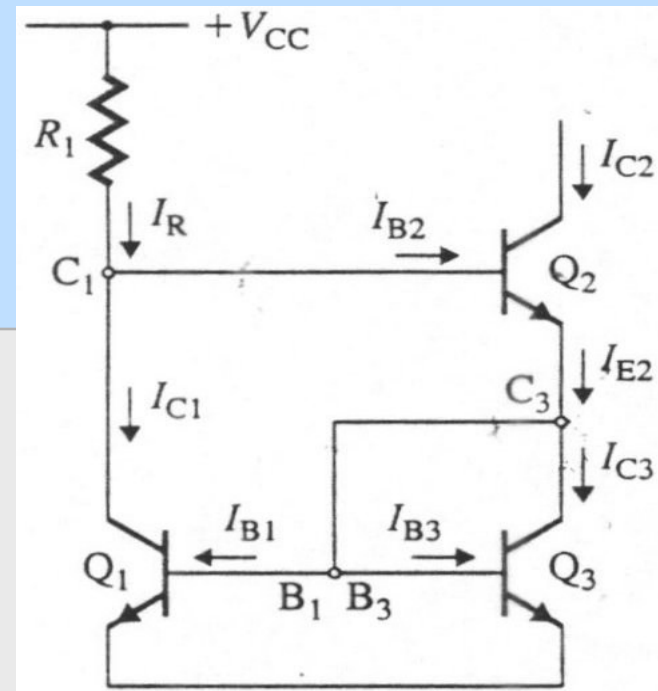
$$R_O = r_{o2} \left[1 + \frac{g_{m2} r_{\pi 2}}{2} \right] = 10M \left[1 + \frac{384.6 \times 390k}{2} \right] = 750M\Omega$$



Widlar Current Source

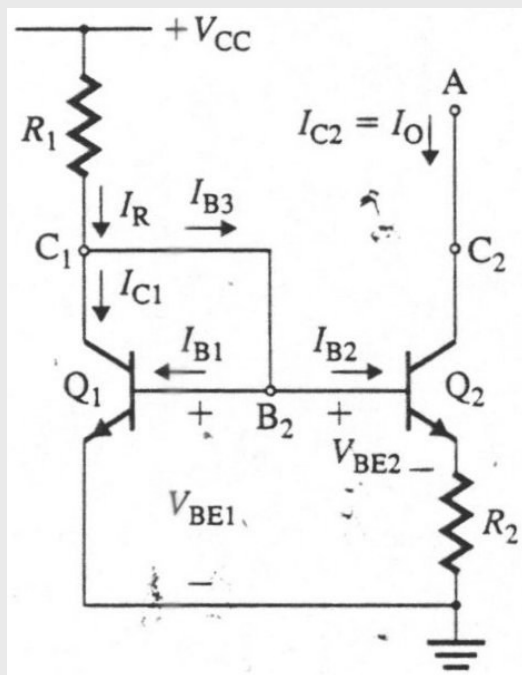Widlar current source which provides biasing currents of low magnitudes, typically $5\mu A$.



- ◆ $I_{C2} \neq I_R$
- ◆ $I_{C2} \ll I_{C1}$ (in μA range, $R < 50k\Omega$)

Applying KVL at the base-emitter loop


- ◆ $V_{BE1} - V_{BE2} - (I_{C2} + I_{B2})R_2 = 0$

Since $I_{C2} \gg I_{B2}$

- ◆ $V_{BE1} - V_{BE2} - I_{C2}R_2 = 0 \quad \dots \dots (1)$



Widlar Current Source

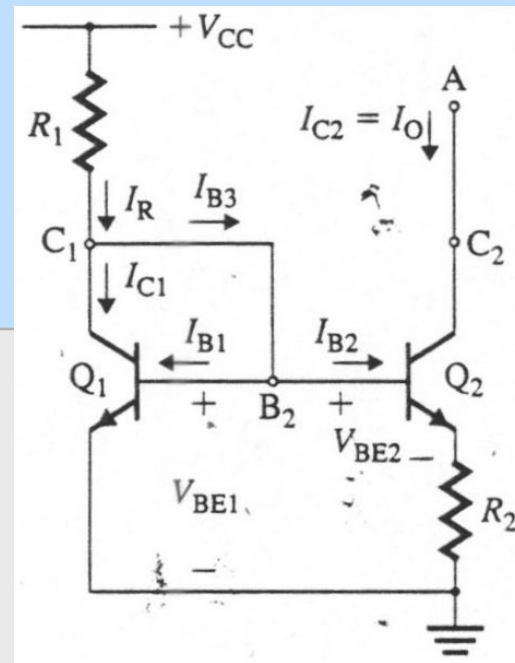

Assume $R_O = \alpha$, $\therefore V_A = \alpha$

$$\diamond I_C = I_S \left[\exp \frac{v_{BE}}{V_T} - 1 \right] \left(1 + \frac{V_{CE}}{V_A} \right) \approx I_S \exp \frac{v_{BE}}{V_T}$$

$$\Rightarrow V_{BE} = V_T \ln \left(\frac{I_C}{I_S} \right)$$

Applying this value into eqn. (1),

$$\diamond V_T \ln \left(\frac{I_{C1}}{I_{S1}} \right) - V_T \ln \left(\frac{I_{C2}}{I_{S2}} \right) - I_{C2} R_2 = 0$$

For identical transistor, i.e. $I_{S1} = I_{S2}$

$$\diamond V_T \ln \left(\frac{I_{C1}}{I_{S1}} \times \frac{I_{S2}}{I_{C2}} \right) - I_{C2} R_2 = 0$$

or,

$$\diamond V_T \ln \left(\frac{I_{C1}}{I_{C2}} \right) = I_{C2} R_2$$

or,

$$\diamond I_{C1} = I_{C2} \exp \frac{I_{C2} R_2}{V_T} \dots \dots (2)$$




Widlar Current Source

- ◆
$$I_R = \frac{V_{CC} - V_{BE1}}{R_1}$$
- ◆
$$I_R = I_{C1} + I_{B1} + I_{B2} = I_{C1} \left(1 + \frac{1}{\beta} \right) + \frac{I_{C2}}{\beta}$$

Putting the value of I_{C1} from eqn. (2),

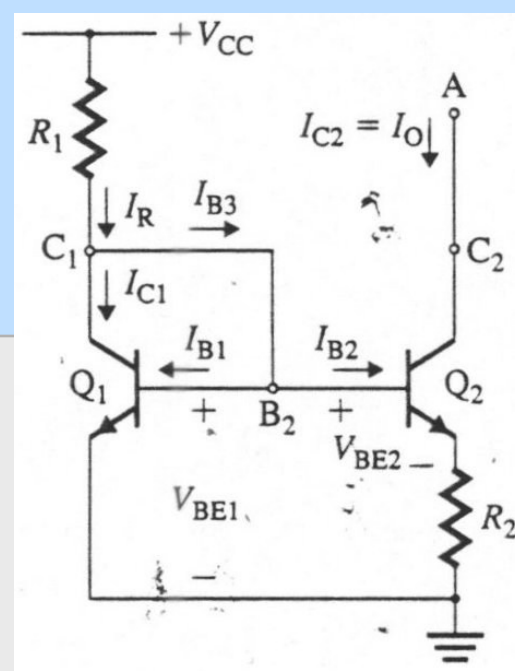- ◆
$$I_R = \frac{1 + \beta}{\beta} I_{C2} \exp \frac{I_{C2} R_2}{V_T} + \frac{I_{C2}}{\beta}$$
- ⇒ I_{C2} is nonlinear function of I_R and R_2 .



Widlar Current Source

Output resistance R_O :

$$\diamond R_e = r_{\pi 1} \parallel \frac{1}{g_{m1}} \parallel R_1 \parallel r_{o1}$$


$$g_m = \frac{\beta I_B}{V_T} = \frac{\beta}{r_\pi} \Rightarrow r_{\pi 1} = \frac{\beta}{g_{m1}}$$

Since $\beta \gg 1$, $r_{\pi 1} \gg \frac{1}{g_{m1}}$ and $R_1 \gg \frac{1}{g_{m1}}$


$$\diamond R_e \approx \frac{1}{g_{m1}}$$

$$\diamond v_3 = i_x [R_2 \parallel (r_{\pi 2} + R_e)]$$
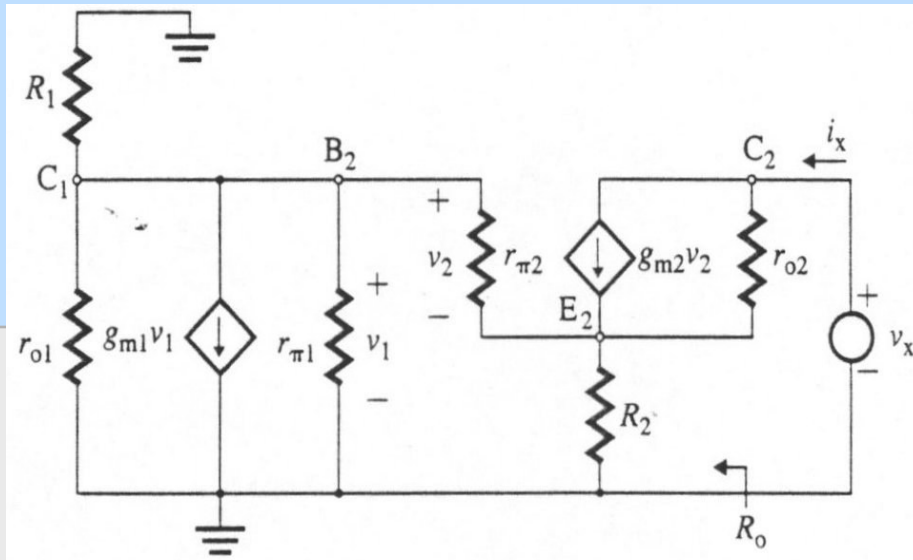
$$\diamond v_2 = -\frac{v_3 r_{\pi 2}}{r_{\pi 2} + R_e} = -\frac{i_x r_{\pi 2} R_2 \parallel (r_{\pi 2} + R_e)}{r_{\pi 2} + R_e}$$




Small-signal equivalent circuit

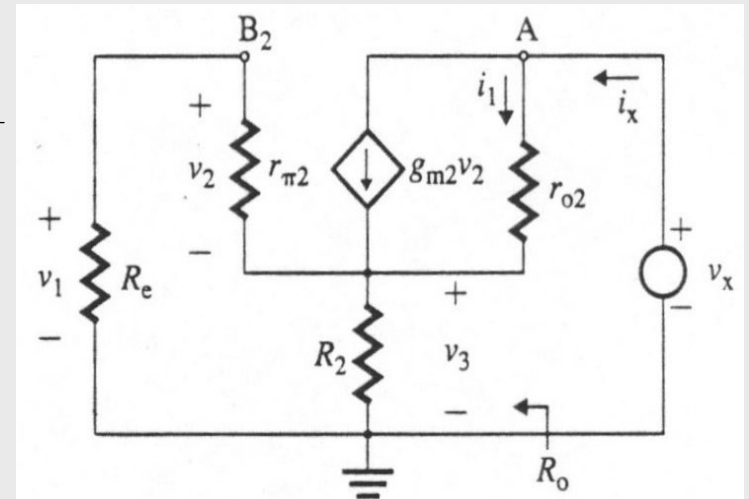


Equivalent circuit



Widlar Current Source

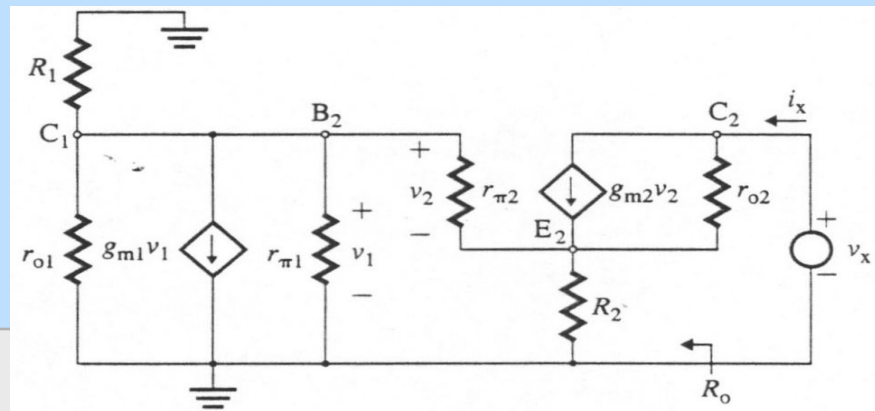

Small-signal equivalent circuit

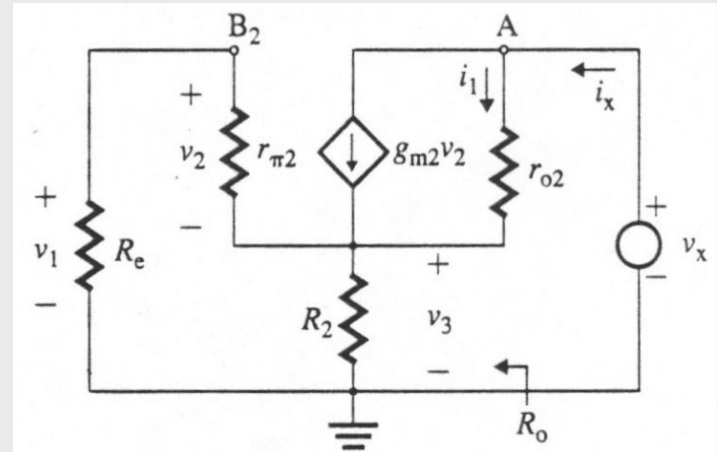

Equivalent circuit

$$i_1 = i_x - g_{m2}v_2$$

$$\begin{aligned} v_x &= v_3 + r_{o2}i_1 = v_3 + r_{o2}i_x - r_{o2}g_{m2}v_2 \\ &= v_3 + r_{o2}i_x + \frac{r_{o2}g_{m2}v_3r_{\pi2}}{r_{\pi2} + R_e} \end{aligned}$$

Putting value of v_3

$$R_o = \frac{v_x}{i_x}$$

$$= R_2 \parallel (r_{\pi2} + R_e) + r_{o2} \left[1 + \frac{g_{m2}r_{\pi2}}{r_{\pi2} + R_e} R_2 \parallel (r_{\pi2} + R_e) \right]$$

$$R_o \approx r_{o2} \left[1 + \frac{g_{m2}r_{\pi2}}{r_{\pi2} + R_e} R_2 \parallel (r_{\pi2} + R_e) \right] \quad \because r_{o2} \gg$$



Widlar Current Source

$$g_m = \frac{I_C}{V_T} = \frac{\beta I_B}{V_T} = \frac{\beta}{r_\pi} \Rightarrow \frac{1}{g_{m1}} = \frac{V_T}{I_{C1}}$$

$$\diamond r_{\pi 2} = \frac{\beta}{g_{m2}} = V_T \frac{\beta}{I_{C2}} = \beta \frac{V_T}{I_{C1}} \times \frac{I_{C1}}{I_{C2}} = \frac{\beta}{g_{m1}} \times \frac{I_{C1}}{I_{C2}}$$


$$I_{C1} \gg I_{C2}, r_{\pi 2} \gg \frac{1}{g_{m1}} \quad \text{and} \quad r_{\pi 2} \gg R_e$$

$$\diamond R_e + r_{\pi 2} \approx r_{\pi 2}$$


$$\diamond R_O \approx r_{o2} [1 + g_{m2} (R_2 \parallel r_{\pi 2})]$$

$$\beta \gg 1 \quad \text{and} \quad r_{\pi 2} = \frac{\beta}{g_{m2}}$$
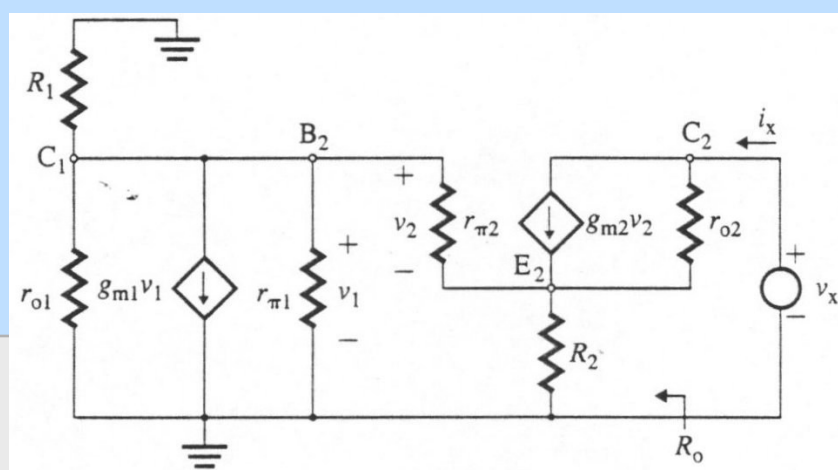
$$\diamond R_O = r_{o2} \frac{g_{m2} R_2 (1 + \beta) + \beta}{g_{m2} R_2 + \beta} = r_{o2} \left[\frac{1 + g_{m2} R_2}{1 + \frac{g_{m2} R_2}{\beta}} \right]$$




Small-signal equivalent circuit

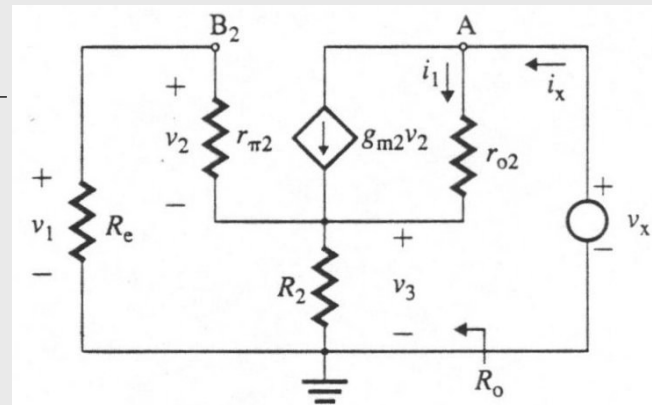

Equivalent circuit




Widlar Current Source

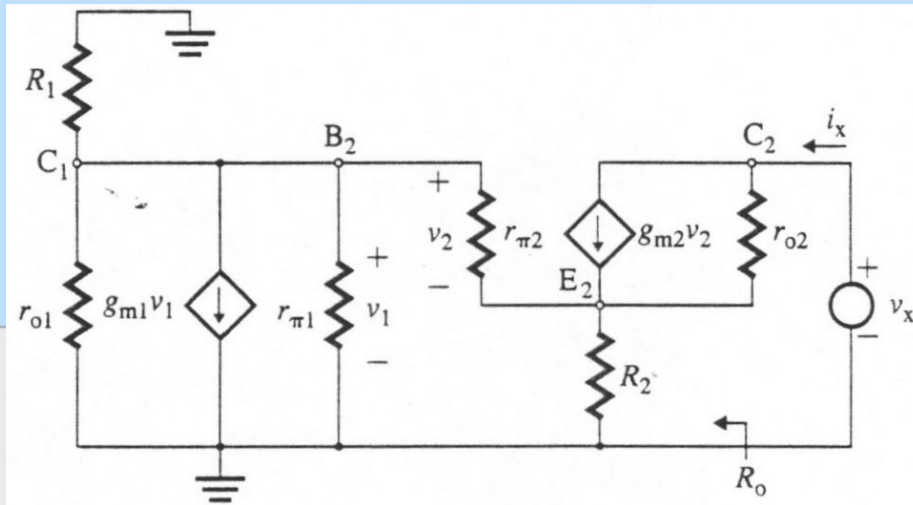

Small-signal equivalent circuit

$$\beta \gg g_{m2}R_2$$
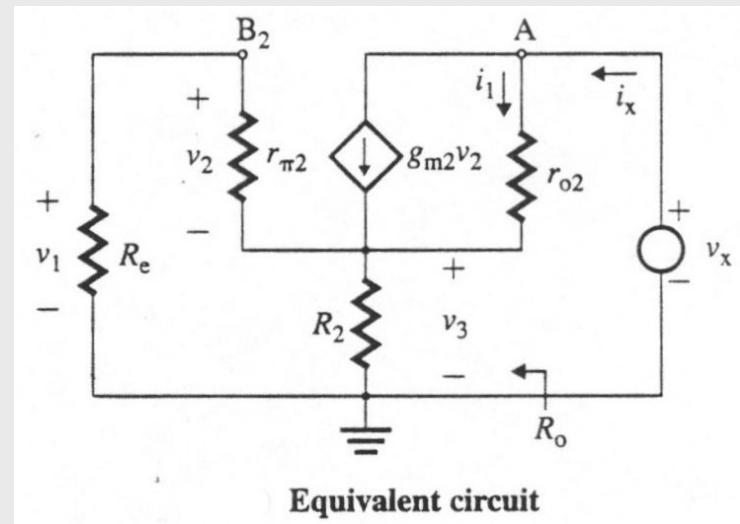
$$\diamond R_o \approx r_{o2}(1 + g_{m2}R_2) \approx r_{o2} \left(1 + \frac{I_{C2}R_2}{V_T} \right)$$



Equivalent circuit

$\Rightarrow R_o$ depends on $I_{C2}R_2$, i.e. the dc voltage drop across R_2 .



Example 4.2.3 (contd.)

We know,

$$I_R = \frac{V_{CC} - V_{BE1}}{R_1}$$


$$R_1 = \frac{V_{CC} - V_{BE1}}{I_R} = \frac{30 - 0.7}{1mA} = 29.3k\Omega$$

We know,


$$I_R = I_{C1} \left(1 + \frac{1}{\beta} \right) + \frac{I_{C2}}{\beta} \Rightarrow 1mA = I_{C1} \left(1 + \frac{1}{100} \right) + \frac{5\mu A}{100} \Rightarrow I_{C1} = 990\mu A$$

Again,

$$V_T \ln \left(\frac{I_{C1}}{I_{C2}} \right) = I_{C2} R_2 \Rightarrow 26mV \ln \left(\frac{990\mu A}{5\mu A} \right) = 5\mu A \times R_2 \Rightarrow R_2 = 27.5k\Omega$$

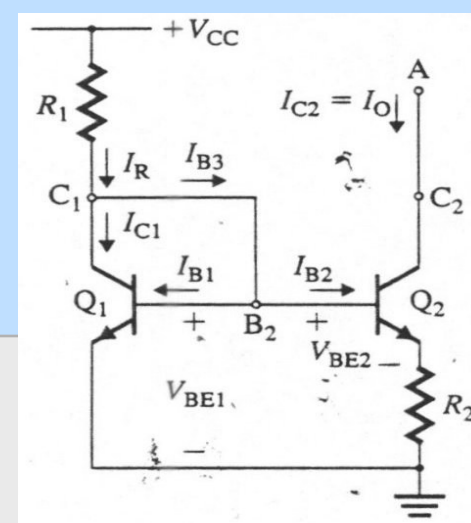

Example 4.2.3 (contd.)

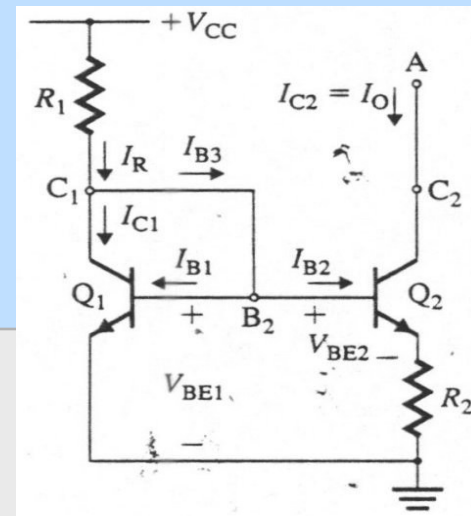

Since,

$$r_{o2} = \frac{V_A}{I_{C2}} = \frac{150}{5\mu A} = 30M\Omega, \quad r_{\pi2} = \frac{V_T \beta}{I_{C2}} = \frac{26mV \times 100}{5\mu A} = 520k\Omega$$

and,

$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{5\mu A}{26mV} = 192.3 \mu A/V$$

Therefore, the output resistance,

$$\begin{aligned} R_O &\approx r_{o2} [1 + g_{m2} (R_2 \parallel r_{\pi2})] = 30M\Omega [1 + 192.3 \mu A/V (27.5k\Omega \parallel 520k\Omega)] \\ &= 180.68M\Omega \end{aligned}$$






FET Current Sources

MOSFET Current Source

MOSFET current sources are analogous to BJT current sources. We can convert a BJT current source to an equivalent MOSFET current source by assuming that the β of the BJTs is finite. Since MOSFETs do not draw any gate current, there is no need for base current compensation as there is with BJTs. The choice of a BJT source or a MOSFET source generally depends on the type of integrated circuit involved (e.g., bipolar or MOS). BJT sources have some advantages over MOSFET sources, such as a wider compliance range and a higher output resistance. However, a higher output resistance can be obtained by cascode-like connections of MOSFETs.



Basic Current Source

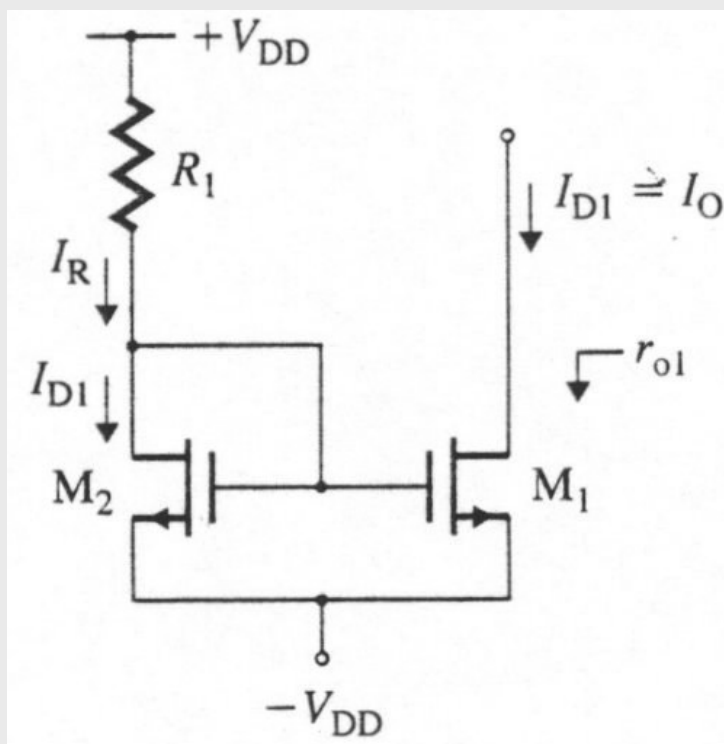

- ◆ Assume M_1 and M_2 are identical.
 - ◆ $I_{D1} = I_{D2} \quad \therefore V_{GS1} = V_{GS2}$
- ◆ Thus, $I_O (= I_{D1})$ will be the mirror of I_{D2}
- ◆ M_2 will be in saturation $\therefore V_{DS2} = V_{GS2}$
- ◆ M_1 will be in saturation for $(V_{GS2} - V_{t2}) \leq V_{DS1} > (V_{GS1} - V_{t1})$



Basic Current Source (contd.)

$$I_D = \frac{1}{2} \frac{WK_x}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

$$= K_P (V_{GS} - V_t)^2 \left(1 + \frac{V_{DS}}{V_M}\right)$$

where V_t = threshold voltage

W = width of the channel, typically $10\ \mu\text{m} - 500\ \mu\text{m}$

L = length of the channel, typically $10\ \mu\text{m} - 500\ \mu\text{m}$


λ = channel modulation length, typically 0.01V^{-1}

$V_M = \frac{1}{\lambda}$ = channel modulation voltage, in V

$K_x = \mu_x C_{ox}$ = channel constant, typically $20\ \mu\text{A}/\text{V}^2$

μ_x = mobility of electrons, typically $500\text{cm}^2/\text{V}$

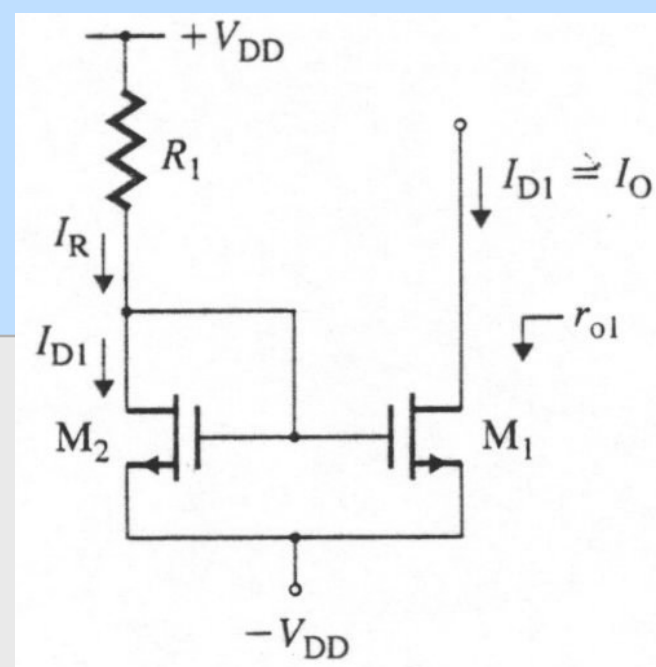
C_{ox} = capacitance per unit area, typically $3.5 \times 10^{-4}\ \text{pF}/\mu\text{m}^2$



$$K_P = \frac{1}{2} \frac{WK_x}{L}$$



Basic Current Source (contd.)

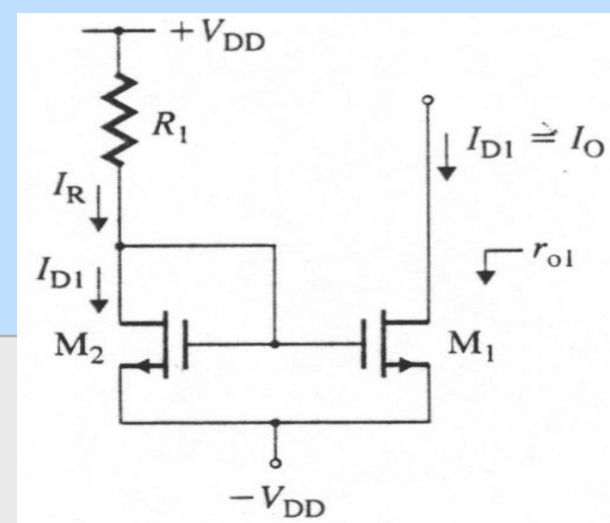

- ◆ $I_{D1} = I_O = K_{P1} (V_{GS1} - V_{t1})^2 (1 + \lambda V_{DS1})$
- ◆ $I_{D2} = I_R = K_{P2} (V_{GS2} - V_{t2})^2 (1 + \lambda V_{DS2})$

As all the components of the current source are processed on the same integrated circuit, therefore K_x and V_t are identical for both devices, thus, the ratio of I_O to I_R is given by

- ◆
$$\frac{I_O}{I_R} = \frac{K_{P1} (1 + \lambda V_{DS1})}{K_{P2} (1 + \lambda V_{DS2})} = \frac{(W/L)_1}{(W/L)_2} \times \frac{(1 + \lambda V_{DS1})}{(1 + \lambda V_{DS2})} = \frac{(W/L)_1}{(W/L)_2} \quad \because \lambda V_{DS} \ll 1$$

We can change I_O by controlling W/L . V_{GS} is usually fixed, V_{DS} varies from device to device to give the desired current ratio I_O/I_R . With $W_1 = W_2$ and $L_1 = L_2$ one can ensure that $I_O \neq I_R$.


Since $V_{GS2} = V_{DD} - R_1 I_R$ and $V_{DS2} = V_{GS2}$

- ◆
$$I_R = I_{D2} = K_{P2} (V_{DD} - R_1 I_R - V_{t2})^2$$



Basic Current Source (contd.)

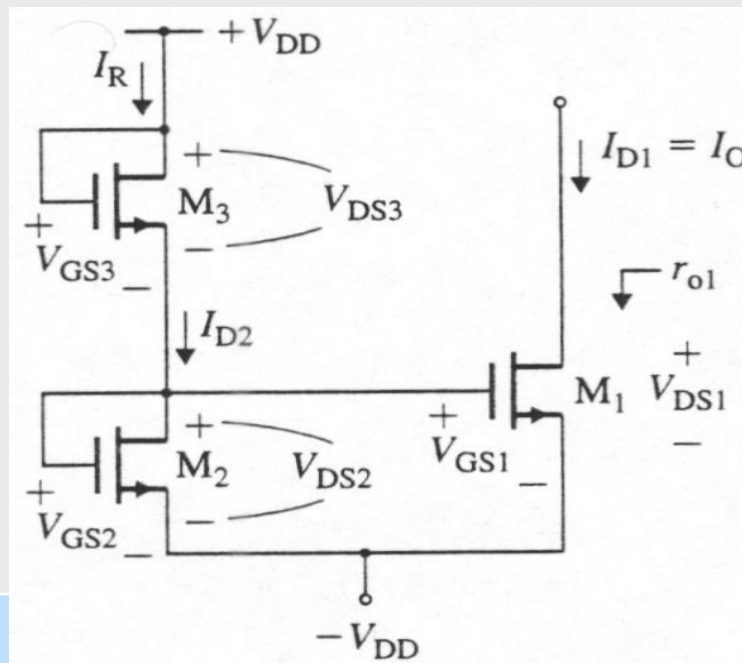Transistors M_2 and M_3 are used as voltage dividers to control the gate-source voltage of transistor M_1 . If M_1 and M_2 are identical, the output current I_O exactly mirrors the drain current through M_2 and M_3 . The value of V_{GS1} should be made as low as possible without taking M_1 out of the saturation region.



Basic Current Source (contd.)

Output Resistance R_O :

The small-signal drain-source resistance r_{ds1} can be derived from the equation,

$$I_D = \frac{1}{2} \frac{WK_x}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS}) = K_P (V_{GS} - V_t)^2 \left(1 + \frac{V_{DS}}{V_M}\right)$$

$$\Rightarrow \frac{1}{r_{ds1}} = \frac{\delta i_{D1}}{\delta v_{DS1}} = \frac{K_{P1}}{V_M} (V_{GS} - V_t)^2 \approx \frac{I_{D1}}{V_M}$$

Thus, the small-signal output resistance of the current source becomes

$$R_O = r_{ds1} = \frac{V_M}{I_{D1}} = \frac{1}{\lambda I_{D1}}$$

which is relatively small. This small output resistance is a disadvantage of having only one MOSFET M_1 at the output side of a current source.

