

Name: _____

MODEL ANSWER

Matric No: _____

Section: _____



الجامعة الإسلامية العالمية ماليزيا

INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA

**MID-TERM EXAMINATION
SEMESTER I, 2013/2014 SESSION
KULLIYAH OF ENGINEERING**

Programme : ENGINEERING Level of Study : UG 2
Time : 8:00 pm-10:00 pm Date : 06/11/2013
Duration : 2 Hours
Course Code : ECE 2133 Section(s) : 1 & 2
Course Title : **Electronic Circuits**

This Question Paper consists of **Eight (8)** Printed Pages (Including Cover and a blank page) with **Three (3)** Questions.

INSTRUCTION(S) TO CANDIDATES

DO NOT OPEN UNTIL YOU ARE ASKED TO DO SO

- Use only pen for writing answer.
- Do not use your own sheet.
- A total mark of this examination is 60.
- This examination is worth 30% of the total assessment.
- For drawing you may use pencil
- Answer **ALL THREE(3)** questions.
- Answer on the question paper.

Any form of cheating or attempt to cheat is a serious offence which may lead to dismissal.

	Question 1	Question 2	Question 3	Total Marks
Marks	20	20	20	60
Marks Obtained				

Q.1 [20 marks]

- (a) Consider the circuit shown in Fig. 1(a), derive the expression (step by step) for the voltage transfer function $T(s) = \frac{v_o(s)}{v_i(s)}$ and find the time constant and the corner frequency. **(8 marks)**

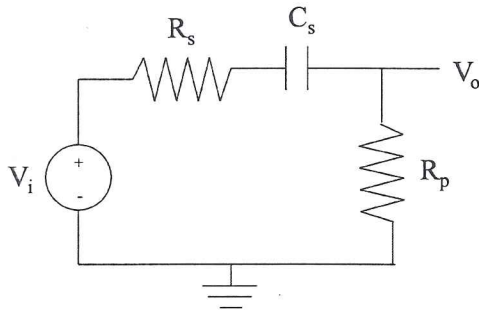


Fig. 1(a)

$$T(s) = \frac{v_o(s)}{v_i(s)} = \frac{R_p}{R_p + R_s + \frac{1}{sC_s}} = \frac{R_p s C_s}{1 + (R_p + R_s) s C_s}$$


$$= \frac{R_p}{R_p + R_s} \cdot \frac{s(R_p + R_s) C_s}{1 + s(R_p + R_s) C_s} = K \cdot \frac{s\tau_c}{1 + s\tau_c}$$

$$\tau_c = (R_p + R_s) C_s \quad f = \frac{1}{2\pi\tau_c} = \frac{1}{2\pi(R_p + R_s)}$$

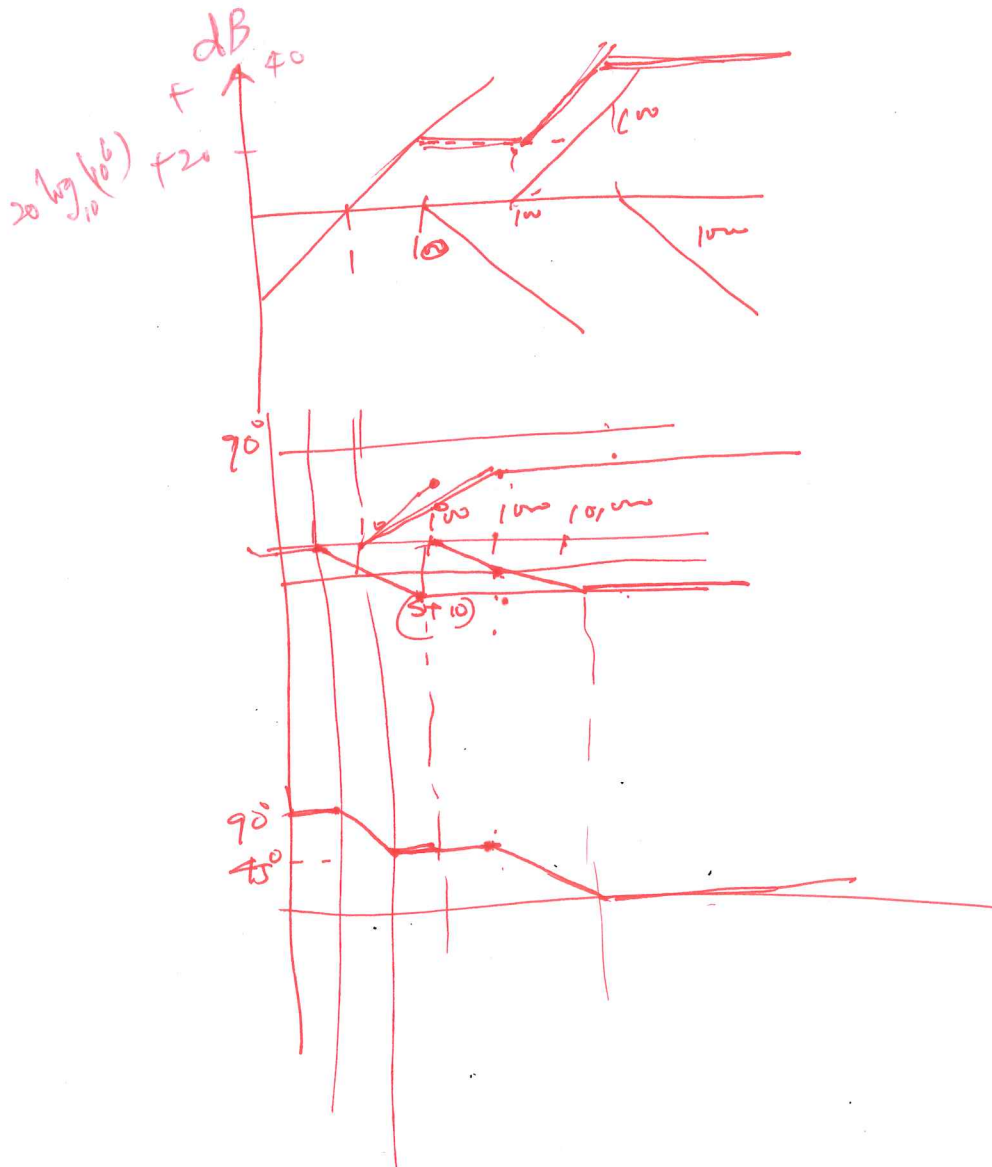(b) Draw the Bode plot (magnitude and phase) of the following transfer function.

(12 marks)

$$T(s) = \frac{10^6 s(s+100)}{(s+10)(s+1000)}$$



Q.2 [20 marks]

(a) Draw the small signal equivalent circuit diagram of the circuit shown in Fig. 2(a) and find the followings: (10 marks)

- (i) the input resistance R_i ,
- (ii) the midband voltage gain $A_v = \frac{v_o}{v_s}$ of the amplifier, and
- (iii) the lower corner frequency due to C_C .

Given that $R_s = 0.5 \text{ k}\Omega$, $R_1 = 330 \text{ k}\Omega$, $R_2 = 85 \text{ k}\Omega$, $R_C = 4 \text{ k}\Omega$, $R_E = 1.5 \text{ k}\Omega$, $C_C = 1 \mu\text{F}$. The transistor has small-signal hybrid- π parameters, $r_\pi = 3 \text{ k}\Omega$, $g_m = 40\text{mA/V}$ and $r_o = \infty$.

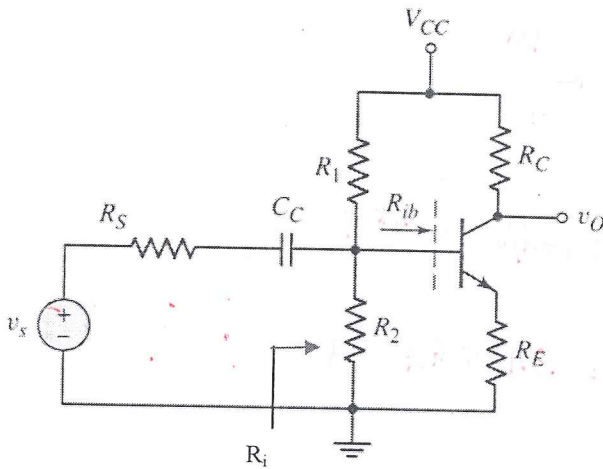


Fig. 2(a)


$$R_{ib} = r_\pi + (1 + \beta) R_E$$

$$= 3 + (1 + 120) \cdot 1.5 = 184.5$$

$$\beta = r_\pi \times g_m$$

$$= 3 \times 40 = 120$$
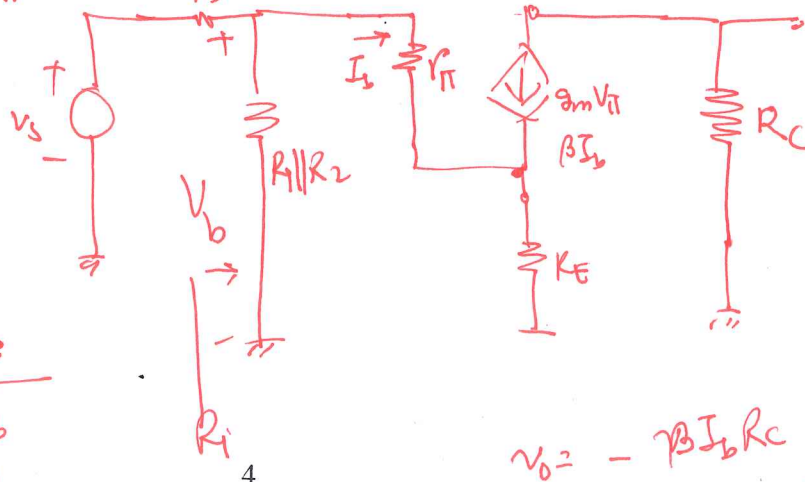
$$R_i = R_1 \parallel R_2 \parallel R_{ib} = 49.468 \text{ k}\Omega$$



$$\therefore A_v = \frac{v_o}{v_b}$$

$$= - \frac{\beta I_b R_C}{R_{ib} I_b}$$

$$= - \frac{\beta \times R_C}{R_{ib}} = - \frac{120 \times 4}{49.468}$$

$$= - 9.703 = - 2.60$$

$$v_o = - \beta I_b R_C$$

$$v_b = (r_\pi + (1 + \beta) R_E) I_b$$

$$= R_{ib} I_b$$

$$A_{vd} = A_{VA} \times \frac{R_i}{R_i + R_s} = \overset{-2.6}{-9.753} \times \frac{49.468}{49.468 + 0.5}$$

$$= -\cancel{9.606} -2.57$$

$$(ii) \tau = R_{eq} C_c$$

$$= (0.5 + 49.468) \mu\text{s}$$

$$= 49.968 \mu\text{s}$$

$$\therefore \omega = \frac{1}{\tau} = 20.0128 \text{ rad/s} = 2\pi f$$

$$\therefore f = \frac{\omega}{2\pi} = 3.185 \text{ Hz} \leftarrow$$

(b) Draw the small signal equivalent circuit diagram of the circuit shown in Fig. 2(b) and find the followings: (10 marks)

- (i) the midband voltage gain $A_v = \frac{v_o}{v_i}$,
- (ii) the output resistance R_o of the amplifier, and
- (iii) the corner frequency due to $C_L = 4$ pF assumed that $C_C \rightarrow \infty$.

Given that $R_{Si} = 2$ k Ω , $R_1 = 180$ k Ω , $R_2 = 330$ k Ω , $R_S = 1.0$ k Ω , $R_L = 10$ K Ω . The transistor parameters are $g_m = 0.65$ mA/V and $r_o = 100$ k Ω .


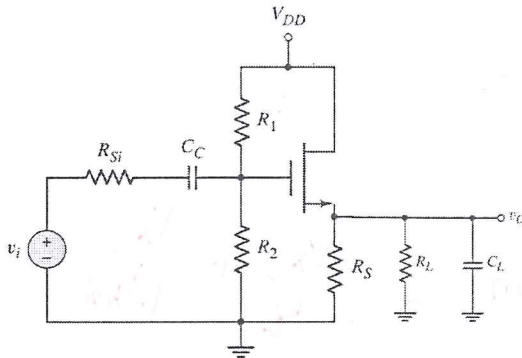


Fig. 2(b)

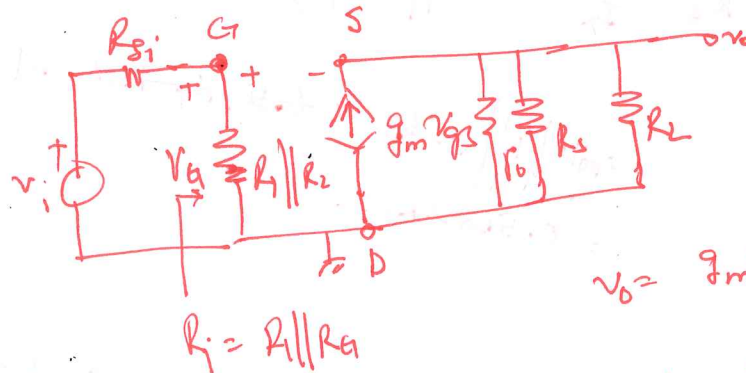

$$v_o = g_m v_{gs} R_L' \quad (R_L' = R_L || R_1 || R_2)$$

$$R_i = R_1 || R_2$$

$$v_{gs} = v_{gs} + v_o$$

$$= v_{gs} + g_m v_{gs} R_L'$$

$$= (1 + g_m R_L') v_{gs}$$

$$\therefore A_{vA} = \frac{v_o}{v_{gs}} = \frac{g_m v_{gs} R_L'}{(1 + g_m R_L') v_{gs}}$$

$$= \frac{g_m R_L'}{1 + g_m R_L'} = \frac{0.3696}{1 + 0.372} = 0.2696$$

$$g_m R_L' = 0.65 \times 10 || 1 || 100 = 0.586$$


$$\therefore A_v = A_{vA} \times \frac{R_i}{R_i + R_S} = 0.2696 \times \frac{116.47}{116.47 + 2} = 0.2657 \text{ V/V}$$

$$= 0.3633 \text{ V/V}$$

$$R_i = 180 || 330 = 116.47$$

2b

$R_o = ?$

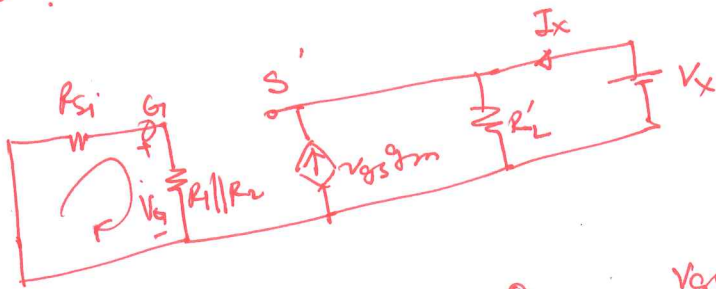

$$V_g = v_{gs} + V_x = 0 \quad \therefore v_{gs} = -V_x$$

$$I_x = \frac{V_x}{R_L} + v_{gs} g_m$$

$$= \frac{V_x}{R_L} + V_x g_m = \frac{V_x}{R_L} + \frac{V_x}{\left(\frac{1}{g_m}\right)}$$

$$\therefore R_o = \frac{V_x}{I_x} = R_L \parallel \left(\frac{1}{g_m}\right) \quad \frac{1}{g_m} = \frac{1}{0.65} = 1.538 \text{ K}$$

$$= 10 \parallel 0.1 \parallel 1.538 = \cancel{0.5714 \text{ K}\Omega} \\ = 0.5682 \text{ K}\Omega$$

iii) $\tau = R_{eq} \times C_L = 0.5682 \text{ K} \times 4 \text{ p} = 2.272 \text{ ns.}$

$$= \frac{1}{\tau} \quad f_H = \frac{1}{2\pi\tau} = 70 \text{ MHz}$$

Q.3 [20 marks]

(a) Draw the simplified high frequency small-signal equivalent circuit diagram of the ac circuit shown in Fig. 3(a) and derive step by step short circuit current gain $A_i = I_c/I_b$. Then find the beta frequency f_β and cutoff frequency f_T and find the relation between gain and bandwidth. **(10 marks)**


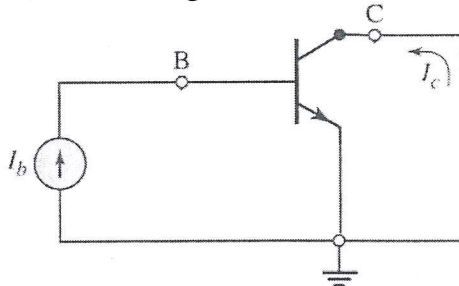


Fig. 3(a)

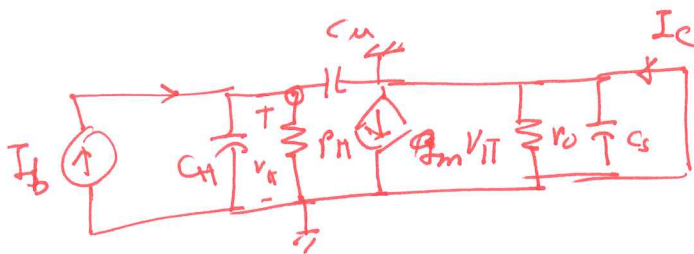

$$I_c = g_m V_{\pi} - \frac{V_{\pi}}{s C_u} = [g_m - s C_u] V_{\pi}$$

$$I_b = \frac{V_{\pi}}{s C_{\pi}} + \frac{V_{\pi}}{r_{\pi}} + \frac{V_{\pi}}{s C_u}$$

$$= V_{\pi} \left[s(C_{\pi} + C_u) + \frac{1}{r_{\pi}} \right] = \frac{V_{\pi}}{r_{\pi}} \left[1 + r_{\pi}(C_{\pi} + C_u) \right]$$

$$\therefore \frac{I_c}{I_b} = \frac{r_{\pi} (g_m - s C_u)}{1 + r_{\pi} s (C_{\pi} + C_u)} \approx \frac{r_{\pi} g_m}{1 + s r_{\pi} (C_{\pi} + C_u)} = \frac{\beta}{1 + s r_{\pi} (C_{\pi} + C_u)}$$

$$\tau = r_{\pi} (C_{\pi} + C_u)$$

$$\therefore f_{\beta} = \frac{1}{2\pi \tau} = \frac{1}{2\pi (C_{\pi} + C_u) r_{\pi}}$$


$$\therefore \omega_T = \frac{\beta}{r_{\pi} (C_{\pi} + C_u)} = \beta \omega_{\beta}$$

$$1 = \frac{\beta}{\sqrt{1 + (r_{\pi} \omega_T (C_{\pi} + C_u))^2}}$$

- (b) The common emitter amplifier is shown in Fig. 3(b) and operated at high frequencies. Draw the simplified high-frequency small signal equivalent circuit diagram and

(i) find the Miller capacitance, and

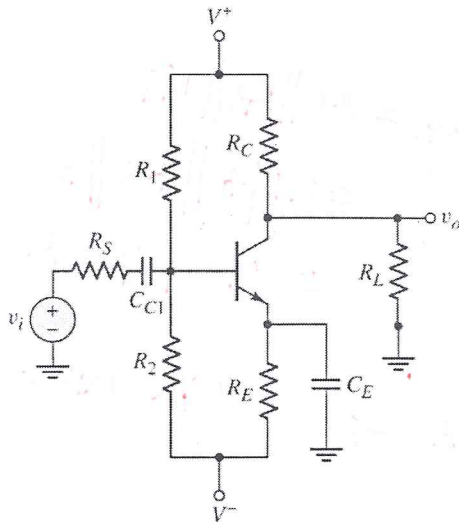- (ii) determine the upper 3dB frequency (f_H) considering Miller capacitance and without considering Miller capacitance. **(10 marks)**




The circuit parameters are:

$R_S = 0.1 \text{ k}\Omega$, $R_1 = 40 \text{ k}\Omega$, $R_2 = 6.8 \text{ k}\Omega$, $R_E = 1.2 \text{ k}\Omega$, $R_C = 5 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $C_C = \infty \mu\text{F}$ and $C_E = \infty \mu\text{F}$, $V^+ = 5\text{V}$, $V^- = 5\text{V}$.

The transistor parameters are:

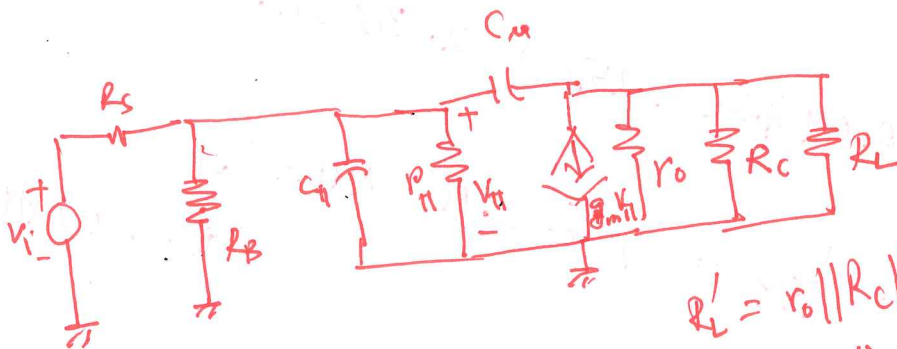$r_\pi = 3 \text{ k}\Omega$, $g_m = 40 \text{ mA/V}$ and $r_o = 100 \text{ k}\Omega$, $C_\pi = 25 \text{ pF}$, and $C_\mu = 2 \text{ pF}$




$$R'_L = r_o \parallel R_C \parallel R_L = 100 \parallel 5 \parallel 10 = 3.226 \text{ k}\Omega$$

$$A_{v_A} = -g_m R'_L = -40 \times 3.226 = -129.03 \text{ V/A}$$

$$\begin{aligned} \text{i) } C_{\pi} &= C_\pi + C_M \\ &= 25 + 260 \\ &= 285 \text{ pF} \end{aligned}$$

$$\begin{aligned} \text{(i) } C_M &= (1 + A_{v_A}) C_\mu \\ &= (1 + 129.03) \times 2 \text{ pF} \\ &= 260 \text{ pF} \end{aligned}$$

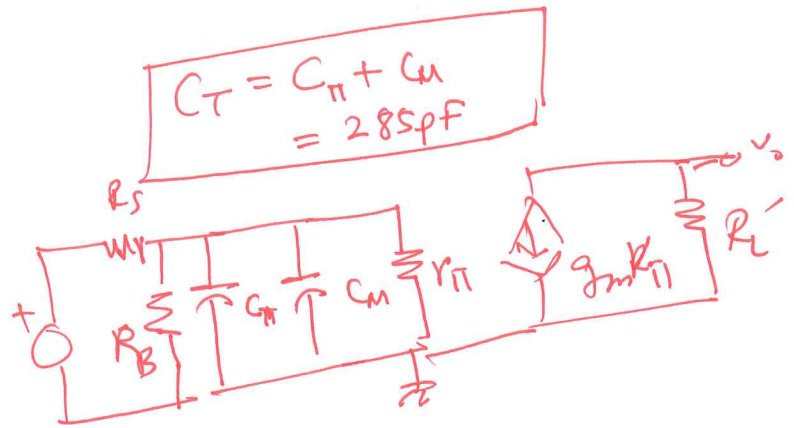ii) $\tau_M = R_{eq} C_M$
 $= R_{eq} \cdot C_T$



ii) $\tau_M = 0.0946 \times 285 \text{ p}$
 $= 26.97 \text{ ns}$

$$R_{eq} = R_s \parallel R_B \parallel R_{\pi}$$

$$= 0.1 \parallel 40 \parallel 4.8 \parallel 3$$

$$= 0.0946 \text{ K}$$

$f_{AM} = \frac{1}{2\pi\tau_M} = 5.9 \text{ MHz}$ ← with Miller effect

$\tau = 0.0946 \text{ K} \times 25 \text{ p} = 2.365 \text{ ns}$

$f_H = \frac{1}{2\pi\tau} = 67.296 \text{ MHz}$ ← without Miller effect