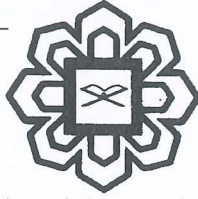


Name: _____

Matric No: _____ Section: _____



الجامعة الإسلامية العالمية ماليزيا

INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA

MID-TERM EXAMINATION
SEMESTER II, 2015/2016 SESSION
KULLIYAH OF ENGINEERING

Programme : ENGINEERING Level of Study : UG 2
Time : 8:00pm-10:00 pm Date : 17/03/2016
Duration : 2 Hours
Course Code : ECE 2133 Section(s) : 1 & 2
Course Title : **Electronic Circuits**

This Question Paper consists of **Twelve (12)** Printed Pages (Including Cover and a blank page) with **Three (3)** Questions.

INSTRUCTION(S) TO CANDIDATES

DO NOT OPEN UNTIL YOU ARE ASKED TO DO SO

- Use only pen for writing answer.
- Do not use your own sheet.
- Useful formulas and values are given in page 10.
- A total mark of this examination is 60.
- This examination is worth 30% of the total assessment.
- For drawing you may use pencil
- Answer **ALL** questions.

Any form of cheating or attempt to cheat is a serious offence which may lead to dismissal.

	Q 1a	Q 1b	Q 2	Q 3	Total Marks
Marks	10	10	20	20	60
Marks Obtained					

Q.1 [20 marks]

(a) Derive the transfer function of the circuit shown in Fig. 1(a).

(10 marks)

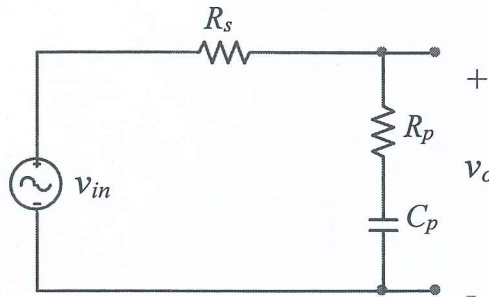


Fig. 1(a)

$$\text{Transfer function } T(s) = \frac{v_o(s)}{v_{in}(s)} = \frac{Z_p}{Z_p + Z_s}$$

$$Z_p = R_p + \frac{1}{sC_p} \quad Z_s = R_s$$

$$Z_p + Z_s = (R_p + R_s) + \frac{1}{sC_p} = \frac{1 + sC_p(R_p + R_s)}{sC_p}$$

$$\therefore T(s) = \frac{Z_p}{Z_p + Z_s} = \frac{\frac{1 + sC_p R_p}{sC_p}}{\frac{1 + sC_p(R_p + R_s)}{sC_p}}$$

$$\therefore T(s) = \frac{Z_p}{Z_p + Z_s} = \frac{\frac{1 + sC_p R_p}{sC_p}}{\frac{1 + sC_p(R_p + R_s)}{sC_p}}$$

$$= \frac{1 + sC_p R_p}{1 + sC_p(R_p + R_s)}$$

$$= \frac{1 + sC_p R_p}{1 + sC_p(R_p + R_s)}$$

$$Z_p = (C_p R_p)$$

$$Z_s = (R_p + R_s)$$



(b) Draw the Bode magnitude and phase plots of the following transfer function:



$$T(s) = 10^6 \frac{s(s + 200)}{(s + 10)(s + 50)} \quad (5+5 \text{ marks})$$

$$T(s) = \frac{10^6 \times s \times 200 \left[1 + \frac{s}{200}\right]}{10 \left[1 + \frac{s}{10}\right] 50 \left[1 + \frac{s}{50}\right]} = \frac{4 \times 10^6 s \left(1 + \frac{s}{200}\right)}{\left(1 + \frac{s}{10}\right) \left(1 + \frac{s}{50}\right)}$$

Corner frequencies,
 $\omega_{c1} = 200 \text{ rad/sec}$, $\omega_{c2} = 10 \text{ rad/sec}$, $\omega_{c3} = 50 \text{ rad/sec}$

Magnitude plot

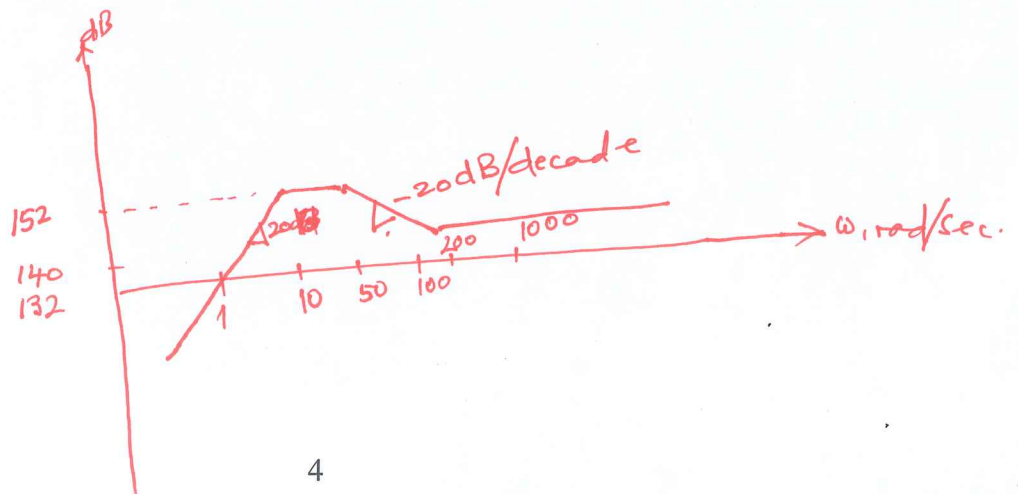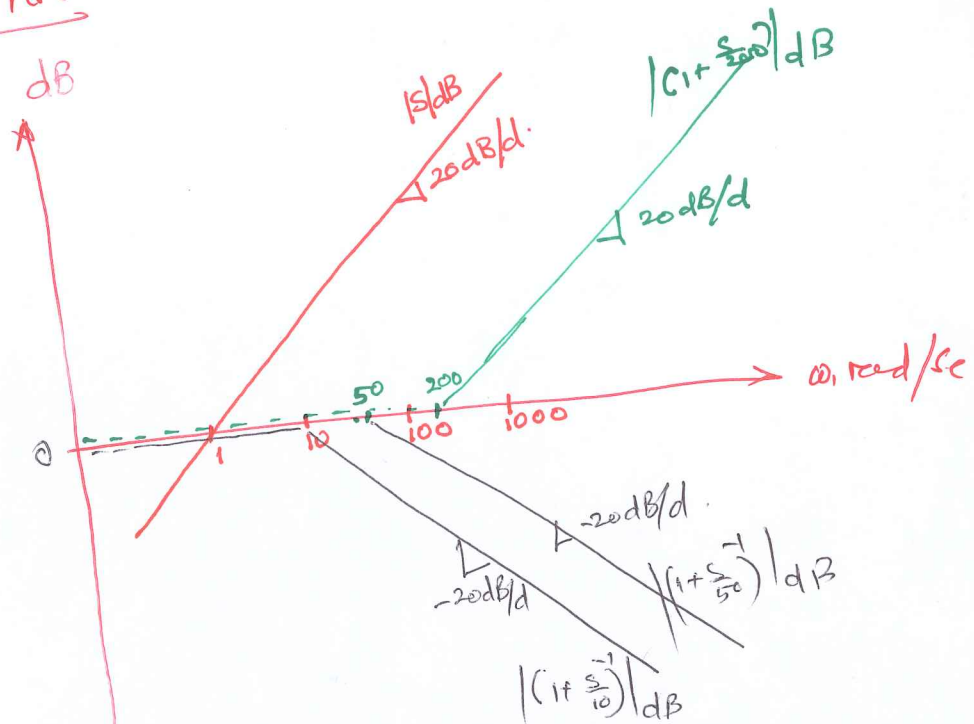

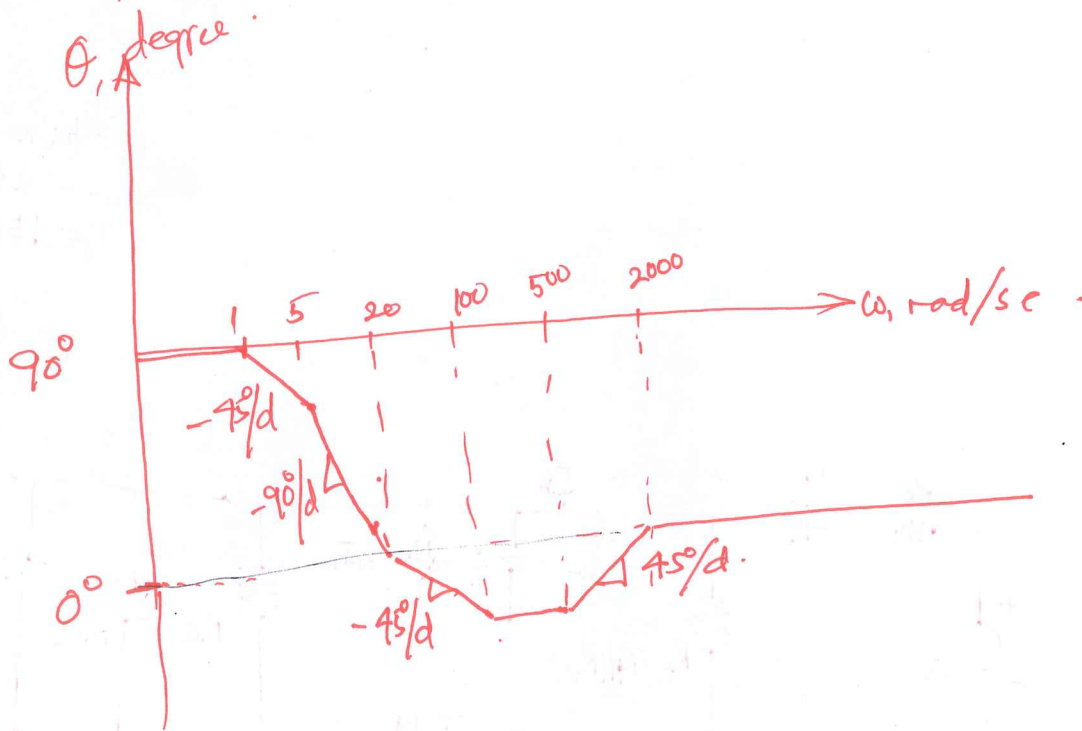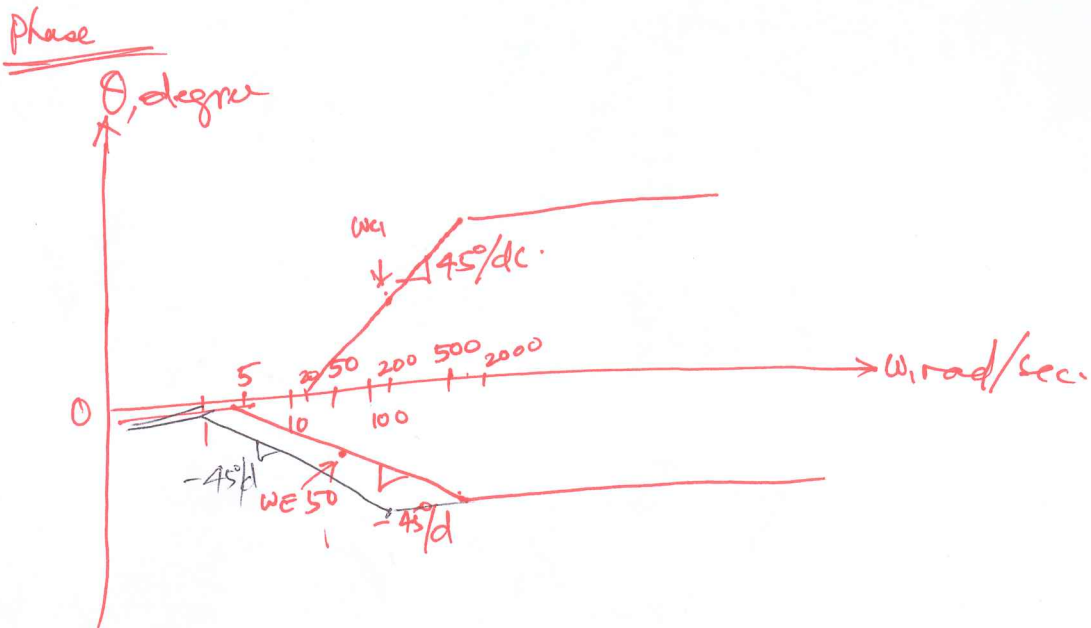

Q.2 [20 marks]

For the BJT amplifier circuit shown in Fig. 2(a) with transistor parameters, $g_m = 50 \text{ mA/V}$, $r_\pi = 3 \text{ k}\Omega$ and $r_o = \infty$,

- (i) Draw the small signal equivalent circuit diagram of the amplifier (4 marks)
- (ii) Find the lower corner frequency due to coupling capacitor C_{C1} (5 marks)
- (iii) Find the midband voltage gain, $A_v = \frac{v_o}{v_s}$ of the amplifier in dB (6 marks)
- (iv) Find the bandwidth of the amplifier (5 marks)


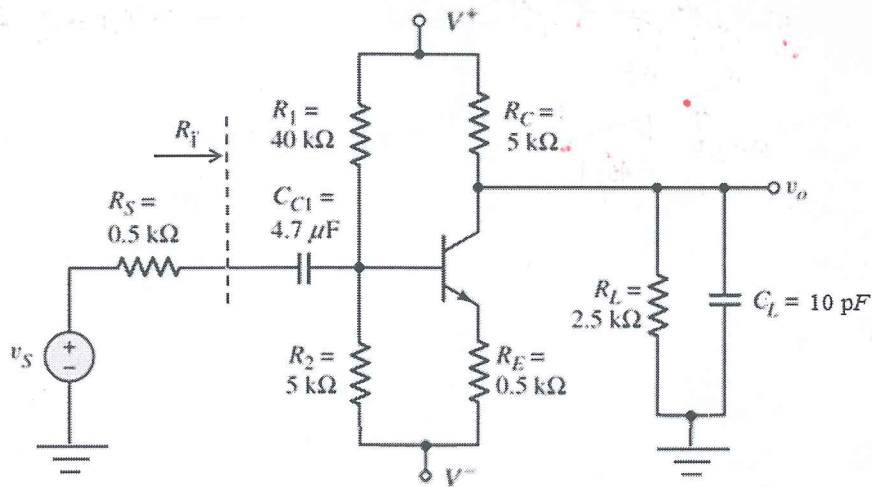


Fig. 2(a)

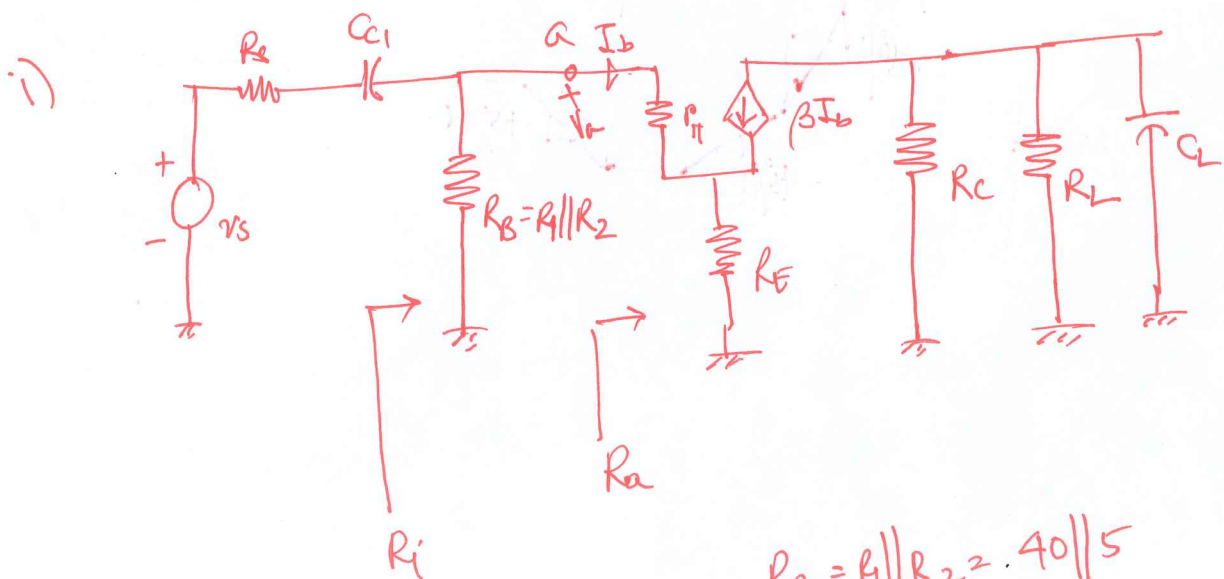$\beta = g_m r_\pi$
 $= 50 \times 3$
 $= 150$



$R_B = R_1 || R_2 = 40 || 5$
 $= 4.44 \text{ k}\Omega$

$$\text{(ii)} \quad R_a = \frac{v_a}{i_b} = \frac{r_{\pi} I_b + (1 + \beta) I_b R_E}{I_b} = r_{\pi} + (1 + \beta) R_E$$

$$= 3 + (1 + 150) 0.5 = 78.5 \text{ K}$$

$$R_i = R_1 \parallel R_2 \parallel R_a = 40 \parallel 5 \parallel 78.5 = 4.206 \text{ K}$$

$$\tau = C \times (R_i + R_s) = 4.7 \mu \times (4.206 + 0.5) \text{ K}$$

$$= 22.12 \text{ ns}$$

$$\therefore f_L = \frac{1}{2\pi\tau} = 7.195 \text{ Hz} \quad \leftarrow$$

$$\text{(iii)} \quad A_{vA} = \frac{v_o}{v_a} = \frac{-\beta I_b R'_L}{[r_{\pi} + (1 + \beta) R_E] I_b}$$

$$= - \frac{\beta R'_L}{r_{\pi} + (1 + \beta) R_E} = - \frac{150 \times 1.67 \text{ K}}{78.5 \text{ K}}$$

$$R'_L = R_C \parallel R_L = 1.67 \text{ K}$$

$$= -3.185$$

$$\therefore A_v = A_{vA} \times \frac{R_i}{R_i + R_s} = -3.185 \times \frac{4.206}{4.206 + 0.5}$$

$$= -2.846 = 9.086 \text{ dB}$$

$$\text{(iv)} \quad \tau_H = C_L \times R'_L = 10 \text{ p} \times 1.67 \text{ K} = 16.7 \text{ ns}$$

$$f_H = \frac{1}{2\pi\tau_H} = 9.53 \text{ MHz}$$

$$\text{BW} = f_H - f_L \approx f_H = 9.53 \text{ MHz} \quad \leftarrow$$

Q.3 [20 marks]

The common drain amplifier is shown in Fig. 3 that operated at high frequencies. The transistor parameters are: $g_m = 2.2 \text{ mA/V}$, $r_o = 100 \text{ k}\Omega$, $C_{gs} = 10 \text{ pF}$, and $C_{gd} = 1 \text{ pF}$.

- (i) Draw the simplified high-frequency small signal equivalent circuit diagram. (3 marks)
- (ii) Draw the Miller equivalent circuit diagram. (2 marks)
- (iii) Calculate the value of Miller capacitance. (5 marks)
- (iv) Evaluate the higher corner frequency (f_{HM}) considering Miller capacitance (4 marks)
- (v) Evaluate the higher corner frequency (f_H) without considering Miller capacitance. (4 marks)
- (vi) Which frequency is considered for determining bandwidth of the amplifier out of above two corner frequencies? Justify. (2 mark)



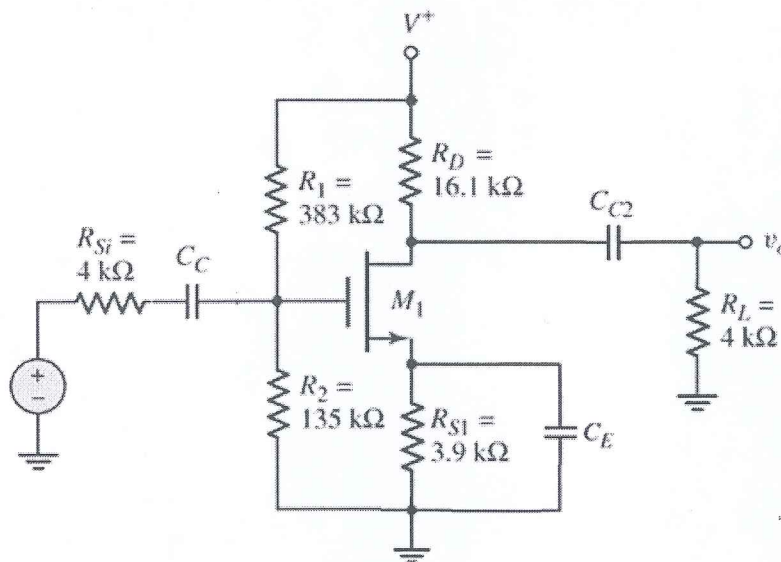


Fig. 3

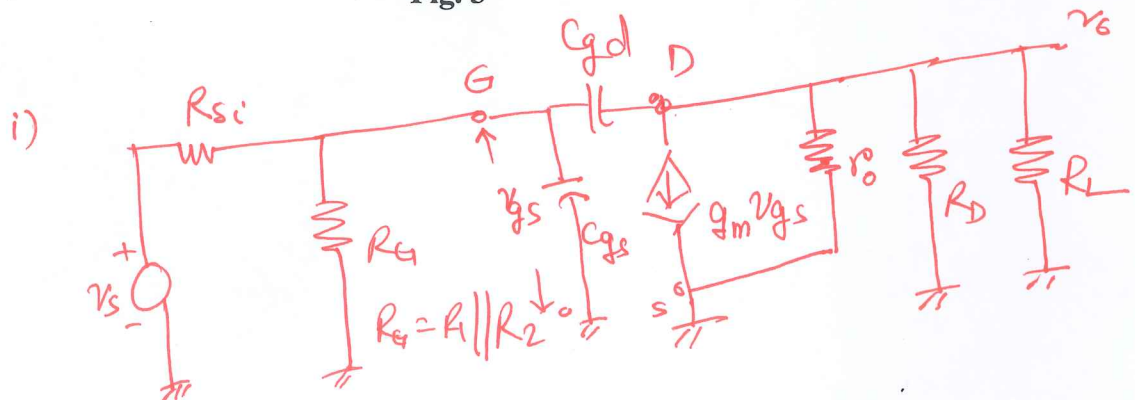

ii)

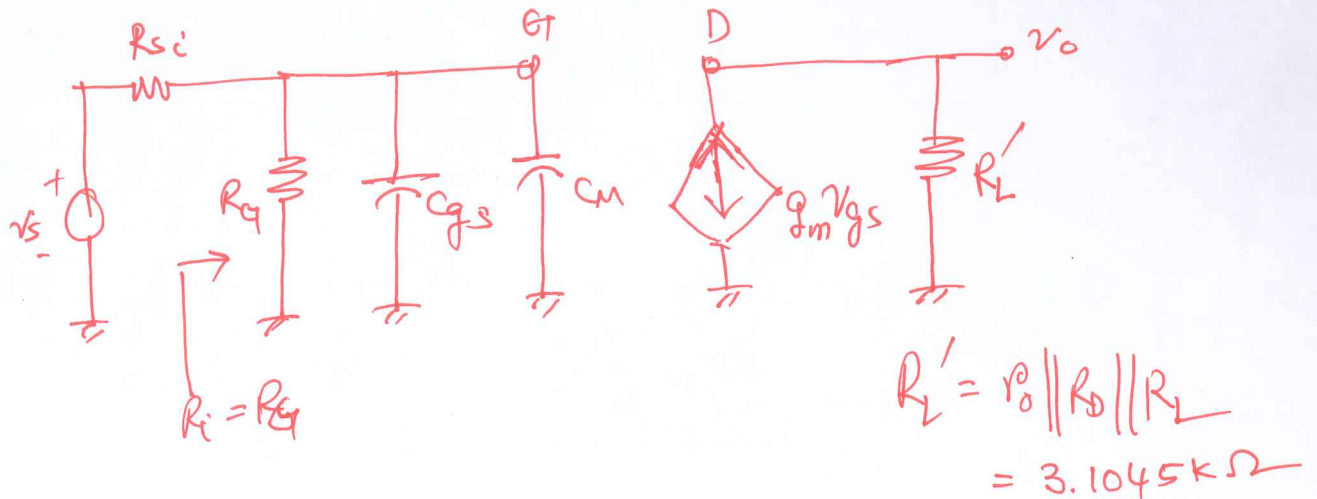

$$(iii) \quad C_M = C_{gd} (1 - A_{vA})$$

$$A_{vA} = \frac{-g_m v_{gs} R_L'}{v_{gs}} = -g_m R_L'$$

$$\therefore C_M = C_{gd} [1 + g_m R_L'] = 10 \text{ p} \times [1 + 2.2 \times 100 \parallel 16.1 \parallel 4] = 7.83 \text{ pF}$$

$$R_{eq} = R_{si} \parallel R_G = 4 \parallel 383 \parallel 135 = 3.846 \text{ k}\Omega$$

$$iv) \quad C_T = C_{gs} + C_M = 10 \text{ p} + 7.83 \text{ p} = 17.83 \text{ p}$$

$$\tau_M = R_{eq} C_T = 68.57 \text{ ns}$$

$$f_{HM} = \frac{1}{2\pi \tau_M} = 2.32 \text{ MHz}$$

$$\tau_H = R_{eq} C_{gs} = 38.46 \text{ ns}$$

$$v) \quad C_T = C_{gs}$$

$$\therefore f_{H_{Cgs}} = 4.14 \text{ MHz}$$

$$vi) \quad f_H = 2.32 \text{ MHz}$$

after this frequency voltage gain starts to drop below 3dB.