

Matric No.: [ ]

Section: [ ]

Name: [ ]



الجامعة الإسلامية العالمية ماليزيا  
INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA  
جامعة إسلامية دولية ماليزيا

### KULLIYYAH OF ENGINEERING

#### MIDTERM EXAMINATION SEMESTER I, 2023/2024 SESSION

Programme : BEEE

Level of Study : UG 2

Time : 8:00 pm - 10:00 pm

Date : 22/11/2023

Duration : 2 Hrs.

Section(s) : 1-3

Course Code : EECE 2313

Course Title : Electronic Circuits

This Question Paper Consists of 6 (Six) Printing Pages (Including Cover Page) with 3 (Three) Questions.

#### INSTRUCTION(S) TO CANDIDATES

- Total mark of this examination is 25.
- This examination is worth 25% of the total course assessment.
- Answer ALL QUESTIONS.
- Marks assigned to each problem are listed in the margins.
- Write your answer on the question paper only, no additional page will provided.
- Write your answer using a pen, however, you can use a pencil for drawing the figure.

Q1	Q2	Q3	Total
8	6	11	25

## Question 1 [8 marks]

- (a) Derive the voltage transfer function step by step for the RC-circuit shown in Fig. 1 (a) as standard format. (3 marks)

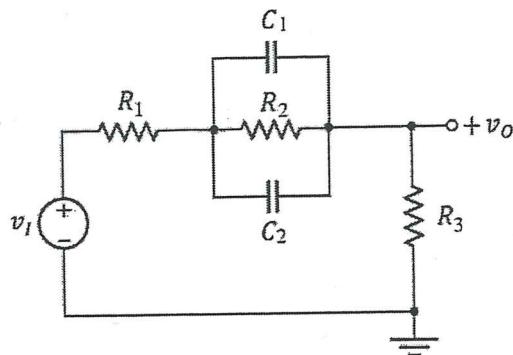


Fig. 1(a)

$$C_B = C_1 + C_2$$

$$Z_2 = R_2 \parallel \frac{1}{sC_B} = \frac{R_2 s C_B}{R_2 + s C_B}$$

$$= \frac{R_2}{1 + s C_B R_2}$$

$$Z_s = R_1 + \frac{R_2}{1 + s C_B R_2}$$

$$Z_s + Z_p = R_1 + \frac{R_2}{1 + s C_B R_2} + R_3 = \frac{(R_1 + R_2 + R_3) + (R_1 + R_2) s C_B R_2}{1 + s C_B R_2}$$

$$T(s) = \frac{Z_p}{Z_s + Z_p} = \frac{R_3 (1 + s C_B R_2)}{R_1 + R_2 + R_3 + s (R_1 + R_2) R_3 C_B}$$

$$= \frac{R_3}{R_1 + R_2 + R_3} \cdot \frac{1 + s C_B R_2}{1 + \frac{s (R_1 + R_2) R_3 C_B}{R_1 + R_2 + R_3}}$$

$$= K_1 \cdot \frac{1 + s \tilde{\gamma}_1}{1 + s \tilde{\gamma}_2}$$

$$\tilde{\gamma}_1 = C_B R_2 \leftarrow$$

$$\tilde{\gamma}_2 = C_B (R_1 + R_2) \parallel R_3 \leftarrow$$

- (b) Assume that the circuit components of Fig. 1(a) are  $R_1 = 1.0 \text{ k}\Omega$ ,  $R_2 = 5.0 \text{ k}\Omega$ ,  $R_3 = 2.5 \text{ k}\Omega$ ,  $C_1 = 5.0 \text{ pF}$ , and  $C_2 = 15.0 \text{ pF}$  respectively. (3 marks)

- Determine the -3dB corner frequency for the circuit
- Determine the magnitude of the transfer function at -3dB corner frequency
- Determine the phase of the transfer function at -3dB corner frequency

$$(i) \quad f_1 = \frac{1}{2\pi C_1} = \frac{1}{2\pi \times 20 \text{ pF} \times 5 \text{ K}} = 1.59 \text{ MHz}$$

$$f_2 = \frac{1}{2\pi C_2} = \frac{1}{2\pi \times 20 \text{ pF} \times 1.7647 \text{ K}} = 4.509 \text{ MHz}$$

$$C_1 = (R_1 + R_2) R_3 = (5 + 15) \text{ pF} \times 2.5 \text{ K} = 20 \text{ pF} \times 2.5 \text{ K}$$

$$C_2 = (R_1 + R_2) R_3 = (5 + 15) \text{ pF} \times 1.7647 \text{ K} = 20 \text{ pF} \times 1.7647 \text{ K}$$

$$\frac{C_1}{C_2} = \frac{5 \text{ K}}{1.7647 \text{ K}} = 2.83$$

$$K = \frac{R_3}{R_1 R_2 + R_3} = \frac{2.5}{8.5} = 0.29$$

$$(ii) \quad T_{H_1} = 0.29 \times \frac{1+j1}{1+2.83}$$

$$T_{H_2} = 0.29 \times \frac{1+j2.83}{1+j1}$$

- (c) The transfer function of an RC-circuit is represented as, (2 marks)

$$T(j\omega) = 5.0 + j10.72$$

Represent the transfer function in,

- Exponential form

- Polar form

$$\text{Polar} = \sqrt{5^2 + 10.72^2} \angle \tan^{-1} \frac{10.72}{5} = 11.828 \angle 64.99^\circ$$

$$\text{Exponential } T = 11.828 e^{j64.99^\circ}$$

**Question 2 [6 marks]**

- (a) Plot the Bode magnitude and phase for the following transfer function. (4 marks)

$$T(s) = \frac{10^{-2}(s + 30)(s + 50)}{s(s + 60)}$$



- (b) Determine the magnitude and phase from the plot at angular frequency, (2 marks)
- 
- $s = 550 \text{ rad/sec}$

$$T = 10^{-2} \times \frac{30 \times 50}{60} = 0.25$$

$$T_{dB} = -12 \text{ dB}$$

$$T = 0.25 \times \frac{\frac{s}{30} \times \frac{s}{50}}{\frac{s}{30} \times \frac{s}{60}} = 0.25 \times \frac{60}{30 \times 50} = 0.01$$

$$T_{s=550} = -40 \text{ dB}$$

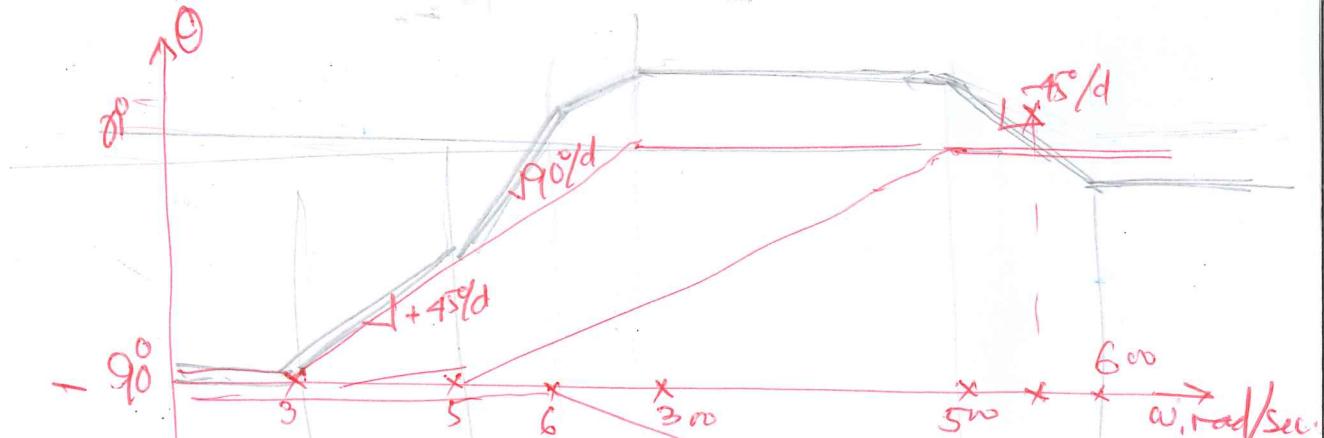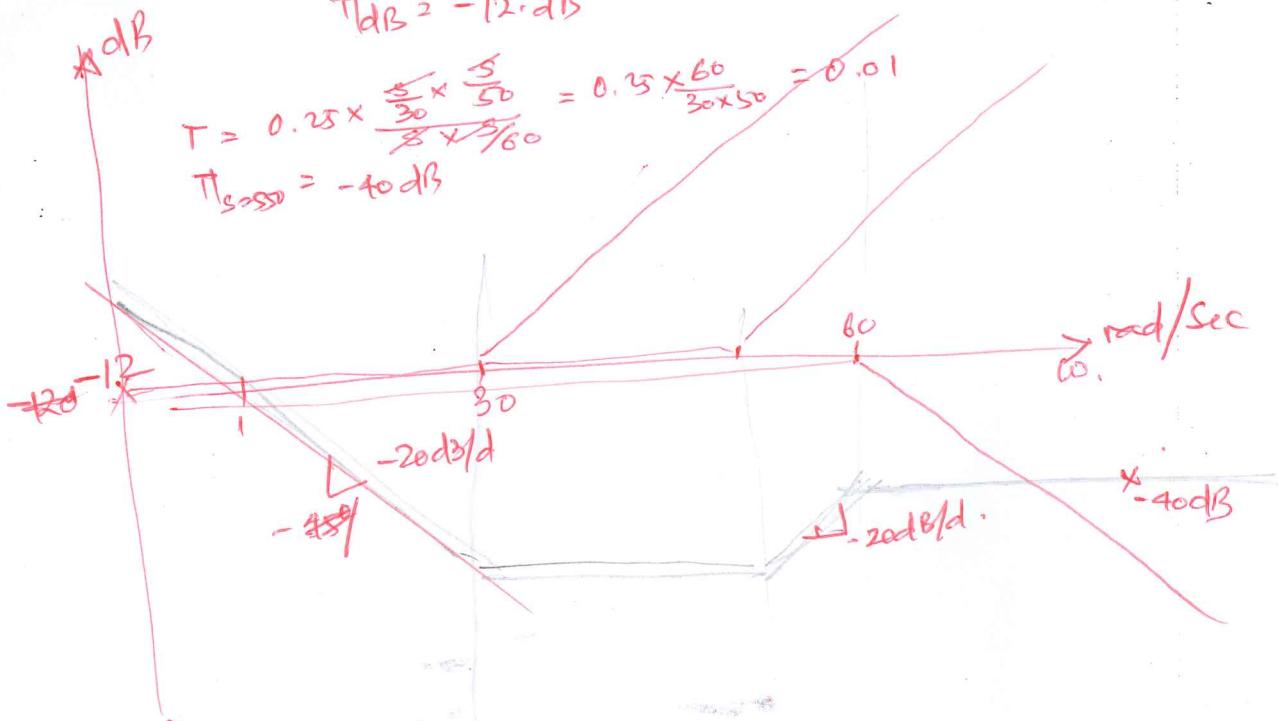

$$\theta = -90^\circ + \tan^{-1} \frac{550}{30} + \tan^{-1} \frac{-1550}{50} - \tan^{-1} \frac{550}{60}$$

$$= -90^\circ + 86.87^\circ + 84.8^\circ - 83.77^\circ = -2.1^\circ$$

**Question 3 [11 marks]**

A common source audio amplifier is shown in Fig. 3 with the following circuit component values,  $R_{Si} = 7.5 \text{ k}\Omega$ ,  $R_G = 15 \text{ k}\Omega$ ,  $R_S = 1.0 \text{ k}\Omega$ ,  $R_D = 5 \text{ k}\Omega$ ,  $R_L = 5 \text{ k}\Omega$  and  $C_{C1} = \infty$ . The MOSFET has AC small-signal parameters,  $g_m = 5.0 \text{ mA/V}$ , and  $r_0 = \infty$ .

- (a) Design the amplifier circuit for the lower corner frequency 20 Hz. (marks 2)
- (b) Draw the small-signal equivalent circuit and determine the maximum voltage gain of the designed amplifier in dB. (marks 3)

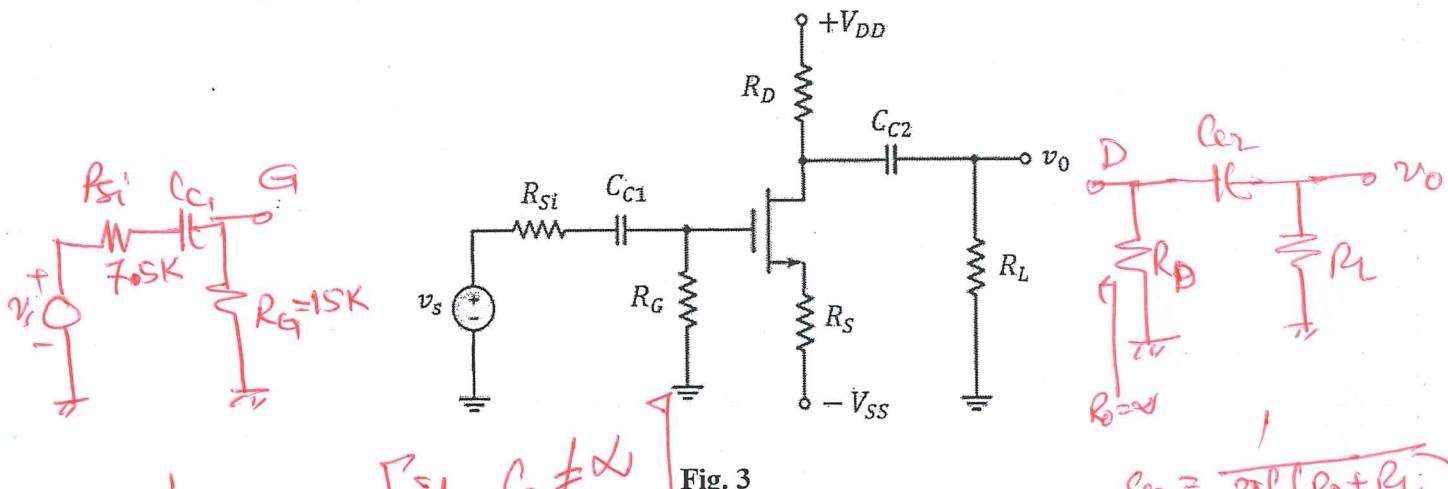


Fig. 3

$$A_{i1} = \frac{1}{2\pi f (R_{Si} + R_G)} \\ = \frac{1}{2\pi \times 20 [7.5 + 15] \text{ k}} \\ = 0.3536 \mu\text{A}$$

$$R'_i = R_G = 15 \text{ k}$$

$$A_{VA} = \frac{-g_m V_{GS} R'_i}{r_s + g_m V_{GS} R_S}$$

$$= \frac{-g_m R'_i}{1 + g_m R_S} = \frac{5 \text{ mA} \times 2.5 \text{ k}}{1 + 5 \text{ mA} \times 1 \text{ k}} = -\frac{12.5}{1+5} = -2.08$$

$$A_V = A_{VA} \times \frac{R'_i}{R_{Si} + R_G} = -2.08 \times \frac{15}{(7.5 + 15)} = -1.388$$

$$A_V \text{ dB} = 20 \log_{10} (1.388) = 2.853 \text{ dB} \leftarrow$$

- (c) A short-circuit common-emitter amplifier small-signal equivalent circuit using a simplified BJT high-frequency model is shown in Fig. 3(c).
- Derive the high frequency short-circuit current gain expression stepwise and determine the  $f_B$  frequency. (4 marks)
  - If the BJT small-signal parameters values are,  $\beta_0 = 100$ ,  $r_\pi = 750\Omega$ ,  $r_o = 100 k\Omega$ ,  $C_\pi = 10 pF$  and  $C_\mu = 2 pF$  determine the cut-off frequency of the transistor. (2 marks)

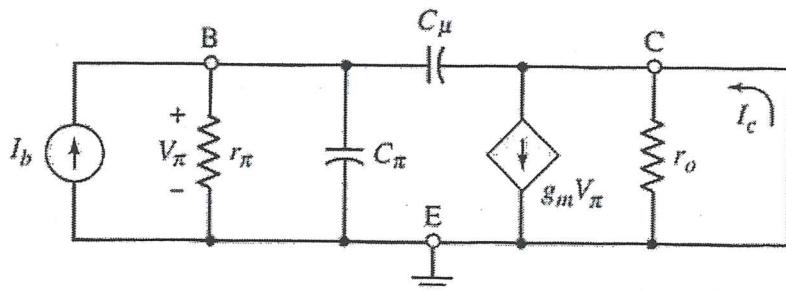


Fig. 3(c)

$$\textcircled{1} \quad I_b = \frac{V_\pi}{r_\pi} + \frac{V_\pi}{Y_s C_\mu} + \frac{V_\pi}{Y_s C_\pi} = \frac{V_\pi}{r_\pi} \left[ 1 + s r_\pi (C_\mu + C_\pi) \right]$$

$$I_c = g_m V_\pi - V_\pi s C_\mu = V_\pi \left[ g_m - s C_\mu \right]$$

$$\therefore A_T = \frac{I_c}{I_b} = \frac{V_\pi (g_m - s C_\mu)}{V_\pi \left[ 1 + s r_\pi (C_\mu + C_\pi) \right]} = \frac{g_m r_\pi - s C_\mu r_\pi}{1 + s r_\pi (C_\mu + C_\pi)}$$

$$= \frac{g_m r_\pi}{1 + s r_\pi (C_\mu + C_\pi)} \quad \therefore f_B = \frac{1}{2\pi r_\pi} \quad \therefore f_B = \frac{1}{2\pi r_\pi (C_\mu + C_\pi)}$$

$$= \frac{\beta}{1 + s r_\pi (C_\mu + C_\pi)} = \frac{\beta}{1 + s^2 \beta} \quad \therefore f_B = \frac{1}{2\pi \beta}$$

$$\textcircled{2} \quad f_B = \frac{1}{2\pi r_\pi (C_\mu + C_\pi)} = \frac{1}{2\pi 750 (10^{-12} + 2 \times 10^{-12})} = 17.6838 \text{ MHz}$$

$$\therefore f_T = \beta f_B = 100 \times 17.6838 = \underline{\underline{1.768 \text{ GHz}}}$$