

Matric No.:

Section:

Name:



الجامعة الإسلامية العالمية ماليزيا  
INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA  
يُونَيْتِي إِسْلَامِيَّةٌ اِبْتَدَائِيَّةٌ مَلَيْسِيَّةٌ

**KULLIYAH OF ENGINEERING**

**MIDTERM EXAMINATION  
SEMESTER II, 2022/2023 SESSION**

Programme : **Engineering** Level of Study : **UG 2**  
Time : **8:00 pm - 10:00 pm** Date : **19/04/2023**  
Duration : **2 Hrs**  
Course Code : **EECE 2313** Section(s) : **1**  
Course Title : **Electronic Circuits**

This Question Paper Consists of **5 (Five)** Pages (Including Cover Page) with **4 (Four)** Questions.


**INSTRUCTION(S) TO CANDIDATES**

- Total mark of this examination is **25**.
- This examination is worth **25%** of the total course assessment.
- Answer **ALL QUESTIONS**.
- Marks assigned to each problem are listed in the margins.
- Write your answer on the question paper, no additional page will be provided.
- Write your answer using pen, however you can use pencil for drawing the figure.

Q1 (6)	Q2 (7)	Q3 (8)	Q4 (4)	Total (25)
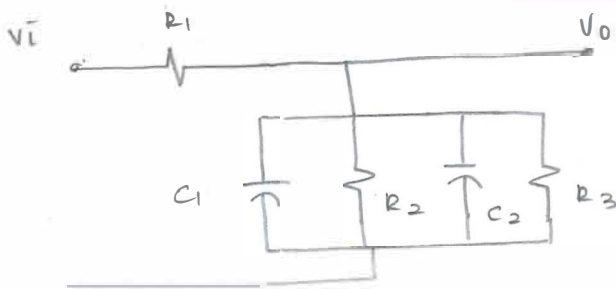
## Question 1 [6 marks]

Consider the circuit shown in the Fig. 1, derive the expression (step by step) for the voltage transfer function, . Find the time constant and corner frequency of the circuit. (6 marks)



$$T(s) = \frac{Z_p}{Z_s + Z_p} \quad C_3 = C_1 + C_2$$

$$Z_p = (R_2 \parallel R_3 \parallel \frac{1}{sC_3})$$

$$Z_p = \left( \frac{1}{R_2 R_3} + \frac{1}{R_3} + \frac{sC_3}{R_2 R_3} \right)^{-1}$$

$$Z_p = \left( \frac{R_2 + R_3 + sC_3 R_2 R_3}{R_2 R_3} \right)^{-1}$$

$$Z_s = R_1$$

$$Z_p + Z_s = R_1 + \frac{R_2 R_3}{R_2 + R_3 + sC_3 R_2 R_3}$$

$$Z_p + Z_s = \frac{R_1 (R_2 + R_3 + sC_3 R_2 R_3) + R_2 R_3}{R_2 + R_3 + sC_3 R_2 R_3}$$

$$Z_p + Z_s = \frac{(R_1 R_2 + R_1 R_3 + R_2 R_3) + sC_3 R_1 R_2 R_3}{R_2 + R_3 + sC_3 R_2 R_3}$$

$$T(s) = \frac{Z_p}{Z_p + Z_s} = \frac{R_2 R_3}{(R_1 R_2 + R_1 R_3 + R_2 R_3) + sC_3 R_1 R_2 R_3}$$

$$T(s) = \frac{R_2 R_3}{(R_1 R_2 + R_1 R_3 + R_2 R_3) \left( 1 + \frac{sC_3 R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} \right)}$$

$$T(s) = k \cdot \frac{1}{1 + s\tau}$$

$$k = \frac{R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} \quad ; \quad \tau = C_3 \left( \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} \right)$$

$$f = \frac{1}{2\pi\tau} = \frac{1}{2\pi C_3 \left( \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} \right)}$$

Question 2 [7 marks]

Plot the Bode magnitude and phase for the following transfer function.

$$T(s) = \frac{10^3(s + 10)}{s(s + 100)}$$



and determine the magnitude and phase at angular frequency (50 rad/sec.)

$$T(s) = \frac{10^3(10)}{(100)} \cdot \frac{(1 + \frac{s}{10})}{s(1 + \frac{s}{100})} = 100 \frac{(1 + \frac{s}{10})}{s(1 + \frac{s}{100})}$$

$$20 \log(100) = 40 \text{ dB} \#$$

$$|T(s)|_{\omega=50} = 100 \frac{(\frac{50}{10})}{5(1)} = 10$$

$$20 \log(10) = 20 \text{ dB} \#$$

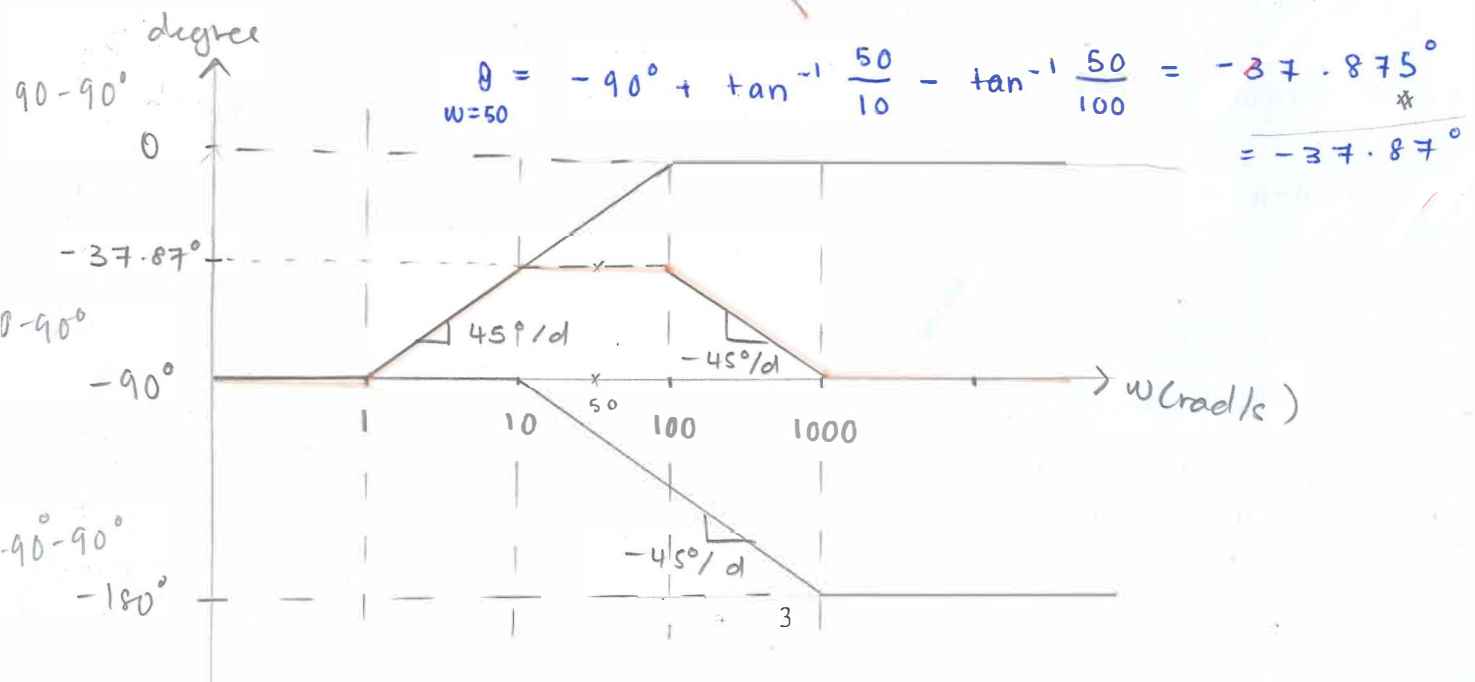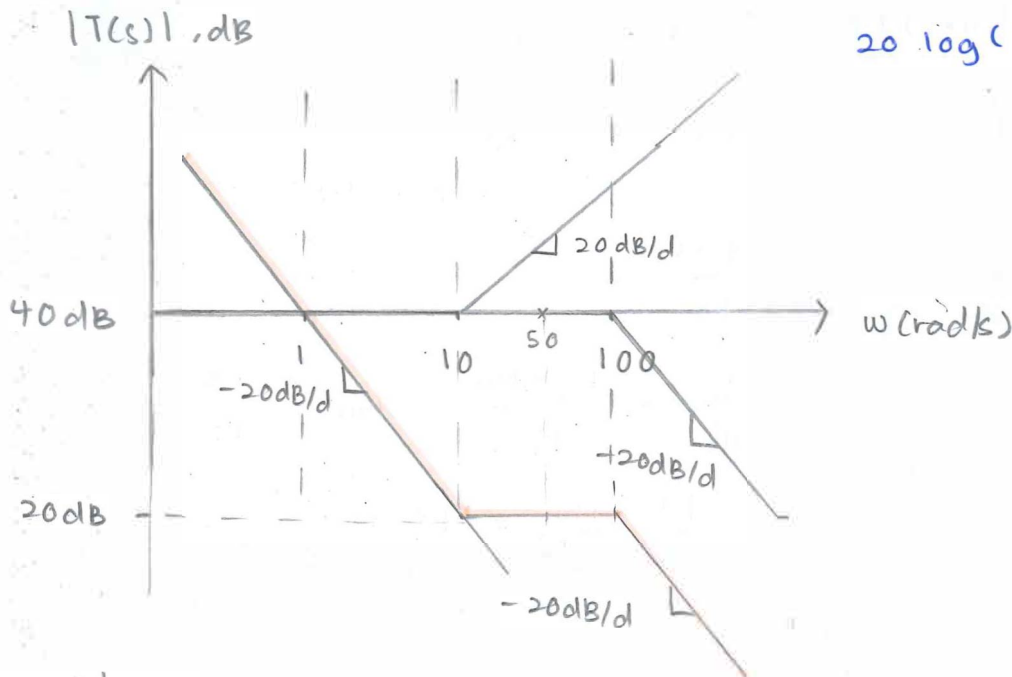

Question 3 [8 marks]

The common ~~drain~~<sup>source</sup> amplifier is shown in Fig. 3 The MOSFET has AC small-signal hybrid- $\pi$  parameters,  $g_m = 2 \text{ mA/V}$ .

- (a) Design the amplifier circuit for the lower corner frequency of 50 Hz and upper corner frequency of 50KHz (3 marks)
- (b) Draw the small-signal equivalent circuit and determine the maximum voltage and current gain of the designed amplifier in dB. (3 marks)
- (c) Write the low frequency voltage gain expression considering  $C_c$  and  $C_{c2} = \infty$ . (2 marks)

$R_i = R_g = (R_1 \parallel R_2) = 99.8166 \text{ k}\Omega$

$(R_D \parallel R_L) = 3.204 \text{ k}\Omega$



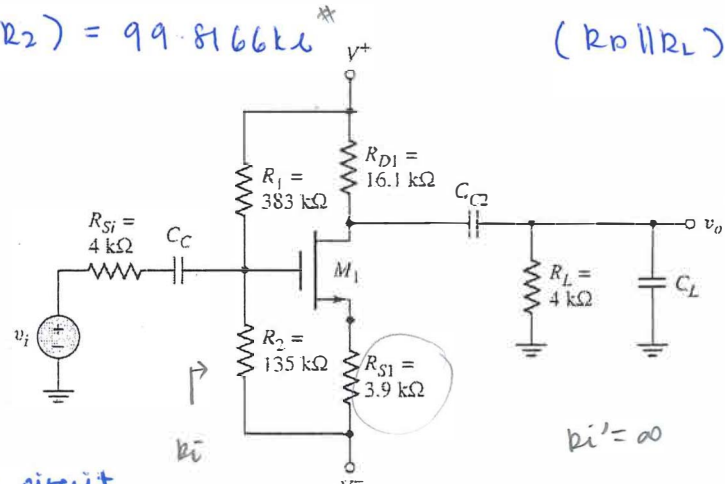


Fig. 3

(a) input eq. circuit

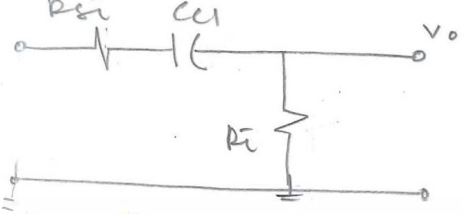

output eq. circuit

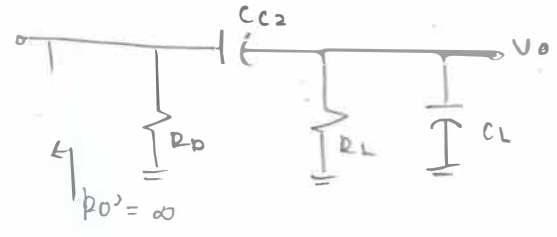

$f_{L1} = \frac{1}{2\pi C_{C1} [R_{Si} + R_i]} = 50 \text{ Hz}$

$3.066 \times 10^{-8} \text{ F}$

$C_{C1} = \frac{1}{2\pi (50) (4\text{k} + 99.8166\text{k})} = 30.66 \text{ nF}$

$f_{L2} = \frac{1}{2\pi C_{C2} [R_D + R_L]} = 50 \text{ Hz}$

$1.584 \times 10^{-7} \text{ F}$

$C_{C2} = \frac{1}{2\pi (50) (16.1\text{k} + 4\text{k})} = 0.1584 \mu\text{F}$

$f_H = \frac{1}{2\pi C_L [R_D \parallel R_L]} = 50 \text{ kHz}$


$9.935 \times 10^{-10} \text{ F}$

$C_L = \frac{1}{2\pi (50\text{k}) (3.204\text{k})} = 0.9935 \text{ nF}$

3. (b) small-signal eq circuit :

$$R_g = (R_1 || R_2) = (383 || 135)$$

$$R_g = 99.8166 \text{ k}\Omega$$

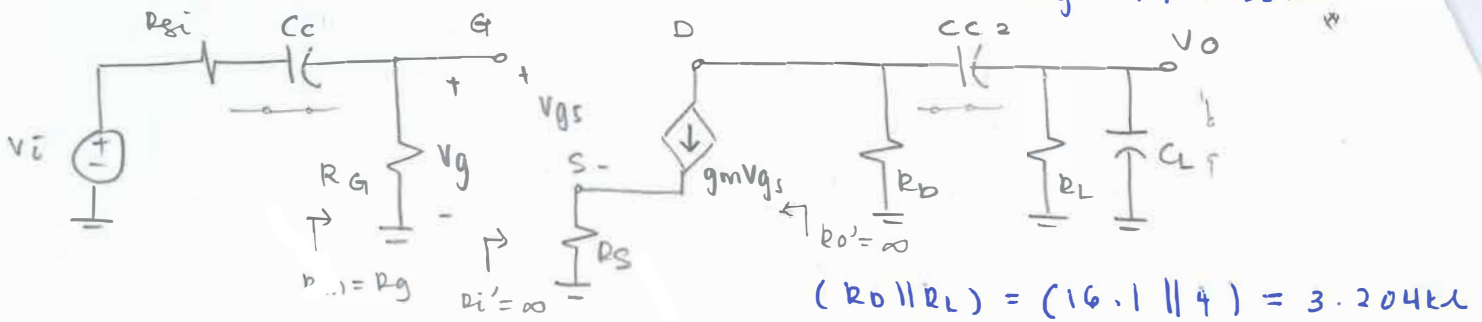

$$\text{voltage gain} = A_v = \frac{V_o}{V_i} = \frac{V_o}{V_g} \times \frac{V_g}{V_i}$$

$$A_{vA} = \frac{V_o}{V_g} = \frac{-g_m V_{gs} (R_D || R_L)}{V_{gs} + g_m V_{gs} R_S} = \frac{-g_m (R_D || R_L)}{1 + g_m R_S} = \frac{-2\text{m} (3.204\text{k})}{1 + 2\text{m} (3.9\text{k})} = -0.728$$

$$\frac{V_g}{V_i} = \frac{R_g}{R_g + R_{s_i}} = \frac{(R_1 || R_2)}{(R_1 || R_2) + R_{s_i}} = \frac{99.8166\text{k}}{(99.8166 + 4)\text{k}} = 0.96147$$

$$A_v = A_{vA} \times \frac{V_g}{V_i} = -0.728 (0.96147) = -0.70$$

(midband)

$$20 \log(0.7) = -3.098 \text{ dB}$$

current gain :

$$A_I = \frac{I_o}{I_i} = \frac{V_o / R_L}{V_i / R_g + R_{s_i}} = \frac{V_o}{V_i} \times \frac{R_g + R_{s_i}}{R_L}$$

$$A_I = A_{vA} \times \frac{R_g}{R_g + R_{s_i}} \times \frac{R_g + R_{s_i}}{R_L} = A_{vA} \times \frac{R_g}{R_L}$$

$$A_I = -0.728 \times \frac{99.8166}{4} = -18.167$$

(midband)

$$20 \log(18.167) = 25.186 \text{ dB}$$

3(c) low frequency voltage gain :  $C_C, C_{C2} = \infty$

$$C_{C2} = \infty$$

$$A_v|_{\text{low}} = A_{vA} \times \frac{R_g}{R_g + R_{s_i} + \frac{1}{sC_C}}$$

$$C_C = 30.66 \text{ nF}$$

$$A_v|_{\text{low}} = \frac{-g_m V_{gs} (R_D || R_L)}{V_{gs} + g_m V_{gs} R_S} \times \frac{R_g}{R_g + R_{s_i} + \frac{1}{sC_C}}$$

$$A_v|_{\text{low}} = \frac{-g_m (R_D || R_L)}{1 + g_m R_S} \times \frac{R_g}{R_g + R_{s_i} + \frac{1}{sC_C}} = -0.728 \times \frac{99.8166}{99.8166 + 4 + \frac{1}{sC_C}}$$

$$A_v|_{\text{low}} = -0.728 \times \frac{99.8166}{103.8166 + \frac{1}{s(30.66\text{n})}} = \frac{-72.67}{103.8166 + \frac{1}{s(20.66\text{n})}}$$

Question 4 [5 marks]

Step by step derive the output resistance  $R_o$  for midband frequency of the circuit shown in Fig. 4 and also identify the type of the amplifier. (4 marks)


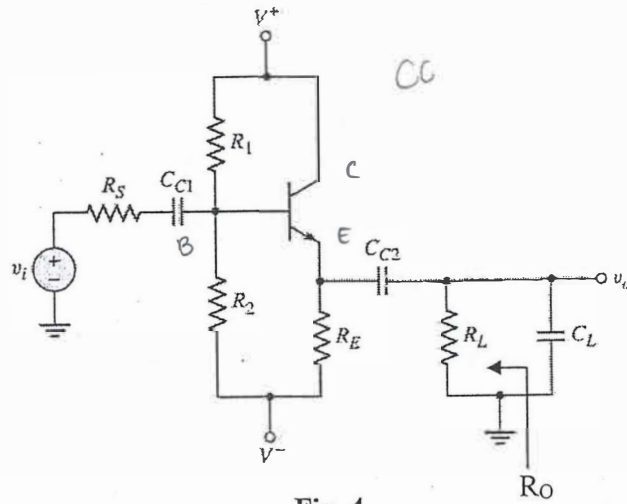
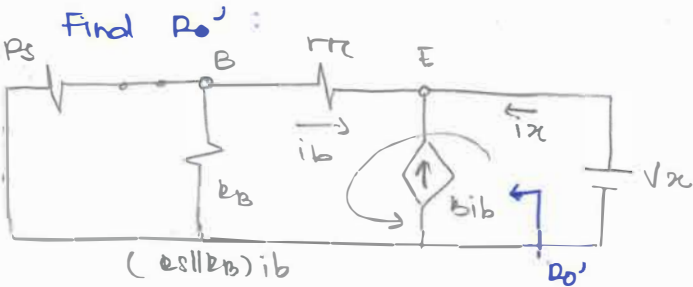


Fig. 4

$$R_B = (R_1 \parallel R_2)$$

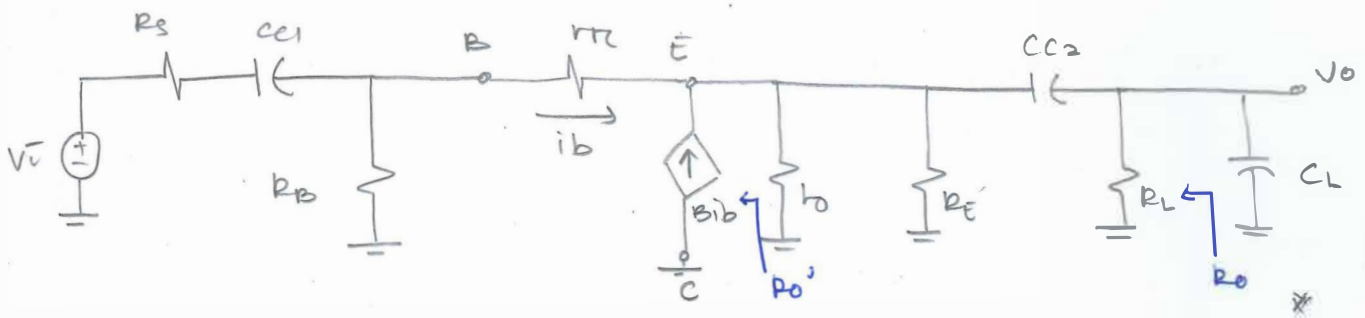

$$-v_x - r_{\pi} i_b - (R_s \parallel R_B) i_b = 0$$

$$v_x = -i_b (r_{\pi} + R_s \parallel R_B)$$

$$R_{o'} = \frac{v_x}{i_x}$$

$$v_x = -r_{\pi} i_b - (R_s \parallel R_B) i_b - (i_b + \beta i_b)$$

$$i_x = -i_b (1 + \beta)$$

$$R_{o'} = \frac{r_{\pi} + (R_s \parallel R_B)}{1 + \beta}$$

$$R_{o'} = \frac{r_{\pi} + (R_s \parallel R_1 \parallel R_2)}{1 + \beta}$$

$$R_o = (R_L \parallel R_E \parallel r_o \parallel R_{o'})$$

$$R_o = (R_L \parallel R_E \parallel r_o \parallel \frac{r_{\pi} + (R_s \parallel R_1 \parallel R_2)}{1 + \beta})$$

Type of amplifier: Common Collector Amplifier