

$$I_R = I_0 \left(1 + \frac{2}{1+\beta} \right)$$

2 transistors current source

$$R_0 = r_{o2} = \frac{V_A}{I_{e2}}$$

$$I_{c2} = I_0$$


$$I_R = I_0 \left(1 + \frac{2}{\beta(1+\beta)} \right)$$

3 transistors current source

$$R_0 = r_{o2} = \frac{V_A}{I_{e2}}$$


$$I_{c2} = I_0$$

Ideal Current Source

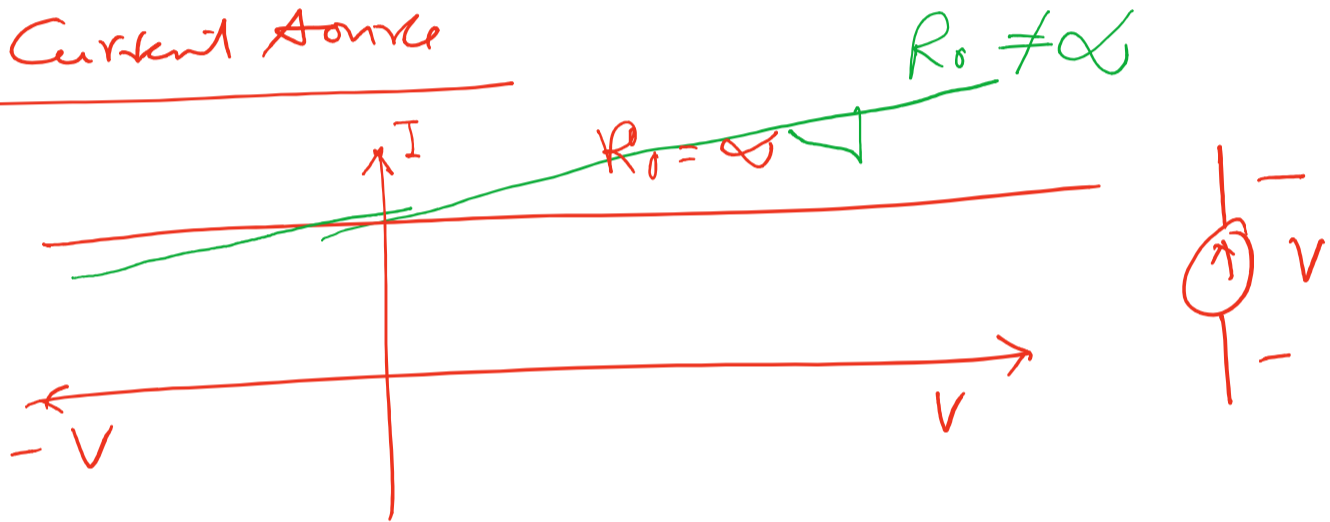

1) Wilson Current Source.

$$R_0 = \beta r_{o2}$$

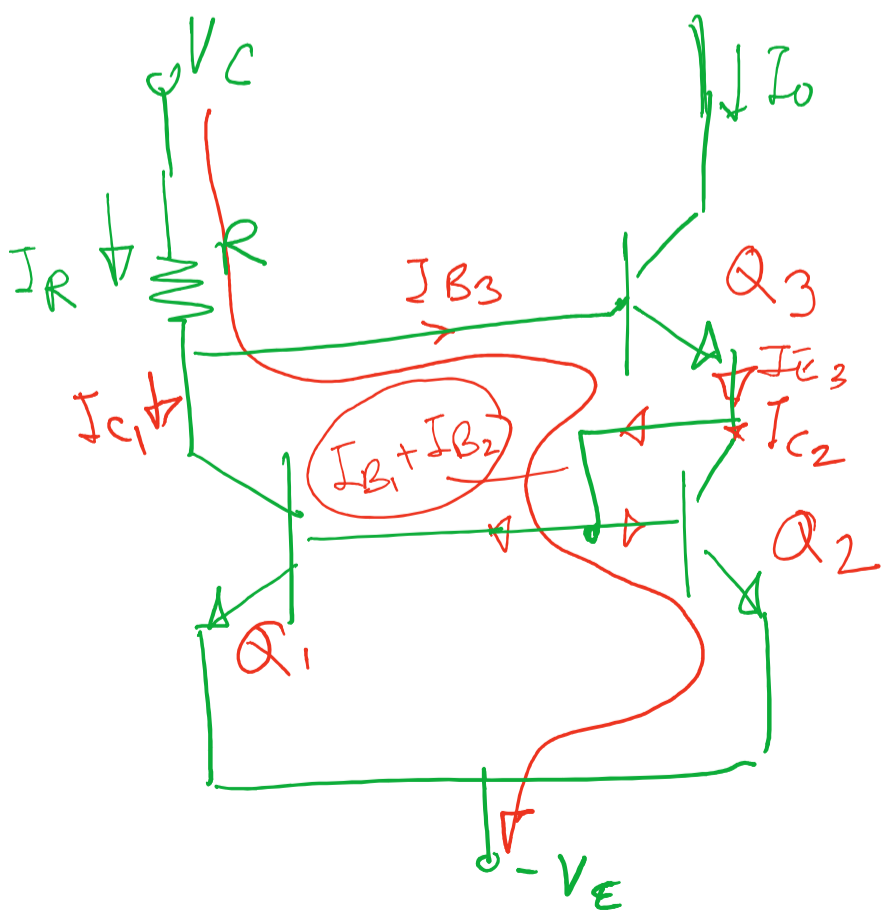

$$V_C = I_R R + V_{BE3} + V_{BE2} - V_E$$

$$R = \frac{V_C + V_E - V_{BE3} - V_{BE2}}{I_R}$$

$$I_0 = 100 \mu A$$

$$\beta = 100$$

$$V_{BE} = 0.7 V$$

$$I_R = I_{C1} + I_{B3}$$

$$V_{BE1} = V_{BE2}$$

$$I_{B1} = I_{B2}$$

$$I_{C1} = I_{C2}$$

$$I_{E3} = (1 + \beta) I_{B3}$$

$$I_{E3} = I_{B1} + I_{B2} + I_{C2}$$

$$= 2I_{B2} + I_{C2} = \frac{2I_{C2}}{\beta} + I_{C2}$$

$$= I_{C2} \left[1 + \frac{2}{\beta} \right] = (1 + \beta) I_{B3}$$

$$\therefore I_{C2} = \frac{(1 + \beta)}{\left(1 + \frac{2}{\beta}\right)} I_{B3} = \frac{(1 + \beta)\beta}{(\beta + 2)} I_{B3}$$

$$I_R = I_{C1} + I_{B3}$$

$$= I_{C2} + I_{B3}$$

$$= \frac{(1 + \beta)\beta}{(\beta + 2)} I_{B3} + I_{B3}$$

$$= \left(\frac{(1 + \beta)\beta}{(\beta + 2)} + 1 \right) I_{B3}$$

$$= \left[\frac{(1 + \beta)\beta}{(\beta + 2)} + 1 \right] \frac{I_{C3}}{\beta}$$

$$I_R = \left(\frac{101 \times 100}{102} + 1 \right) \frac{100 \mu}{100}$$


$$= 100 \mu A$$

$$R = \frac{5 + 5 - 1.4}{100 \text{ mA}}$$

$$V_C = V_E = 5 \text{ V}$$

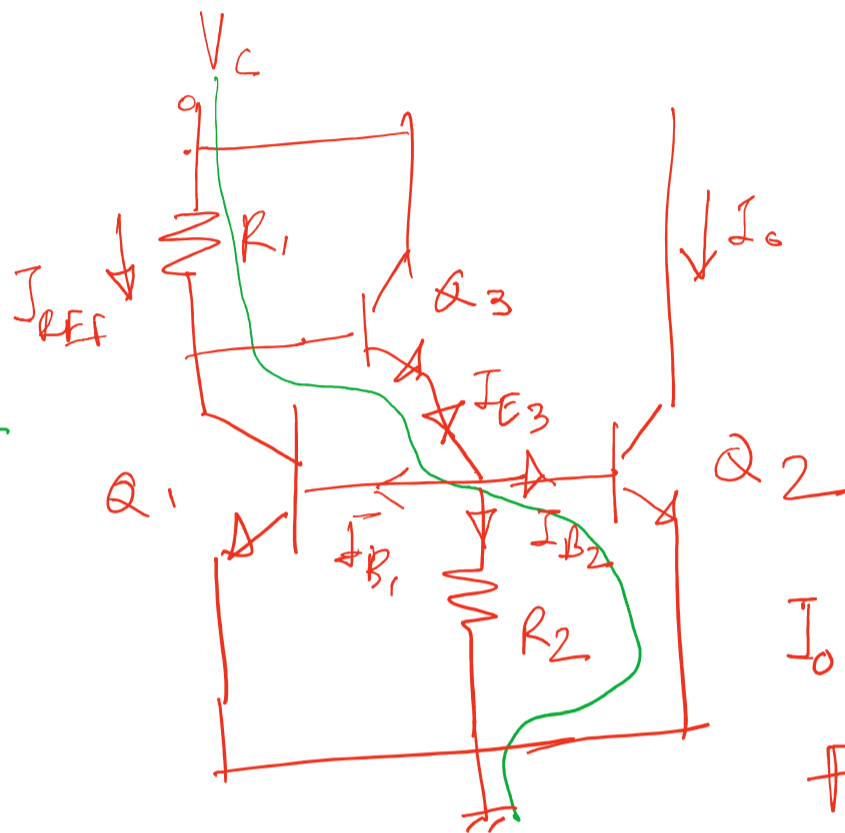10.17 Prob.

$$R_1 = \frac{V_C - V_{BE3} - V_{BE2}}{I_R}$$



$$V_C = 10 \text{ V}$$

$$\beta = 80$$

$$V_{BE} = 0.7$$

$$V_A = \infty$$

$$I_0 = 0.7 \text{ mA}$$

$$\text{For } R_2 = 10 \text{ k}\Omega$$

$$I_0 = f(I_{REF}, \beta, R_2)$$

$$I_{E3} = I_{B1} + I_{B2} + \frac{V_{BE}}{R_2}$$

$$= 2 I_{B2} + \frac{V_{BE}}{R_2} = (1 + \beta) I_{B3}$$

$$I_{B3} = \frac{2 I_{B2}}{(1 + \beta)} + \frac{V_{BE}}{R_2 (1 + \beta)}$$

$$I_R = I_{C1} + I_{B3}$$

$$= I_{C2} + \frac{2 I_{B2}}{1 + \beta} + \frac{V_{BE}}{R_2 (1 + \beta)}$$

$$= I_{C2} + \frac{2 I_{C2}}{(1 + \beta) \beta} + \frac{V_{BE}}{R_2 (1 + \beta)}$$

$$= \left[1 + \frac{2}{\beta (1 + \beta)} \right] I_{C2} + \frac{V_{BE}}{R_2 (1 + \beta)}$$

$$= \left[1 + \frac{1}{\beta(1+\beta)} \right] I_{C2} \quad R_2(1+\beta)$$


Wilder Current Source.

* Low Design Resistance.

* high output resistance

$$R_o = r_{o2} \left(1 + g_{m2} R_E' \right)$$

$$R_E' = R_E \parallel r_{\pi 2}$$

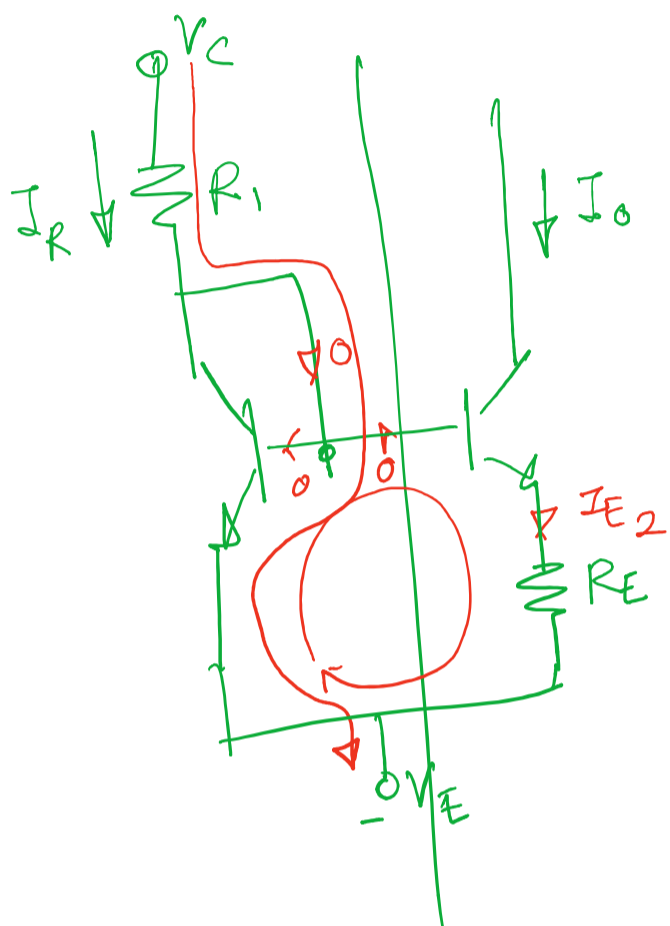

Base current is negligible

$$V_{BE1} \neq V_{BE2}$$

$$V_{BE1} = V_{BE2} + I_{E2} R_E$$

$$I_{C2} = I_{E2} = I_o$$

Given

I_R
I_o
V_{BE}

$$\therefore V_{BE1} = V_{BE2} + I_o R_E \quad \text{--- (1)}$$

$$R_1 = \frac{V_c + V_E - V_{BE1}}{I_R}$$

$$I_c = I_s \left(e^{V_{BE}/V_T} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$

$$V_A = \infty$$

$$I_c = I_s \left(e^{V_{BE}/V_T} - 1 \right)$$

$$\approx I_s e^{V_{BE}/V_T}$$

$$I_R \quad I_c \quad e^{V_{BE1}/V_T} \quad \cdot \frac{V_{BE1} - V_{BE2}}{V_T}$$

$$\frac{I_R}{I_0} = \frac{I_S e^{-V_{BE1}/V_T}}{I_S e^{-V_{BE2}/V_T}} = e^{-\frac{V_{BE1} - V_{BE2}}{V_T}}$$

$$\ln \frac{I_R}{I_0} = \ln e^{-\frac{V_{BE1} - V_{BE2}}{V_T}}$$

$$\ln \frac{I_R}{I_0} = -\frac{V_{BE1} - V_{BE2}}{V_T}$$

$$V_{BE1} - V_{BE2} = V_T \ln \frac{I_R}{I_0}$$

$$V_{BE1} - V_{BE2} = I_0 R_E$$

$$I_0 R_E = V_T \ln \frac{I_R}{I_0}$$

$$I_{RFF} = 0.5 \text{ mA}$$

$$I_0 = 50 \mu\text{A}$$

D 10.29

$$R_E = \frac{V_C + V_E - V_{BE1}}{I_R}$$

$$V_C = 5 \text{ V}$$

$$V_E = 5$$

$$= \frac{5 + 5 - 0.7}{0.5 \text{ mA}} = 18.6 \text{ k}\Omega$$

=

$$R_E = V_T \ln \frac{I_R}{I_0} = 0.026 \times \ln \frac{0.5 \text{ mA}}{50 \mu\text{A}}$$

$V_T = \frac{kT}{q}$

k ← Boltzmann const

T ← Temp in Kelvin
 $273 + (27) = 300\text{K}$

q ← Charge in C.
 $1.6 \times 10^{-19} \text{ C}$

0.0258