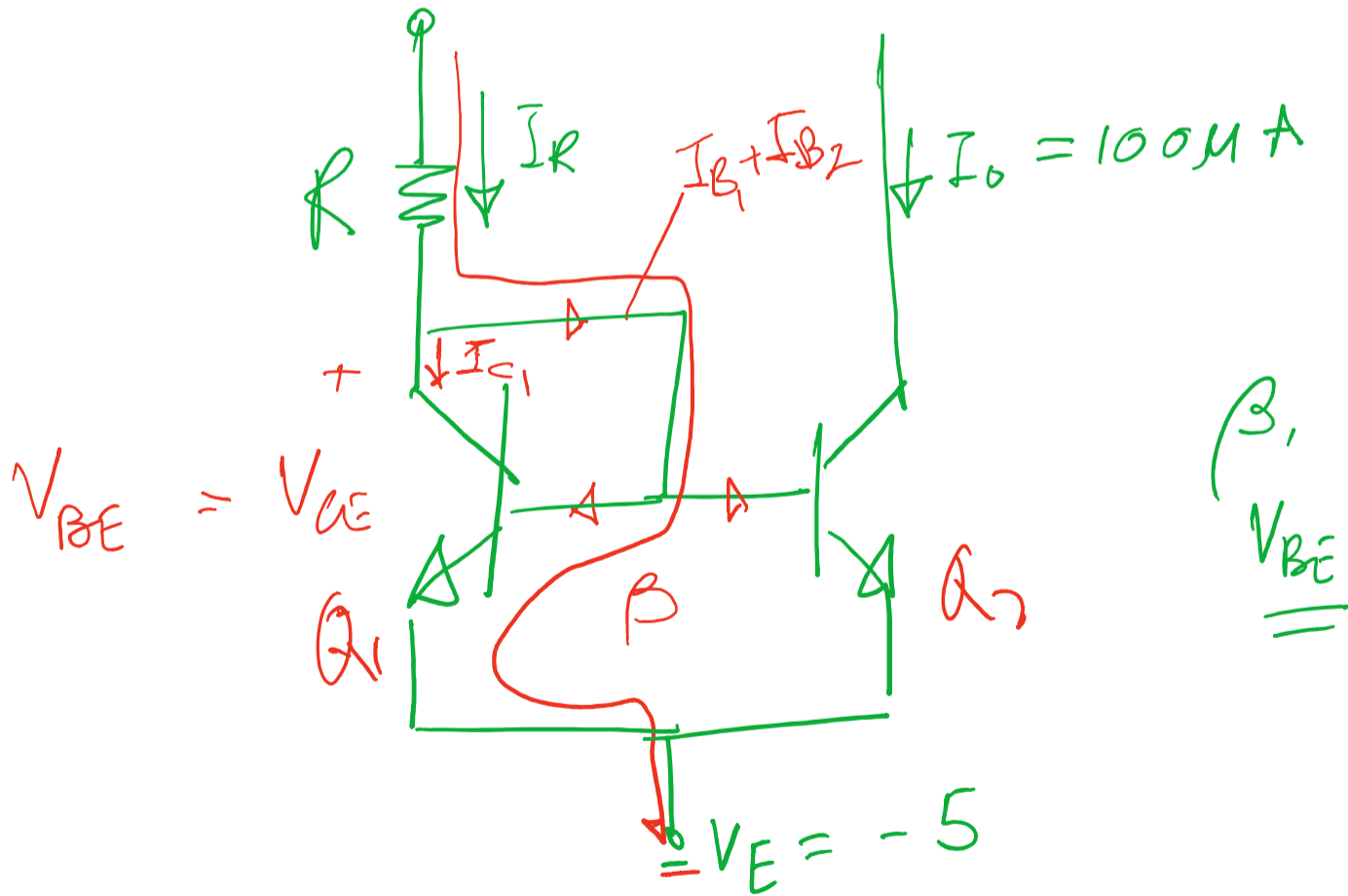


$$A_{v_A} = - \frac{\beta R_L'}{r_{\pi} + (1+\beta) R_E}$$

$$V_C = 5$$




$$V_{BE} = V_{CE}$$

$$\beta, \underline{V_{BE}}$$

$$V_C = I_R R + V_{BE} - V_E$$
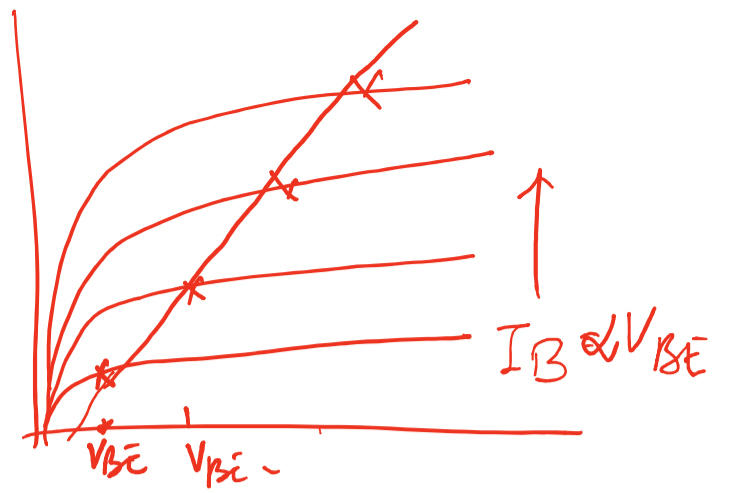
$$\therefore R = \frac{V_C + V_E - V_{BE}}{I_R}$$



$$V_{BE1} = V_{BE2}$$

$$I_{B1} = I_{B2}$$

$$I_{C1} = I_{C2} = \beta I_B$$


$$\begin{aligned} I_R &= I_{C1} + I_{B1} + I_{B2} = I_{C1} + 2I_{B1} \\ &= I_{C2} + 2I_{B2} \\ &= I_{C2} + \frac{2I_{C2}}{\beta} \end{aligned}$$

$$I_R = I_{C2} \left( 1 + \frac{2}{\beta} \right) = I_B \left( 1 + \frac{2}{\beta} \right)$$


$$\beta = 100, \quad V_{BE} = 0.7$$

$$I_R = 100 \mu \left( 1 + \frac{2}{100} \right) = 102 \mu A$$
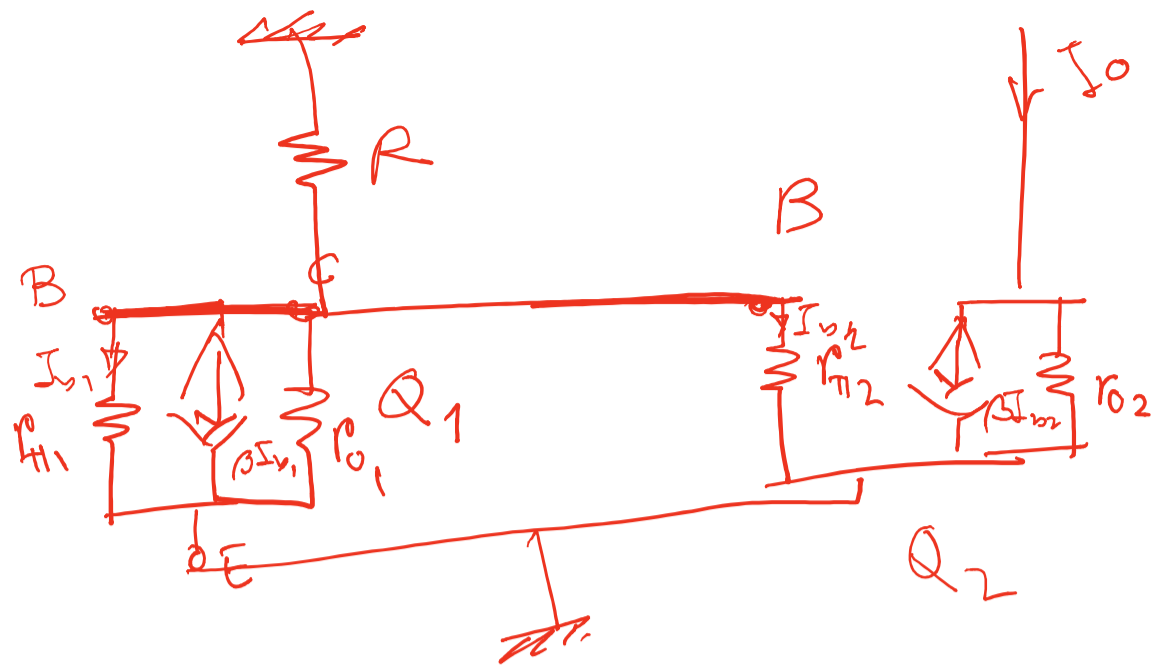
$$R = \frac{5 + 5 - 0.7}{102 \mu A} = 91.17 \text{ k}\Omega$$



$$R_o = r_{o2} = \frac{V_A}{I_o}$$

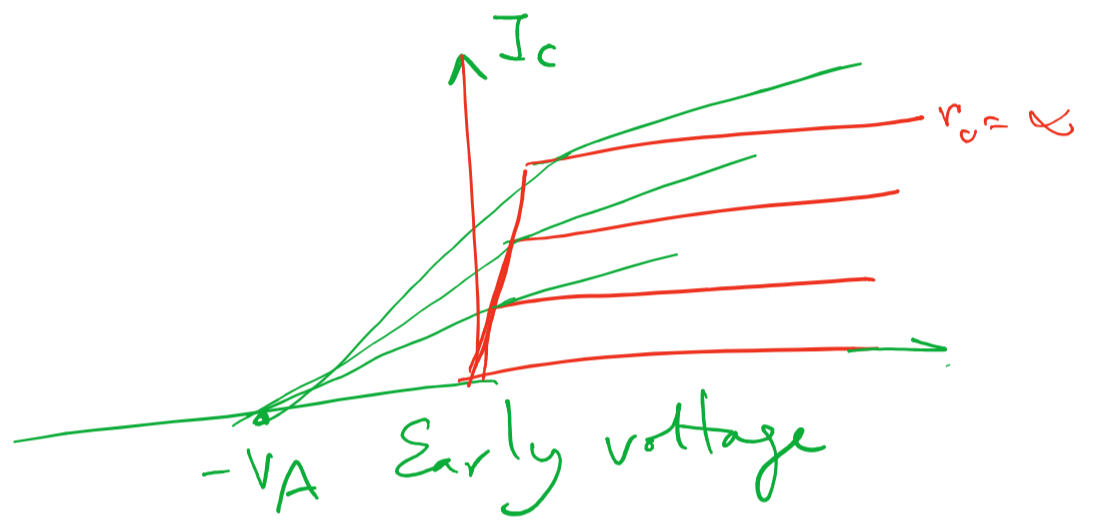


$$I_c = I_s \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) \left( 1 + \frac{V_{CE}}{V_A} \right)$$

$$\frac{I_{c1}}{I_{c2}} = \frac{\left( 1 + \frac{V_{CE1}}{V_A} \right)}{\left( 1 + \frac{V_{CE2}}{V_A} \right)}$$

$$= \frac{1 + \frac{V_{BE}}{V_A}}{\left( 1 + \frac{V_{CE2}}{V_A} \right)}$$

# MODIFIED TRANSISTOR BIASING CIRCUIT

3-transistors.

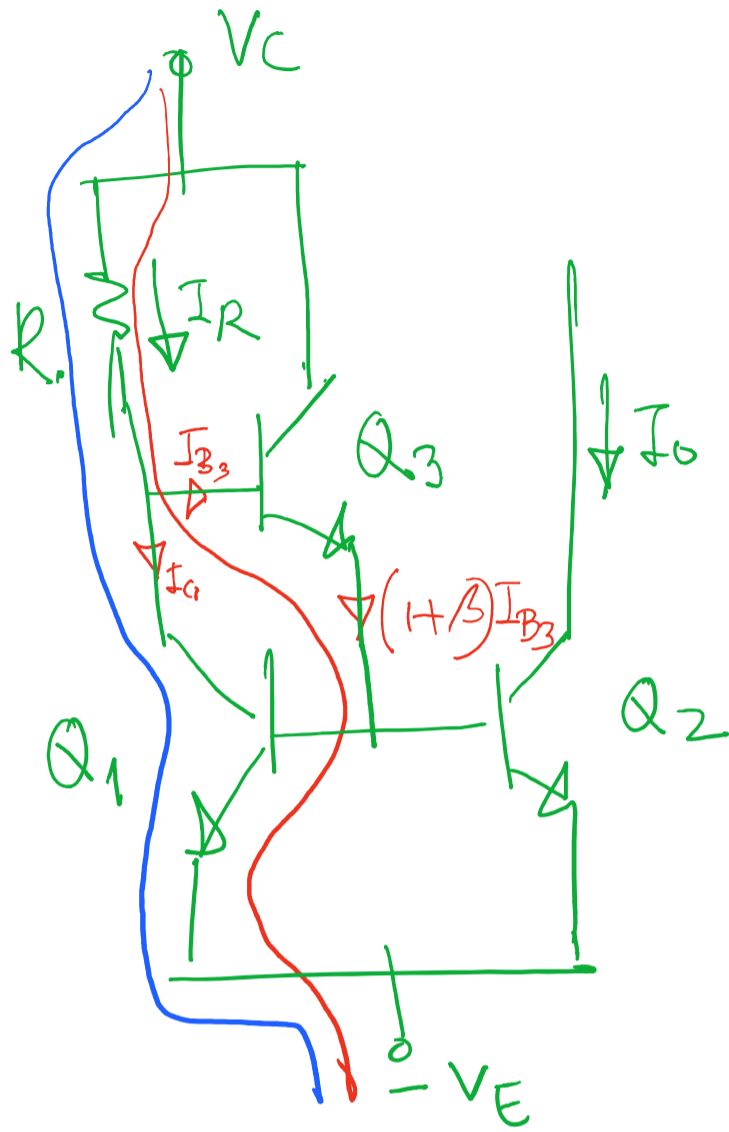

$$R = \frac{V_C + V_E - V_{BE3} - V_{BE1}}{I_R}$$

$$= \frac{V_C + V_E - 2V_{BE}}{I_R}$$

$$I_R = I_{C1} + I_{B3}$$

$$I_{E3} = (1 + \beta) I_{B3}$$

$$I_{E3} = I_{B1} + I_{B2} = 2I_{B1} = 2I_{B2}$$

$$I_R = I_{C1} + I_{B3}$$

$$= I_{C2} + \frac{I_{E3}}{(1 + \beta)}$$

$$= I_{C2} + \frac{2I_{B2}}{(1 + \beta)}$$

$$= I_{C2} + \frac{2I_{C2}}{\beta(1 + \beta)}$$

$$= I_{c2} \left[ 1 + \frac{2}{\beta(1+\beta)} \right]$$

$$I_R = I_0 \left[ 1 + \frac{2}{\beta(1+\beta)} \right]$$

$$= 100\mu \left[ 1 + \frac{2}{100 \times 101} \right] = 100\mu A$$

