

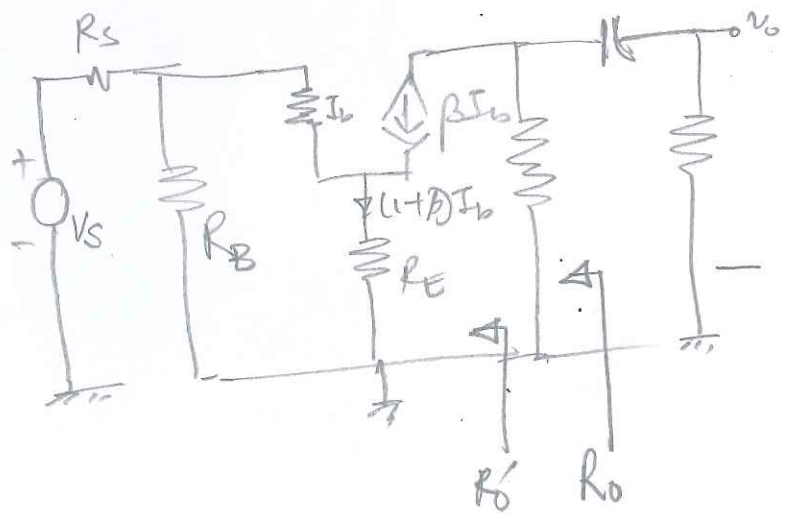


CE

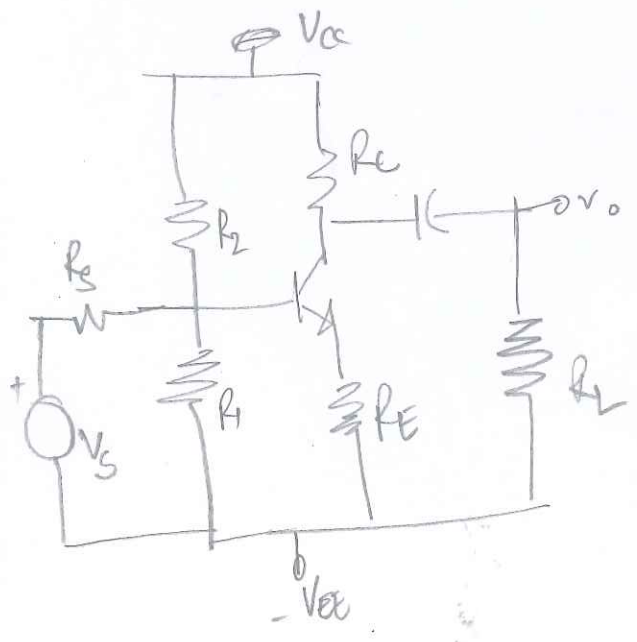

$R_o = ?$

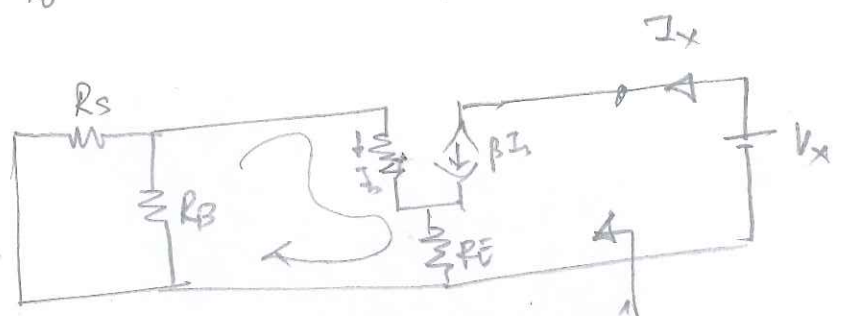

$$I_x = \beta I_B$$




$$R_o = \frac{V_x}{I_x} = \infty$$

$$(R_S \parallel R_B) I_B + r_{\pi} I_B + (1 + \beta) I_B R_E = 0 \quad \therefore I_B = 0$$

$$\therefore R_o = R_o' \parallel R_E = R_C$$

$$\therefore \tau_c = (R_C + r_{\pi}) C_C$$

CS

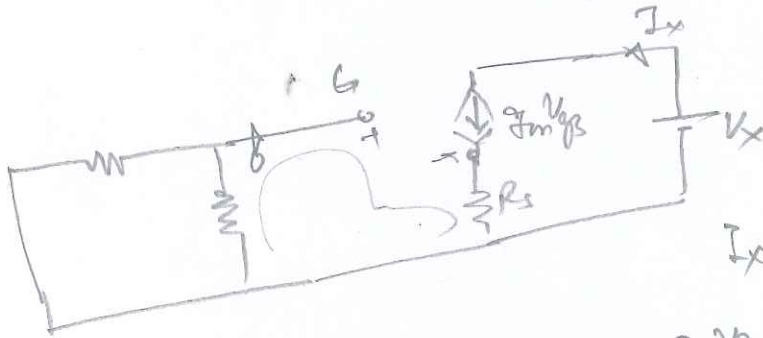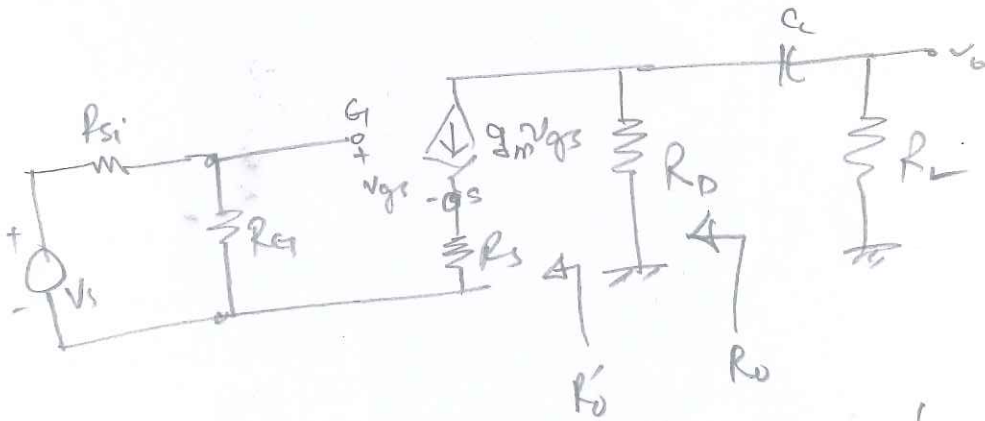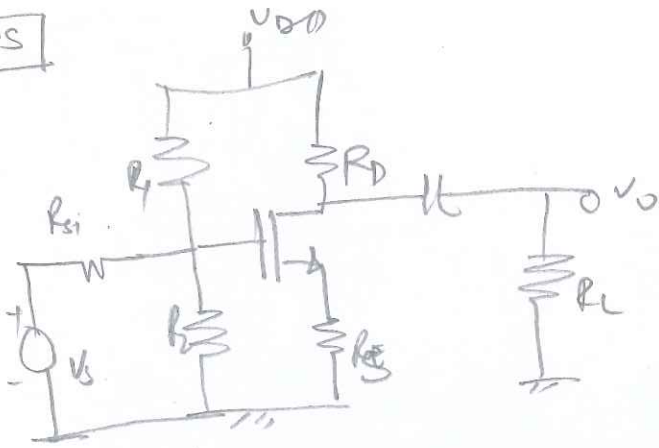

$$R_o' = \frac{v_x}{I_x}$$

$$I_x = g_m v_{gs}$$

$$(R_{si} \parallel R_1 \parallel R_2) v_{gs} + v_{gs} + g_m v_{gs} R_S = 0$$



$$\therefore v_{gs} = 0$$

$$\therefore I_x = 0$$



$$\therefore R_o' = \frac{v_x}{I_x} = \frac{v_x}{0} = \infty$$

$$R_o = R_o' \parallel R_D = R_D$$

$$\tau = (R_D + R_L) C_c \rightarrow$$

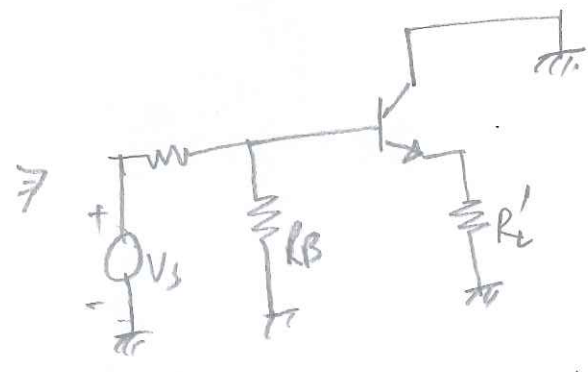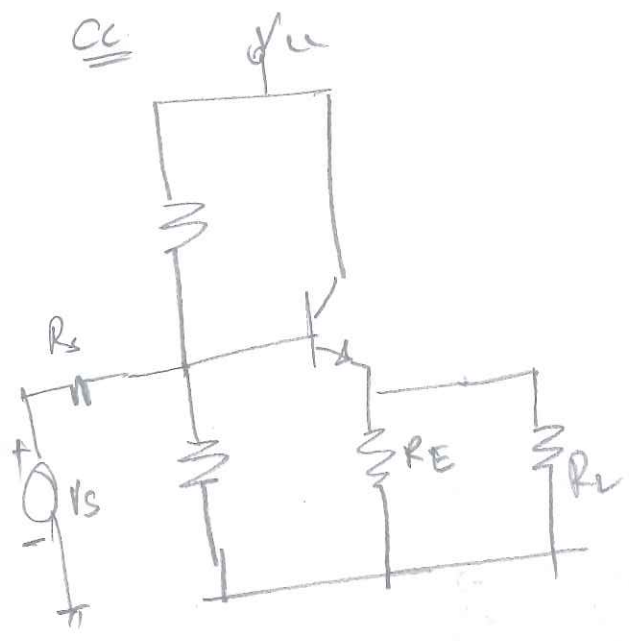

$$R'_L = R_E \parallel R_L$$

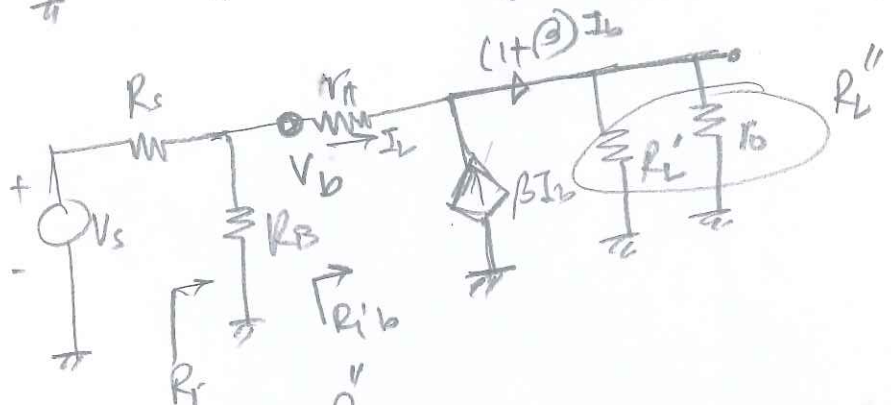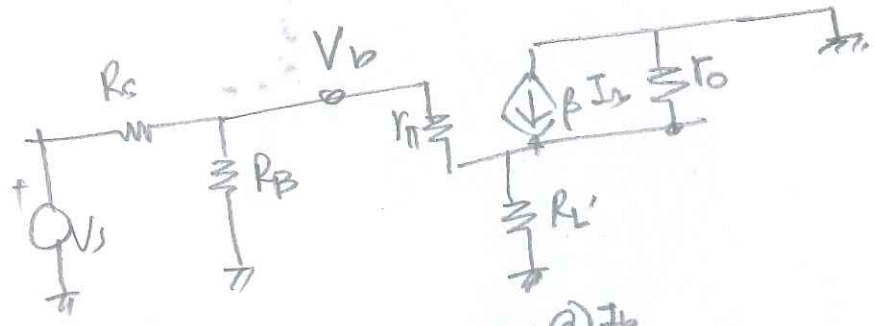

$$V_o = (1 + \beta) I_b R''_L$$

$$V_b = r_{\pi} I_b + (1 + \beta) I_b R'_L$$

$$A_{VA} = \frac{V_o}{V_b} = \frac{(1 + \beta) R''_L}{r_{\pi} + (1 + \beta) R'_L}$$


Less than 1.

$$R_{ib} = \frac{V_b}{I_b} = r_{\pi} + (1 + \beta) R'_L$$

$$A_v = A_{VA} \cdot \frac{R_i}{R_i + R_s}$$


$$R_i = R_B \parallel R_{ib}$$

Input Coupling Cap.

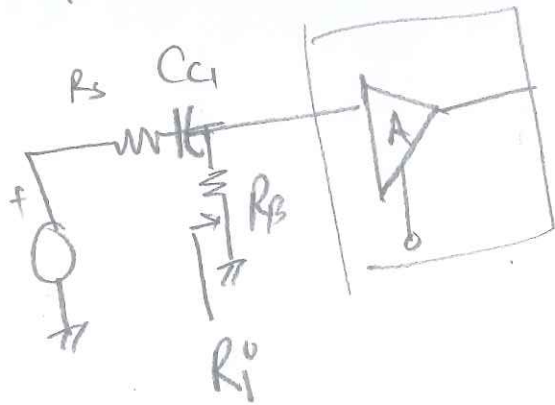


$$\tau = (R_s + R_i) C_{c1}$$

Output Coupling Cap.

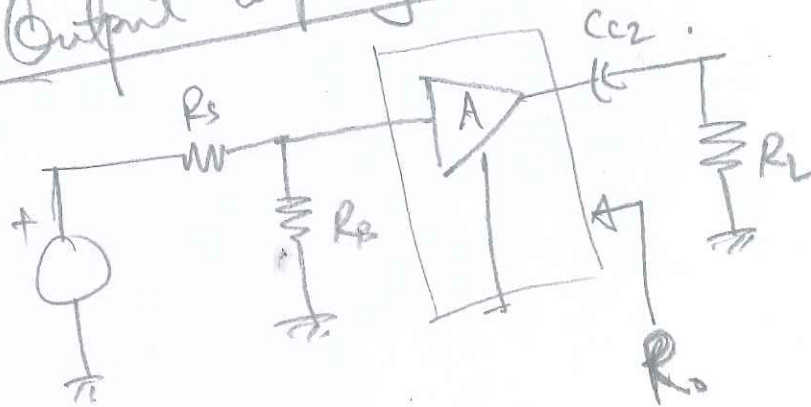


$$\therefore \tau = (R_o + R_L) C_{c2}$$

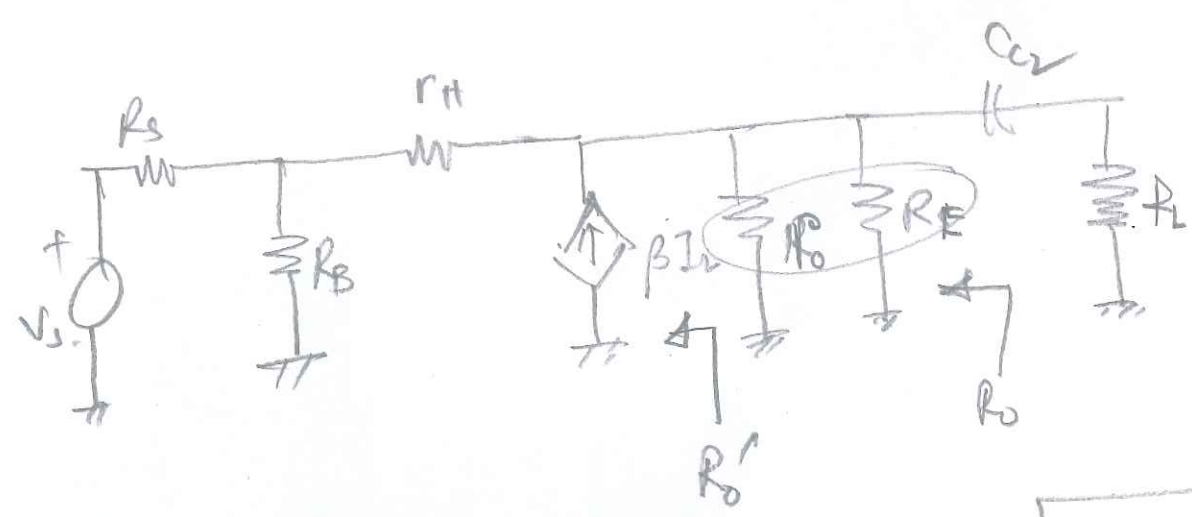


$R'_0 = ?$

$R_0 = R'_0 \parallel r_o \parallel R_E$

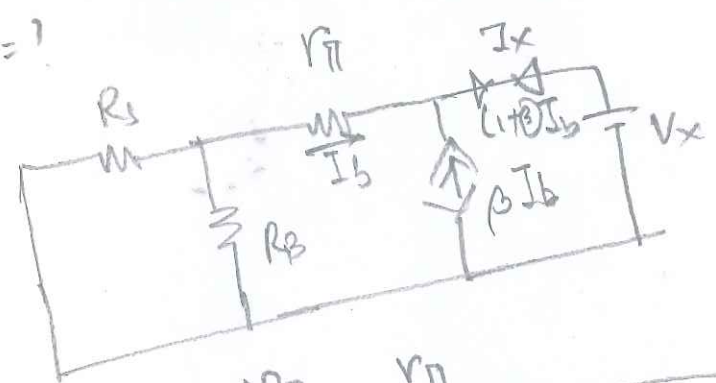

$I_x = -(1 + \beta) I_b$

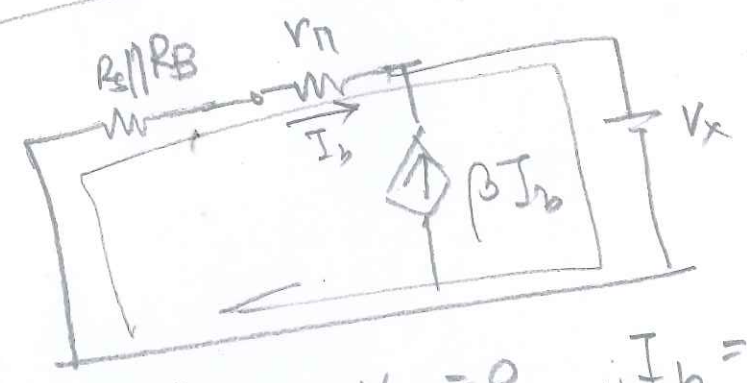

$(R_s \parallel R_B + r_\pi) I_b + V_x = 0 \quad \therefore I_b = -\frac{V_x}{(R_s \parallel R_B + r_\pi)}$

$\therefore I_x = \frac{V_x (1 + \beta)}{(R_s \parallel R_B + r_\pi)}$

$\therefore R'_0 = \frac{V_x}{I_x} = \frac{(R_s \parallel R_B + r_\pi)}{(1 + \beta)}$


$\therefore R_0 = \frac{R_s \parallel R_B + r_\pi}{(1 + \beta)} \parallel r_o \parallel R_E$

$\tau = (R_s + R_L) C_{C2}$





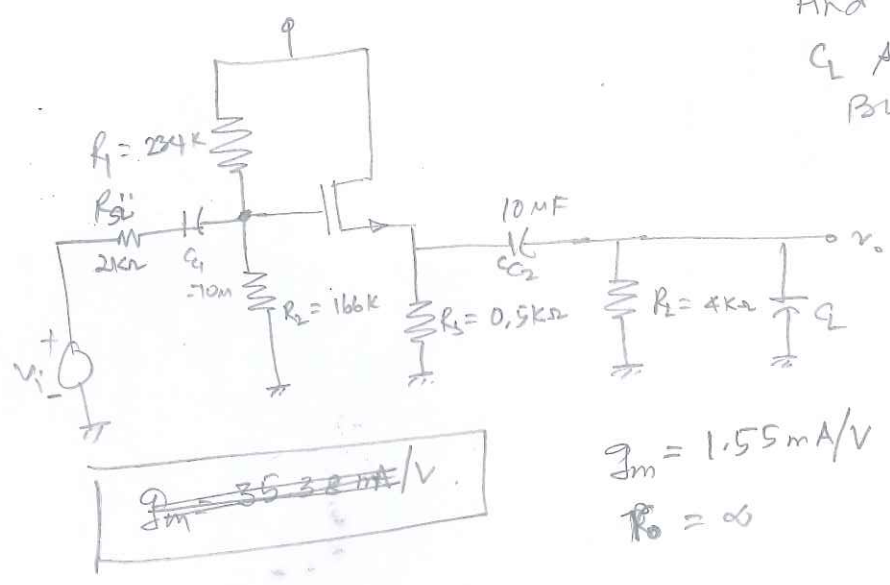
7.39

①

Find the max^m value of C_L such that the BW is at least BW = 5MHz.



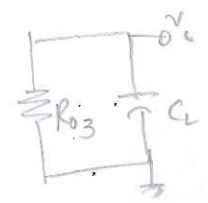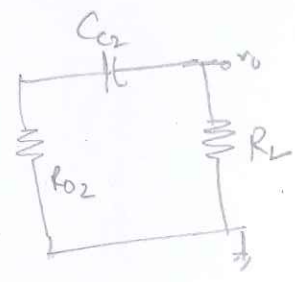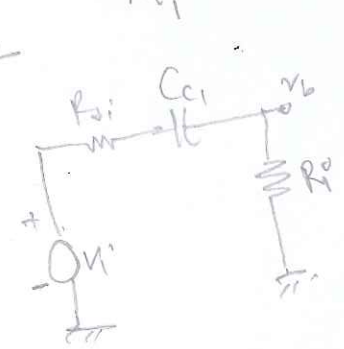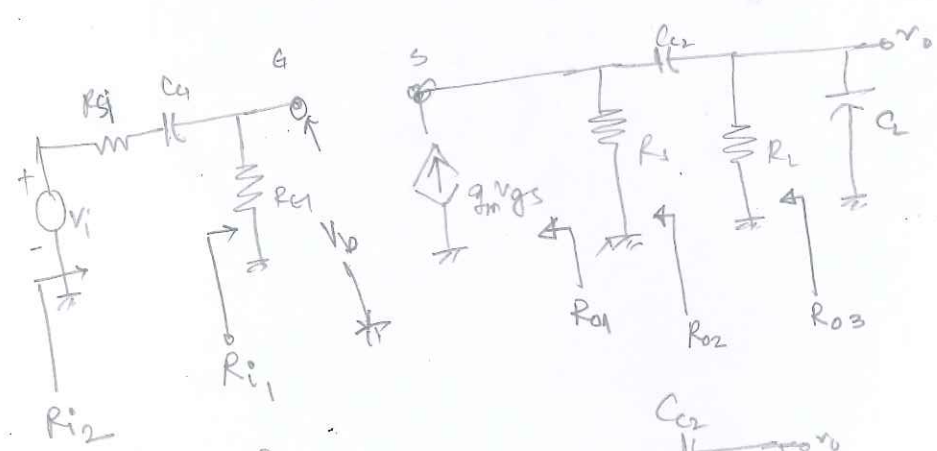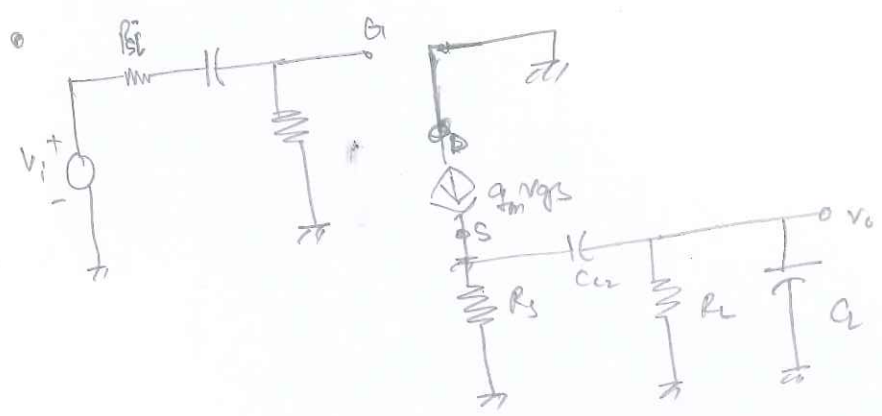$g_m = 1.55 \text{ mA/V}$ \leftarrow
 $R_o = \infty$



* Midband Voltage gain

$$v_o = g_m v_{gs} R_L'$$

$$R_L' = R_s \parallel R_L$$

$$v_b = v_{gs} + g_m v_{gs} R_L'$$

$$A_{vA} = \frac{v_o}{v_b}$$

$$A_{vA} = \frac{g_m R_L'}{(1 + g_m R_L')}$$

$$R_{i1} = R_{C1} = R_i$$

$$A_v = A_{vA} \times \frac{R_i}{R_{s1} + R_i}$$

$$R_{i1} = R_a$$

$$f_{L_{C1}} = R_{s1} \frac{1}{2\pi \tau_{C1}}$$

$$\tau_{C1} = (R_{s1} \parallel R_i) C_{C1}$$


$$f_{L_{C2}} = \frac{1}{2\pi \tau_{C2}}$$

$$\tau_{C2} = (R_{o2} + R_L) C_{C2}$$

$$f_{H_{C2}} = \frac{1}{2\pi \tau_{C2}}$$

$$\tau_{C2} = R_{o3} C_L$$

$R_{o1} = ?$

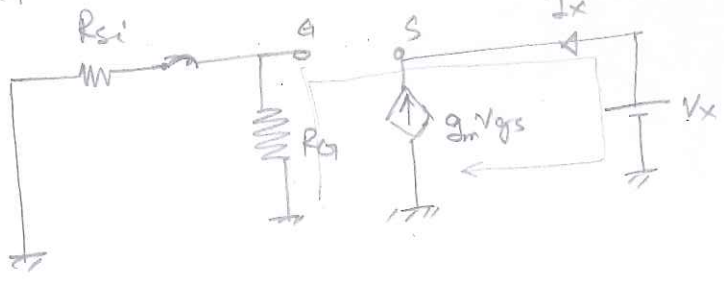

$$I_x = -g_m v_{gs}$$

$$R_s \times 0 + v_{gs} + V_x = 0$$

$$\therefore v_{gs} = -V_x$$

$$\therefore I_x = g_m V_x$$

$$\therefore R_{o1} = \frac{V_x}{I_x} = \frac{1}{g_m}$$

$$R_{o1} = \frac{1}{g_m}$$

$$R_{o2} = R_{o1} \parallel R_s$$

$$R_{o3} = R_{o1} \parallel R_s \parallel R_L$$

$$Q_L = \frac{\tau_{C2}}{R_{o3}} \quad \tau_{C2} = \frac{1}{2\pi f_{H_{C2}}}$$

P. 746

