

$$S_e = S_i - S_{fb}$$

$$S_i = S_e + S_{fb}$$

$$A_f = \frac{S_o}{S_i}$$

~~$$S_e = S_i - S_{fb} = S_i - \beta S_o$$~~

$$S_i = S_e + S_{fb} = \frac{S_o}{A} + \beta S_o = \frac{S_o}{A} [1 + \beta A]$$

$$A_f = \frac{S_o}{S_i} = \frac{A}{1 + \beta A} = \frac{1}{\frac{1}{\beta}}$$



β

$$T = \beta A \equiv \text{loop gain}$$

$$A_f = \frac{A}{1+T}$$

$A = 10^5$ gain variation 10%

$$\frac{A_0 - A_1}{A_0} \times 100 = \frac{\Delta A}{A_0} \times 100$$

$$= \frac{\Delta A}{A_0} \times 100 = 10\%$$



$$\frac{\Delta A_f}{A_f} \% \quad ?$$

$$A_f = \frac{A}{1 + \beta A}$$

$$\Delta A_f \quad | \quad - \quad \frac{A \beta}{1 + \beta A}$$

$$\frac{dA_f}{dA} = \frac{1}{1+\beta A} - \frac{A\beta}{(1+\beta A)^2}$$

$$= \frac{1+\beta A - \beta A}{(1+\beta A)^2}$$

$$= \frac{1}{(1+\beta A)^2}$$

$$\frac{dA_f}{A_f} = \frac{\frac{1}{(1+\beta A)^2} \cdot dA}{A}$$

$$= \frac{1}{(1+\beta A)} \cdot \frac{dA}{A}$$

$$\beta = 0.9$$


$$= \frac{1}{1+0.9 \times 10^5} \times 10\%$$

$$= 111.10 \times 10^{-6} \%$$

$$A_f = ?$$

$$= \frac{10^5}{1+0.9 \times 10^5} = 1.11$$
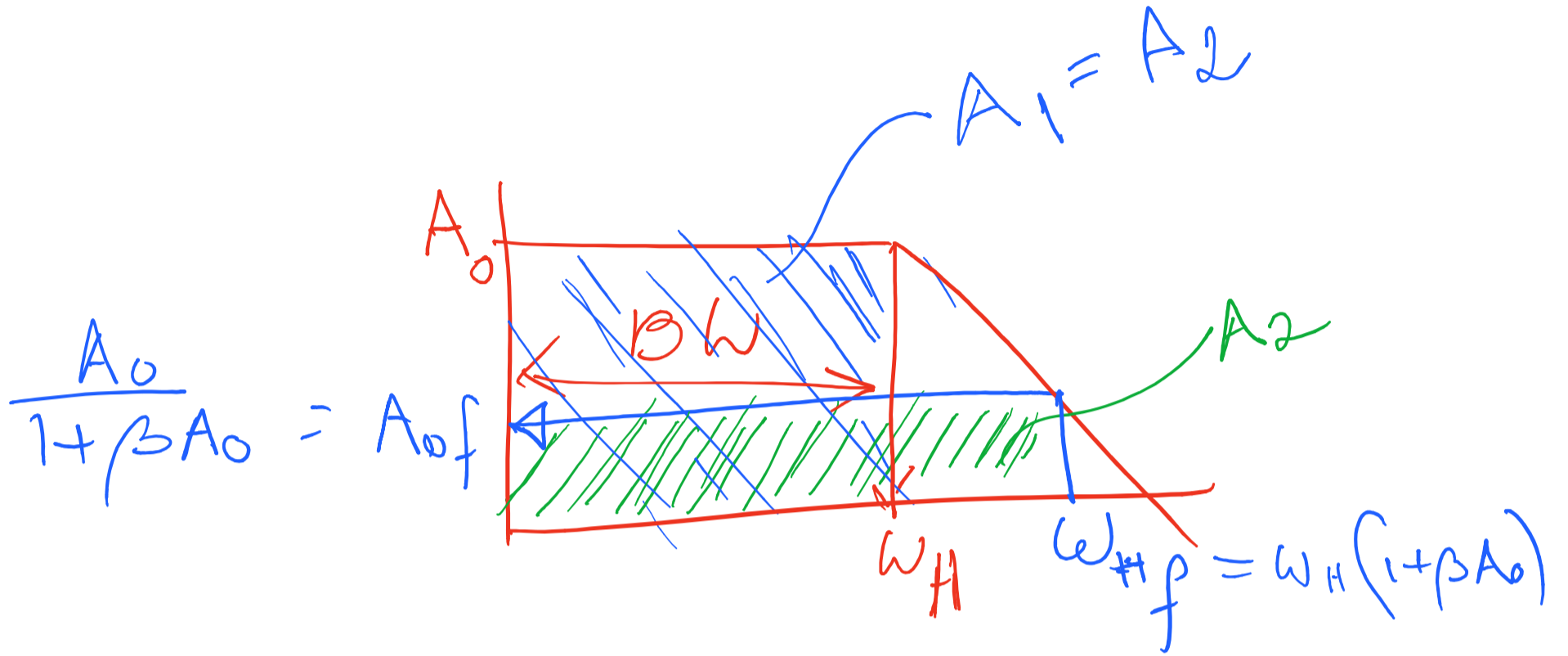
$$= \frac{10}{1 + 0.9 \times 10^5} = 1.1$$



$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_H}}$$

$$A_f(s) = \frac{A(s)}{1 + \beta A(s)}$$

$$= \frac{\frac{A_0}{1 + \frac{s}{\omega_H}}}{1 + \beta \frac{A_0}{\left(1 + \frac{s}{\omega_H}\right)}}$$

$$= \frac{A_0}{1 + \frac{s}{\omega_H} + \beta A_0}$$

$$= \frac{A_0}{(1 + \beta A_0) + \frac{s}{\omega_H}}$$

$$= \frac{A_0}{(1 + \beta A_0) \left[1 + \frac{s}{(1 + \beta A_0) \omega_H} \right]}$$

$$= \frac{A_{of}}{1 + \frac{s}{\omega_{Hf}}}$$

$$\left[\omega_{Hf} = (1 + \beta A_0) \omega_H \right]$$

$$f_{Hf} = (1 + \beta A_0) f_H$$

$$GBW \text{ / open loop} = A_0 \omega_H$$

$$GBW \text{ / closed loop} = A_{of} \omega_{Hf}$$

Gain \times Bandwidth

$$= \frac{A_0 \omega_H (1 + \beta A_0)}{1 + \beta A_0}$$

$$= A_0 \omega_H = GBW \text{ / open loop}$$

Ex 12.3

$$A_o = 10^5$$

$$A_{of} = 100$$

$$f_H = 10 \text{ Hz}$$

$$f_{Hf} = ?$$

$$(K = 1 + \beta A)$$

$$A_f = \frac{A}{1 + \beta A} = \frac{A}{K}$$

$$\therefore K = \frac{A}{A_f} = \frac{10^5}{100} = 10^3$$

$$f_{Hf} = (1 + \beta A) f_H = K \cdot f_H$$
$$= 10^3 \times 10 = \underline{\underline{10 \text{ KHz}}}$$

12.8

$$A = 10^5$$

$$f_H = 4 \text{ Hz}$$

$$A_f = 50$$

$$\therefore f_{Hf} = 5 \text{ Hz}$$

12-10

$$A_{vf} = 50, \quad f_H = 5 \text{ Hz}$$
$$BW = 20 \text{ kHz} \quad A = ?$$

$$A_{vf} \times BW = A_v \times f_H$$

$$f_{Hf} = BW = (1 + \beta) f_H = K f_H$$


$$K = \frac{f_{Hf}}{f_H} = \frac{20 \text{ K}}{5}$$

$$A_f = \frac{A}{1 + \beta A} = \frac{A}{K}$$

$$\therefore A = A_f \times K$$


Series-shunt (v_i, v_o)


Voltage-Amplifier

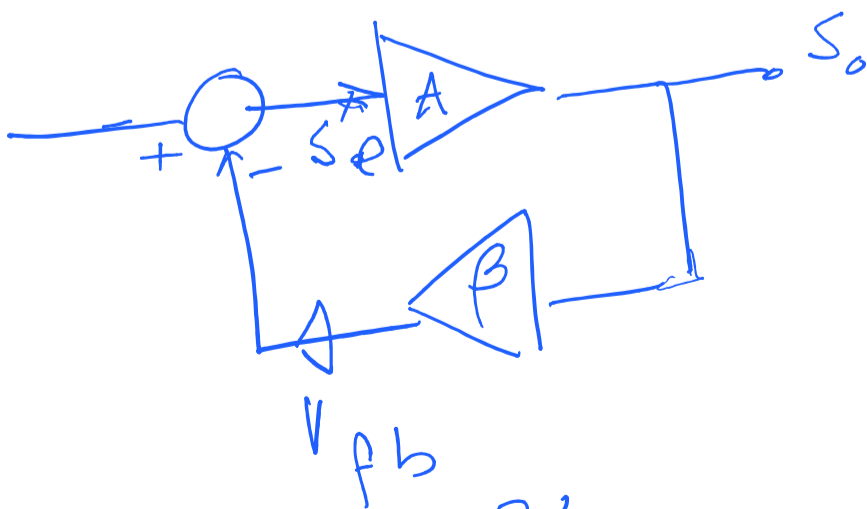

$$R_S = 0$$

$$A_v = \frac{v_o}{v_e}$$

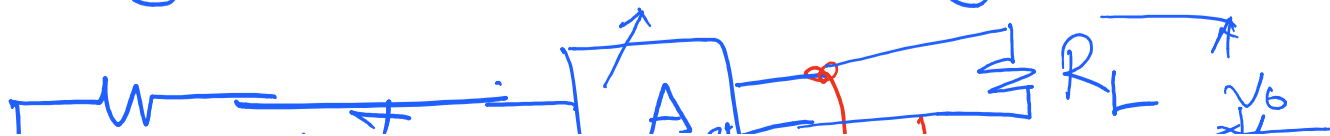

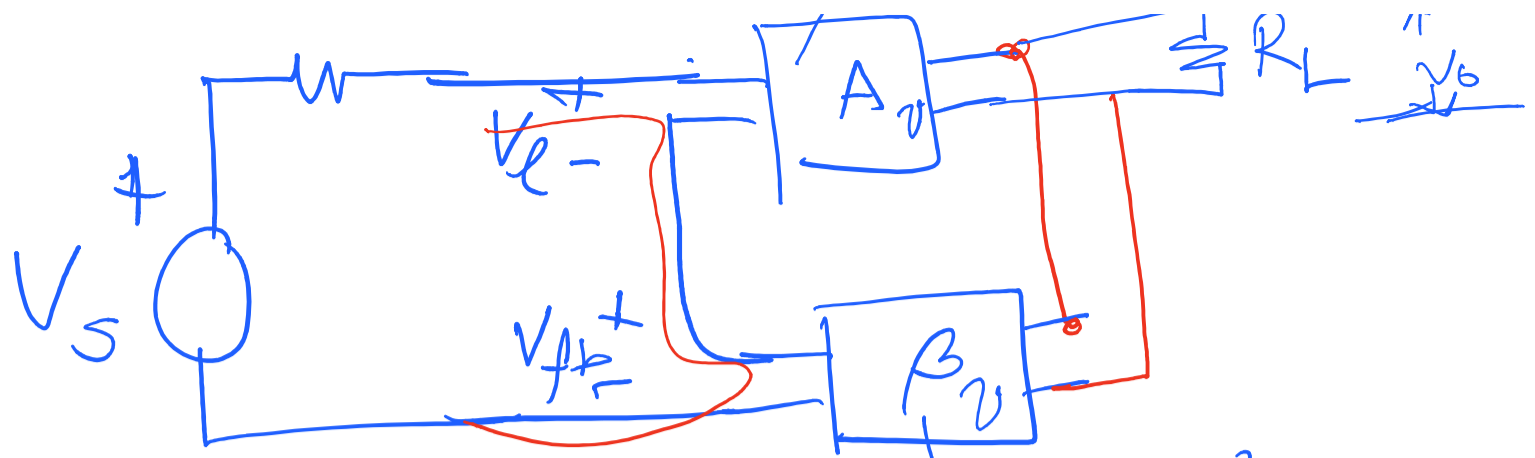


$$\beta_v = \frac{v_{fb}}{v_o}$$

Series-Series.

v_i i_o $R_s = 0$
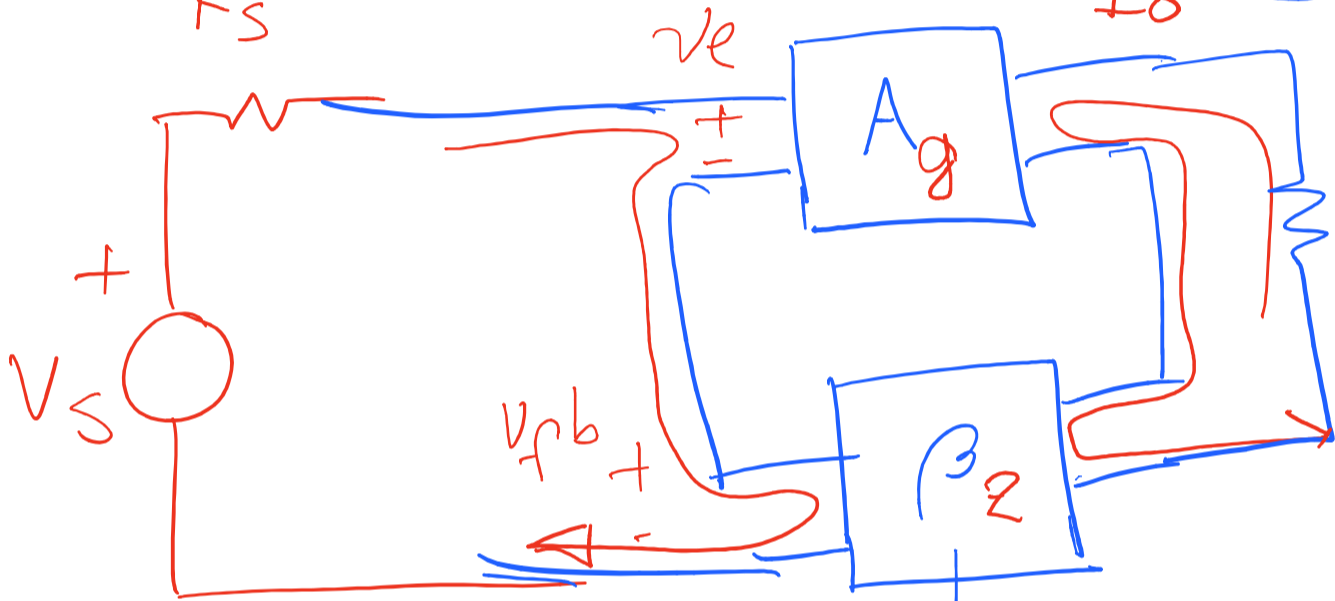
$$A_g = \frac{I_o}{v_e} \quad \text{(transconductance)}$$



$$\beta_z = \frac{v_{fb}}{I_o} \quad \text{(transimpedance)}$$

$$A_{gf} = \frac{I_o}{v_o} \quad \text{transconductance Amplifier}$$