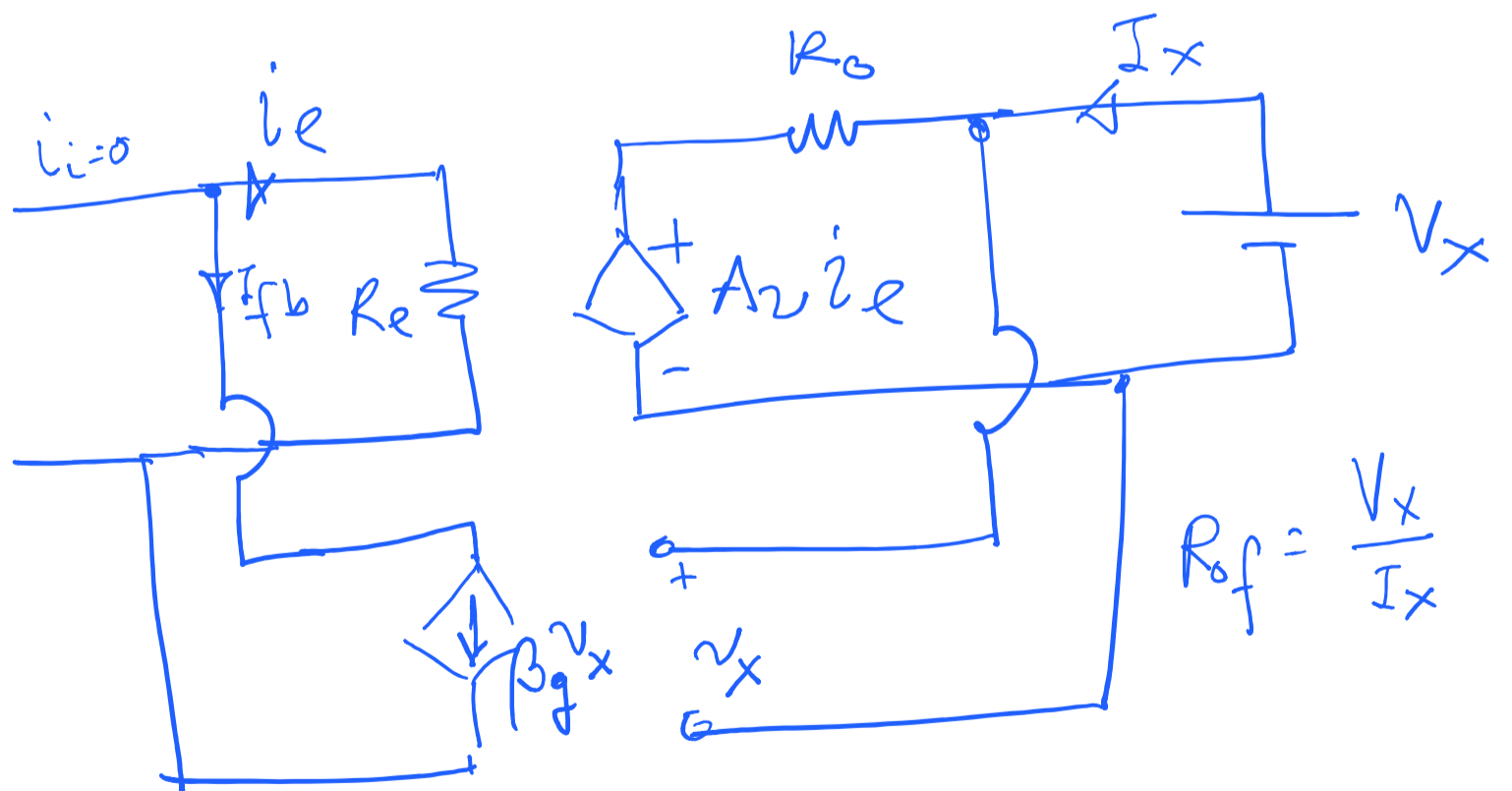


For ideal
 $R_{i\beta} = \infty$
 $R_{o\beta} = \infty$

$R_o = ?$



$$R_{of} = \frac{V_x}{I_x}$$

KVL $V_x = R_o I_x + A_z i_e$

$i_i = 0 \Rightarrow i_e + i_{fb} = 0 \Rightarrow i_e = -i_{fb}$

$$i_i = i_e + i_{fb} = 0 \Rightarrow \dots$$

$$V_x = R_o I_x - A_2 i_{fb}$$

$$= R_o I_x - A_2 \beta_2 V_x$$


$$V_x + A_2 \beta_2 V_x = R_o I_x$$

$$V_x [1 + A_2 \beta_2] = R_o I_x$$

$$R_{of} = \frac{V_x}{I_x} = \frac{R_o}{1 + A_2 \beta_2}$$

Series Series

$$A_g = \frac{i_o}{v_e}$$

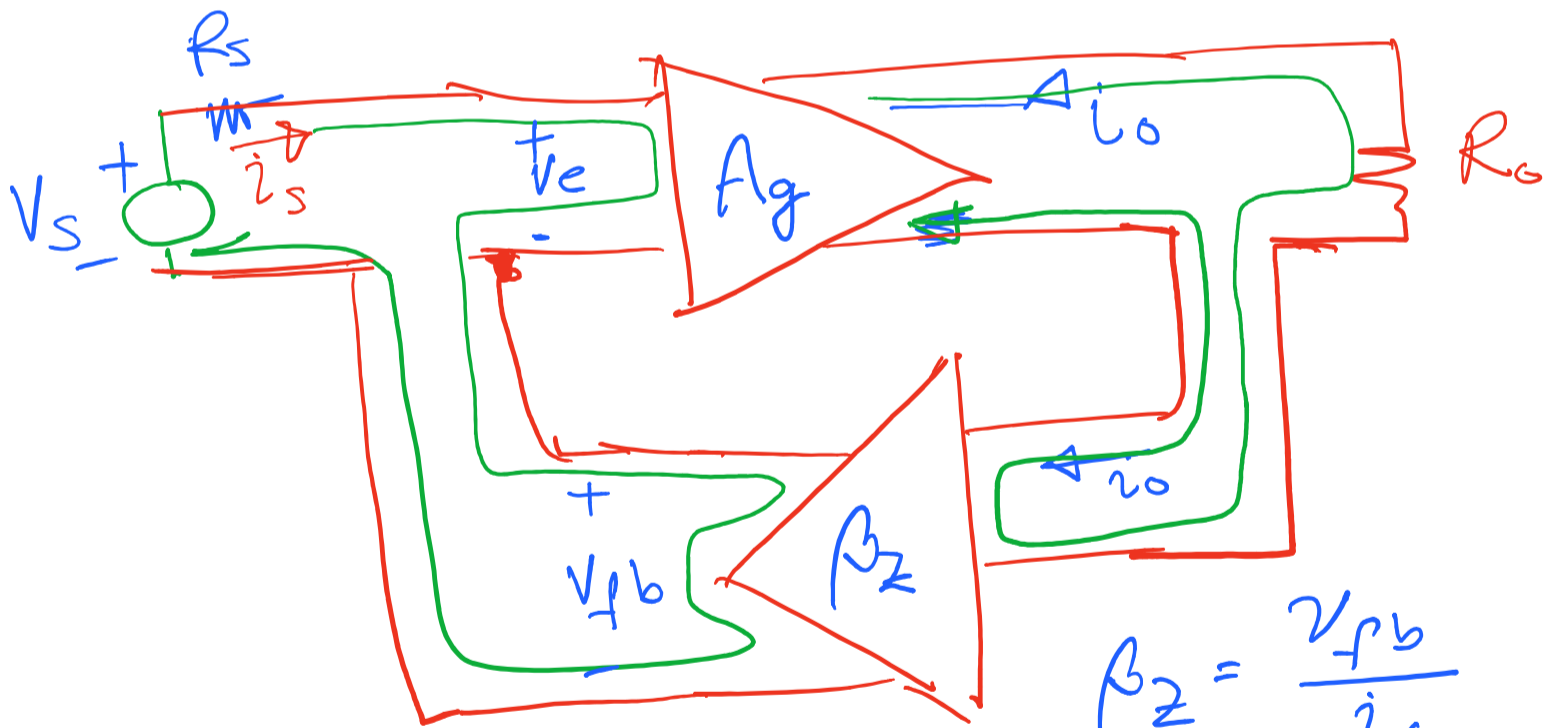

$$\beta_2 = \frac{v_{fb}}{i_o}$$

$$[if R_s = 0]$$

$A_{gf} = ? \cdot \frac{i_o}{V_s}$
 $R_{if} = ?$

$$V_s = v_e + v_{fb}$$

output parameter
(i_o)

$$V_s = \frac{i_o}{A_g} + \beta_2 i_o$$

Input parameter
(v_e)

$$V_s = v_e + v_{fb} = v_e + \beta_2 i_o$$

$$V_s = A_g i_o$$

$$= \frac{i_o}{A_g} [1 + \beta_2 A_g]$$

$$\therefore A_{gf} = \frac{i_o}{v_s} = \frac{A_g}{1 + \beta_2 A_g}$$


$$= v_e + \beta_2 i_o$$

$$= v_e + \beta_2 A_g v_e$$


$$= v_e [1 + \beta_2 A_g]$$

$$R_{if} = \frac{v_s}{i_s} = \frac{v_e [1 + \beta_2 A_g]}{i_s}$$

$$= R_i [1 + \beta_2 A_g]$$

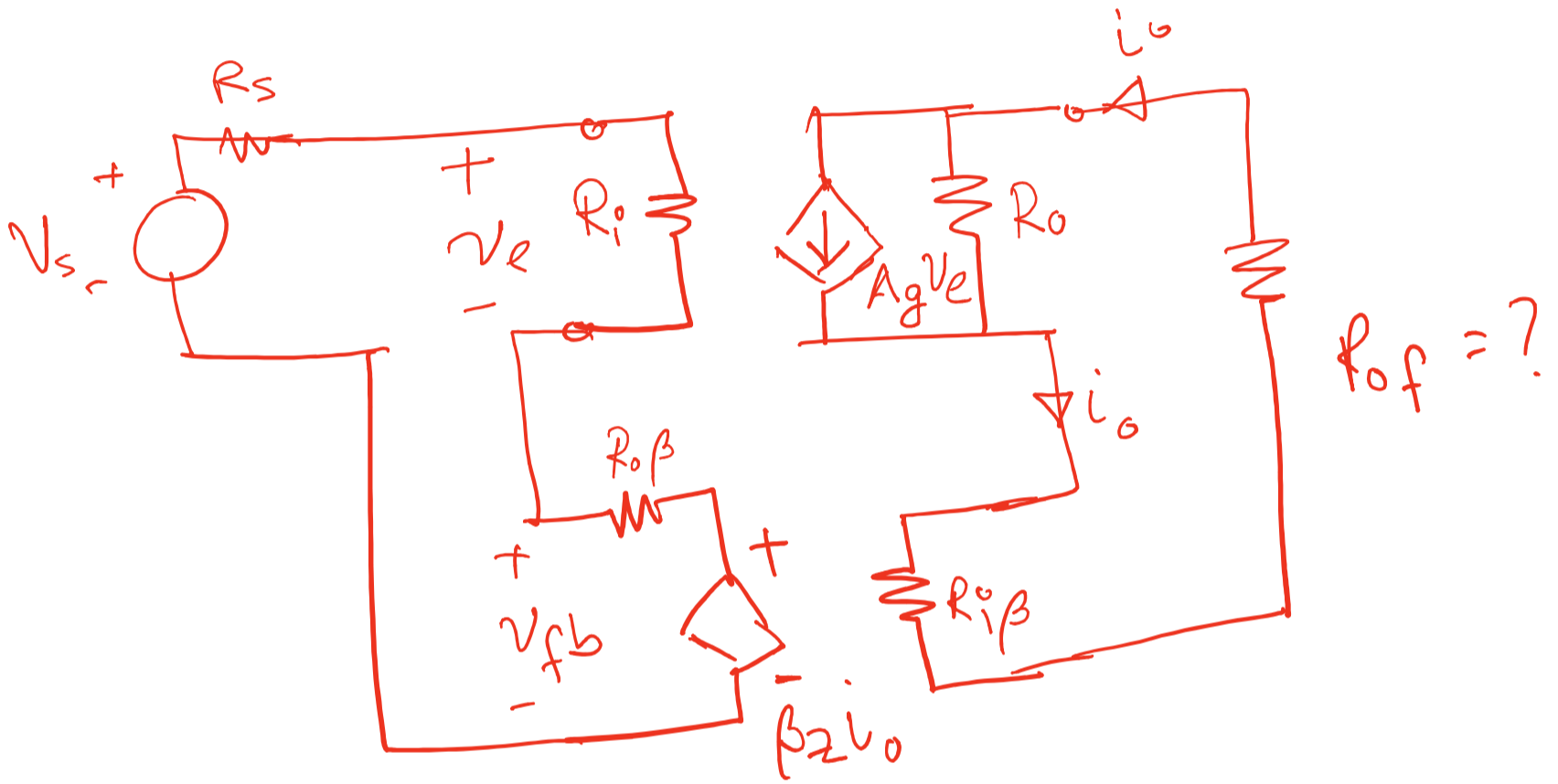

$$V_s = 0$$

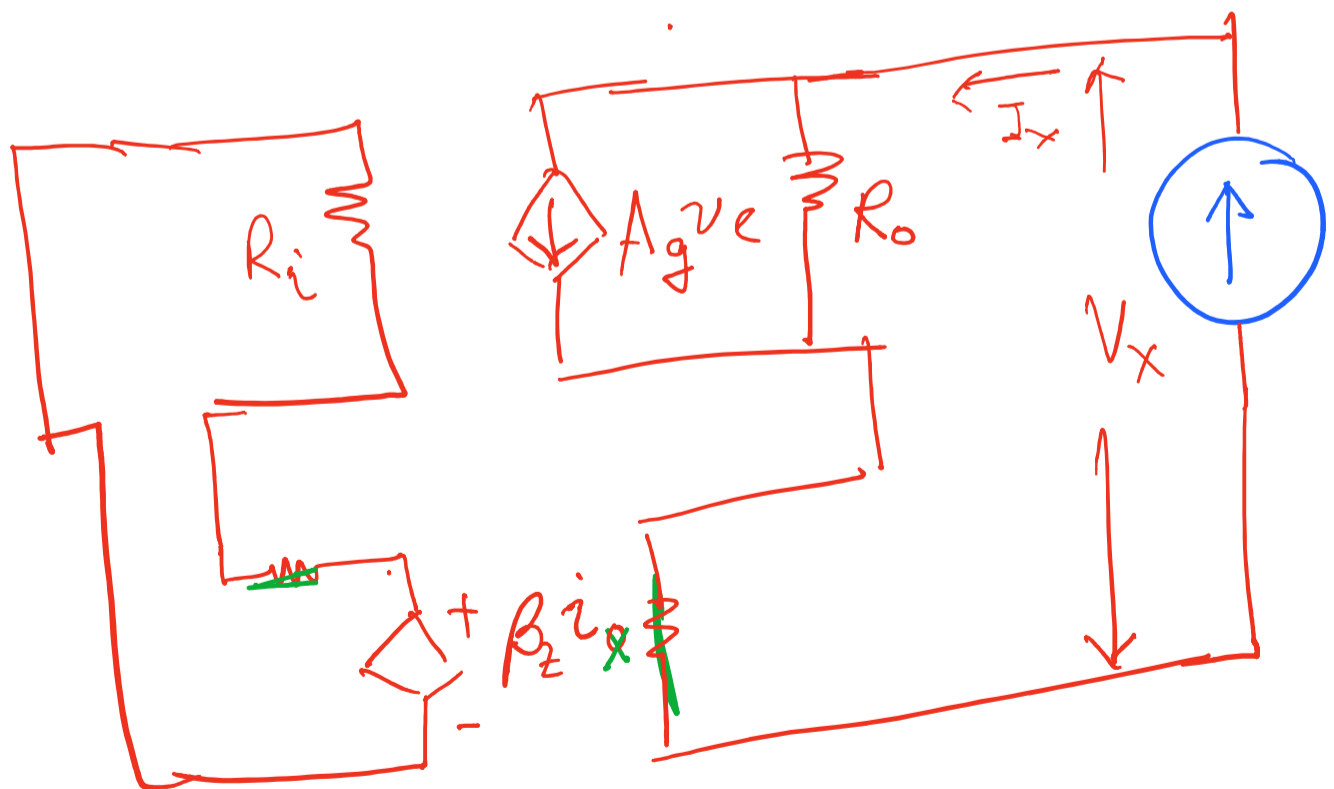

KCL

$$I_x = \frac{V_x}{R_o} + A_g v_e$$

$$[v_s = v_e + v_{fb} = 0] \quad v_e = -v_{fb}$$

$$I_x = \frac{V_x}{R_o} - A_g v_{fb}$$

$$= \frac{V_x}{R_o} - A_g \beta_2 I_x$$

$$I_x [1 + A_g \beta_2] = \frac{V_x}{R_o}$$

$$\therefore R_{of} = \frac{V_x}{I_x} = R_o [1 + A_g \beta_2]$$

Topology	Open loop Gain	Closed loop gain	R_{if}	R_{of}
Series-shunt v v	A_v	$A_{vf} = \frac{A_v}{1 + \beta_v A_v}$	$R_i (1 + \beta_v A_v)$	$\frac{R_o}{1 + \beta_v A_v}$
Shunt-series i i	A_i	$A_{if} = \frac{A_i}{1 + \beta_i A_i}$	$\frac{R_i}{1 + \beta_i A_i}$	$R_o (1 + \beta_i A_i)$
Shunt-shunt i v	A_z	$A_{zf} = \frac{A_z}{1 + \beta_g A_z}$	$\frac{R_i}{1 + \beta_g A_z}$	$\frac{R_o}{1 + \beta_g A_z}$
Series-Series v i	A_g	$A_{gf} = \frac{A_g}{1 + \beta_2 A_g}$	$R_i (1 + \beta_2 A_g)$	$R_o (1 + \beta_2 A_g)$