

PSPICE

A brief primer

Contents

- 1. Introduction**
- 2. Use of PSpice with OrCAD Capture**
 - 2.1 Step 1: Creating the circuit in Capture
 - 2.2 Step 2: Specifying the type of analysis and simulation
 - BIAS or DC analysis
 - DC Sweep simulation
 - 2.3 Step 3: Displaying the simulation Results
 - 2.4 Other types of Analysis:
 - 2.4.1 Transient Analysis
 - 2.4.2 AC Sweep Analysis
- 3. Additional Circuit Examples with PSpice**
 - 3.1 Transformer circuit
 - 3.2 AC Sweep of Filter with Ideal Op-amp (Filter circuit)
 - 3.3 AC Sweep of Filter with Real Op-amp (Filter Circuit)
 - 3.4 Rectifier Circuit (peak detector) and the use of a parametric sweep.
 - Peak Detector simulation
 - Parametric Sweep
 - 3.5 AM Modulated Signal
 - 3.6 Center Tap Transformer
- 4. Adding and Creating Libraries: Model and Part Symbol files**
 - 4.1 Using and Adding Vendor Libraries
 - 4.2 Creating PSpice Symbols from an existing PSpice Model file
 - 4.3 Creating your own PSpice Model file and Symbol Parts

References

1. INTRODUCTION

SPICE is a powerful general purpose analog and mixed-mode circuit simulator that is used to verify circuit designs and to predict the circuit behavior. This is of particular importance for integrated circuits. It was for this reason that SPICE was originally developed at the Electronics Research Laboratory of the University of California, Berkeley (1975), as its name implies:

Simulation Program for Integrated Circuits Emphasis.

PSpice is a PC version of SPICE (which is currently available from OrCAD Corp. of Cadence Design Systems, Inc.). A student version (with limited capabilities) comes with various textbooks. The OrCAD student edition is called [PSpice AD](#) Lite. Information about Pspice AD is available from the OrCAD website: <http://www.orcad.com/pspicead.aspx>

The PSpice Light version has the following limitations: circuits have a maximum of 64 nodes, 10 transistors and 2 operational amplifiers.

SPICE can do several *types of circuit analyses*. Here are the most important ones:

- Non-linear DC analysis: calculates the DC transfer curve.
- Non-linear transient and Fourier analysis: calculates the voltage and current as a function of time when a large signal is applied; Fourier analysis gives the frequency spectrum.
- Linear AC Analysis: calculates the output as a function of frequency. A bode plot is generated.
- Noise analysis
- Parametric analysis
- Monte Carlo Analysis

In addition, PSpice has analog and digital libraries of standard components (such as NAND, NOR, flip-flops, MUXes, FPGAs, PLDs and many more digital components,). This makes it a useful tool for a wide range of analog and digital applications.

All analyses can be done at different temperatures. The default temperature is 300K.

The circuit can contain the *following components*:

- Independent and dependent voltage and current sources
- Resistors
- Capacitors
- Inductors
- Mutual inductors
- Transmission lines
- Operational amplifiers
- Switches
- Diodes
- Bipolar transistors
- MOS transistors
- JFET
- MESFET
- Digital gates
- and other components (see users manual).

2. PSpice with OrCAD Capture (release 9.2 Lite edition)

Before one can simulate a circuit one needs to specify the circuit configuration. This can be done in a variety of ways. One way is to enter the circuit description as a text file in terms of the elements, connections, the models of the elements and the type of analysis. This file is called the SPICE input file or source file and has been described [somewhere else](#).

An alternative way is to use a schematic entry program such as OrCAD CAPTURE. OrCAD Capture is bundled with PSpice Lite AD on the same CD that is supplied with the textbook. Capture is a user-friendly program that allows you to capture the schematic of the circuits and to specify the type of simulation. Capture is non only intended to generate the input for PSpice but also for PCD layout design programs.

The following figure summarizes the different steps involved in simulating a circuit with Capture and PSpice. We'll describe each of these briefly through a couple of examples.

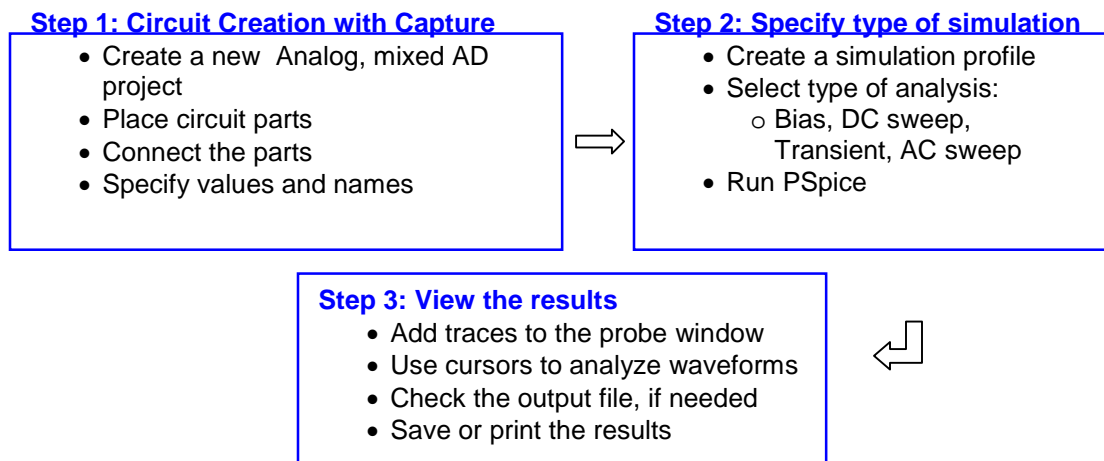


Figure 1: Steps involved in simulating a circuit with PSpice.

The values of elements can be specified using scaling factors (upper or lower case):

T or Tera (= 1E12);
G or Giga (= E9);
MEG or Mega (= E6);
K or Kilo (= E3);
M or Milli (= E-3);

U or Micro (= E-6);
N or Nano (= E-9);
P or Pico (= E-12)
F of Femto (= E-15)

Both upper and lower case letters are allowed in PSpice and HSpice. As an example, one can specify a capacitor of 225 picofarad in the following ways:

225P, 225p, 225pF; 225pFarad; 225E-12; 0.225N

Notice that Mega is written as MEG, e.g. a 15 megaOhm resistor can be specified as 15MEG, 15MEGohm, 15meg, or 15E6. Be careful not to use M for Mega! When you write 15Mohm or 15M, Spice will read this as 15 milliOhm!

We'll illustrate the different types of simulations for the following circuit:

 


Figure 2: Circuit to be simulated (screen shot from OrCAD Capture).

2.1 Step 1: Creating the circuit in Capture

2.1.1 Create new project:

1. Open OrCAD Capture
2. Create a new Project: FILE MENU/NEW_PROJECT
3. Enter the name of the project
4. Select Analog or Mixed-AD
5. When the Create PSpice Project box opens, select "Create Blank Project".

A new page will open in the Project Design Manager as shown below.

 


Figure 3: Design manager with schematic window and toolbars (OrCAD screen capture)

2.1.2. Place the components and connect the parts

1. Click on the Schematic window in Capture.
2. To Place a part go to PLACE/PART menu or click on the Place Part Icon. This will open a dialog box shown below.

 


Figure 4: Place Part window

3. Select the library that contains the required components. Type the beginning of the name in the Part box. The part list will scroll to the components whose name contains the same letters. If the library is not available, you need to add the library, by clicking on the Add Library button. This will bring up the Add Library window. Select the desired library. For Spice you should select the libraries from the Capture/Library/PSpice folder.

Analog: contains the passive components (R,L,C), mutual inductance, transmission line, and voltage and current dependent sources (voltage dependent voltage source E, current-dependent current source F, voltage-dependent current source G and current-dependent voltage source H).

Source: give the different type of independent voltage and current sources, such as Vdc, Idc, Vac, Iac, Vsin, Vexp, pulse, piecewise linear, etc. Browse the library to see what is available.

Eval: provides diodes (D...), bipolar transistors (Q...), MOS transistors, JFETs (J...), real opamp such as the u741, switches (SW_tClose, SW_tOpen), various digital gates and components.

Abm: contains a selection of interesting mathematical operators that can be applied to signals, such as multiplication (MULT), summation (SUM), Square Root (SWRT), Laplace (LAPLACE), arctan (ARCTAN), and many more.

Special: contains a variety of other components, such as PARAM, NODESET, etc.

- Place the resistors, capacitor (from the Analog library), and the DC voltage and current source. You can place the part by the left mouse click. You can rotate the components by clicking on the R key. To place another instance of the same part, click the left mouse button again. Hit the ESC key when done with a particular element. You can add initial conditions to the capacitor. Double-click on the part; this will open the Property window that looks like a spreadsheet. Under the column, labeled IC, enter the value of the initial condition, e.g. 2V. For our example we assume that IC was 0V (this is the default value).
- After placing all part, you need to place the Ground terminal by clicking on the GND icon (on the left side toolbar). When the Place Ground window opens, select GND/CAPSYM and **give it the name 0 (i.e. zero)**. Do not forget to change the name to 0, otherwise PSpice will give an error or "Floating Node". The reason is that SPICE needs a ground terminal as the reference node that has the node number or name 0 (zero).

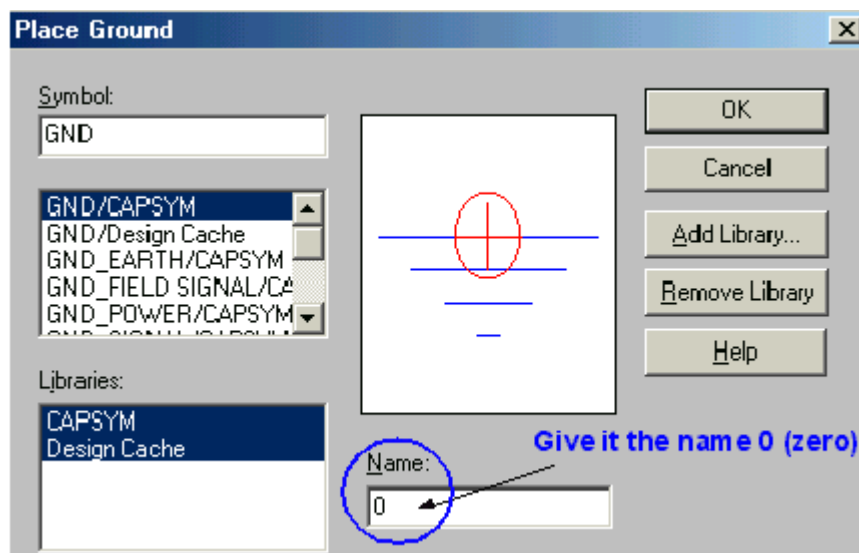


Figure 5: Place the ground terminal box; the ground terminal should have the name 0

- Now connect the elements using the Place Wire command from the menu (PLACE/WIRE) or by clicking on the Place Wire icon.
- You can assign names to nets or nodes using the Place Net Alias command (PLACE/NET ALIAS menu). We will do this for the output node and input node. Name these Out and In, as shown in Figure 2.

2.1.3. Assign Values and Names to the parts

- Change the values of the resistors by double-clicking on the number next to the resistor. You can also change the name of the resistor. Do the same for the capacitor and voltage and current source.
- If you haven't done so yet, you can assign names to nodes (e.g. Out and In nodes).
- Save the project

2.1.4. Netlist

The netlist gives the list of all elements using the simple format:

```
R_name node1 node2 value
C_name nodex nodey value, etc.
```

1. You can generate the netlist by going to the PSPICE/CREATE NETLIST menu.
2. Look at the netlist by double clicking on the Output/name.net file in the Project Manager Window (in the left side File window).

Note on Current Directions in elements:

The positive current direction in an element such as a resistor is from node 1 to node 2. Node 1 is either the left pine or the top pin for an horizontal or vertical positioned element (.e.g a resistor). By rotating the element 180 degrees one can switch the pin numbers. To verify the node numbers you can look at the netlist:

```
e.g. R_R2 node1 node2 10k
e.g. R_R2 0 OUT 10k
```

Since we are interested in the current direction from the OUT node to the ground, we need to rotate the resistor R2 twice so that the node numbers are interchanged:

```
R_R2 OUT 0 10k
```

2.2 Step 2: Specifying the type of analysis and simulation

As mentioned in the introduction, Spice allows you do to a DC bias, DC Sweep, Transient with Fourier analysis, AC analysis, Montecarlo/worst case sweep, Parameter sweep and Temperature sweep. We will first explain how to do the Bias and DC Sweep on the circuit of Figure 2.

2.2.1 BIAS or DC analysis

1. With the schematic open, go to the PSPICE menu and choose NEW SIMULATION PROFILE.
2. In the Name text box, type a descriptive name, e.g. Bias
3. From the Inherit From List: select none and click Create.
4. When the Simulation Setting window opens, for the Analysis Type, choose Bias Point and click OK.
5. Now you are ready to run the simulation: PSPICE/RUN
6. A window will open, letting you know if the simulation was successful. If there are errors, consult the Simulation Output file.
7. To see the result of the DC bias point simulation, you can open the Simulation Output file or go back to the schematic and click on the V icon (Enable Bias Voltage Display) and I icon (current display) to show the voltage and currents (see Figure 6).

The check the direction of the current, you need to look at the netlist: the current is positive flowing from node1 to node1 (see note on Current Direction above).

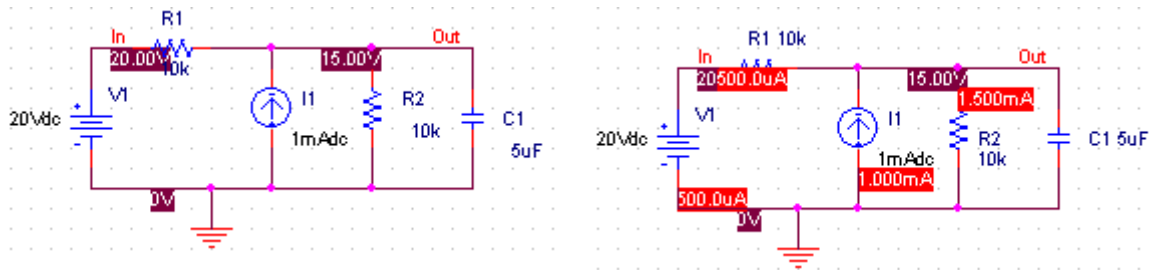


Figure 6: Results of the Bias simulation displayed on the schematic.

2.2.2 DC Sweep simulation

We will be using the same circuit but will evaluate the effect of sweeping the voltage source between 0 and 20V. We'll keep the current source constant at 1mA.

1. Create a new New Simulation Profile (from the PSpice Menu); We'll call it DC Sweep
2. For analysis select DC Sweep; enter the name of the voltage source to be swept: V1. The start and end values and the step need to be specified: 0, 20 and 0.1V, respectively (see Fig. below).

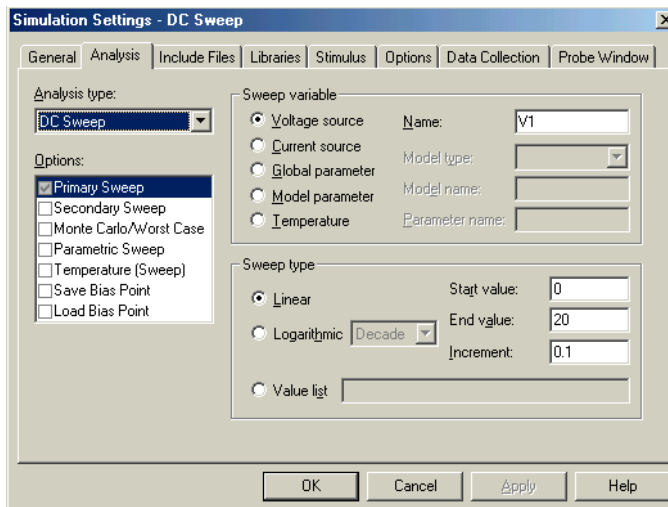


Figure 7: Setting for the DC Sweep simulation.

3. Run the simulation. PSpice will generate an output file that contains the values of all voltages and currents in the circuit.

2.3 Step 3: Displaying the simulation Results

PSpice has a user-friendly interface to show the results of the simulations. Once the simulation is finished a Probe window will open.

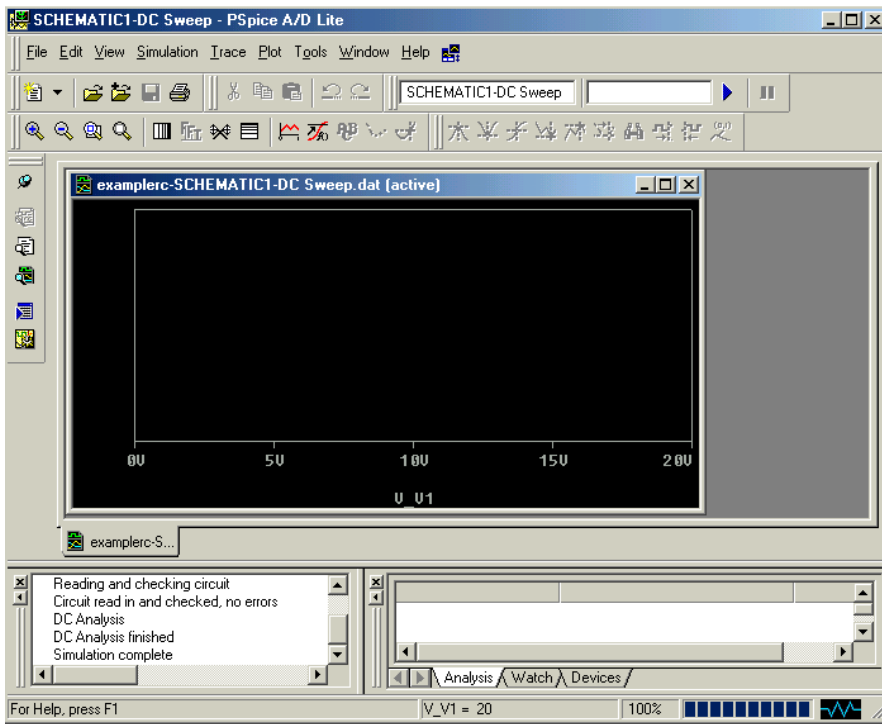


Figure 8: Probe window

1. From the TRACE menu select ADD TRACE and select the voltages and current you like to display. In our case we'll add V(out) and V(in). Click OK.

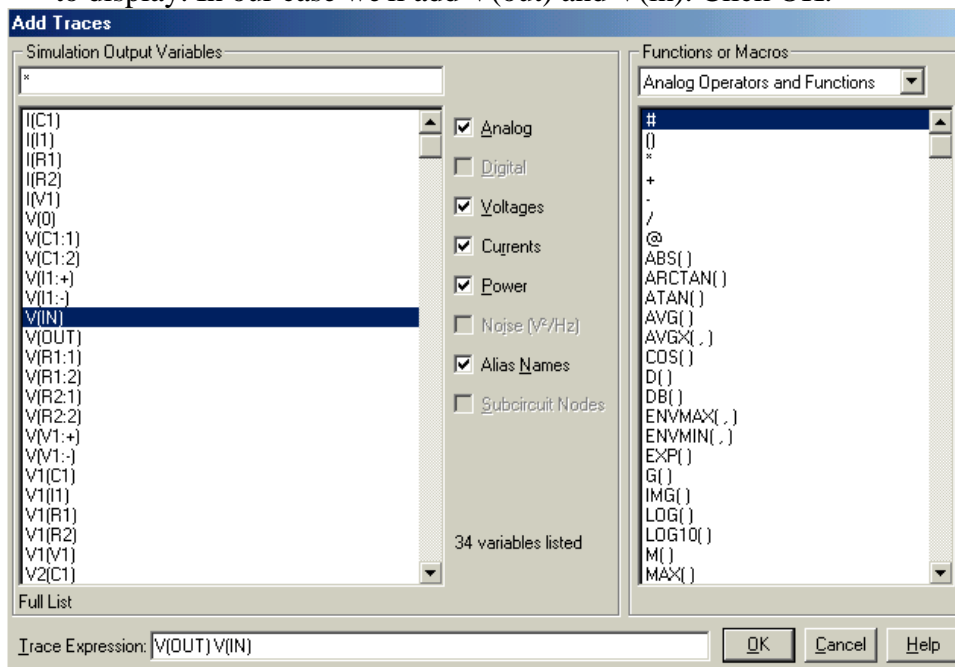


Figure 9: Add Traces window

2. You can also add traces using the "Voltage Markers" in the schematic. From the PSPICE menu select MARKERS/VOLTAGE LEVELS. Place the makers on the Out and In node. When done, right click and select End Mode.

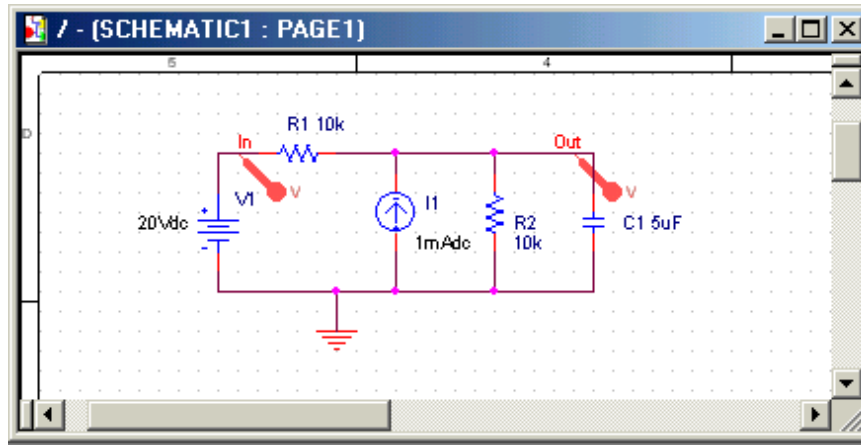


Figure 10: Using Voltage Markers to show the simulation result of V(out) and V(in)

3. Go to back to PSpice. You will notice that the waveforms will appear.
4. You can add a second Y Axis and use this to display e.g. the current in Resistor R2, as shown below. Go to PLOT/Add Y Axis. Next, add the trace for I(R2).
5. You can also use the cursors on the graphs for Vout and Vin to display the actual values at certain points. Go to TRACE/CURSORS/DISPLAY
6. The cursors will be associated with the first trace, as indicated by the small small rectangle around the legend for V(out) at the bottom of the window. Left click on the first trace. The value of the x and y axes are displayed in the Probe window. When you right click on V(out) the value of the second cursor will be given together with the difference between the first and second cursor.
7. To place the second cursor on the second trace (for V(in)), right click the legend for V(in). You'll notice the outline around V(in) at the bottom of the window. When you right click the second trace the cursor will snap to it. The values of the first and second cursor will be shown in Probe window.
8. You can change the X and Y axes by double clicking on them.
9. When adding traces you can perform mathematical calculations on the traces, as indicated in the Add Trace Window to the right of Figure 9.

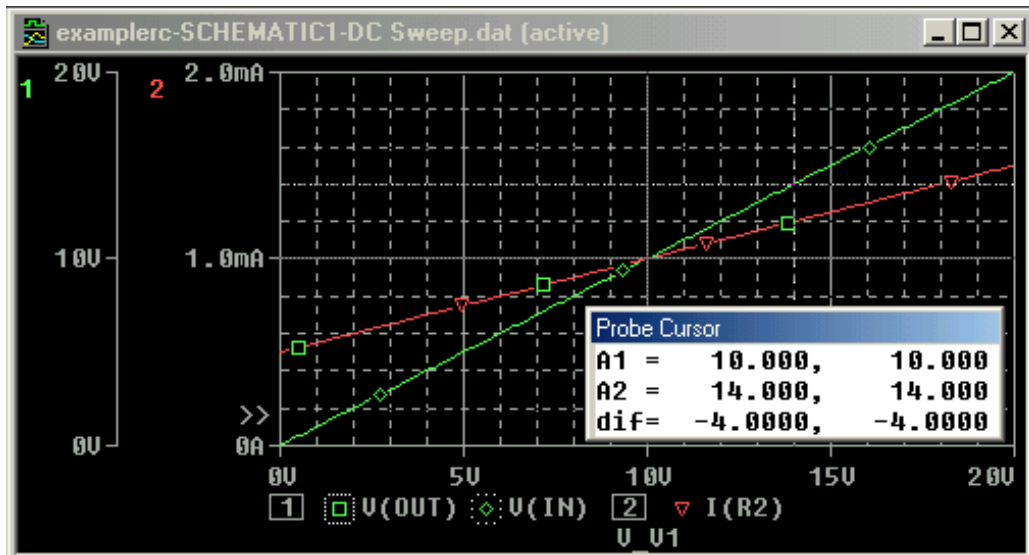


Figure 11: Result of the DC sweep, showing V_{out} , V_{in} and the current through resistor R_2 . Cursors were used for V_{out} and V_{in} .

2.4 Other types of Analysis

2.4.1 Transient Analysis

We'll be using the same circuit as for the DC sweep, except that we'll apply the voltage and current sources by closing a switch, as shown in Figure 12.

 


Figure 12: Circuit used for the transient simulation.

1. Insert the SW_TCLOSE switch from the EVAL Library as shown above. Double click on the switch TCLOSE value and enter the value when the switch closes. Lets make TCLOSE = 5 ms.
2. Set up the Transient Analysis: go to the PSPICE/NEW SIMULATION PROFILE.
3. Give it a name (e.g. Transient). When the Simulation Settings window opens, select "Time Domain (Transient)" Analysis. Enter also the Run Time. Lets make it 50 ms. For the Max Step size, you can leave it blank or enter 10us.
4. Run PSpice.
5. A Probe window in PSpice will open. You can now add the traces to display the results. In the figure below we plotted the current through the capacitor in the top window and the voltage over the capacitor on the bottom one. We use the cursor to find the time constant of the exponential waveform (by finding the $0.632 \times V_{out}max = 9.48$. The

cursor gave a corresponding time of 30ms which gives a time constant of $30-5=25$ ms (5 ms is subtracted because the switch closed at 5ms).

 


Figure 13: Results of the transient simulation of Figure 12.

6. Instead of using a switch we can also use a voltage source that changes over time. This was done in Figure 14 where we used the VPULSE and IPULSE sources from the SOURCE Library. We entered the voltage levels (V1 and V2), the delay (TD), Rise and Fall Times, Pulse Width (PW) and the Period (PER). The values are indicated in the figure below.

 


Figure 14: Circuit with a PULSE voltage and current source.

7. After doing the transient simulation results can be displayed as was done before
8. The last example of a transient analysis is with a sinusoidal signal VSIN. The circuit is shown below. We made the amplitude 10V and frequency 10 Hz.

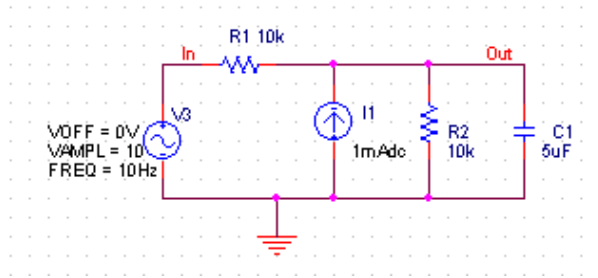


Figure 15: Circuit with a sinusoidal input.

9. Create a Simulation Profiler for the transient analysis and run PSpice.
10. The result of the simulation for Vout and Vin are given in the figure below.

 


Figure 16: Transient simulation with a sinusoidal input.

2.4.2 AC Sweep Analysis

The AC analysis will apply a sinusoidal voltage whose frequency is swept over a specified range. The simulation calculates the corresponding voltage and current amplitude and phases for each frequency. When the input amplitude is set to 1V, then the output voltage is basically the transfer function. In contrast to a sinusoidal transient analysis, the AC analysis is not a time domain simulation but rather a simulation of the sinusoidal steady state of the circuit. When the circuit contains non-linear element such as diodes and transistors, the elements will be replaced their small-signal models with the parameter values calculated according to the corresponding biasing point.

In the first example, we'll show a simple RC filter corresponding to the circuit of Figure 17.


 


Figure 17: Circuit for the AC sweep simulation.

 1. Create a new project and build the circuit
2. For the voltage source use VAC from the Sources library.
3. Make the amplitude of the input source 1V.
4. Create a Simulation Profile. In the Simulation Settings window, select AC Sweep/Noise.
5. Enter the start and end frequencies and the number of points per decade. For our example we use 0.1Hz, 10 kHz and 11, respectively.
6. Run the simulation
7. In the Probe window, add the traces for the input voltage. We added a second window to display the phase in addition to the magnitude of the output voltage. The voltage can be displayed in dB by specifying Vdb(out) in the Add Trace window (type Vdb(out) in the Trace Expression box. For the phase, type VP(out).
8. An alternative to show the voltage in dB and phase is to use markers on the schematics: PSPICE/MARKERS/ADVANCED/dBMagnitude or Phase of Voltage, or current. Place the markers on the node of interest.
9. We used the cursors in Figure 18 to find the 3dB point. The value is 6.49 Hz corresponding to a time constant of 25 ms ($R1 \parallel R2 \cdot C$). At 10 Hz the attenuation of Vout is 11.4db or a factor of 3.72. This corresponds to the value of the amplitude of the output voltage obtained during the transient analysis of Figure 16 above.



3. Additional Circuit Examples with PSpice

3.1 Transformer circuit

SPICE has no model for an ideal transformer. An ideal transformer is simulated using mutual inductances such that the transformer ratio $N1/N2 = \sqrt{L1/L2}$. The part in PSpice is called TFRM_LINEAR (in the Analog Library). Make the coupling factor K close to or equal to one (ex. $K=1$) and choose L such that $\omega L \gg$ the resistance seen by the inductor. The secondary circuit needs a DC connection to ground. This can be accomplished by adding a large resistor to ground or giving the primary and secondary circuits a common node. The following example illustrates how to simulate a transformer.



Figure 3.1.1: Circuit with ideal transformer

For the above example, let's make $\omega L2 \gg 500 \text{ Ohm}$ or $L2 > 500 / (60 * 2\pi)$; let's make $L2$ at least 10 times larger, ex. $L2=20\text{H}$. $L1$ can then be found from the turn ratio: $L1/L2 = (N1/N2)^2$. For a turn ratio of 10 this makes $L1=L2 \times 100=2000\text{H}$. The circuit as entered in PSpice Capture is shown in Figure 3.1.2 and the result in Figure 3.1.3

 


Figure 3.1.2: Circuit with ideal transformer as entered in PSpice Capture (the transformer TX is modeled by the part XFRM_LINEAR of the Analog Library).

 


Figure 3.1.3: Results of the transient simulation of the above circuit.

3.2 AC Sweep of Filter with Ideal Op-amp (Filter circuit)

The following circuit will be simulated with PSpice.


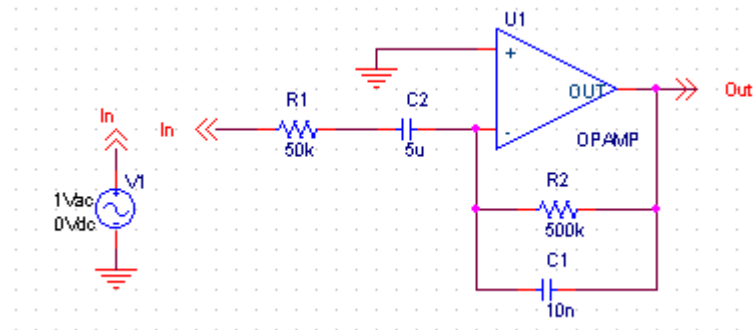


Figure 3.2.1: Active Filter Circuit with ideal op-amp.

We have used off-page connectors (OFFPAGELEFT-R from the CAPSYM library; or by clicking on the off-page icon) for the input and outputs. The name of the connectors can be changed by double-clicking on the name of the off-page connector. By giving the same name to two connectors (or nodes), the two nodes will be connected (no wires are needed). For the voltage source we used the VAC from the SOURCE Library. We gave it an amplitude of 1V so that the output voltage will correspond to the amplification (or transfer function) of the filter. In the Simulation Analysis, select AC Sweep, and enter the starting, ending frequency and the number of points per decade.

The result is given in the figure below. The magnitude is given on the left Y axis while the phase is given by the right Y axis. The cursors have been used to find the 3db points of the bandpass filters, corresponding to 0.63 Hz and 32 Hz for the low and high breakpoints, respectively. These numbers correspond to the values of the time constants given in Fig. 3.2.1. The phase at these points is -135 and -224 degrees.

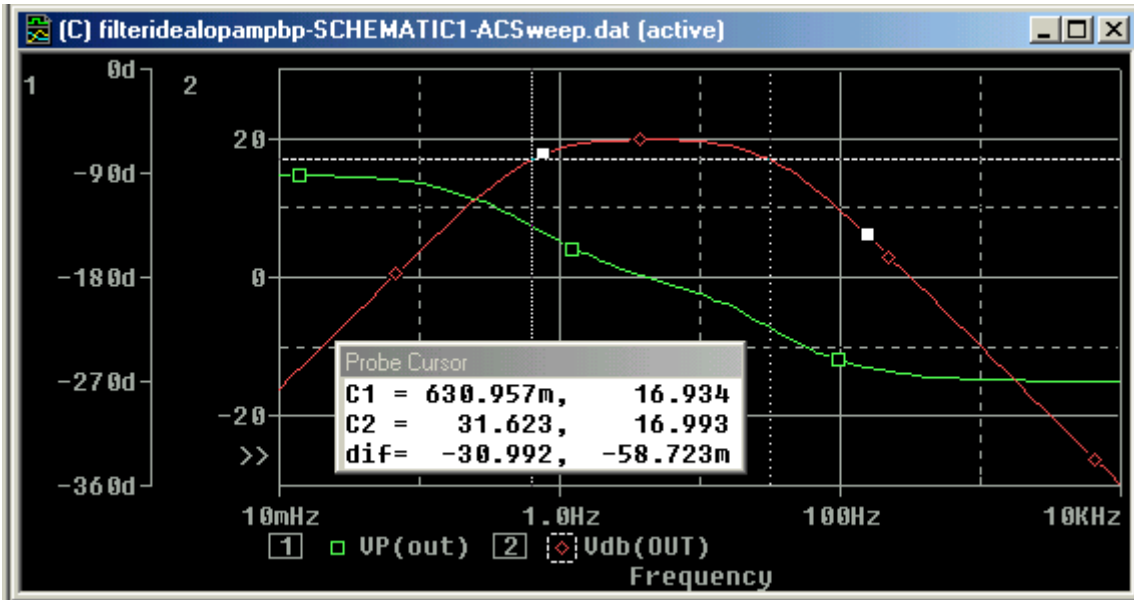

3.3 AC Sweep of Filter with Real Op-amp (Filter circuit)

The circuit with a real op-amp is shown below. We selected the U741 op-amp to build the filter. The simulation results are shown in Figure 3.3.2. As one would expect the differences between the filter with the real and ideal op-amps are minimal in this frequency range.

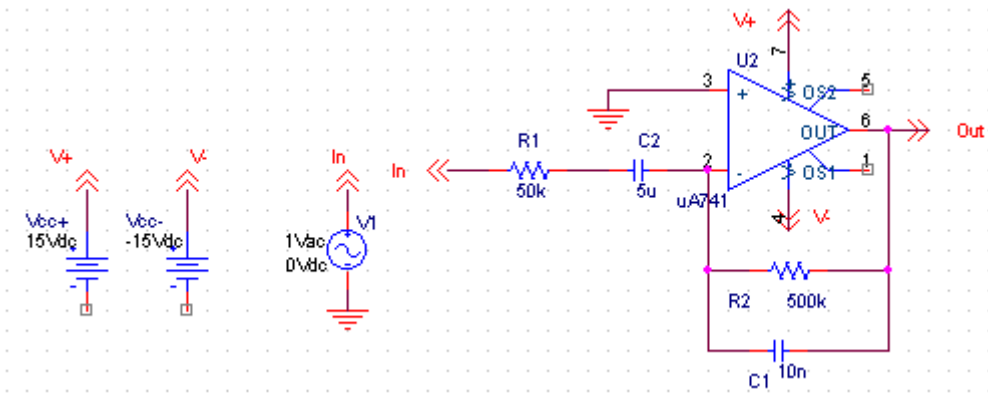


Figure 3.3.1: Active Filter Circuit with the U741 Op-amp.

 


Figure 3.3.2: Results of the AC sweep of the Active Filter Circuit with real Op-amp (U741) of the figure above.

3.4 Rectifier Circuit (peak detector) and the use of a parametric sweep.

3.4.1: Peak Detector simulation

 


Figure 3.4.1: Rectifier circuit with the D1N4148 diode and a load resistor of 500 Ohm.

The results of the simulation are given in Fig. 3.4.2. The ripple has a peak-to-peak value of 777mV as indicated by the cursors. The maximum output voltage is 13.997V which is one volt below the input of 15V.

 


Figure 3.4.2: Simulation results of the rectifier circuit.

3.4.2 Parametric Sweep

It is interesting to see the effect of the load resistance on the output voltage and its ripple voltage. This can be done using the PARAM part.

 


Figure 3.4.3: Circuit used for the parametric sweep of the load resistor.

a. Adding the Parameter Part

- Double click on the value (500 Ohms) of the load resistor $R1$ to $\{Rval\}$. Use curly brackets. PSpice interprets the text between curly brackets as an expression that it evaluate to a numerical expression. Click OK when done.
- Add the PARAM part to the circuit. You'll find this part in the SPECIAL library.
- Double click on the PARAM part. This will open a spreadsheet like window showing the PARAM definition. You will need to add a new column to this spread sheet. Click on NEW COLUMN and enter for Property Name, $Rlval$ (without the curly brackets).
- You will notice that the new column $Rlval$ has been created. Below the $Rlval$ enter the initial value for the resistor: lets make it 500, as shown in Figure 3.4.4 below.

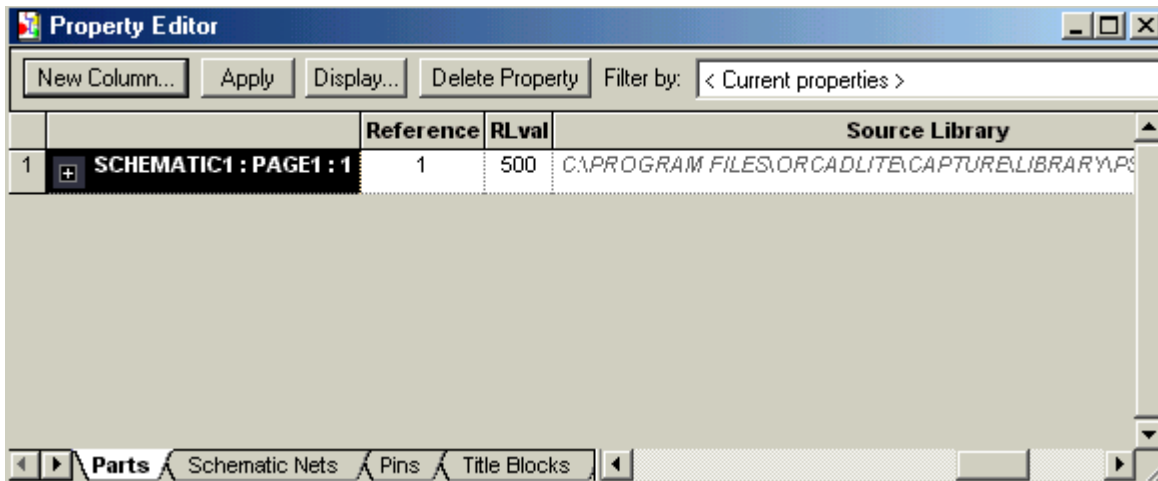


Figure 3.4.4: Property Editor window for the PARAM part, showing the newly created RLval column.

- e. While the cell in which you entered the value 500 still selected click the DISPLAY button. You can now specify what to display: select Name and Value. Click OK.
- f. Click the APPLY button before closing the Property editor.
- g. Save the design.

b. Create the Simulation Profile for the Parametric Analysis

- a. Select PSPICE/NEW_SIMULATION_PROFILE
- b. Type in the name of the profile, e.g. Parametric
- c. In the Simulation Setting window, select Analysis Tab if the window does not open.
- d. For the Analysis type select Transient (or the type of analysis you intend to perform; in this example we'll do a transient analysis)
- e. Under Option, select Parametric sweep as shown in Figure 3.4.5.
- f. For the Sweep Variable, select Global Parameter and enter the Parameter name: RLval. Under sweep type give the start, end and increment for the parameter. We'll use 250, 1kOhm and 250, respectively (see Figure 3.4.5).
- g. Click OK

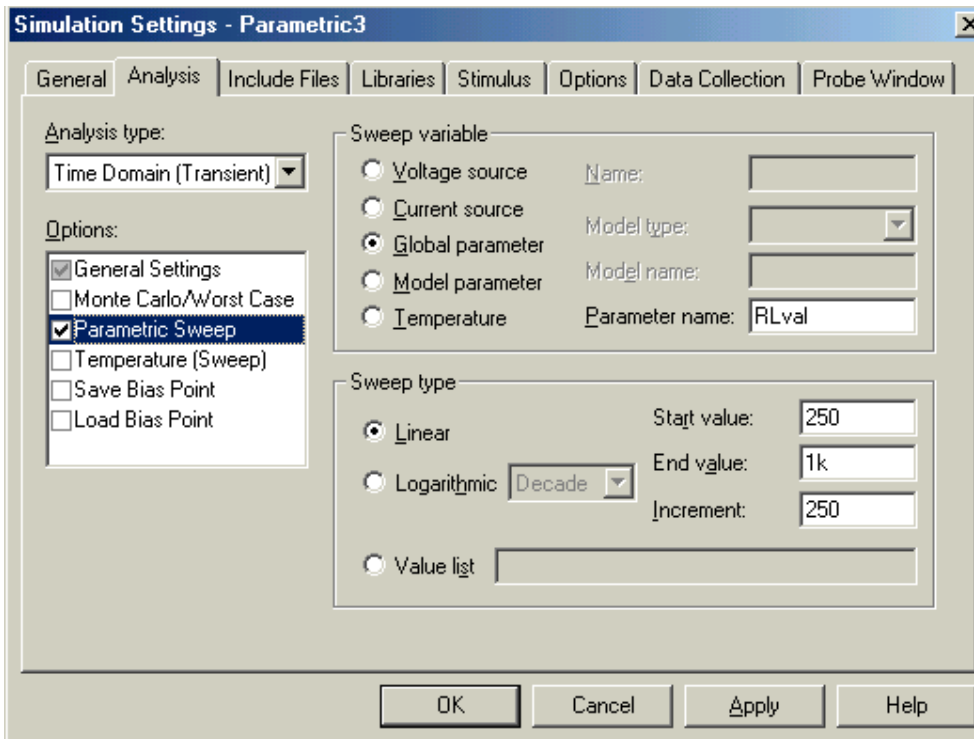


Figure 3.4.5: Window for the Simulation Settings of the Parametric Sweep.

c. Run Spice and Display the waveforms.

- a. Run PSpice
- b. When the simulation is finished the Probe window will open and display a pop up box with the Available Selection. Select ALL and OK.
- c. The multiple traces will show, as given in Figure 3.4.6.
- d. You can use the cursors to determined specific values on the traces; you can also adjust the axis by double-clicking on the Y and X axes.

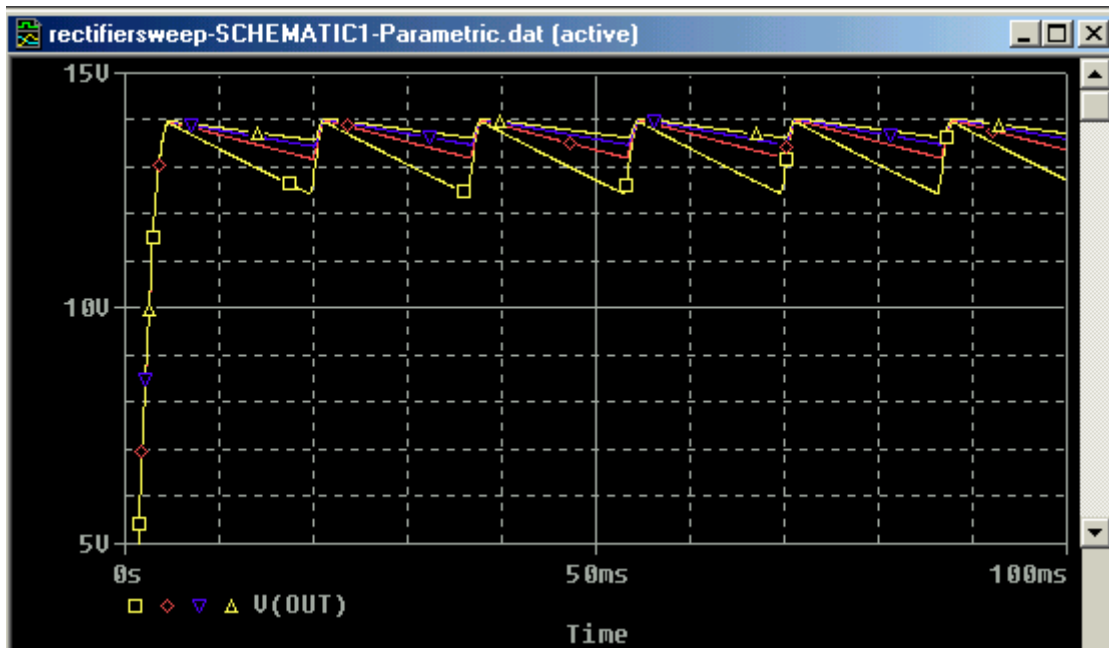


Figure 3.4.6: Results of the parametric sweep of the load resistor, varying from 250 to 1000 Ohm in steps of 250 Ohm.

3.5 AM Modulated Signal (AM Modulation)

An Amplitude modulated (AM) signal has the expression,

$$v_{am}(t) = [(A + V_m \cos(2\pi f_m t))] \cos(2\pi f_c t) = A[1 + m \cos(2\pi f_m t)] \cos(2\pi f_c t)$$

in which a sinusoidal high frequency carrier waveform $\cos(2\pi f_c t)$ is modulated by a sinusoidal modulating of frequency f_m . The modulating frequency can be any signal. For this example we'll assume it is a sinusoid. The modulation index is called m .

To generate a AM signal in PSpice we can make use of the Multiplication function MULT that can be found in the ABM library. Figure 3.5.1 shows the schematic that generates the AM signal over the resistor R1.

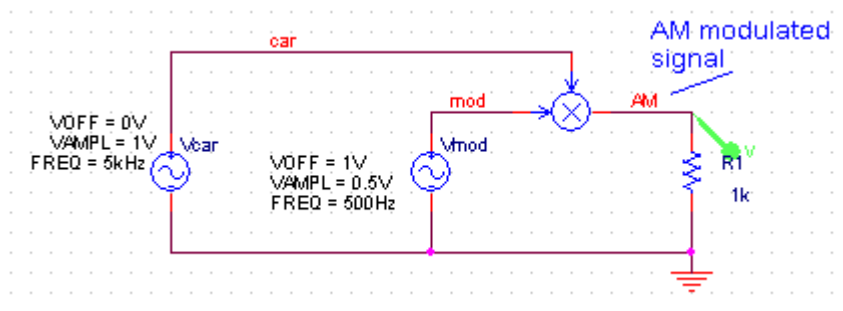


Figure 3.5.1: Schematic for the generation of an AM signal

The result of a transient simulation is shown in the figure below. One can also look at the Fourier of the simulated output signal. In the Probe window click on the FFT icon, located on the top toolbar, or go to the PSPICE/FOURIER menu. The Fourier spectrum of the displayed trace will be shown. You can change the X axis by double-clicking on it. Figure 3.5.3 gives the Fourier spectrum with the main peak corresponding to the carrier frequency of 5kHz and two side peaks at 4.5 and 5.5 kHz, indicating that the modulating frequency is 500Hz. You can use the cursors to get accurate readings.

 


Figure 3.5.2: Simulated waveform (transient analysis) of the circuit above, with $(A=1V, f_m=500\text{ Hz}, f_c=5\text{kHz}$ and $m=0.5)$

 


Figure 3.5.3: Fourier spectrum of the waveform of Figure 3.5.2.

3.6. Center Tap Transformer

There is no direct model in PSpice for a center tap transformer. However, one can use mutually coupled inductors to simulate a center tap transformer. Figure 3.6.1 shows the schematic of the circuit. We used one primary inductor L1 and two secondary inductors L1 and L2 put in series. In addition we added a K-Linear element.

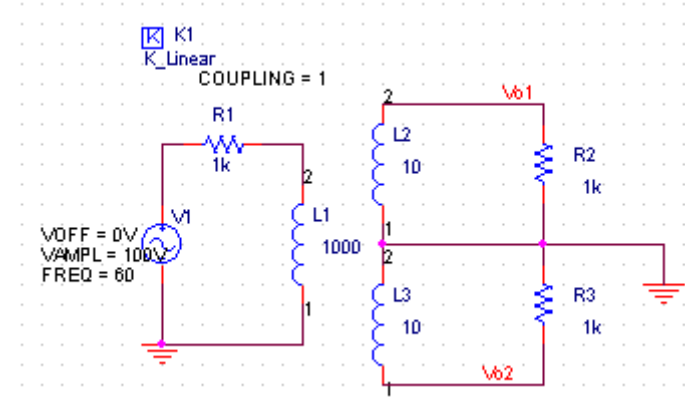


Figure 3.6.1: Circuit with Center Tap Transformer with a ratio of 10:1.

After placing the element on the schematic give each element its value. Use of the input voltage a sinoid with amplitude of 100 V and frequency 60 Hz. Notice that we added a small resistor R1 in series with the voltage source and the inductor. This was needed to prevent a short circuit in DC (Spice would give an error without this resistor). We have kept it small equal to 1 Ohm. Assume that we want to have a step-down transformer with a ratio of 10:1 to each secondary output. The ratios of the inductors $L2/L1$ and $L3/L1$ must then be equal to $1/10^2$ (or $=\sqrt{L2/L1}=0.1$). We made $L1=1000$ and $L2-L3=10H$.

Double-click on the K-Linear element and type under the column headings for L1, L2, L3, the values LP, Ls1, Ls2. When done, click the APPLY button and close the properties window.

Go to PSpice/CREATE_NETLIST to generate the netlist. To see the list, go to the Project Manager and double-click on OUTPUTS: name.net file. The netlist looks as follows:

```
* source CENTERTAPTRANSFOR2
Kn_K1      L_Lp L_Ls1 L_Ls2  1
L_Lp      0 N00241 1000
L_Ls1     0 VO1  10
L_Ls2     VO2 0  10
V_V1      N00203 0
+SIN 0V 100V 60 0 0 0
R_R1      N00203 N00241 1k
R_R2      0 VO1  1k
R_R3      VO2 0  1k
```

Create a new Simulation Profile (Transient) with "Time to run = 50ms". The result is shown in Figure 3.6.2. Notice that the max output is 10V as one would expect from a transformer ratio of 10:1 with an input voltage of 100Vmax.. The two outputs are 180 degrees out of phase.

 


Figure 3.6.2: Output of the circuit of Fig. 3.6.1.

4. Adding and Creating Libraries: Model and Parts files

4.1 Using and Adding Vendor Libraries

We assume that the model (.lib) as well as the Part Symbols files (.olb) is available from the vendor. In case only the model file is available see the next section on how to create a Part Symbol.

In some cases you may want to add model libraries and symbols from vendors that contain the devices you want to use in your design. The ORCAD PSpice website list many vander-contributed models. You can download these files. You will need both the model definition file (with extension .lib) and the symbol file (extension .olb). When entering the symbols in the schematic you will need to "add the library". You need also to tell the simulator that the file exists. You do this in the Schematics when defining the Simulation Profile:

In the Simulation Setting window, select the Libraries tab. In the Filename box, enter the name of the new library (the full path name or the library name if it is located in the same folder as the standard libraries). You can make the library modesl global so that it will be available for every schematic or you can keep it local (for the current schematic only). Figure 4.1 shows who we added the library nat_semi-.lib as a global library (click on the Add as Global).

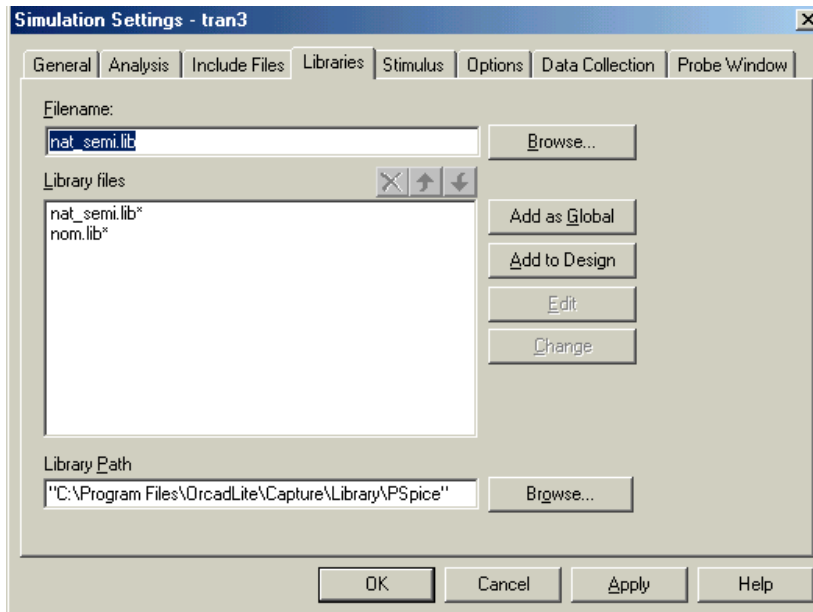


Figure 4.1: Adding a library

4.2 Creating Symbol Parts file from a Model file

In many cases you may have the models of devices available but not the Part Symbol that is used in PSpice Capture. In this case you need to create the symbol file (.olb). In many cases you will have a model file that contains models of many devices including subcircuits. This section describes how to use the model file to create a Part Symbol for the corresponding devices in the model file [9].

The model file is a text file that can be read using a text editor (.e.g Notepad). In many cases existing vendor Spice files will have the extension .cir or .mod. We assume that you have such a file available but not the Part Symbol.

- 4.2.1 Open the **PSpice Model Editor** (this program came with the PSpice package).
 - a. Under the FILE Menu, select NEW
 - b. Next, under the MODEL menu, select IMPORT and find the model file for which you need to create the Part Symbol file. This will open the model file.
 - c. Save this file with the extension .lib and put it in a directory where you store the library files (you can put it in any directory; the default libraries are stored in Program Files/OrCadLite/Capture/Library/PSpice/).
 - d. The next step is to create the Parts for Capture. While the model file (.lib) is still open, go to FILE/CREATE_CAPTURE_FILE menu. A window (Create parts for Library) will pop up as shown below. Click on the top Browse Button and find the location of the model library is stored (.lib). This will automatically fill the Output Part Library entry with the same file name as the model library but with the .olb extension.

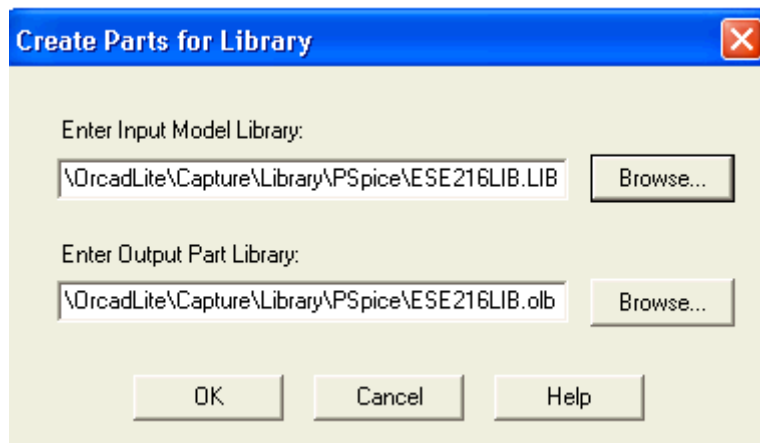


Figure 4.2.1 Create Parts for Library window. In this example we created a Model Library called ESE216LIB.lib and Parts ESE216LIB.olb

- e. Click the OK button. A window will open, giving the status of the library creation. This should give you no errors.
- f. Click OK in the Status window.

The next step is to edit the Part Symbols that you just created.

4.4.2. Editing the Part Symbol

- a. Open OrCad Capture.
- b. Go to the FILE/OPEN/LIBRARY menu. Browse for the location of the newly created file (e.g. ESE216LIB.OLB). Click OK. This will open the PCB window for the library, as shown below. In our example, our library contains two devices (NMOS and PMOS devices). In practical cases the library can contain many different devices and subcircuits. An example is the sedra_lib.lib and sedra_lib.olb that comes with the textbook [10], shown in Figure 4.2.3.

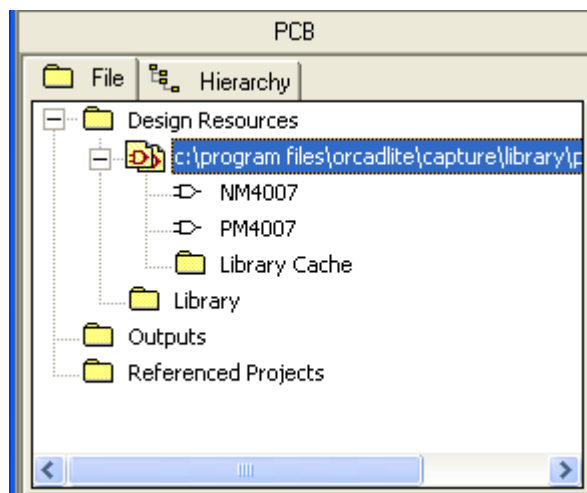


Figure 4.2.2 Library Editor Window in OrCAD Capture

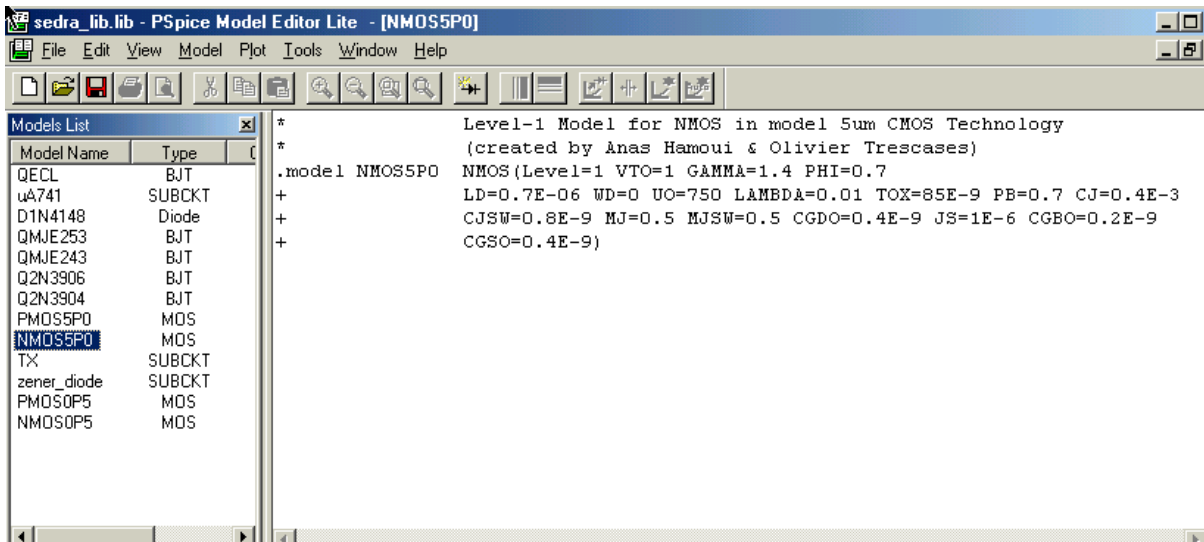


Figure 4.2.3 Library sedra_lib.lib showing the various devices in the library file. The left window pane list all the devices and subcircuits. The right pane shows the model of the NMOS5PO (highlighted on the left).

- c. To edit the symbol of any of the devices double click on it in the Library Editor window. Lets select e.g. the NMOS5PO device. This will open the Part Symbol window, as shown in Figure 4.2.4. OrCad Capture is smart enough to know when a model corresponds to a transistor and will create a transistor model, as shown in Figure 4.2.4. However for subcircuits is will usually give you a generic box. You can than modify this box using the editing tools of Capture.

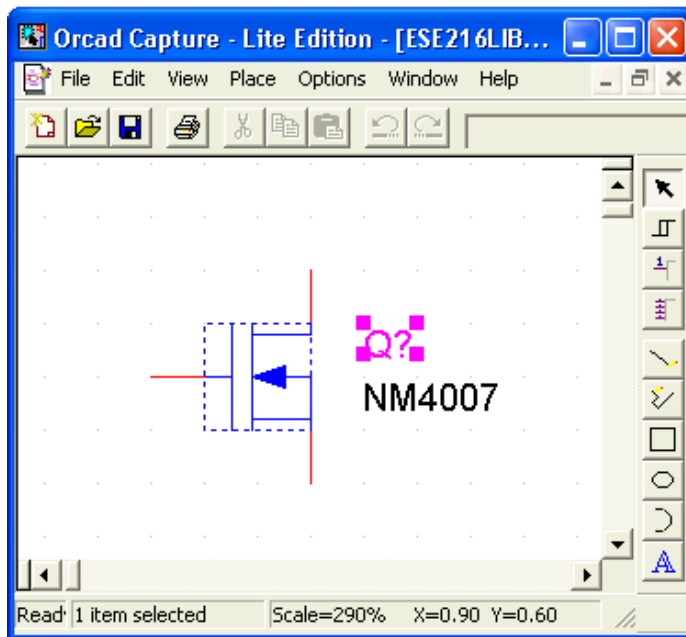


Figure 4.2.4 Part Symbol Window allowing you to edit the part. The example shown here is a NMOS symbol without a separate bulk contact. In that case the source and bulk are automatically shorted together.

- d. The red line on the Parts symbol correspond to pins. These can be added by clicking on the "Place Pin" icon on the right side menu bar (or PLACE/PIN menu). This will open the Place Pin window shown below.
- e. You can edit the pins by first selecting it and then right clicking and selecting Edit Properties. The pin name and type are important. In general you should not change the pin names since these relate back to the Spice model. The pin type is usually "Input" or "Output." If you make a pin a "Power" type, it will be invisible in the part symbol. For shape you can select "Line" or "Short" which corresponds to a short line. Check out the other options. In case you create a symbol for a subcircuit you can give the pin numbers that correspond to those of the datasheet.
- f. When the part symbol is finished, save the library. You are now ready to use your newly created library and symbols. Before doing a simulation you need to add the library to the library path, in both the schematic and the simulator setting. See section on "[Adding Vendor Libraries](#)" above.

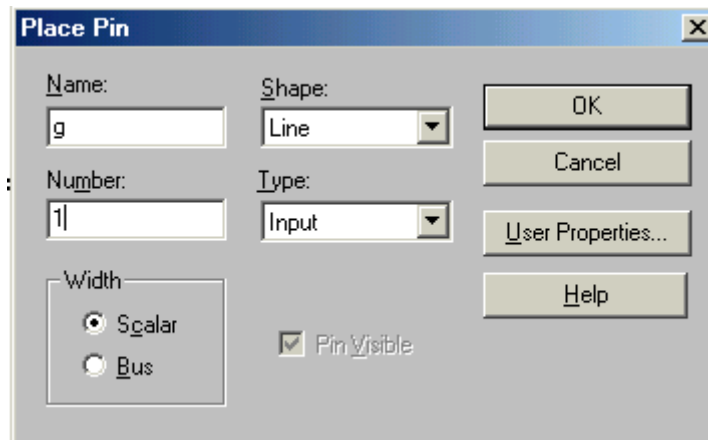


Figure 4.2.5: Place Pin window.

References

1. OrCAD [website for PSpice](http://www.orcad.com/pspicead.aspx) (<http://www.orcad.com/pspicead.aspx>), has application notes, download, examples and interesting links.
2. OrCAD [website for CAPTURE](http://www.orcad.com/orcadcapture.aspx). (<http://www.orcad.com/orcadcapture.aspx>)
3. [PSpice User's manual](#), OrCAD Corp. (Cadence Design Systems, Inc.)
4. [PSpice Reference Guide](#), OrCAD Corp. (Cadence Design Systems, Inc.)
5. [PSpice Library Guide](#), OrCAD Capture User's Guide, (Cadence Design Systems, Inc.)
6. [OrCAD Capture User's Guide](#), OrCAD Corp., (Cadence Design Systems, Inc.)
7. SPICE [Tutorial](#)
8. A. Vladimirescu, "The Spice Book," J. Wiley & Sons, New York, 1994.
9. B. Carter, "[Using Texas Instruments Spice Models in PSpice](#)", Application Report, SLOA070, Texas Instruments, Dallas, TX, September 2001.

10. A. Sedra and K. C. Smith, "Microelectronic Circuits," Oxford University Press, 2004, with accompanying Rom CD containing Spice Circuit Examples.